

# *HAWKINS ELECTRICAL GUIDE · N<sup>o</sup> 5*

*WITH QUESTIONS ANSWERS & ILLUSTRATIONS*

TK  
146  
.H3  
V.5

The A. H. Hill Library



North Carolina State College

TK146

H3

v. 5

TK146  
H3  
v.5

7159  
Hawkins electrical  
gui

7159

This book must not be  
taken from the Library  
building.

DATE

16 Sep '41

7 Aug '42

16 Sep '40

7 Aug '42





THE THOUGHT IS IN THE QUESTION THE INFORMATION IS IN THE ANSWER

HAWKINS

# ELECTRICAL GUIDE

NUMBER  
FIVE

QUESTIONS  
ANSWERS  
&

ILLUSTRATIONS

A PROGRESSIVE COURSE OF STUDY  
FOR ENGINEERS, ELECTRICIANS, STUDENTS  
AND THOSE DESIRING TO ACQUIRE A  
WORKING KNOWLEDGE OF

## ELECTRICITY AND ITS APPLICATIONS

A PRACTICAL TREATISE

HAWKINS  AND STAFF

THEO. AUDEL & CO. 72 FIFTH AVE. NEW YORK.

COPYRIGHTED, 1914,  
BY  
THEO. AUDEL & CO.,  
NEW YORK.

# TABLE OF CONTENTS

## GUIDE NO. 5.

### ALTERNATING CURRENTS - - - 997 to 1,066

The word "*alternating*" — advantages of alternating current — direct current apparatus; alternating current apparatus — disadvantages of alternating current — **alternating current principles** — the sine — application and construction of the sine curve — **illustrated definitions**: cycle, alternation, amplitude, period, periodicity, frequency — commercial frequencies — advantages of low frequency — **phase** — phase difference — phase displacement — synchronism — "in phase" — curves illustrating "in phase" and "out of phase" — **illustrated definitions**: in phase; in quadrature, current leading; in quadrature, current lagging; in opposition — **maximum** volts and amperes — **average** volts and amperes — elementary alternator developing one average volt — **virtual** volts and amperes — **effective** volts and amperes — relation between shape of wave and **form factor** — wave form — oscillograph wave form records — what determines wave form — effect of one coil per phase per pole — **single phase current**; hydraulic analogy — **two phase current**; hydraulic analogy — two phase current distribution — **three phase current**; hydraulic analogy; distribution — **inductance** — **the henry** — inductive and non-inductive coils — hydraulic analogy of inductance — inductance coil calculations — **ohmic value of inductance** — **capacity**: hydraulic analogy — the farad — specific inductive capacity — condenser connections — **ohmic value of capacity** — lag and lead — mechanical analogy of lag — lag measurement — steam engine analogy of current flow at zero pressure — **reactance** — examples — choking coil — impedance curve — **resonance** — critical frequency — skin effect.

7159

PROPERTY OF  
J. A. M. COLLEGE LIBRARY

## ALTERNATING CURRENT DIA-

GRAMS - - - - - 1,067 to 1,100

Definitions: impressed pressure, active pressure, self-induction pressure, reverse pressure of self-induction — rate of change in current strength — properties of right angle triangles — equations of the right triangle — representation of forces by wires — parallelogram of forces; **the resultant** — **circuits containing resistance and inductance** — graphical method of obtaining the impressed pressure — **equations for ohmic drop and reactance drop** — examples — diagram for impedance, angle of lag, etc. — **circuits containing resistance and capacity** — capacity in series, and in parallel — amount of lead — action of condenser — the condenser pressure — capacity pressure — equation for impedance — examples and diagrams — **circuits containing resistance, inductance, and capacity** — impedance equation — examples and diagrams — equation for impressed pressure — examples and diagrams.

## THE POWER FACTOR - - - - - 1,101 to 1,124

Definition of power factor — true watts — apparent watts — ferry boat analogy of power factor — limits of power factor — effect of lag or lead — **how to obtain the power curve** — nature of the power curve — synchronism of current and pressure; **power factor unity** — case of synchronism of current and pressure with power factor less than unity — steam engine analogy of power factor — "wattless current"; **power factor zero** — examples of phase difference nearly 90 degrees — mechanical analogy of wattless current — **why the power factor is equal to  $\cos \phi$**  — graphical method of obtaining the active component — examples and diagrams — effect of capacity — diagrams illustrating why the power factor is unity when there is no resultant reactance in the circuit — usual value of power factor — power factor test — **how alternators are rated; kva.** — curves illustrating power factor — **how to keep the power factor high** — why power factor is important in station operation — wattmeter method of three phase power measurement.

## ALTERNATORS - - - - - 1,125 to 1,186

Uses of alternators — classes of alternator — **single phase alternators**; essential features; width of armature coils —

ALTERNATORS—*Continued*

elementary single phase alternator — **polyphase alternators** — uses for two and three phase current — elementary three phase alternator — starting difficulty with single phase motors — six and twelve phase windings — **belt or chain driven alternators** — sub-base and ratchet device for tightening the belt — **horse power transmitted by belts** — best speeds for belts — advantages of chain drive; objections — **direct connected alternator** — “direct connected” and “direct coupled” units — **revolving armature alternators**; their uses — **revolving field alternators** — marine view showing that motion is purely a relative matter — essential parts of revolving field alternator — the terms “stator” and “rotor” — inductor alternators: classes, use, defects — hunting or surging in alternators — **amortisseur** windings — **monocyclic alternators** — diagram of connections — teaser coil — **armature reaction** — distortion of field — strengthening and weakening effects — superpositions of fields — three phase reactions — **magnetic leakage** — **field excitation of alternators** — self-excited alternator — direct connected exciter — gear driven exciters — **slow speed alternators** — **fly wheel alternators** — **high speed alternators** — **water wheel alternators** — construction of rotor — **turbine driven alternators** — construction — step bearing — **alternators of exceptional character** — asynchronous alternators — image current alternators — extra high frequency alternators — self-exciting image current alternators.

## CONSTRUCTION OF ALTERNA-

## TORS - - - - - 1,187 to 1,266

**Essential parts of an alternator** — field magnets — **methods of excitation**: self-excited, separately excited, compositely excited — magneto — construction of stationary magnets — revolving field — slip rings — spider for large alternator — provision for shifting armature to give access to field — **armatures** — core construction — advantages of slotted core armatures — **armature windings** — **classification**: revolving and stationary windings — half coil and whole coil windings — **concentrated** or uni-coil winding; features; wave form — **distributed** or multi-coil windings: breadth of coil, partial and fully distributed coils — the Kapp coefficient — general equation for voltage — wire, strap, and bar windings — condition, governing type of inductor — coil covering — single and double layer multi-wire inductors and methods of placing them

CONSTRUCTION OF ALTERNATORS—*Continued*

on the core—**insulation**—core stamping—single and multi-slot windings—arrangement in slot of two layer bar winding—table of relative effectiveness of windings—**single phase windings**—advantage of half coil winding—**two phase windings**—shape of coil ends—**three phase windings**—shape of coil ends—kind of coil used with three phase windings—**grouping of phases**—two phase **star connection**—two phase **mesh connection**—three phase star connection—winding diagrams with star and  $\Delta$  connections—three phase  $\Delta$  connection—three phase winding with “short” coils—three phase lap winding star connection—three phase wave winding star connection—**output of star and delta connected alternators**—gramme ring armatures showing three phase star and mesh connections with direction of currents in the coils—features of star connection—characteristics of delta connection—proper ends to connect to star point—determination of path and value of currents in delta connection—points to be noted with Y connection—diagram of Y connection with return wire—chain or basket winding—skew winding—fed-in winding—imbricated winding—spiral winding—mummified winding—shuttle winding—creeping winding—**turbine alternator winding**: how the high voltage is obtained with so few poles; table of frequency and revolutions—**turbine alternator construction**—form of armature generally used—two pole radial slot field—parallel slot field—difficulty experienced with revolving armatures—how the field design is modified to reduce centrifugal force—examples of revolving fields.

## CHAPTER XLVI

## ALTERNATING CURRENTS

The word "alternating" is used with a large number of electrical and magnetic quantities to denote that their magnitudes vary continuously, passing repeatedly through a definite cycle of values in a definite interval of time.


As applied to the flow of electricity, an alternating current may be defined as: *A current which reverses its direction in a periodic manner, rising from zero to maximum strength, returning to zero, and then going through similar variations in strength in the opposite direction;* these changes comprise the *cycle* which is repeated with great rapidity.

The properties of alternating currents are more complex than those of continuous currents, and their behavior more difficult to predict. This arises from the fact that the magnetic effects are of far more importance than those of steady currents. With the latter the magnetic effect is constant, and has no reactive influence on the current when the latter is once established. The lines of force, however, produced by alternating currents are changing as rapidly as the current itself, and they thus induce electric pressures in neighboring circuits, and even in adjacent parts of the same circuit. This inductive influence in alternating currents renders their action very different from that of continuous current.


**Ques.** What are the advantages of alternating current over direct current?

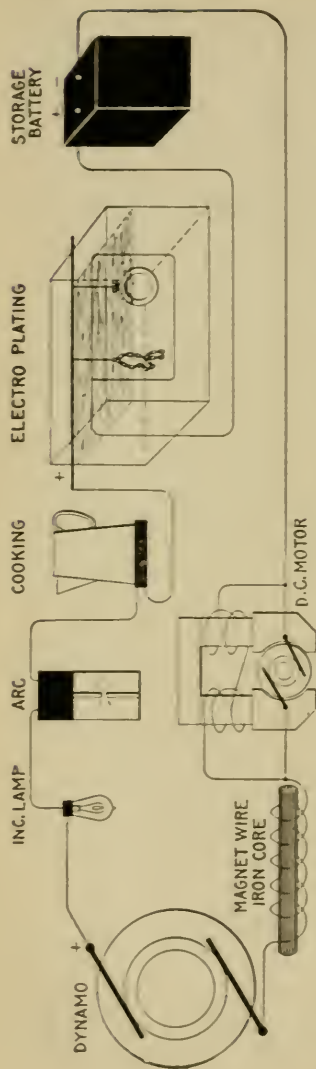**Ans.** The reduced cost of transmission by use of high voltages and transformers, greater simplicity of generators and motors,





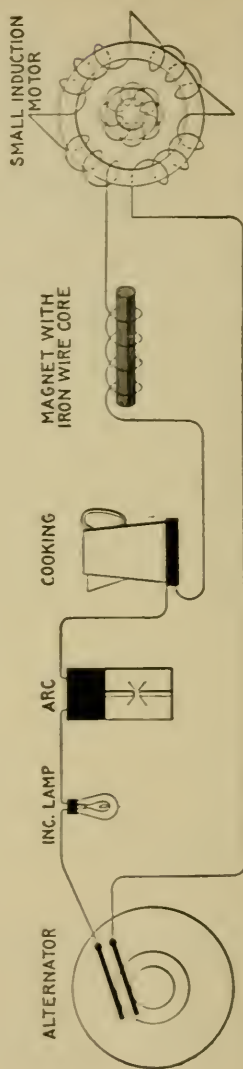FIGS. 1,212 TO 1,217.—Apparatus which operates successfully on a direct current circuit. The direct current will operate incandescent lamps, arc lamps, electric heating apparatus, electro-plating and typing bath, direct current motors; charge storage batteries, produce electro-chemical action. It will flow through a straight wire or just as freely through the same wire when wound over an iron bar.



FIGS. 1,213 TO 1,217.—Apparatus which operates successfully on an alternating circuit. The alternating current will operate incandescent lamps, arc lamps, electric heating apparatus, alternating current motors. It will flow through a straight wire with slightly increased retarding effect, but if the wire be wound on an iron bar its strength is greatly reduced.



facility of transforming from one voltage to another (either higher or lower) for different purposes.

The size of wire needed to transmit a given amount of electrical energy (watts) with a given percentage of drop, being *inversely proportional to the square of the voltage employed*, the great saving in copper by the use of alternating current at high pressure must be apparent. This advantage can be realized either by a saving in the weight of wire required, or by transmitting the current to a greater distance with the same weight of copper.

In alternating current electric lighting, the primary voltage is usually at least 1,000 and often 2,000 to 10,000 volts.

**Ques. Why is alternating current used instead of direct current on constant pressure lighting circuits?**

**Ans.** It is due to the greater ease with which the current can be transformed from higher to lower pressures.

**Ques. How is this accomplished?**

**Ans.** By means of simple transformers, consisting merely of two or more coils of wire wound upon an iron core.

Since there are no moving parts, the attention required and the likelihood of the apparatus getting out of order are small. The apparatus necessary for direct current consists of a motor dynamo set which is considerably more costly than a transformer and not so efficient.

**Ques. What are some of the disadvantages of alternating current?**

**Ans.** The high pressure at which it is used renders it dangerous, and requires more efficient insulation; alternating current cannot be used for such purposes as electroplating, charging storage batteries, etc.

**Alternating Current Principles.**—In the operation of a direct current generator or *dynamo*, as explained in Chapter XIII, alternating currents are generated in the armature winding

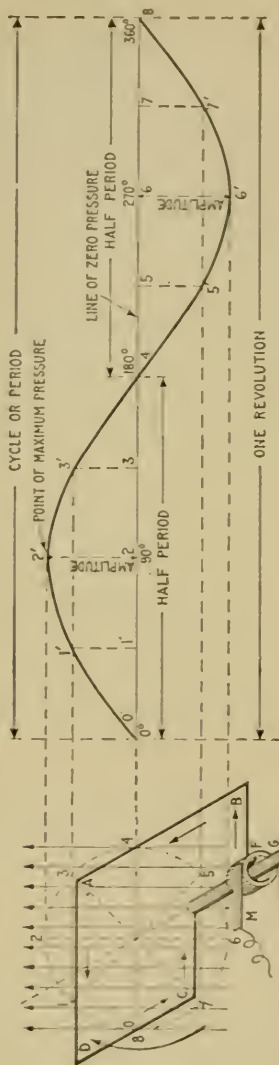


FIG. 1,218.—Application and construction of the sine curve. The sine curve is a wavelike curve used to represent the changes in strength and direction of an alternating current. At the left of the figure is shown an elementary alternator, consisting of a loop of wire ABCD, whose ends are attached to the ring F, and shaft G, being arranged to revolve in a uniform magnetic field, as indicated by the vertical arrows representing magnetic lines at equal distances. The alternating current induced in the loop is carried to the external circuit through the brushes M and S. The loop, as shown, is in its horizontal position at right angles to the magnetic field. The dotted circle indicates the circular path described by A or C or D during the revolution of the loop. Now, as the loop rotates, the induced electric pressure will vary in such a manner that its intensity at any point of the rotation is proportional to the sine of the angle corresponding to that point. Hence, on the horizontal line which passes through the center of the dotted circle, take any length as OS, and divide into any number of equal parts representing fractions of a revolution, as  $0^\circ$ ,  $90^\circ$ ,  $180^\circ$ , etc. Erect perpendiculars at these points, and from the corresponding points on the dotted circle project lines (parallel to OS) to the perpendiculars; these intersections give points, on the sine curve, for instance, through 2 at the  $90^\circ$  point of the revolution of the loop, and projecting over to the corresponding perpendicular gives 2'. The curve length is proportional to the electric pressure at that point. In like manner other points are obtained, and the curved line through them will represent the variation in the electric pressure for all points of the revolution. At  $90^\circ$  the pressure is at a maximum, hence by using a pressure scale such that the length of the perpendicular  $2'2$  for  $90^\circ$  will measure the maximum pressure, the length of the perpendicular at any other point will represent the actual pressure at that point. The curve lies above the horizontal axis during the first half of the revolution and below it during the second half, which indicates that the current flows in one direction for a half revolution, and in the opposite direction during the remainder of the revolution.

and are changed into direct current by the action of the commutator. It was therefore necessary in that chapter, in presenting the basic principles of the dynamo, to explain the generation of alternating currents at length, and the graphic method of representing the alternating current cycle by the sine curve. In order to avoid unnecessary repetition, the reader

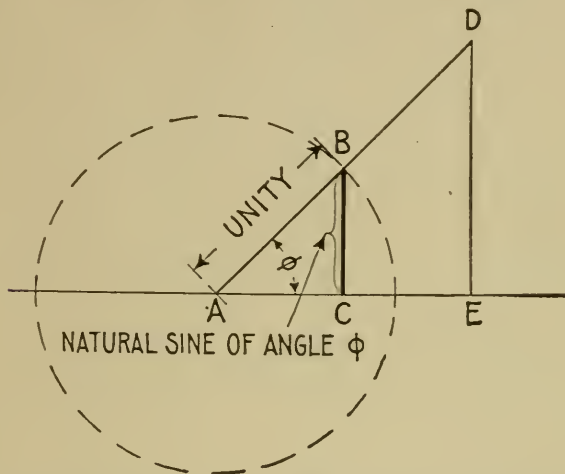


FIG. 1,219—Diagram illustrating the sine of an angle. In order to understand the sine curve, it is necessary to know the meaning of the sine of an angle. This is defined as *the ratio of the perpendicular let fall from any point in one side of the angle to the other side divided by the hypotenuse of the triangle thus formed*. For instance, in the diagram, let AD and AE be the two sides of the angle  $\phi$ , and DE a perpendicular let fall from any point D of the side AD to the other side AE. Then, the sine of the angle (written  $\sin \phi$ ) =  $DE \div AD$ . It is evident that if the perpendicular be let fall at a unit's distance from the apex A, as at B,

$$\sin \phi = \frac{BC}{AB} = \frac{BC}{1} = BC$$

This line BC is called the natural sine of the angle, and its values for different angles are given in the table on page 451.

should carefully review the above mentioned chapter before continuing further. The diagram fig. 168, showing the construction and application of the sine curve to the alternating current, is however for convenience here shown enlarged (fig. 1,218).

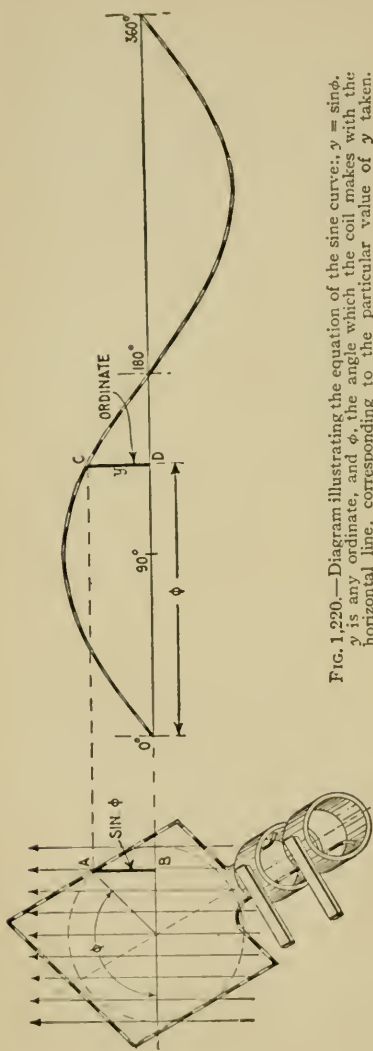


FIG. 1,220.—Diagram illustrating the equation of the sine curve:  $y = \sin \phi$ .  $y$  is any ordinate, and  $\phi$ , the angle which the coil makes with the horizontal line, corresponding to the particular value of  $y$  taken.

In the diagram the various alternating current terms are graphically defined.

The alternating current, as has been explained, rises from zero to a maximum, falls to zero, reverses its direction, attains a maximum in the new direction, and again returns to zero; this comprises the *cycle*.

This series of changes can best be represented by a curve, whose abscissæ represent time, or degrees of armature rotation, and whose ordinates, either current or pressure. The curve usually chosen for this purpose is the sine curve, as shown in fig. 1,218, because it closely agrees with that given by most alternators.

The equation of the sine curve is

$$y = \sin \phi$$

in which  $y$  is any ordinate, and  $\phi$ , the angle of the corresponding position of the coil in which the current is being generated as illustrated in fig. 1,220.

# **Ques. What is an alternation?**

Ans. The changes which the current undergoes in rising from zero to maximum pressure and returning back to zero; that is, a single positive or negative "wave" or half period, as shown in fig. 1,221.

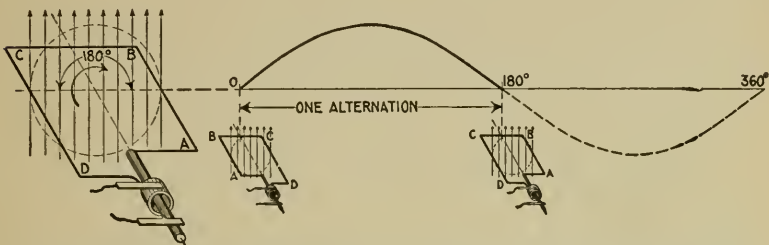


FIG. 1,221.—Diagram showing one *alternation* of the current in which the latter varies from zero to maximum and back to zero while the generating loop ABCD makes one half revolution.

# **Ques. What is the amplitude of the current?**

Ans. The greatest value of the current strength attained during the cycle.

The foregoing definitions are also illustrated in fig. 1,218.

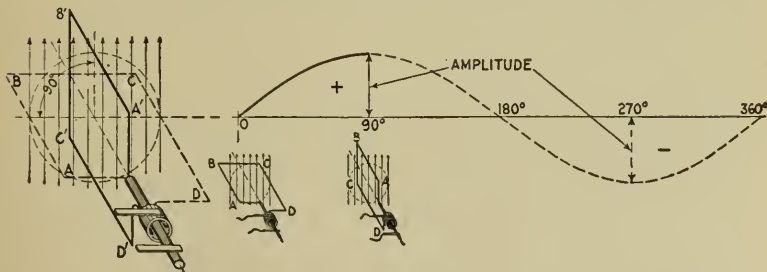


FIG. 1,222.—Diagram illustrating *amplitude* of the current. The current reaches its amplitude or maximum value in one quarter period from its point of zero value, as, for instance, while the generating loop moves from position ABCD to A'B'C'D'. At three-quarter revolution, the current reaches its maximum value in the opposite direction.

**Ques.** Define the term “period.”

**Ans.** This is the time of one cycle of the alternating current.

**Ques.** What is periodicity?

**Ans.** A term sometimes used for *frequency*.

**Frequency.**—If a slowly varying alternating current be passed through an incandescent lamp, the filament will be seen to vary in brightness, following the change of current strength. If,

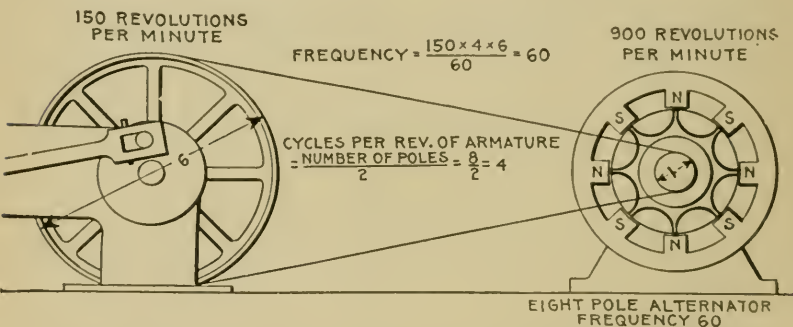


FIG. 1,223.—Diagram of alternator and engine, illustrating *frequency*. The frequency or cycles per second is equal to the revolution of armature per second multiplied by one-half the number of poles per phase. In the figure the armature makes 6 revolutions to one of the engine; one-half the number of poles =  $8 \div 2 = 4$ , hence frequency =  $(150 \times 4 \times 6) \div 60 = 60$ . The expression in the parenthesis gives the cycles per minute, and dividing by 60, the cycles per second.

however, the alternations take place more rapidly than about 50 to 60 per second, the eye cannot follow the variations and the lamp appears to burn steadily. Hence it is important to consider the rate at which the alternations take place, or as it is called, the *frequency*, which is defined as: *the number of cycles per second*.

In a two pole machine, the frequency is the same as the number of revolutions *per second*, but in multipolar machines, it is greater in proportion to the number of *pairs* of poles per phase.


Thus, in an 8 pole machine, there will be four cycles per revolution. If the speed be 900 revolutions per minute, the frequency is

$$\frac{8}{2} \times \frac{900}{60} = 60 \text{ —}$$

The symbol — is read “cycles per second.”

**Ques.** What frequencies are used in commercial machines?

**Ans.** The two standard frequencies are 25 and 60 cycles.

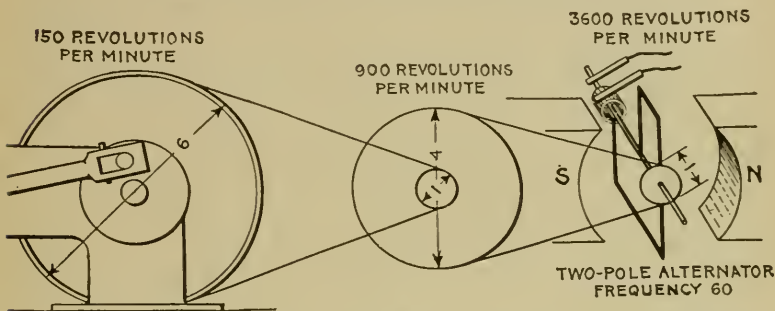

**FIG. 1,224—**Diagram answering the question: Why are alternators always built multipolar? They are made multipolar because it is desirable that the frequency be high. It is evident from the figure that to obtain high frequency would require too many revolutions of the armature of a bipolar machine for mechanical safety—especially in large alternators. Moreover a double reduction gear in most cases would be necessary, adding complication to the drive. Comparing the above illustration with fig. 1,223, shows plainly the reason for multipolar construction.

**Ques.** For what service are these frequencies adapted?

**Ans.** The 25 cycle frequency is used for conversion to direct current, for alternating current railways, and for machines of large size; the 60 cycle frequency is used for general distribution for lighting and power.

The frequency of 40 cycles, which once was introduced as a compromise between 25 and 60 has been found not desirable, as it is somewhat low for general distribution, and higher than desirable for conversion to direct current.



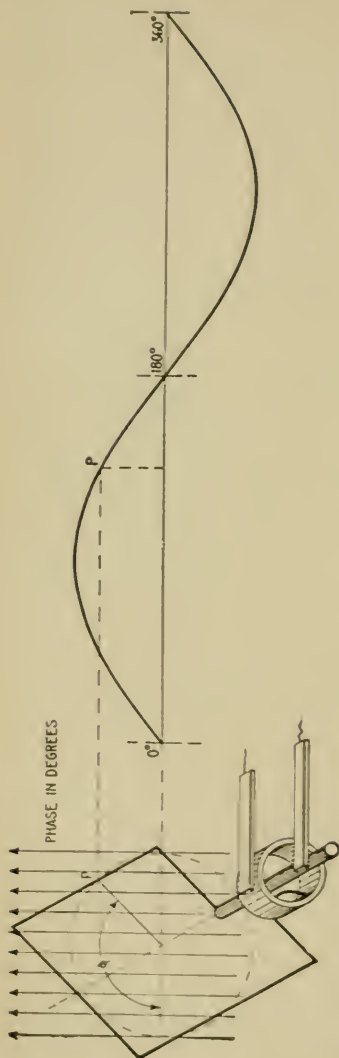


FIG. 1,225.—Diagram illustrating "phase." In wave, vibratory, and simple harmonic motion, phase may be defined as: *the portion of one complete vibration, measured either in angle or in time, that any moving point has executed.*

**Ques.** What are the advantages of low frequency?

**Ans.** The number of revolutions of the *rotor* is correspondingly low; are lamps can be more readily operated; better pressure regulation; small motors such as fan motors can be operated more easily from the circuit.

**Phase.**—As applied to an alternating current, phase denotes *the angle turned through by the generating element reckoned from a given instant.* Phase is usually measured in degrees from the initial position of zero generation.

If in the diagram fig. 1,225, the elementary armature or loop be the generating element, and the curve at the right be the sine curve representing the current, then the phase of any point *p* will be the angle  $\phi$  or angle moved through from the horizontal line, the starting point.




**Ques.** What is phase difference?

**Ans.** The angle between the phases of two or more alternating current quantities as measured in degrees.

**Ques.** What is phase displacement?

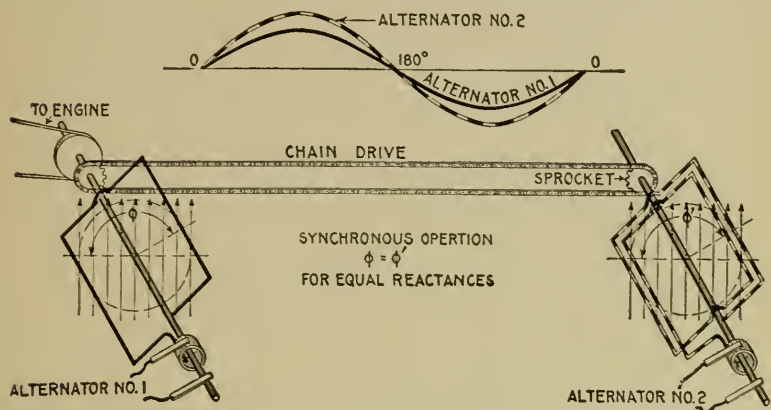**Ans.** A change of phase of an alternating pressure or current.



FIGS. 1,226 and 1,227.—Diagram and sine curves illustrating *synchronism*. If two alternators, with coils in parallel planes, be made to rotate at the same speed by connecting them with chain drive or equivalent means, they will then be “in synchronism” that is, the alternating pressure or current in one will vary in step with that in the other. In other words, the cycles of one take place with the same frequency and at the same time as the cycles of the other as indicated by the curves, fig. 1,226. It should be noted that the maximum values are not necessarily the same but the maximum and zero values must occur at the same time in both machines, and the maximum value must be of the same sign. If the waves be distorted the maximum values may not occur simultaneously. See fig. 1,348.

**Synchronism.**—This term may be defined as: *the simultaneous occurrence of any two events*. Thus two alternating currents or pressures are said to be “in synchronism” *when they have the same frequency and are in phase*.

**Ques.** What does the expression “in phase” mean?

**Ans.** Two alternating quantities are said to be in phase, when there is no phase difference between; that is when the angle of phase difference equals zero.

Thus the current is said to be in phase with the pressure when it neither lags nor leads, as in fig. 1,228.

A rotating cylinder, or the movement of an index or trailing arm is brought into synchronism with another rotating cylinder or another index or trailing arm, not only when the two are moving with exactly the same speed, but when in addition they are *simultaneously moving over similar portions of their respective paths.*

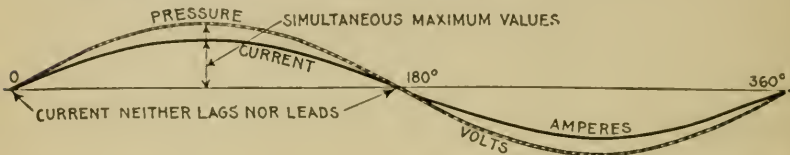


FIG. 1,228—Pressure and current curves illustrating the term “in phase.” The current is said to be *in phase* with the pressure when it *neither lags nor leads*.

When there is phase difference, as between current and pressure, they are said to be “out of phase” the phase difference being measured as in fig. 1,229 by the angle  $\phi$ .

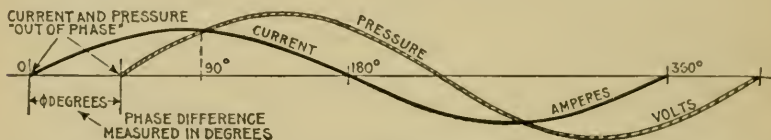



FIG. 1,229—Pressure and current curves illustrating the term “out of phase.” The current is said to be *out of phase* with the pressure when it *either lags or leads*, that is when the current is not in synchronism with the pressure. In practice the current and pressure are nearly always out of phase.

When the phase difference is  $90^\circ$  as in fig. 1,231 or 1,232, the two alternating quantities are said to be *in quadrature*; when it is  $180^\circ$ , as in fig. 1,233, they are said to be *in opposition*.

When they are in quadrature, one is at a maximum when the other is at zero; when they are in opposition, one reaches a positive maximum when the other reaches a negative minimum, being at each instant opposite in sign.

**Ques.** What is a departure from synchronism called?

**Ans.** Loss of synchronism.

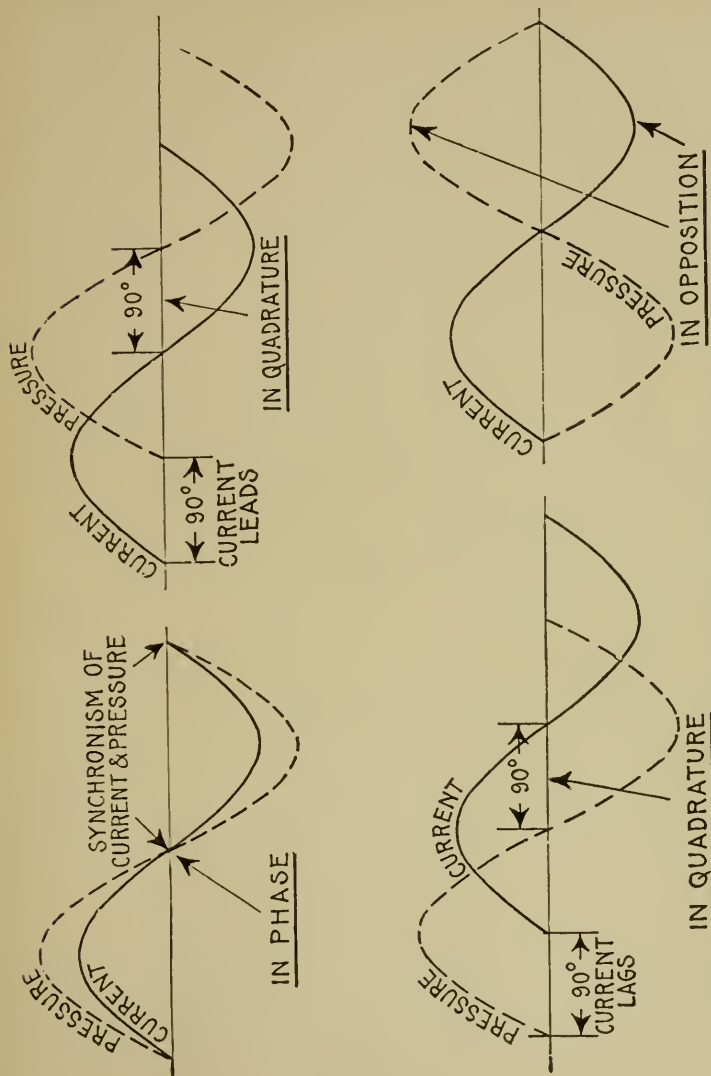

FIGS. 1,230 to 1,233.—Curves showing some phase, relations between current and pressure. Fig. 1,230, synchronism of current and pressure, expressed by the term "in phase," meaning simultaneous zero values, and simultaneous maximum values of the same sign; fig. 1,231, in quadrature, current leading  $90^\circ$ ; fig. 1,232 in quadrature, current lagging  $90^\circ$ ; fig. 1,233, in opposition, meaning that the phase difference between current and pressure is  $180^\circ$ .

**Maximum Volts and Amperes.**—In the operation of an alternator, the pressure and strength of the current are continually rising, falling and reversing. During each cycle there are two points at which the pressure or current reaches its greatest value, being known as the *maximum value*. This maximum value is not used to any great extent, but it shows the maximum to which the pressure rises, and hence, the greatest strain to which the insulation of the alternator is subjected.

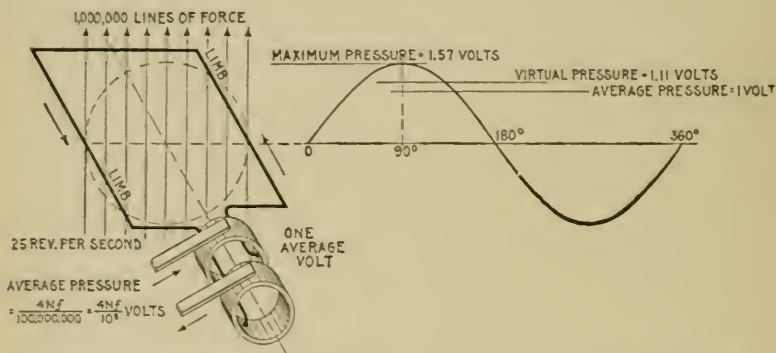


FIG. 1,234.—Elementary alternator developing one average volt. If the loop make one revolution per second, and the maximum number of lines of force embraced by the loop in the position shown (the zero position) be denoted by  $N$ , then each limb will cut  $2N$  lines per second, because it cuts every line during the right sweep and again during the left sweep. Hence each limb develops an average pressure of  $2N$  units (C.G.S. units) and as both limbs are connected in series, the total pressure is  $4N$  units *per revolution*. Now, if the loop make  $f$  revolutions *per second* instead of only one, then  $f$  times as many lines will be cut *per second*, and the average pressure will be  $4Nf$  units. Since the C.G.S. unit of pressure is so extremely small, a much greater practical unit called the *volt* is used, which is equal to 100,000,000, or  $10^8$  C.G.S. units is employed. Hence average voltage =  $4Nf \div 10^8$ . The value of  $N$  in actual machines is very high, being several million lines of force. The illustration shows one set of conditions necessary to generate one average volt. The maximum pressure developed is  $1 \div .637 = 1.57$  volts; virtual pressure =  $1.57 \times .707 = 1.11$  volts.

**Average Volts and Amperes.**—Since the sine curve is used to represent the alternating current, the *average value* may be defined as: *the average of all the ordinates of the curve for one-half of a cycle.*

**Ques.** Of what use is the average value?

**Ans.** It is used in some calculations but, like the maximum value, not very often. The relation between the average and virtual value is of importance as it gives the form factor.

**Virtual Volts and Amperes.**—The virtual\* value of an alternating pressure or current *is equivalent to that of a direct pressure or current which would produce the same effect*; those

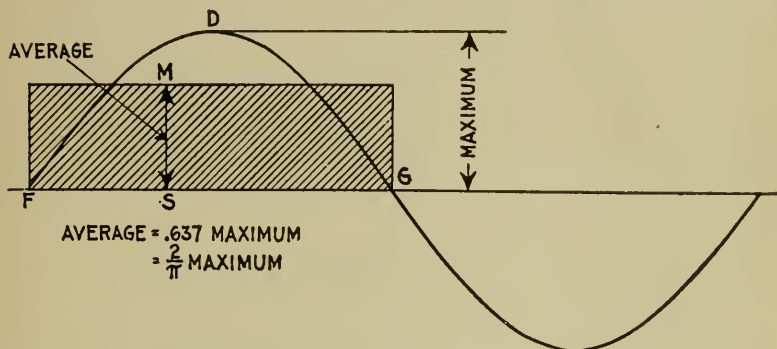


FIG. 1,235.—Maximum and average values of the sine curve. The average value of the sine curve is represented by an ordinate MS of such length that when multiplied by the base line FG, will give a rectangle MFSG whose area is equal to that included between the curve and base line FDGS.

effects of the pressure and current are taken which are not affected by rapid changes in direction and strength,—in the case of pressure, the reading of an electrostatic voltmeter, and in the case of current, the heating effect.

\*NOTE.—“I adhere to the term *virtual*, as it was in use before the term *efficace* which was recommended in 1889 by the Paris Congress to denote the *square root of mean square* value. The corresponding English adjective is *efficacious*; but some engineers mistranslate it with the word *effective*. I adhere to the term *virtual* mainly because the adjective *effective* is required in its usual meaning in kinematics to represent the resolved part of a force which acts obliquely to the line of motion, the effective force being the whole force multiplied by the cosine of the angle at which it acts with respect to the direction of motion. Some authors use the expression ‘R. M. S. value’ (meaning ‘root mean square’) to denote the virtual or quadratic mean value.”—S. P. Thompson.

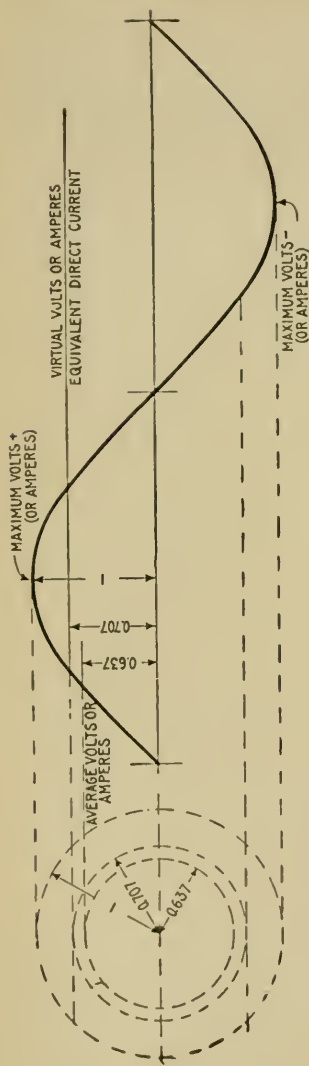


FIG. 1.236.—Diagram illustrating "virtual" volts and amperes. The word *virtual* is defined as: *Being in essence or effect, not in fact; not actual, but equivalent, so far as effect is concerned.* As applied to the alternating current, it denotes an imaginary direct current of such value as will produce an effect equivalent to that of the alternating current. Thus, a *virtual pressure* of 1,000 volts is one that would produce the same deflection in an electrostatic voltmeter as a direct pressure of 1,000 volts; a *virtual current* of 10 amperes is that current which would produce the same heating effect as a direct current of 10 amperes. Both pressure and current vary continually above, and below the virtual values in alternating current circuits. Distinction should be made between the virtual and "effective" values of an alternating current. See fig. 1.237. The word *effective* is commonly used erroneously for *virtual*. See note page 1.011.

The attraction (or repulsion) in electrostatic voltmeters is proportional to the square of the volts.

The readings which these instruments give, if first calibrated by using steady currents, are not true means, but are the *square roots of the means of the squares*.

Now the mean of the squares of the sine (taken over either one quadrant or a whole circle) is  $\frac{1}{2}$ ; hence the *square root of mean square* value of the sine functions is obtained by multiplying their maximum value by  $1 \div \sqrt{2}$ , or by 0.707.

The arithmetical mean of the values of the sine, however, is 0.637. Hence an alternating current, if it obey the sine law, will produce a heating effect greater than that of a steady current of the same average strength, by the ratio of 0.707 to 0.637; that is, about 1.11 times greater.

If a Cardew voltmeter be placed on an alternating circuit in which the volts are oscillating between maxima of +100 and -100 volts, it will read 70.7 volts, though the arithmetical mean is really only 63.7; and 70.7 steady volts would be required to produce an equal reading.



The matter may be looked at in a different way. If an alternating current is to produce in a given wire the same amount of effect as a continuous current of 100 amperes, since the alternating current goes down to zero twice in each period, it is clear that it must at some point in the period rise to a maximum greater than 100 amperes. How much greater must the maximum be? The answer is that, if it undulate up and down with a pure wave form, its maximum must be  $\sqrt{2}$  times as great as the virtual mean; or conversely the virtual amperes will be equal to the maximum divided by  $\sqrt{2}$ . In fact, to produce equal effect, the equivalent direct current will be a kind of mean between the

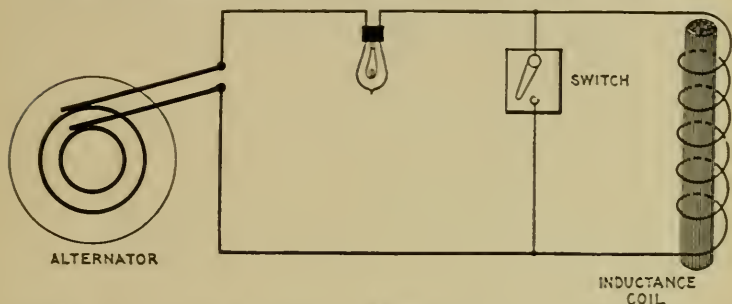


FIG. 1,237.—Diagram illustrating *virtual* and *effective* pressure. If the coil be short circuited by the switch and a constant virtual pressure be impressed on the circuit, the whole of the impressed pressure will be effective in causing current to flow around the circuit. In this case the virtual and effective pressures will be equal. If the coil be switched into circuit, the reverse pressure due to self induction will oppose the virtual pressure; hence, the effective pressure (which is the difference between the virtual and reverse pressures) will be reduced, the virtual or impressed pressure remaining constant all the time. A virtual current is that indicated by an ammeter regardless of the phase relation between current and pressure. An effective current is that indicated by an ammeter when the current is in phase with the pressure. In practice, the current is hardly ever in phase with the pressure, usually lagging, though sometimes leading in phase. Now the greater this phase difference, either way, the less is the power of a given virtual current to do work. With respect to this feature, effective current may be defined as: *that proportion of a given virtual current which can do useful work*. If there be no phase difference, then effective current is equal to virtual current.

maximum and the zero value of the alternating current; but it must not be the arithmetical mean, nor the geometrical mean, nor the harmonic mean, but the *quadratic* mean; that is, it will be the *square root of the mean of the squares* of all the instantaneous values between zero and maximum.

**Effective Volts and Amperes.**—Virtual pressure, although already explained, may be further defined as the pressure *impressed* on a circuit. Now, in nearly all circuits the impressed

or virtual pressure meets with an opposing pressure due to inductance and hence the *effective* pressure is something less than the virtual, being defined as *that pressure which is available for driving electricity around the circuit, or for doing work*. The difference between virtual and effective pressure is illustrated in fig. 1,237.

**Ques.** Does a given alternating voltage affect the insulation of the circuit differently than a direct pressure of the same value?

**Ans.** It puts more strain on the insulation in the same proportion as the maximum pressure exceeds the virtual pressure.

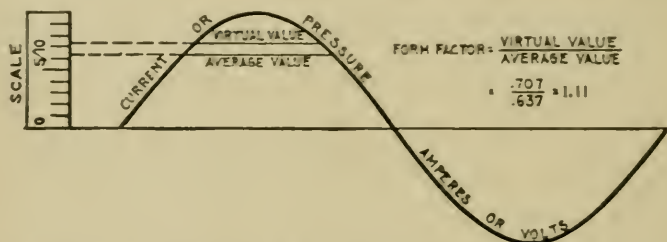


FIG. 1,233.—Current or pressure curve illustrating *form factor*. It is simply the *virtual value* divided by the *average value*. For a sine wave the virtual value is  $\frac{1}{\sqrt{2}}$  times the maximum, and the average is  $\frac{2}{\pi}$  times the maximum, so that the form factor is  $\frac{\frac{1}{\sqrt{2}}}{\frac{2}{\pi}}$  or 1.11. The induction wave which generates an alternating pressure wave has a maximum value proportional to the area, that is, to the average value of the pressure wave. Hence the induction values corresponding to two pressure waves whose virtual values are equal, will be inversely proportional to their form factors. This is illustrated by the fact that a *peaked* wave causes less hysteresis loss in a transformer core than a *flat topped* wave, owing to the higher form factor of the peaked wave. See wave forms, figs. 1,245 to 1,248.

**Form Factor.**—This term was introduced by Fleming, and denotes the ratio of the virtual value of an alternating wave to the average value. That is

$$\text{form factor} = \frac{\text{virtual value}}{\text{average value}} = \frac{.707}{.637} = 1.11$$




**Ques.** What does this indicate?

**Ans.** It gives the relative heating effects of alternating and direct currents, as illustrated in figs. 1,239 and 1,240.

That is, the alternating current will have about 11 per cent. more heating power than the direct current which is of the same *average* strength.

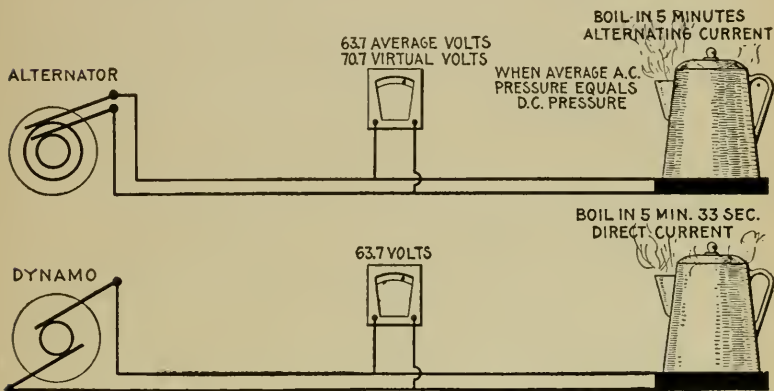If an alternating current voltmeter be placed upon a circuit in which the volts range from  $+100$  to  $-100$ , it will read 70.7 volts, although the arithmetical average, irrespective of  $+$  or  $-$  sign, is only 63.7 volts. If the voltmeter be connected to a direct current circuit, the pressure necessary to give the same reading would be 70.7 volts.




FIGS. 1,239 and 1,240.—Relative heating effects of alternating and direct currents. If it take, say five minutes to produce a certain heating effect with alternating current at say 63.7 *average* volts, it will take 33 seconds longer with direct current at the same pressure, that is, the alternating current has about 11 per cent. more heating power than the direct current of the same *average* pressure. The reader should be careful not to get a wrong conception of the above; it does not mean that there is a saving by using alternating current. When both voltmeters read the same, that is, when the *virtual* pressure of the alternating current is the same as the direct current pressure, the heating effect is of course the same.

**Ques.** What is the relation between the shape of the wave curve and the form factor?

**Ans.** The more peaked the wave, the greater the value of its form factor.

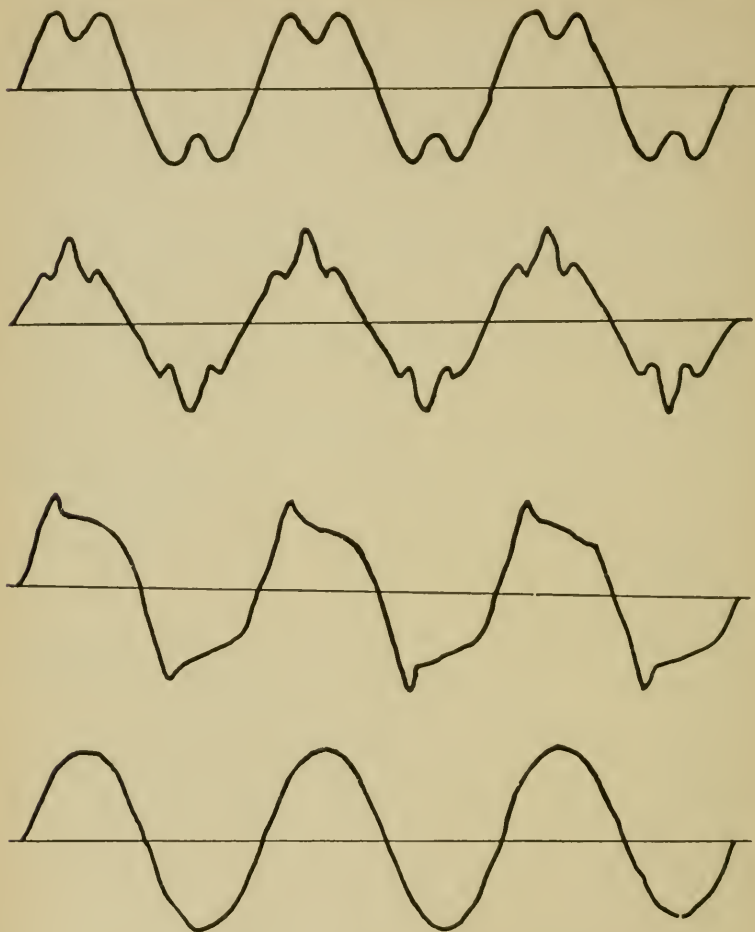
A form factor of unity would correspond to a rectangular wave; this is the least possible value of the form factor, and one which is not realized in commercial machines.



FIGS. 1,241 to 1,244.—Various forms of pressure or current waves. Figs. 1,241 to 1,243 show the general shape of the waves produced by some alternators used largely for lighting work and having toothed armatures. The effect of the slots and shape of pole pieces is here very marked. Fig. 1,244 shows a wave characteristic of large alternator, designed for power transmission and having multi-slot or distributed windings.

**Wave Form.**—There is always more or less irregularity in the shape of the current waves as met in practice, depending upon the construction of the alternator.

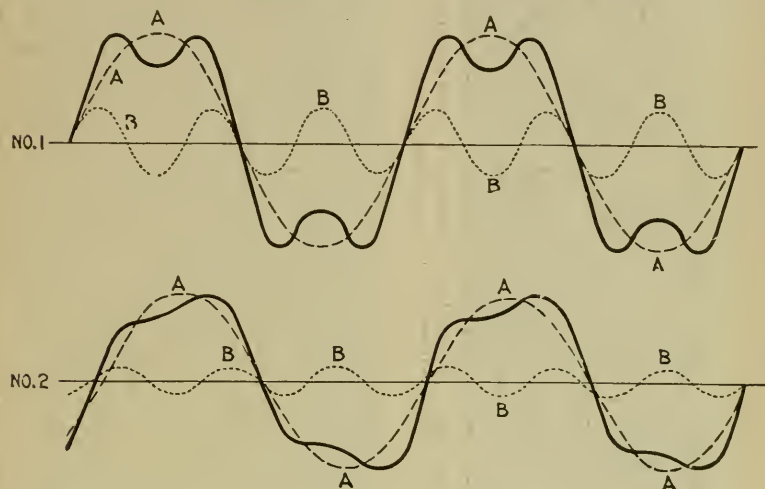The ideal wave curve is the so called *true sine wave*, and is obtained with a rate of cutting of lines of force, by the armature coils, equivalent to the swing of a pendulum, which increases



FIGS. 1,245 and 1,246.—Resolution of complex curves into sine curves. The heavy curve can be resolved into the simpler curves A and B shown in No. 1, the component curves A and B have in the ratio of three to one; that is, curve B has three times as many periods per second as curve A. All the curves, however, cross the zero line at the same time, and the resultant curve, though curiously unlike either of them, has a certain symmetry. In No. 2 the component curves, besides having periods in the ratio of three to one, cross the zero line at different points. The resultant curve produced is still less similar to its components, and is curiously and unsymmetrically humped. At first sight it is difficult to believe that such a curious curve could be resolved into two such simple and symmetrical ones. In both figures the component curves are sine curves, and as the curves for sine and cosine functions are exactly similar in form, the simplest supposition that can be made for the variation of pressure or of current is that both follow a *sine law*.

in speed from the end to the middle of the swing, decreasing at the same rate after passing the center. This swing is expressed in physics, as "simple harmonic motion."



FIG. 1,247.—Reproduction of oscillograph record of wave form of alternator with one coil per phase per pole. Here the so-called "super-imposed harmonic" is clearly indicated.



FIG. 1,248.—Reproduction of oscillograph record of Wagner alternator having three coils per phase per pole.

The losses in all secondary apparatus are slightly lower with the so called *peaked* form of wave. For the same virtual voltage, however, the top of the peak will be much higher, thereby submitting the insulation to that much greater strain. By reason of the fact that the losses are less under such wave forms, many manufacturers in submitting performance data on transformers recite that the figures are for sine wave conditions, stating further that if the transformers are to be operated in a circuit more peaked than the sine wave, the losses will be less than shown.

The slight saving in the losses of secondary apparatus, obtained with a peaked wave, by no means compensates for the increased insulation strains and an alternator having a true sine wave is preferred.

**Ques. What determines the form of the wave?**

Ans. 1. The number of coils per phase per pole, 2, shape of pole faces, 3, eddy currents in the pole pieces, and 4, the air gap.

**Ques. What are the requirements for proper rate of cutting of the lines of force?**

Ans. It is necessary to have, as a minimum, two coils per phase per pole in three phase work.

**Ques. What is the effect of only one coil per phase per pole?**

Ans. The wave form will be distorted as shown in fig. 1,247.

**Ques. What is the least number of coils per phase per pole that should be used for two and three phase alternators?**

Ans. For three phase, two coils, and for two phase, three coils, per phase per pole.


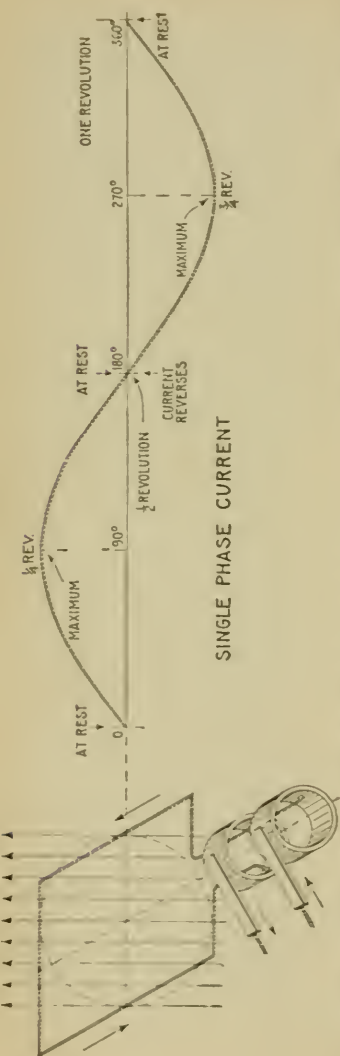


FIG. 1,249.—Elementary one loop alternator and sine curve illustrating single phase alternating current. There are three points during the revolution at which there is no current: at 0° the position shown, 180°, and 360°; in other words, at the beginning, middle point and end of the cycle. The current reaches a maximum at 90°, reverses at 180°, and reaches a maximum in the reverse direction at 270°.

**Single or Monophase Current.**—This kind of alternating current is generated by an alternator having a single winding on its armature. Two wires, a lead and return, are used as in direct current.

An elementary diagram showing the working principles is illustrated in fig. 1,249, a similar hydraulic cycle being shown in figs. 1,250 to 1,252.

**Two Phase Current.**—In most cases two phase current actually consists of two distinct single phase currents flowing in separate circuits. There is often no electrical connection between them; they are of equal period and equal amplitude, but differ in phase by one quarter of a period. With this phase relation one of them will be at a maximum when the other is at zero. Two phase current is illustrated

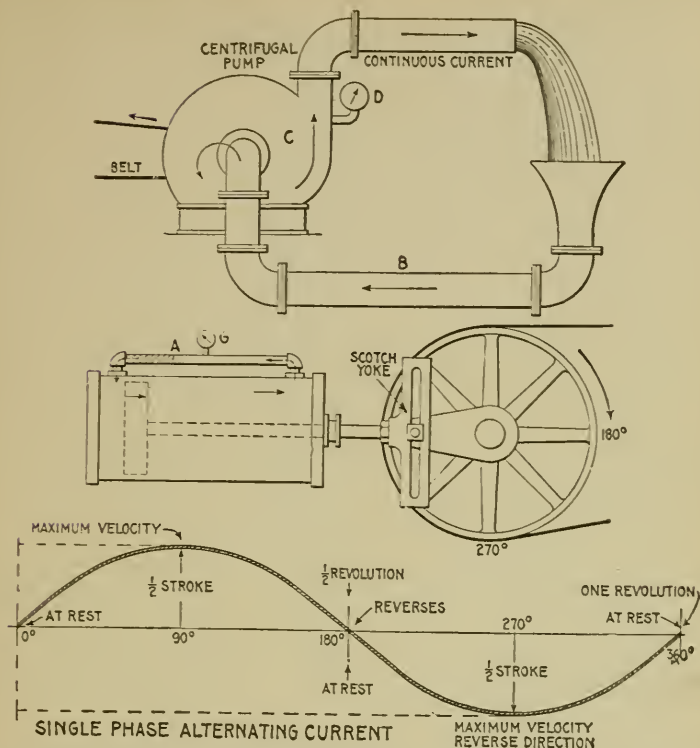

FIGS. 1,250 to 1,252.—Hydraulic analogy illustrating the difference between *direct* (continuous) and *alternating* current. In fig. 1,250 a centrifugal pump C forces water to the upper pipe, from which it falls by gravity to the lower pipe B and re-enters the pump. The current is continuous, always flowing in one direction, that is, it does not reverse its direction. Similarly a direct electric current is constant in direction (does not reverse), though not necessarily constant in value. A direct current, constant in both value and direction as a result of constant pressure, is called "continuous" current. Similarly in the figure the flow is constant, and a gauge D placed at any point will register a constant pressure, hence the current may be called, in the electrical sense, "continuous." The conditions in fig. 1,251 are quite different. The illustration represents a double acting cylinder with the ends connected by a pipe A, and the piston driven by crank and Scotch yoke as shown. In operation, if the cylinder and pipe be full of water, a current of water will begin to flow through the pipe in the direction indicated as the piston begins its stroke, increasing to maximum velocity at one-quarter revolution of the crank, decreasing and coming to rest at one-half revolution, then reversing and reaching maximum velocity in the reverse direction at three-quarter revolution, and coming to rest again at the end of the return stroke. A pressure gauge at G will register a pressure which varies with the current. Since the alternating electric current undergoes similar changes, the sine curve will apply equally as well to the pump cycle as to the alternating current cycle.



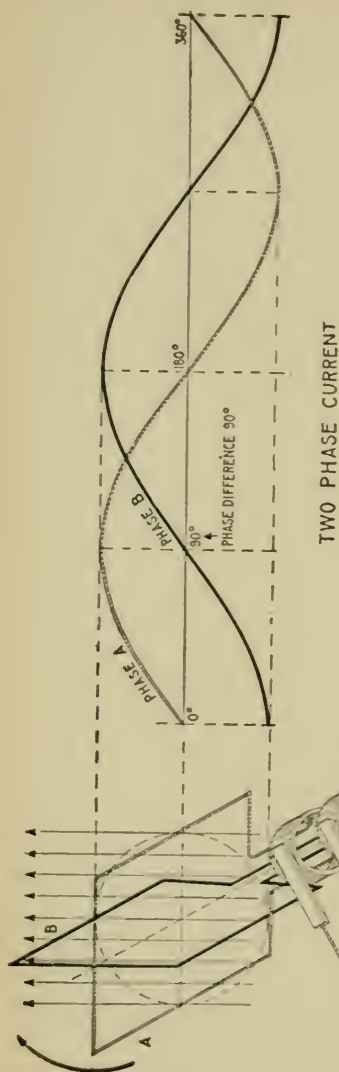


FIG. 1,253.—Elementary two loop alternator and sine curves, illustrating two phase alternating current. If the loops be placed on the alternator armature at 90 magnetic degrees, a single phase current will be generated in each of the windings, the current in one winding being at its maximum value when the other is at zero. In this case four transmission conductors are generally used, two for each separate circuit, and the motors to which the current is led have a double winding corresponding to that on the alternator armature.

by sine curves in fig. 1,253, and by hydraulic analogy in figs. 1,254 and 1,255.


If two identical simple alternators have their armature shafts coupled in such a manner, that when a given armature coil on one is directly under a field pole, the corresponding coil on the other is midway between two poles of its field, the two currents generated will differ in phase by a half alternation, and will be two phase current.

**Ques.** How must an alternator be constructed to generate two phase current?

**Ans.** It must have two independent windings, and these must be so spaced out that when the volts generated in one of the two phases are at a maximum, those generated in the other are at zero.



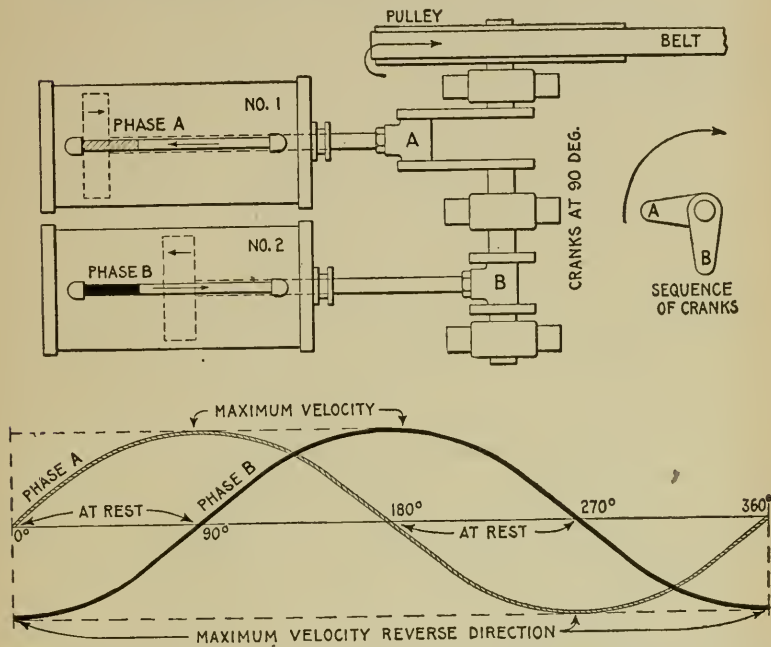In other words, the windings, which must be alike, of an equal number of turns, must be displaced along the armature by an angle corresponding to one-quarter of a period, that is, to half the pole pitch.



FIGS. 1,254 and 1,255.—Hydraulic analogy illustrating two phase alternating current. In the figure two cylinders, similar to the one in fig. 1,251, are shown, operated from one shaft by crank and Scotch yoke drive. The cranks are at 90° as shown, and the cylinders and connecting pipes full of water. In operation, the same cycle of water flow takes place as in fig. 1,251. Since the cranks are at 90°, the second piston is one-half stroke behind the first; the flow of water in No. 1 (phase A) is at a maximum when the flow in No. 2 (phase B) comes to rest, the current conditions in both pipes for the entire cycle being represented by the two sine curves whose phase difference is 90°. Comparing these curves with fig. 1,253, it will be seen that the water and electric current act in a similar manner.


The windings of the two phases must, of course, be kept separate, hence the armature will have four terminals, or if it be a revolving armature it will have four collector rings.

As must be evident the phase difference may be of any value between 0° and 360°, but in practice it is almost always made 90°.

**Ques.** In what other way may two phase current be generated?

**Ans.** By two single phase alternators coupled to one shaft.

**Ques.** How many wires are required for two phase distribution?

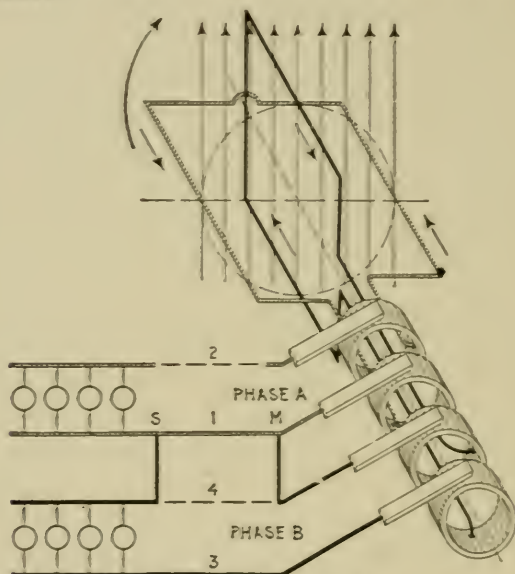


**FIG. 1,256** — Diagram of three wire two phase current distribution. In order to save one wire it is possible to use a common return conductor for both circuits, as shown, the dotted portion of one wire 4 being eliminated by connecting across to 1 at M and S. For long lines this is economical, but the interconnection of the circuits increases the chance of trouble from grounds or short circuits. The current in the conductor will be the resultant of the two currents, differing by  $90^\circ$  in phase.

**Ans.** A two phase system requires four lines for its distribution; two lines for each phase as in fig. 1,253. It is possible, but not advisable, to reduce the number to 3, by employing one rather thicker line as a common return for each of the phases as in fig. 1,256.

If this be done, the voltage between the A line and the B line will be equal to  $\sqrt{2}$  times the voltage in either phase, and the current in the line used as common return will be  $\sqrt{2}$  times as great as the current in either line, assuming the two currents in the two phases to be equal.

**Ques.** In what other way may two phase current be distributed?

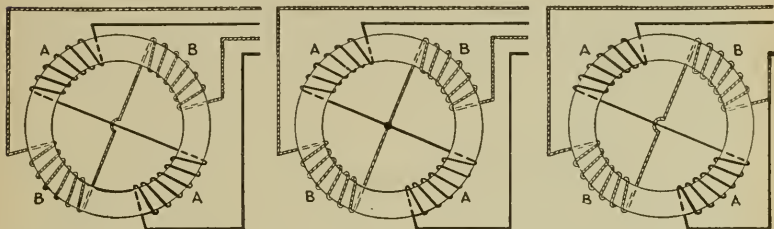**Ans.** The mid point of the windings of the two phases may be united in the alternator at a common junction.



FIGS. 1,257 to 1,259—Various two phase armature connections. Fig. 1,257, two separate circuit four collector ring arrangement; fig. 1,258, common middle connection, four collector rings; fig. 1,259, circuit connected in armature for three collector rings. In the figures the black winding represents phase A, and the light winding, phase B.

This is equivalent to making the machine into a four phase alternator with half the voltage in each of the four phases, which will then be in successive quadrature with each other.

**Ques.** How are two phase alternator armatures wound?

**Ans.** The two circuits may be separate, each having two collector rings, as shown in fig. 1,257, or the two circuits may be coupled at a common middle as in fig. 1,258, or the two circuits may be coupled in the armature so that only three collector rings are required as shown in fig. 1,259.

**Three Phase Current.**—A three phase current consists of three alternating currents of equal frequency and amplitude, but differing in phase from each other by one-third of a period. Three phase current as represented by sine curves is shown in fig. 1,260, and by hydraulic analogy in fig. 1,262. Inspection of the


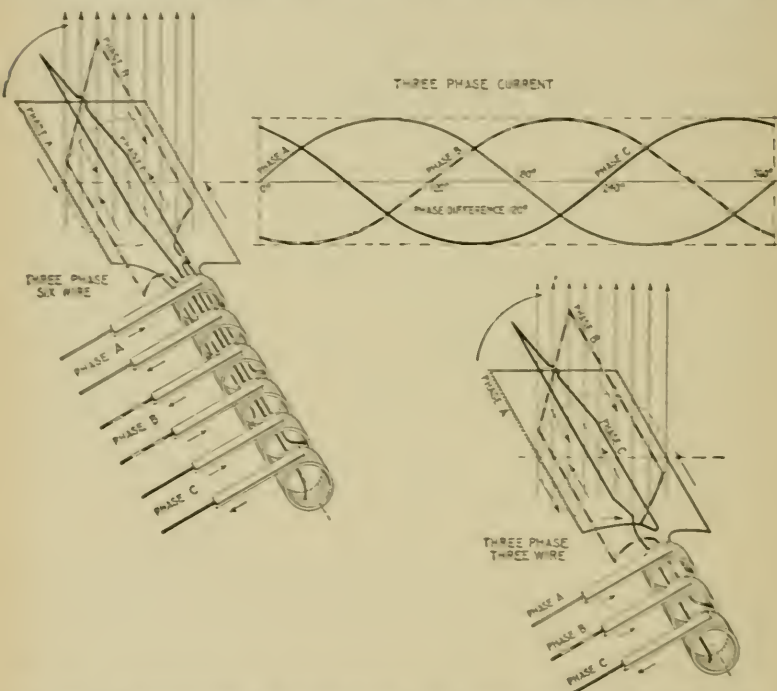
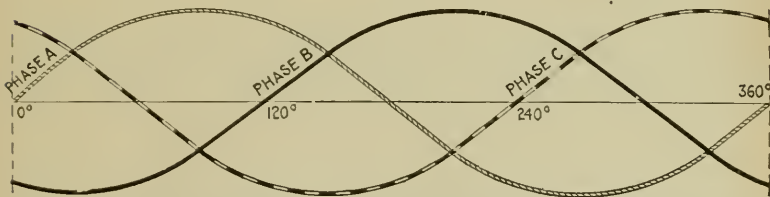


FIG. 1,260.—Elementary three loop alternator and sine curves, illustrating three phase alternating current. If the loops be placed on the alternator armature at 120 magnetic degrees from one another, the current in each will attain its maximum at a point one-third of a cycle distant from the other two. The arrangement here shown gives three independent single phase currents and requires six wires for their transmission. A better arrangement and the one generally used is shown in fig. 1,261.

FIG. 1,261.—Elementary three wire three phase alternator. For the transmission of three phase current, it is not customary to use six wires, as in fig. 1,260, instead, three ends [one end of each of the loops] are brought together to a common connection as shown, and the other ends, connected to the collector rings, giving only three wires for the transmission of the current.

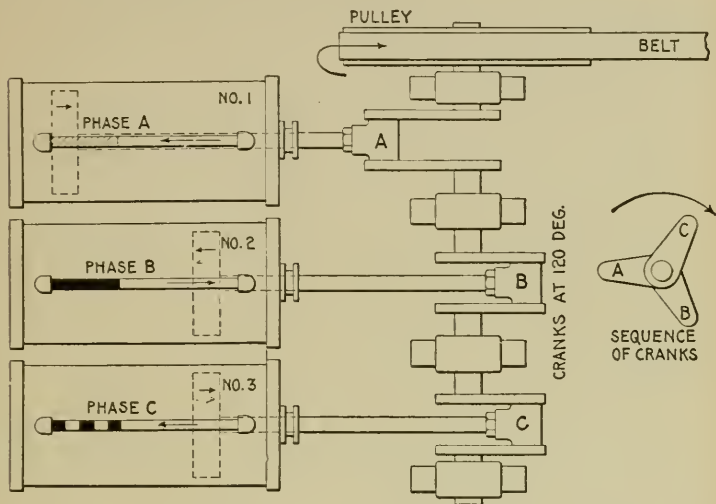figures will show that when any one of the currents is at its maximum, the other two are of half their maximum value, and are flowing in the opposite direction.



FIGS. 1,262 and 1,263.—Hydraulic analogy illustrating three phase alternating current. Three cylinders are here shown with pistons connected through Scotch yokes to cranks placed 120° apart. The same action takes place in each cylinder as in the preceding cases, the only difference being the additional cylinder, and difference in phase relation.

**Ques.** How is three phase current generated?

**Ans** It requires three equal windings on the alternator armature, and they must be spaced out over its surface so as

to be successively  $\frac{1}{3}$  and  $\frac{2}{3}$  of the period (that is, of the double pole pitch) apart from one another.

**Ques.** How many wires are used for three phase distribution?

**Ans.** Either six wires or three wires.

Six wires, as in fig. 1,260, might be used where it is desired to supply entirely independent circuits, or as is more usual only three wires are used as shown in fig. 1,261. In this case it should be observed that if the voltage generated in each one of the three phases separately  $E$  (virtual) volts, the voltage generated between any two of the terminals will be equal to  $\sqrt{3} \times E$ . Thus, if each of the three phases generate 100 volts, the voltage from the terminal of the A phase to that of the B phase will be 173 volts.

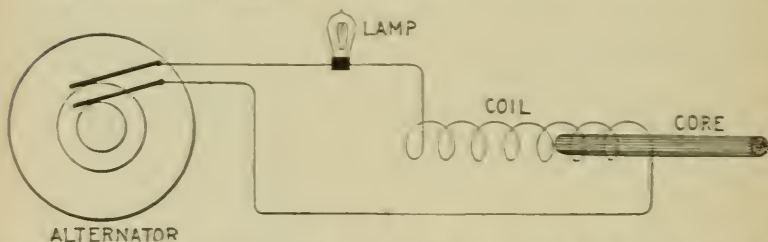


FIG 1,264.—Experiment illustrating self-induction in an alternating current circuit. If an incandescent lamp be connected in series with a coil made of one pound of No. 20 magnet wire, and connected to the circuit, the current through the lamp will be decreased due to the self-induction of the coil. If now an iron core be gradually pushed into the coil, the self-induction will be greatly increased and the lamp will glow thus showing the great importance which self-induction plays in alternating current work.

**Inductance.**—Each time a direct current is started, stopped or varied in strength, the magnetism changes, and induces or tends to induce a pressure in the wire which always has a direction opposing the pressure which originally produced the current. *This self-induced pressure tends to weaken the main current at the start and prolong it when the circuit is opened.*

The expression *inductance* is frequently used in the same sense as *coefficient of self-induction*, which is a quantity pertaining to an electric

circuit depending on its geometrical form and the nature of the surrounding medium.

If the direct current maintain the same strength and flow steadily, *there will be no variations in the magnetic field surrounding the wire and no self-induction*, consequently the only retarding effect of the current will be the "*ohmic resistance*" of the wire.

If an alternating current be sent through a circuit, there will be two retarding effects:

1. The *ohmic* resistance;
2. The *spurious* resistance.

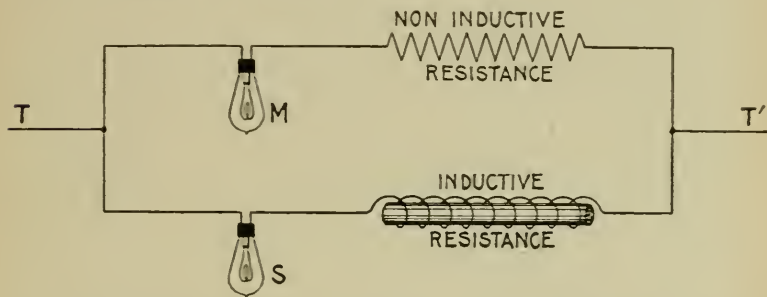


FIG. 1.265.—Non-inductive and inductive resistances. Two currents are shown joined in parallel, one containing a lamp and non-inductive resistance, and the other a lamp and inductive resistance. The two resistances being the same, a sufficient direct pressure applied at T, T' will cause the lamps to light up equally. If, however, an alternating pressure be applied, M will burn brightly, while S will give very little or no light because of the effect of the inductance of the inductive resistance.

**Ques.** Upon what does the ohmic resistance depend?

**Ans.** Upon the length, cross sectional area and material of the wire.

**Ques.** Upon what does the spurious resistance depend?

**Ans.** Upon the frequency of the alternating current, the shape of the conductor, and nature of the surrounding medium.



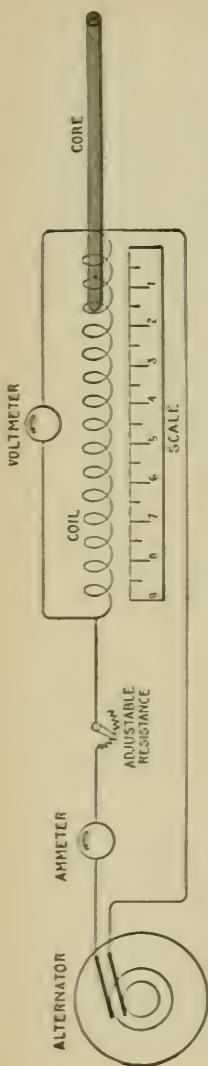


FIG. 1,266. — Inductance test, illustrating the self-induction of a coil which is gradually increased by moving an iron wire core inch by inch into the coil. The current is kept constant with the adjustable resistance throughout the test and readings taken, first without the iron core, and again when the core is put in the coil and moved to the 1, 2, 3, 4, etc., inch marks. By plotting the voltmeter readings and the position of the iron core on section paper, a curve is obtained showing graphically the effect of the self-induction. A curve of this kind is shown in fig. 1,302.

### Ques. Define inductance.

Ans. It is the total magnetic flux threading the circuit per unit current which flows in the circuit, and which produces the flux.

In this it must be understood that if any portion of the flux thread the circuit more than once, this portion must be added in as many times as it makes linkage.

Inductance, or the coefficient of self-induction is the capacity which an electric circuit has of producing induction within itself.

Inductance is considered as the ratio between the total induction through a circuit to the current producing it.

### Ques. What is the unit of inductance?

Ans. The henry.

### Ques. Define the henry.

Ans. A coil has an inductance of one henry when the product of the number of lines enclosed by the coil multiplied by the number of turns in the coil, when a current of one ampere is flowing in the coil, is equal to 100,000,000 or  $10^8$ .

An inductance of one henry exists in a circuit when a current changing at the rate of one ampere per second induces a pressure of one volt in the circuit.


# **Ques. What is the henry called?**

**Ans.** The coefficient of self-induction.

The henry is the coefficient by which the time rate of change of the current in the circuit must be multiplied, in order to give the pressure of self-induction in the circuit.

The formula for the henry is as follows:

$$\text{henrys} = \frac{\text{magnetic flux} \times \text{turns}}{\text{current} \times 100,000,000}$$

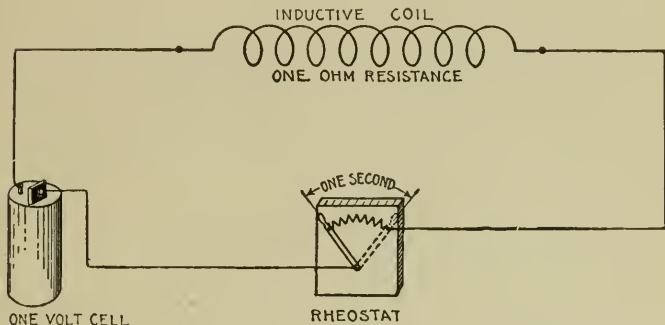

**FIG. 1,267.**—Diagram illustrating the henry. By definition: *A circuit has an inductance of one henry when a rate of change of current of one ampere per second induces a pressure of one volt.* In the diagram it is assumed that the internal resistance of the cell and resistance of the connecting wires are zero.

or

$$L = \frac{N \times T}{10^8} \dots \dots \dots (1)$$

where



L = coefficient of self induction in henrys;

N = total number of lines of force threading a coil when the current is one ampere;

T = number of turns of coil.

If a coil had a coefficient of self-induction of one henry, it would mean that if the coil had one turn, one ampere would set up 100,000,000, or  $10^8$ , lines through it.

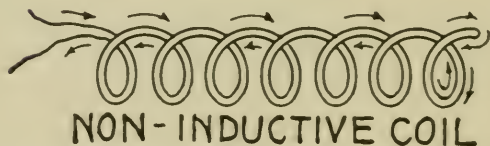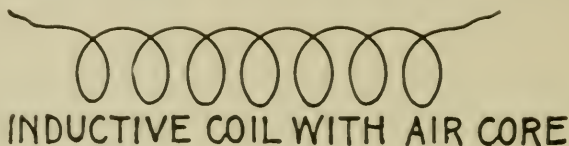The henry is too large a unit for use in practical computations, which involves that the millihenry, or  $\frac{1}{1,000}$ th henry, is the accepted unit. In pole suspended lines the



FIGS. 1,268 to 1,270.—Various coils. The inductance effect, though perceptible in an air core coil, fig. 1,268, may be greatly intensified by inserting a core made of numerous pieces of iron wire, as in fig. 1,269. Fig. 1,270 shows a non-inductive coil. When wound in this manner, a coil will have little or no inductance because each half of the coil neutralizes the magnetic effect of the other. This coil, though non-inductive, will have "capacity." It would be useless for solenoids or electro-magnets, as it would have no magnetic field.

NOTE.—The American physicist, Joseph Henry, was born in 1798 and died 1878. He was noted for his researches in electromagnetism. He developed the electromagnet, which had been invented by Sturgeon in England, so that it became an instrument of far greater power than before. In 1831, he employed a mile of fine copper wire with an electromagnet, causing the current to attract the armature and strike a bell, thereby establishing the principle employed in modern telegraph practice. He was made a professor at Princeton in 1832, and while experimenting at that time, he devised an arrangement of batteries and electromagnets embodying the principle of the telegraph relay which made possible long distance transmission. He was the first to observe magnetic self-induction, and performed important investigations in oscillating electric discharges (1842), and other electrical phenomena. In 1846 he was chosen secretary of the Smithsonian Institution at Washington, an office which he held until his death. As chairman of the U. S. Lighthouse Board, he made important tests in marine signals and lights. In meteorology, terrestrial magnetism, and acoustics, he carried on important researches. Henry enjoyed an international reputation, and is acknowledged to be one of America's greatest scientists.

inductance varies as the metallic resistance, the distance between the wires on the cross arm and the number of cycles per second, as indicated by accepted tables. Thus, for one mile of No. 8 B. & S. copper wire, with a resistance of 3,406 ohms, the coefficient of self-induction with 6 inches between centers is .00153, and, with 12 inches, .00175.

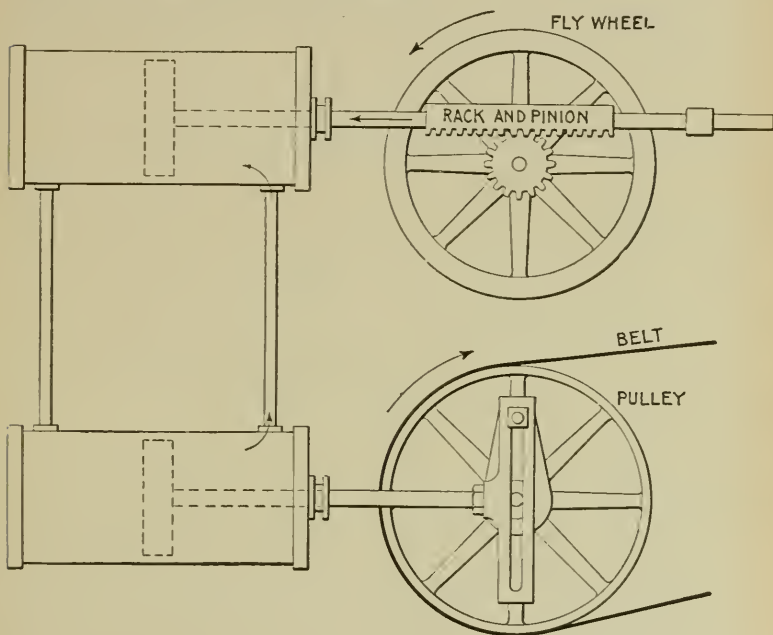


FIG. 1,271.—Hydraulic-mechanical analogy illustrating *inductance* in an alternating current circuit. The two cylinders are connected at their ends by the vertical pipes, each being provided with a piston and the system filled with water. Reciprocating motion is imparted to the lower pulley by Scotch yoke connection with the drive pulley. The upper piston is connected by rack and pinion gear with a fly wheel. In operation, the to and fro movement of the lower piston produces an alternating flow of water in the upper cylinder which causes the upper piston to move back and forth. The rack and pinion connection with the fly wheel causes the latter to revolve first in one direction, then in the other, in step with the upper piston. The inertia of the fly wheel causes it to resist any change in its state, whether it be at rest or in motion, which is transmitted to the upper piston, causing it to offer resistance to any change in its rate or direction of motion. Inductance in the alternating current circuit has precisely the same effect, that is, it *opposes any change in the strength or direction of the current*.

**Ques.** How does the inductance of a coil vary with respect to the core?

**Ans.** It is least with an air core; with an iron core, it is greater in proportion to the permeability\* of the iron.

The coefficient  $L$  for a given coil is a constant quantity so long as the magnetic permeability of the material surrounding the coil does not change. This is the case where the coil is surrounded by air. When iron is present, the coefficient  $L$  is practically constant, provided the magnetism is not forced too high.

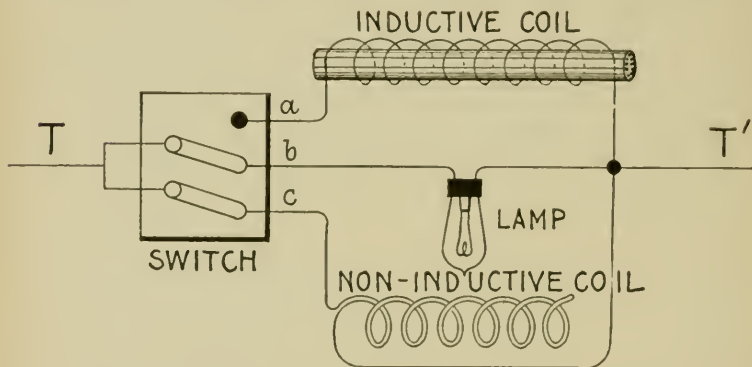


FIG. 1,272.—Experiment showing effect of inductive and non-inductive coils in alternating current circuit. The apparatus is connected up as shown; by means of the switch, the lamp may be placed in parallel with either the inductive or non-inductive coil. These coils should have the same resistance. Pass an alternating current through the lamp and non-inductive coil, of such strength that the lamp will be dimly lighted. Now turn the switch so as to put the lamp and inductive coil in parallel and the lamp will burn with increased brilliancy. The reason for this is because of the opposition offered by the inductive coil to the current, less current is shunted from the lamp when the inductive coil is in the circuit than when the non-inductive coil is in the circuit. That is, each coil has the same ohmic resistance, but the inductive coil has in addition the spurious resistance due to inductance, hence it shunts less current from the lamp than does the non-inductive coil.

In most cases arising in practice, the coefficient  $L$  may be considered to be a constant quantity, just as the resistance  $R$  is usually considered constant. The coefficient  $L$  of a coil or circuit is often spoken of as its *inductance*.

\* NOTE.—The permeability of iron varies from 500 to 1,000 or more. The permeability of a given sample of iron is not constant, but decreases in value as the magnetizing force increases. Therefore the inductance of a coil having an iron core is not a constant quantity as is the inductance of an air core coil.

**Ques.** Why is the iron core of an inductive coil made with a number of small wires instead of one large rod?

**Ans.** It is laminated in order to reduce eddy currents and consequent loss of energy, and to prevent excessive heating of the core.

**Ques.** How does the number of turns of a coil affect the inductance?

**Ans.** The inductance varies as the square of the turns.

That is, if the turns be doubled, the inductance becomes four times as great.

The inductance of a coil is easily calculated from the following formulæ:

$$L = 4\pi^2 r^2 n^2 \div (l \times 10^9) \dots\dots\dots (1)$$

for a thin coil with air core, and

$$L = 4\pi^2 r^2 n^2 \mu \div (l \times 10^9) \dots\dots\dots (2)$$

for a coil having an iron core. In the above formulæ:

$L$  = inductance in henrys;

$\pi$  = 3.1416;

$r$  = average radius of coil in centimeters;

$n$  = number of turns of wire in coil;

$\mu$  = permeability of iron core;

$l$  = length of coil in centimeters.


**EXAMPLE.**—An air core coil has an average radius of 10 centimeters and is 20 centimeters long, there being 500 turns, what is the inductance?

Substituting these values in formula (1)

$$L = 4 \times (3.1416)^2 \times 10^2 \times 500^2 \div (20 \times 10^9) = .00494 \text{ henry}$$

**Ques.** Is the answer in the above example in the customary form?

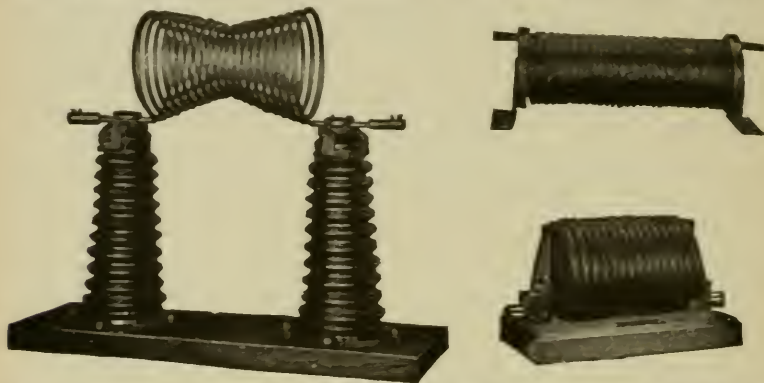**Ans.** No; the henry being a very large unit, it is usual to express inductance in thousandths of a henry, that is, in *milli-henrys*. The answer then would be  $.04935 \times 1,000 = 49.35$  milli-henrys.



**FIGS. 1,273 TO 1,275.**—General Electric choke coils. Fig 1,273, hour glass coil, 35,000 volts; fig. 1,274, 4,600 volt coil; fig. 1,275, 6,600 volt coil. A choke coil is a coil with large inductance and small resistance, used to impede alternating currents. The choke coil is used extensively as an auxiliary to the lightning arrester. In this connection the primary objects of the choke coil should be: 1, to hold back the lightning disturbance from the transformer or generator until the lightning arrester discharges to earth. If there be no lightning arrester the choke coil evidently cannot perform this function. 2, to lower the frequency of the oscillation so that whatever charge gets through the choke coil will be of a frequency too low to cause a serious drop of pressure around the first turns of the end coil in either generator or transformer. Another way of expressing this is from the standpoint of wave front: a steep wave front piles up the pressure when it meets an inductance. The second function of the choke coil is, then, to smooth out the wave front of the surge. The principal electrical condition to be avoided is that of resonance. The coil should be so arranged that if continual surges be set up in the circuit, a resonant voltage due to the presence of the choke coil cannot build up at the transformer or generator terminals. In the types shown above, the hour glass coil has the following advantages on high voltages: 1, should there be any arcing between adjacent turns the coils will reinsulate themselves, 2, they are mechanically strong, and sagging is prevented by tapering the coils toward the center turns, 3, the insulating supports can be best designed for the strains which they have to withstand. Choke coils should not be used in connection with cable systems.

**EXAMPLE.**—An air core coil has an inductance of 50 milli-henrys; if an iron core, having a permeability of 600 be inserted, what is the inductance?

The inductance of the air core coil will be multiplied by the permeability of the iron; the inductance then is increased to

$$50 \times 600 = 30,000 \text{ milli-henrys, or } 30 \text{ henrys.}$$



**Ohmic Value of Inductance.**—The rate of change of an alternating current at any point expressed in degrees is equal to the product of  $2\pi$  multiplied by the frequency, the maximum current, and the cosine of the angle of position  $\theta$ ; that is (using symbols)

$$\text{rate of change} = 2\pi f I_{\max} \cos \theta.$$

The numerical value of the rate of change is independent of its positive or negative sign, so that the sign of the  $\cos \phi$  is disregarded.

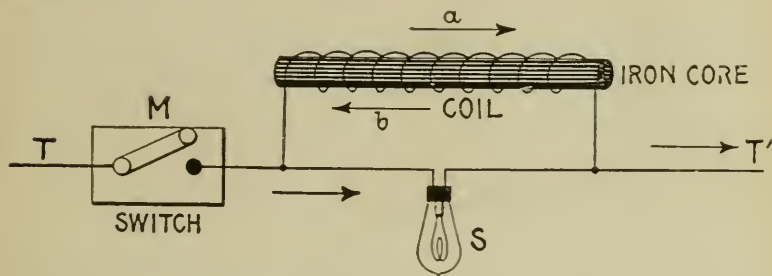


FIG. 1,276.—Inductance experiment with intermittent direct current. A lamp S is connected in parallel with a coil of fairly fine wire having a removable iron core, and the terminals T, T' connected to a source of direct current, a switch M being provided to interrupt the current. The voltage of the current and resistance of the coil are of such values that when a steady current is flowing, the lamp filament is just perceptibly red. *At the instant of making the circuit, the lamp will momentarily glow more brightly than when the current is steady; on breaking the circuit the lamp will momentarily flash with great brightness.* In the first case, the reverse pressure, due to inductance, as indicated by arrow b, will momentarily oppose the normal pressure in the coil, so that the voltage at the lamp will be momentarily increased, and will consequently send a momentarily stronger current through the lamp. On breaking the main circuit at M, the field of the coil will collapse, generating a momentary much greater voltage than in the first instance, in the direction of arrow a, the lamp will flash up brightly in consequence.

The period of greatest rate of change is that at which  $\cos \phi$  has the greatest value, and the maximum value of a cosine is when the arc has a value of zero degrees or of 180 degrees, its value corresponding, being 1. (See fig. 1,037, page 1,068.)

The pressure due to inductance is equal to the product of the rate of change by the inductance; that is, calling the inductance L,

the pressure due to it at the point of maximum value or

$$E_{\max} = 2 \pi f I_{\max} \times L \dots \dots \dots (1)$$

Now by Ohm's law

$$E_{\max} = R I_{\max} \dots \dots \dots (2)$$

for a current  $I_{\max}$ , hence substituting equation (2) in equation (1)

$$R I_{\max} = 2 \pi f I_{\max} \times L$$

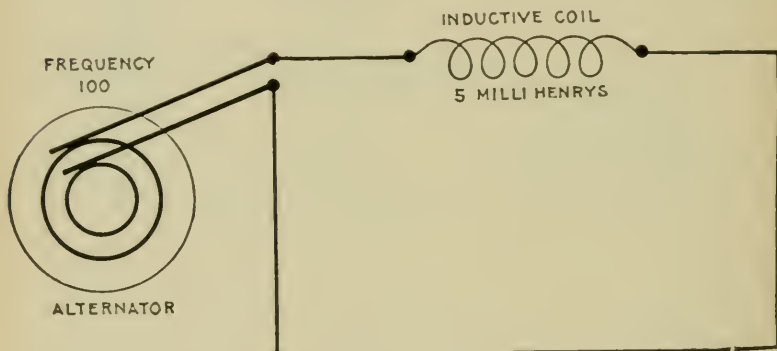


FIG. 1.277.—Diagram showing alternating circuit containing inductance. Formula for calculating the ohmic value of inductance or "inductance reactance," is  $X_i = 2 \pi f L$  in which  $X_i$  = inductance reactance;  $\pi = 3.1416$ ;  $f$  = frequency;  $L$  = inductance in henrys (not millihenrys).  $L = 15$  millihenrys =  $15 \div 1000 = .015$  henrys. Substituting,  $X_i = 2 \times 3.1416 \times 100 \times .015 = 9.42$  ohms.

from which, dividing both sides by  $I_{\max}$ , and using  $X_i$  for  $R$

$$X_i = 2 \pi f L \dots \dots \dots (3)$$

which is the ohmic equivalent of inductance.

The frequency of a current being the number of periods or waves per second, then, if  $T$  = the time of a period, the frequency

of a current may be obtained by dividing 1 second by the time of a period; that is

$$\text{frequency} = \frac{\text{one second}}{\text{time of one period}} = \frac{1}{T} \dots\dots\dots (4)$$

substituting  $\frac{1}{T}$  for  $f$  in equation (3)

$$X_c = 2 \pi \frac{L}{T}$$

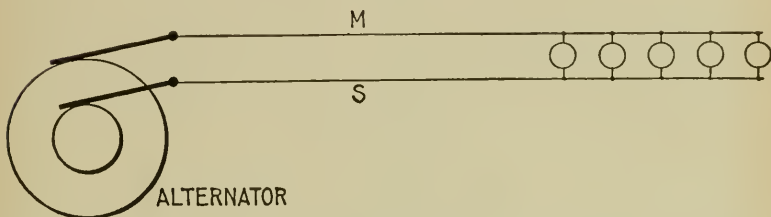


FIG. 1,278.—Diagram illustrating effect of capacity in an alternating circuit. Considering its action during one cycle of the current, the alternator first "pumps," say from M to S; electricity will be heaped up, so to speak, on S, and a deficit left on M, that is, S will be + and M -. If the alternator be now suddenly stopped, there would be a momentary return flow of electricity from S to M through the alternator. If the alternator go on working, however, it is obvious that the electricity heaped up on S helps or increases the flow when the alternator begins to pump from S to M in the second half of the cycle, and when the alternator again reverses its pressure, the + charge on M flows round to S, and helps the ordinary current. The above circuit is not strictly analogous to the insulated plates of a condenser, but, as is verified in practice, that with a rapidly alternating pressure, the condenser action is not perceptibly affected if the cables be connected across by some non-inductive resistance as for instance incandescent lamps.

**Capacity.**—When an electric pressure is applied to a condenser, the current plays in and out, charging the condenser in alternate directions. As the current runs in at one side and out at the other, the dielectric becomes charged, and tries to discharge itself by setting up an opposing electric pressure. This opposing pressure rises just as the charge increases.

A mechanical analogue is afforded by the bending of a spring, as in fig. 1,279, which, as it is being bent, exerts an opposing force

equal to that applied, provided the latter do not exceed the capacity of the spring.

**Ques.** What is the effect of capacity in an alternating circuit?

**Ans.** It is exactly opposite to that of inductance, that is, it assists the current to rise to its maximum value sooner than it would otherwise.

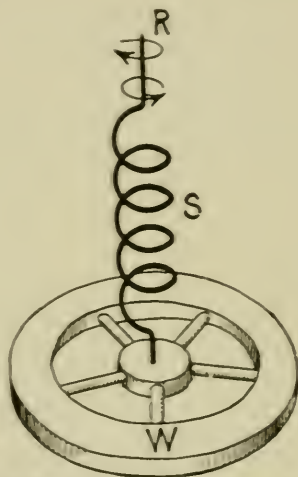


FIG. 1,279.—Mechanical analogy illustrating effect of capacity in an alternating circuit. If an alternating twisting force be applied to the top R of the spring S, the action of the latter may be taken to represent capacity, and the rotation of the wheel W, alternating current. The twisting force (impressed pressure) must first be applied *before* the rotation of W (current) will begin. The resiliency or rebounding effect of the spring will, in time, cause the wheel W to move (amperes) in advance of the twisting force (voltage), thus representing the current leading in phase.

**Ques.** Is it necessary to have a continuous metallic circuit for an alternating current?

**Ans.** No, it is possible for an alternating current to flow through a circuit which is divided at some point by insulating material.

**Ques.** How can the current flow under such condition?

**Ans.** Its flow depends on the capacity of the circuit and accordingly a condenser may be inserted in the circuit as in fig. 1,286, thus interposing an insulated gap, yet permitting an alternating flow in the metallic portion of the circuit.

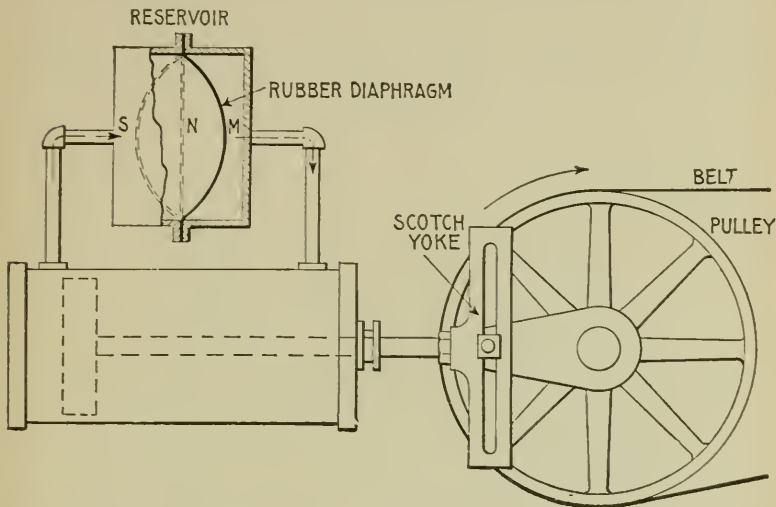


FIG. 1,280.—Hydraulic analogy illustrating capacity in an alternating current circuit. A chamber containing a rubber diaphragm is connected to a double acting cylinder and the system filled with water. In operation, as the piston moves, say to the left from the center, the diaphragm is displaced from its neutral position N, and stretched to some position M, in so doing offering increasing resistance to the flow of water. On the return stroke the flow is reversed and is assisted by the diaphragm during the first half of the stroke, and opposed during the second half. The diaphragm thus acts with the flow of water one-half of the time and in opposition to it one-half of the time. This corresponds to the electrical pressure at the terminals of a condenser connected in an alternating current circuit, and it has a maximum value when the current is zero and a zero value when the current is a maximum.

**Ques.** Name the unit of capacity and define it.

**Ans.** The unit of capacity is called the *farad* and its symbol is C. A condenser is said to have a capacity of one farad if one coulomb (that is, one ampere flowing one second), when stored

on the plates of the condenser will cause a pressure of one volt across its terminals.

The farad being a very large unit, the capacities ordinarily encountered in practice are expressed in millionths of a farad, that is, in *microfarads*—a capacity equal to about three miles of an Atlantic cable.

It should be noted that the microfarad is used only for convenience, and that in working out problems, capacity should always be expressed in farads before substituting in formulæ,

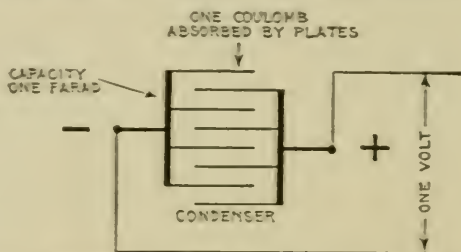


FIG. 1281—Diagram illustrating a farad. A condenser is said to have a capacity of one farad if it will absorb one coulomb of electricity when subjected to a pressure of one volt. The farad is a very large unit, and accordingly the microfarad or one millionth of a farad is often used, though this must be reduced to farads before substituting in formulæ.

because the farad is chosen with respect to the volt and ampere, as above defined, and hence must be used in formulæ along with these units.

For instance, a capacity of 8 microfarads as given in a problem would be substituted in a formula as .000008 of a farad.

The charge  $Q$  forced into a condenser by a steady electric pressure  $E$  is

$$Q = E C$$

in which

$Q$  = charge in coulombs.

$E$  = electric pressure in volts;

$C$  = capacity of condenser in farads;

**Ques.** What is the material between the plates of a condenser called?

**Ans.** The *dielectric*.

**Ques.** Upon what does the capacity of a condenser depend?

**Ans.** It is proportional to the area of the plates, and inversely proportional to the thickness of the dielectric between the plates, a correction being required unless the thickness of dielectric be very small as compared with the dimensions of the plates.

The capacity of a condenser is also proportional to the *specific inductive capacity* of the dielectric between the plates of the condenser.

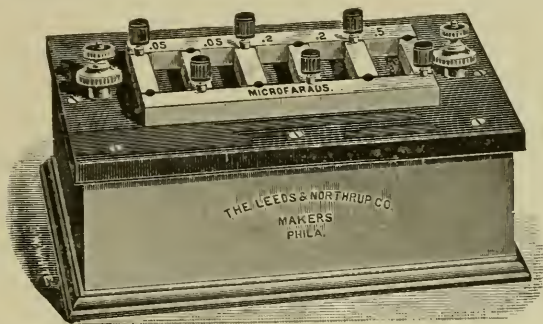


FIG. 1,282.—Condenser of one microfarad capacity. It is subdivided into five sections of .5, .2, .2, .05 and .05 microfarad. The plates are mounted between and carried by lateral brass bars which are fastened to a hard rubber top. Each pair of condenser terminals is fastened to small binding posts mounted on hard rubber insulated posts.

**Specific Inductive Capacity.**—Faraday discovered that different substances have different powers of carrying lines of electric force. Thus the charge of two conductors having a given difference of pressure between them depends on the medium between them as well as on their size and shape. The number indicating the magnitude of this property of the medium is called its *specific inductive capacity*, or *dielectric constant*.



The specific inductive capacity of air, which is nearly the same as that of a vacuum, is taken as unity. In terms of this unit the following are some typical values of the dielectric constant: Water 80, glass 6 to 10, mica 6.7, gutta percha 3, india rubber 2.5, paraffin wax, 2, ebonite 2.5, castor oil 4.8.

In underground cables for very high pressures, the insulation, if homogeneous throughout, would have to be of very great thickness in order to have sufficient dielectric strength. By employing material of high specific inductive capacity close to the conductor, and material of lower specific inductive capacity toward the outside, that is, by *grading* the insulation, a considerably less total thickness affords equally high dielectric strength.

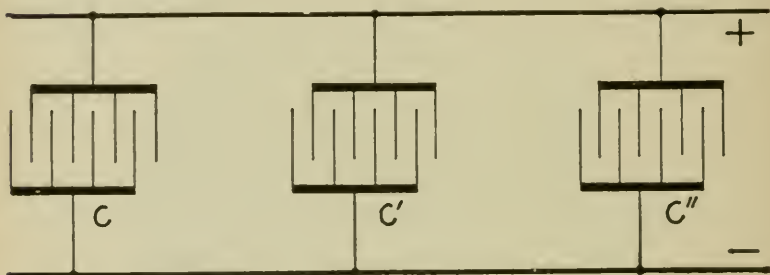


FIG. 1,283.—Parallel connection of condensers. Like terminals are joined together. The joint capacity of such arrangement is equal to the sum of the respective capacities, that is  $C = c + c' + c''$ .

**Ques.** How are capacity tests usually made?

**Ans.** By the aid of standard condensers.

**Ques.** How are condensers connected?

**Ans.** They may be connected in parallel as in fig. 1,283, or in series (cascade) as in fig. 1,284.

Condensers are now constructed so that the two methods of arranging the plates may conveniently be combined in one condenser, thereby obtaining a wider range of capacity.

**Ques.** How may the capacity of a condenser, wire, or cable be tested?

**Ans.** This may be done by the aid of a standard condenser, trigger key, and an astatic or ballistic galvanometer.

In making the test, first obtain a "constant" by noting the deflection  $d$ , due to the discharge of the standard condenser after a charge of, say, 10 seconds from a given voltage. Then discharge the other condenser, wire, or cable through the galvanometer after 10 seconds charge, and note the deflection  $d'$ . The capacity  $C'$  of the latter is then

$$C' = C \times \frac{d'}{d}$$

in which  $C$  is the capacity of the standard condenser.

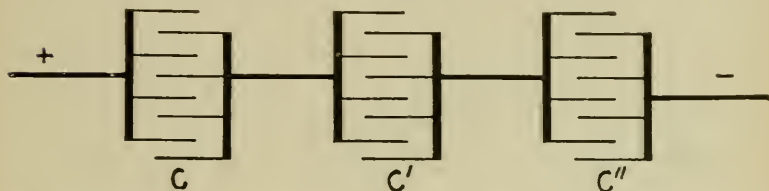



FIG. 1,284.—Series or cascade connection of condensers. Unlike terminals are joined together as shown. The total capacity of such connection is equal to the reciprocal of the sum of the reciprocals of the several capacities, that is,  $C = 1 \div \left( \frac{1}{C} + \frac{1}{C'} + \frac{1}{C''} \right)$

**Ohmic Value of Capacity.**—The capacity of an alternating current circuit is the measure of the amount of electricity held by it when its terminals are at unit difference of pressure. Every such circuit acts as a condenser.

If an alternating circuit, having no capacity, be opened, no current can be produced in it, but if there be capacity at the break, current may be produced as in fig. 1,286.

The action of capacity referred to the current wave is as follows: As the wave starts from zero value and rises to its maximum value, the current is due to the discharge of the

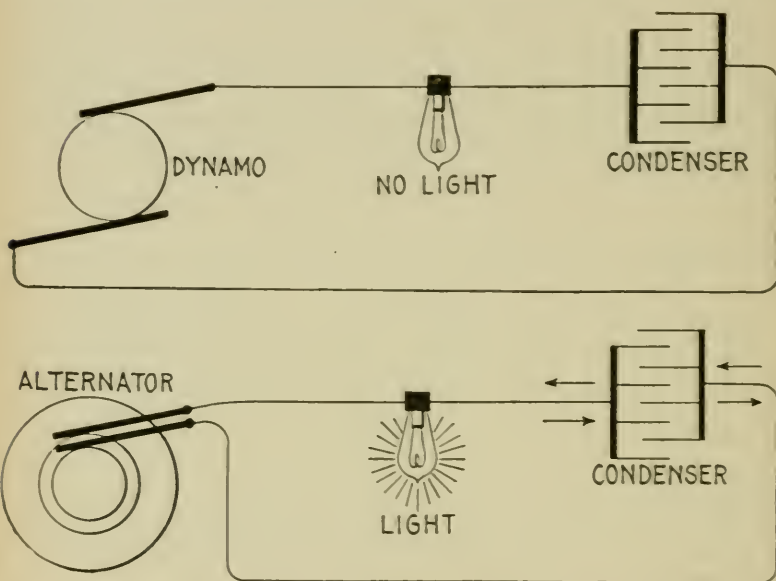capacity, which would be represented by a condenser. In the case of a sine current, the period required for the current to pass from zero value to maximum is one-quarter of a cycle.



FIGS. 1,285 and 1,286.—Diagrams showing effect of condenser in direct and alternating current circuits. Each circuit contains an incandescent lamp and a condenser, one circuit connected to a dynamo and the other to an alternator. Since the condenser interposes a gap in the circuit, evidently in fig. 1,285 no current will flow. In the case of alternating current, fig. 1,286, the condenser gap does not hinder the flow of current in the metallic portion of the circuit. In fact the alternator produces a continual surging of electricity backwards and forwards from the plates of the condenser around the metallic portion of the circuit, similar to the surging of waves against a bulkhead which projects into the ocean. It should be understood that the electric current ceases at the condenser, there being no flow between the plates.

At the beginning of the cycle, the condenser is charged to the maximum amount it receives in the operation of the circuit.

At the end of the quarter cycle when the current is of maximum value, the condenser is completely discharged.

The condenser now begins to receive a charge, and continues to receive it during the next quarter of a cycle, the charge attaining its maximum value when the current is of zero intensity. Hence, the *maximum charge of a condenser* in an alternating circuit is equal to the average value of the current multiplied by the time of charge, which is one-quarter of a period, that is

$$\text{maximum charge} = \text{average current} \times \frac{1}{4} \text{ period} \dots\dots (1)$$

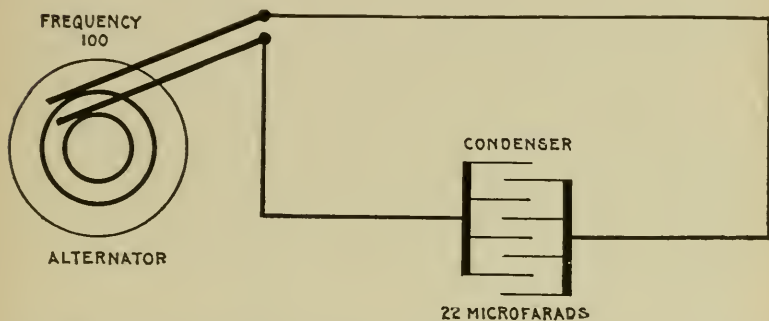


FIG. 1,287.—Diagram showing alternating circuit containing capacity. Formula for calculating the ohmic value of capacity or "capacity reactance" is  $X_c = 1 \div 2\pi f C$ , in which  $X_c$  = capacity reactance;  $\pi = 3.1416$ ;  $f$  = frequency;  $C$  = capacity in farads (not microfarads). 22 microfarads =  $22 \div 1,000,000 = .000022$  farad. Substituting,  $X_c = 1 \div (2 \times 3.1416 \times 100 \times .000022) = 72.4$  ohms.

Since the time of a period =  $1 \div \text{frequency}$ , the time of one-quarter of a period is  $\frac{1}{4} \times (1 \div \text{frequency})$ , or

$$\frac{1}{4} \text{ period} = \frac{1}{4} f \dots\dots\dots (2)$$

$f$ , being the symbol for frequency. Substituting (2) in (1)

$$\text{maximum charge} = I_{av} \times \frac{1}{4} f \dots\dots\dots (3)$$

The pressure of a condenser is equal to the quotient of the charge divided by the capacity, that is

$$\text{condenser pressure} = \frac{\text{charge}}{\text{capacity}} \dots\dots\dots (4)$$

Substituting (3) in (4)

$$\text{condenser pressure} = (I_{av} \times \frac{1}{4f}) \div C = \frac{I_{av}}{4fC} \dots\dots (5)$$

But,  $I_{av} = I_{max} \times \frac{2}{\pi}$ , and substituting this value of  $I_{av}$  in equation (5) gives

$$\text{condenser pressure} = \frac{I_{max} \times \frac{2}{\pi}}{4fC} = \frac{I_{max}}{2\pi fC} \dots\dots\dots (6)$$

This last equation (6) represents the condenser pressure due to capacity at the point of maximum value, which pressure is opposed to the impressed pressure, that is, it is the maximum reverse pressure due to capacity.

Now, since by Ohm's law

$$I = \frac{E}{R}, \text{ or } E = I \times R$$

and as

$$\frac{I_{max}}{2\pi fC} = I_{max} \times \frac{1}{2\pi fC}$$

it follows that  $\frac{1}{2\pi fC}$  is the *ohmic value* of capacity, that

is it expresses the resistance equivalent of capacity; using the symbol  $X_c$  for capacity reactance

$$X_c = \frac{1}{2\pi fC} \dots\dots\dots (7)$$

EXAMPLE.—What is the resistance equivalent of a 50 microfarad condenser to an alternating current having a frequency of 100?

Substituting the given values in the expression for ohmic value

$$X_c = \frac{1}{2\pi fC} = \frac{1}{2 \times 3.1416 \times 100 \times .000050} = \frac{1}{.031416} = 31.8 \text{ ohms.}$$

If the pressure of the supply be, say 100 volts, the current would be  $100 \div 31.8 = 3.14$  amperes.

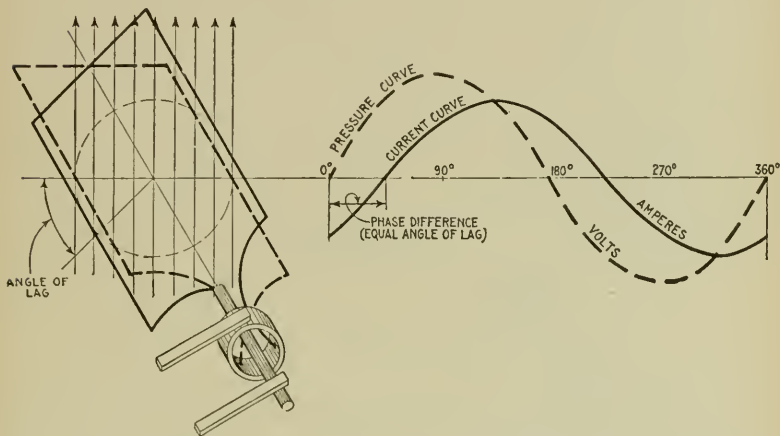


FIG. 1,288.—Pressure and current curves, illustrating *lag*. The effect of inductance in a circuit is to retard the current cycle, that is to say, if the current and pressure be in phase, the introduction of inductance will cause a phase difference, the current wave “lagging” behind the pressure wave as shown. In other words, inductance causes the current wave, indicated in the diagram by the solid curve, to lag behind the pressure wave, indicated by the dotted curve. Following the curves starting from the left end of the horizontal line, it will be noted that the current starts after the pressure starts and reverses after the pressure reverses; that is, the *current lags in phase behind the pressure*, although the frequency of both is the same.

**Lag and Lead.**—Alternating currents do not always keep in step with the alternating volts impressed upon the circuit. If there be inductance in the circuit, the current will *lag*; if there be capacity, the current will *lead* in phase. For example, fig. 1,288, illustrates the lag due to inductance and fig. 1,289, the lead due to capacity.

### Ques. What is lag?

Ans. Lag denotes the condition where the phase of one alternating current quantity lags behind that of another. The term is generally used in connection with the effect of inductance in causing the current to lag behind the impressed pressure.

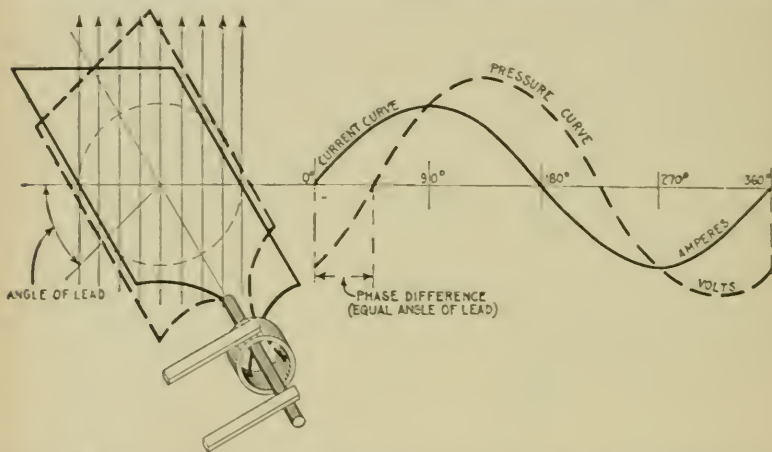


FIG. 1,289.—Pressure and current curves illustrating *lead*. The effect of capacity in a circuit is to cause the current to rise to its maximum value sooner than it would otherwise do; capacity produces an effect exactly the opposite of inductance. The phase relation between current and pressure with current leading is shown graphically by the two armature positions in full and dotted lines, corresponding respectively to current and pressure at the beginning of the cycle.

### Ques. How does inductance cause the current to lag behind the pressure?

Ans. It tends to prevent changes in the strength of the current. When two parts of a circuit are near each other, so that one is in the magnetic field of the other, any change in the strength of the current causes a corresponding change in the magnetic field and sets up a reverse pressure in the other wire.

This induced pressure causes the current to reach its maximum value a little later than the pressure, and also tends to prevent the current diminishing in step with the pressure.



**Ques.** What governs the amount of lag in an alternating current?

**Ans.** It depends on the relative values of the various pressures in the circuit, that is, upon the amount of resistance and inductance which tends to cause lag, and the amount of capacity in the circuit which tends to reduce lag and cause lead.

**Ques.** How is lag measured?

**Ans.** In degrees.

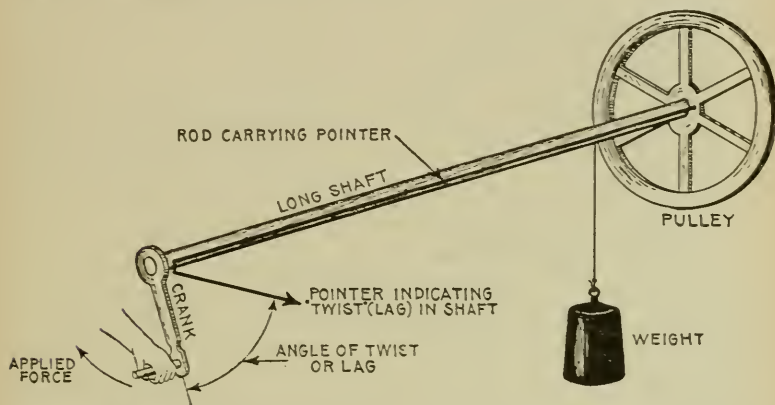


FIG. 1,290.—Mechanical analogy of lag. If at one end force be applied to turn a very long shaft, having a loaded pulley at the other, the torsion thus produced in the shaft will cause it to twist an appreciable amount which will cause the movement of the pulley to lag behind that of the crank. This may be indicated by a rod attached to the pulley and terminating in a pointer at the crank end, the rod being so placed that the pointer registers with the crank when there is no torsion in the shaft. The angle made by the pointer and crank when the load is thrown on, indicates the amount of lag which is measured in degrees.

Thus, in fig. 1,288, the lag is indicated by the distance between the beginning of the pressure curve and the beginning of the current curve, and is in this case  $45^\circ$ .

**Ques.** What is the physical meaning of this?

**Ans.** In an actual alternator, of which fig. 1,288 is an elementary diagram showing one coil, if the current lag, say  $45^\circ$

behind the pressure, it means that the coil rotates  $45^\circ$  from its position of zero induction before the current starts, as in fig. 1,288.

EXAMPLE I.—A circuit through which an alternating current is passing has an inductance of 6 ohms and a resistance of 2.5 ohms. What is the angle of lag?

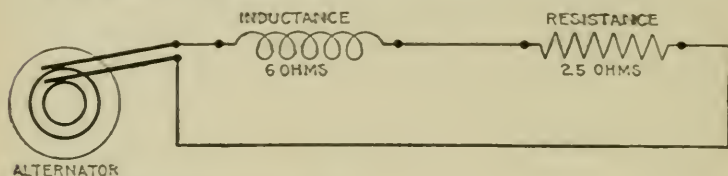


FIG. 1,291.—Diagram of circuit for example I.

Substituting these values in equation (1), page 1,053,

$$\tan \phi = \frac{6}{2.5} = 2.4$$

Referring to the table of natural sines and tangents on page 451 the corresponding angle is approximately  $67^\circ$ .

EXAMPLE II.—A circuit has a resistance of 2.3 ohms and an inductance of .0034 henry. If an alternating current having a frequency of 125 pass through it, what is the angle of lag?

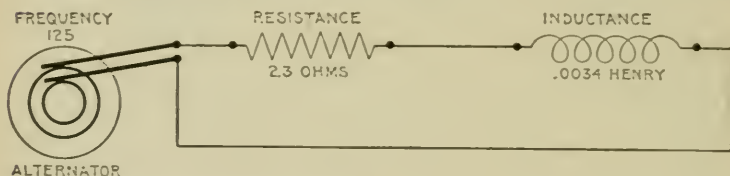


FIG. 1,292.—Diagram of circuit for example II.

Here the inductance is given as a fraction of a henry; this must be reduced to ohms by substituting in equation (3), page 1,038, which gives the ohmic value of the inductance; accordingly, substituting the above given value in this equation

$$\text{inductance in ohms or } X_L = 2 \pi \times 125 \times .0034 = 2.67$$

Substituting this result and the given resistance in equation (1), page 1,053,

$$\tan \phi = \frac{2.67}{2.3} = 1.16$$


the nearest angle from table (page 451) is  $49^\circ$ .

**Ques.** How great may the angle of lag be?

**Ans.** Anything up to  $90^\circ$ .

The angle of lag, indicated by the Greek letter  $\phi$ (phi), is the angle whose tangent is equal to the quotient of the inductance expressed in ohms or "spurious resistance" divided by the ohmic resistance, that is

$$\tan \phi = \frac{\text{reactance}}{\text{resistance}} = \frac{2 \pi f L}{R} \dots\dots\dots (1)$$

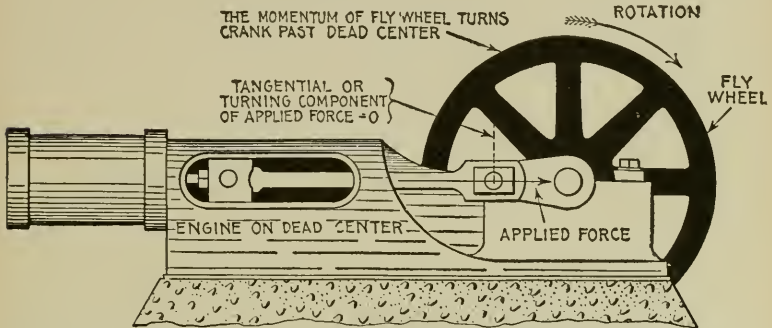

**FIG. 1.293.**—Steam engine analogy of current flow at zero pressure (see questions below). When the engine has reached the dead center point the full steam pressure is acting on the piston, the valve having opened an amount equal to its lead. The force applied at this instant, indicated by the arrow is perpendicular to the crank pin circle, that is, the tangential or *turning* component is equal to zero, hence there is no pressure tending to turn the crank. The latter continues in motion past the dead center because of the momentum previously acquired. Similarly, the electric current, which is here analogous to the moving crank, continues in motion, though the pressure at some instants be zero, because it acts as though it had weight, that is, it cannot be stopped or started instantly.

**Ques.** When an alternating current lags behind the pressure, is there not a considerable current at times when the pressure is zero?

**Ans.** Yes; such effect is illustrated by analogy in fig. 1.293.

**Ques.** What is the significance of this?

**Ans.** It does not mean that current could be obtained from a circuit that showed no pressure when tested with a suitable voltmeter, for no current would flow under such conditions. However, in the flow of an alternating current, the pressure

varies from zero to maximum values many times each second, and the instants of no pressure may be compared to the "dead centers" of an engine at which points there is no pressure to cause rotation of the crank, the crank being carried past these points by the momentum of the fly wheel. Similarly the electric current does not stop at the instant of no pressure because of the "momentum" acquired at other parts of the cycle.

**Ques.** On long lines having considerable inductance, how may the lag be reduced?

**Ans.** By introducing capacity into the circuit. In fact, the current may be advanced so it will be in phase with the pressure or even lead the latter, depending on the amount of capacity introduced.

There has been some objection to the term *lead* as used in describing the effect of capacity in an alternating circuit, principally on the ground that such expressions as "lead of current," "lead in phase," etc., tend to convey the idea that the effect precedes the cause, that is, the current is in advance of the pressure producing it. There can, of course, be no current until pressure has been applied, but if the circuit have capacity, it will lead the pressure, and this peculiar behavior is best illustrated by a mechanical analogy as has already been given.

**Ques.** What effect has lag or lead on the value of the effective current?

**Ans.** As the angle of lag or lead increases, the value of the effective as compared with the virtual current diminishes.

**Reactance.**—The term "reactance" means simply *reaction*. It is used to express certain effects of the alternating current other than that due to the ohmic resistance of the circuit. Thus, *inductance reactance* means the reaction due to the spurious resistance of inductance expressed in ohms; similarly, *capacity reactance*, means the reaction due to capacity, expressed in ohms.

It should be noted that the term *reactance*, alone, that is, unqualified, is generally understood to mean *inductance reactance*, though ill advisedly so.

The resistance offered by a wire to the flow of a direct current is expressed in ohms; this resistance remains constant whether the wire be straight or coiled. If an alternating current flow through the wire, there is in addition to the ordinary or "*ohmic*" resistance of the wire, a "*spurious*" resistance arising from the development of a reverse pressure due to induction, which is

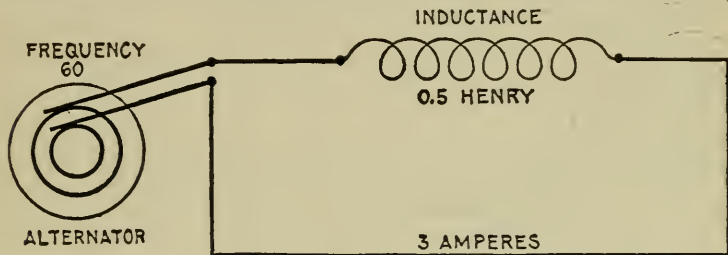


FIG. 1,294—Diagram of the circuit for example I. Here the resistance is taken at zero, but this would not be possible in practice, as all circuits contain more or less resistance though it may be, in some cases, negligibly small.

more or less in value according as the wire be coiled or straight. This *spurious resistance* as distinguished from the *ohmic resistance* is called the *reactance*, and is expressed in ohms.

Reactance, may then be defined with respect to its usual significance, that is, *inductance reactance*, as the component of the impedance which when multiplied into the current, gives the wattless component of the pressure.

Reactance is simply inductance measured in ohms.

EXAMPLE I.—An alternating current having a frequency of 60 is passed through a coil whose inductance is .5 henry. What is the reactance?

Here  $f = 60$  and  $L = .5$ ; substituting these in formula for inductive reactance,

$$X_i = 2 \pi f L = 2 \times 3.1416 \times 60 \times .5 = 188.5 \text{ ohms}$$

The quantity  $2 \pi f L$  or reactance being of the same nature as a resistance is used in the same way as a resistance. Accordingly, since, by Ohm's law

$$E = R I \dots\dots\dots (1)$$

an expression may be obtained for the volts necessary to overcome reactance by substituting in equation (1) the value of reactance given above, thus

$$E = 2 \pi f L I \dots\dots\dots (2)$$

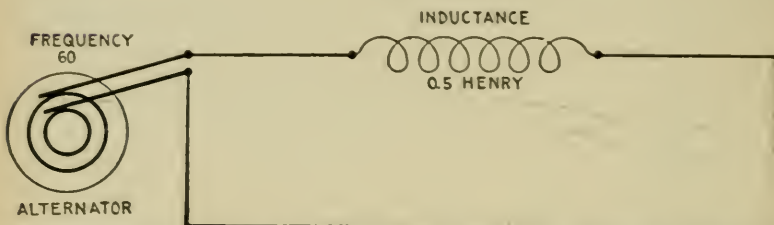


FIG. 1,295.—Diagram of circuit for example II. As in example I, resistance is disregarded.

**EXAMPLE II.**—How many volts are necessary to force a current of 3 amperes with frequency 60 through a coil whose inductance is .5 henry? Substituting in equation (2) the values here given

$$E = 2 \pi f L I = 2 \pi \times 60 \times .5 \times 3 = 565 \text{ volts.}$$

The foregoing example may serve to illustrate the difference in behaviour of direct and alternating currents. As calculated, it requires 565 volts to pass only 3 amperes of alternating current through the coil on account of the considerable spurious resistance. The ohmic resistance of a coil is very small, as compared with the spurious resistance, say 2 ohms. Then by Ohm's law  $I = E \div R = 565 \div 2 = 282.5$  amperes.

Instances of this effect are commonly met with in connection with transformers. Since the primary coil of a transformer has a high reactance, very little current will flow when an alternating pressure is applied. If the same transformer were placed in a direct current circuit



and the current turned on it would at once burn out, as very little resistance would be offered and a large current would pass through the winding.

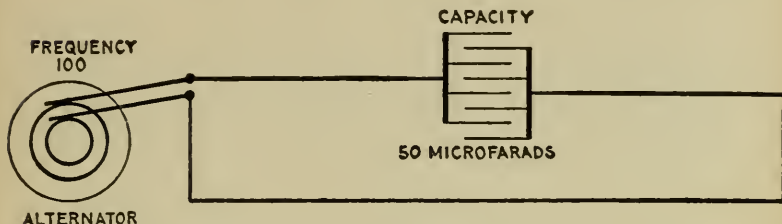


FIG. 1,296.—Diagram of circuit for example III.

**EXAMPLE III.**—In a circuit containing only capacity, what is the reactance when current is supplied at a frequency of 100, and the capacity is 50 microfarads?

$$50 \text{ microfarads} = 50 \times \frac{1}{1,000,000} = .00005 \text{ farad}$$

capacity reactance, or

$$X_c = \frac{1}{2\pi fC} = \frac{1}{2 \times 3.1416 \times 100 \times .00005} = 31.84 \text{ ohms}$$

**Impedance.**—This term, strictly speaking, means the *ratio of any impressed pressure to the current which it produces in a conductor*. It may be further defined as *the total opposition in an electric circuit to the flow of an alternating current*.

All power circuits for alternating current are calculated with reference to impedance. The impedance may be called the combination of:

1. Ohmic resistance;
2. Inductance reactance;
3. Capacity reactance.



The impedance of an inductive circuit which does not contain capacity is equal to the square root of the sum of the squares of the resistance and reactance, that is

$$\text{impedance} = \sqrt{\text{resistance}^2 + \text{reactance}^2} \quad \dots\dots\dots(1)$$

EXAMPLE I.—If an alternating pressure of 100 volts be impressed on a coil of wire having a resistance of 6 ohms and inductance of 8 ohms, what is the impedance of the circuit and how many amperes will flow through the coil? In the example here given, 6 ohms is the resistance and 8 ohms the reactance. Substituting these in equation (1)

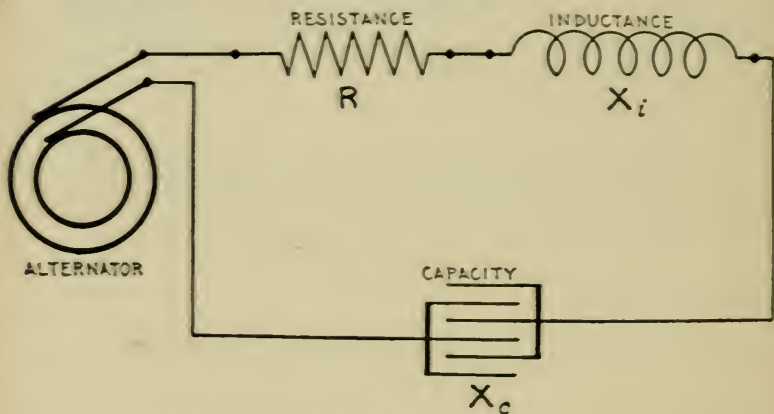


FIG. 1,297.—Diagram showing alternating circuit containing resistance, inductance, and capacity. Formula for calculating the impedance of this circuit is  $Z = \sqrt{R^2 + (X_i - X_c)^2}$  in which,  $Z$  = impedance;  $R$  = resistance;  $X_i$  = inductance reactance;  $X_c$  = capacity reactance. Example: What is the impedance when  $R = 4$ ,  $X_i = 92.4$ , and  $X_c = 72.4$ ? Substituting  $Z = \sqrt{4^2 + 92.4 - 72.4^2} = 22.2$  ohms. Where the ohmic values of inductance and capacity are given as in this example, the calculation of impedance is very simple, but when inductance and capacity are given in milli-henrys and microfarads respectively, it is necessary to first calculate their ohmic values as in figs. 1,295 and 1,296.

$$\text{Impedance} = \sqrt{6^2 + 8^2} = \sqrt{100} = 10 \text{ ohms.}$$

The current in amperes which will flow through the coil is, by Ohm's law using impedance in the same way as resistance.

$$\text{current} = \frac{\text{volts}}{\text{impedance}} = \frac{100 \text{ volts}}{10 \text{ ohms}} = 10 \text{ amperes.}$$

The reactance is not always given but instead in some problems the frequency of the current and inductance of the circuit. An expression to fit such cases is obtained by substituting  $2\pi fL$  for the reactance as follows: (using symbols for impedance and resistance)

$$Z = \sqrt{R^2 + (2\pi fL)^2} \dots \dots \dots (2)$$

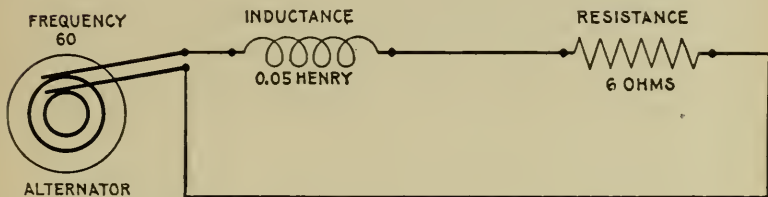


FIG. 1,298.—Diagram of circuit for example II.

EXAMPLE II.—If an alternating current, having a frequency of 60, be impressed on a coil whose inductance is .05 henry and whose resistance is 6 ohms, what is the impedance?

Here  $R = 6$ ;  $f = 60$ , and  $L = .05$ ; substituting these values in (2)

$$Z = \sqrt{6^2 + (2\pi \times 60 \times .05)^2} = \sqrt{393} = 19.8 \text{ ohms.}$$

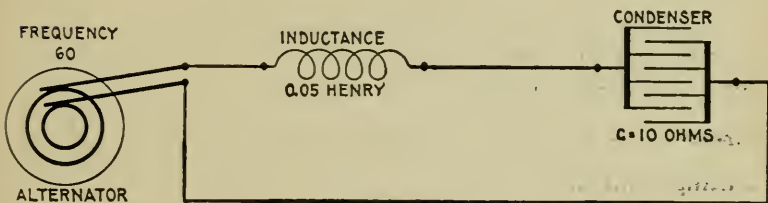


FIG. 1,299.—Diagram of circuit for example III.

EXAMPLE III.—If an alternating current, having a frequency of 60, be impressed on a circuit whose inductance is .05 henry, and whose capacity reactance is 10 ohms, what is the impedance?

$$X_L = 2\pi fL = 2 \times 3.1416 \times 60 \times .05 = 18.85 \text{ ohms}$$

$$Z = X_L - X_C = 18.85 - 10 = 8.85 \text{ ohms}$$

When a circuit contains besides resistance, *both inductance and capacity*, the formula for impedance as given in equation (1), page 1,058, must be modified to include the reactance due to capacity, because, as explained, inductive and capacity reactances work in opposition to each other, in the sense that the reactance of inductance acts in direct proportion to the quantity  $2\pi fL$ , and the reactance of capacity in inverse proportion to the quantity  $2\pi fC$ . The net reactance due to both, when both are in the circuit, is obtained by subtracting one from the other.

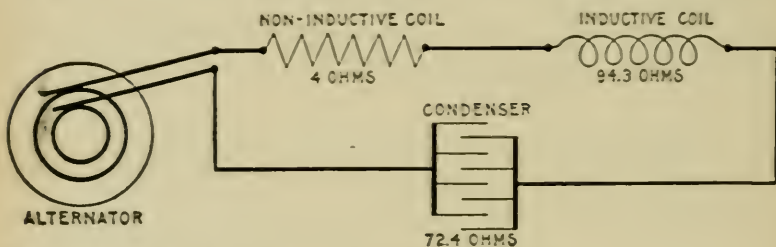


FIG. 1,300.—Diagram of circuit for example IV.

To properly estimate impedance then, in such circuits, the following equation is used:

$$\text{impedance} = \sqrt{\text{resistance}^2 + (\text{inductance reactance} - \text{capacity reactance})^2}$$

or using symbols,

$$Z = \sqrt{R^2 + (X_L - X_C)^2} \dots \dots \dots (3)$$

**EXAMPLE IV.**—A current has a frequency of 100. It passes through a circuit of 4 ohms resistance, of 150 milli-henrys inductance, and of 22 microfarads capacity. What is the impedance?

- a. The ohmic resistance  $R$ , is 4 ohms.
- b. The inductance reactance, or

$$X_L = 2\pi fL = 2 \times 3.1416 \times 100 \times .15 = 94.3 \text{ ohms.}$$

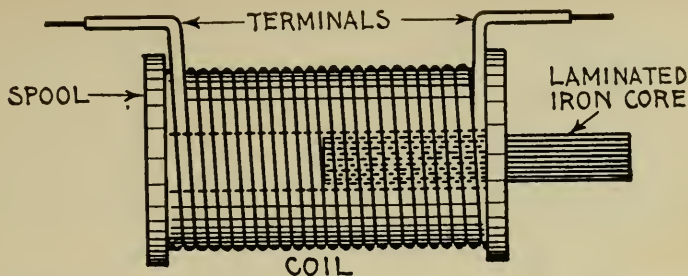


FIG. 1,301.—Simple choking coil. There is an important difference in the obstruction offered to an alternating current by ordinary resistance and by reactance. Resistance obstructs the current by dissipating its energy, which is converted into heat. Reactance obstructs the current by setting up a reverse pressure, and so reduces the current in the circuit, *without wasting much energy*, except by hysteresis in any iron magnetized. This may be regarded as one of the advantages of alternating over direct current, for, by introducing reactance into a circuit, the current may be cut down with comparatively little loss of energy. This is generally done by increasing the inductance in a circuit, by means of a device called variously a *reactance coil*, *impedance coil*, *choking coil*, or "*choker*." In the figure is a coil of thick wire provided with a laminated iron core, which may be either fixed or movable. In the first case, the inductance, and therefore also the reactance of the coil, is invariable, with a given frequency. In the second case, the inductance and consequent reactance may be respectively increased or diminished by inserting the core farther within the coil or by withdrawing it, as was done in fig. 1,266, the results of which are shown in fig. 1,302.

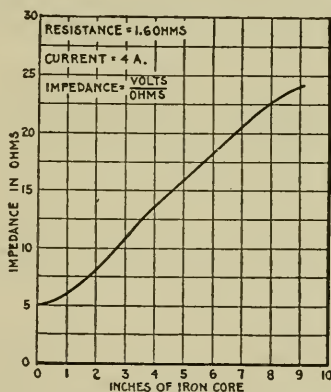


FIG. 1,302.—Impedance curve for coil with variable iron core. The impedance of an inductive coil may be increased by moving an iron wire core into the coil. In making a test of this kind, the current should be kept constant with an adjustable resistance, and voltmeter readings taken, first without the iron core, and again with 1, 2, 3, 4, etc., inches of core inserted in the coil. By plotting the voltmeter readings and the positions of the iron core on section paper as above, the effect of inductance is clearly shown.

(note that 150 milli-henrys are reduced to .15 henry before substituting in the above equation).

c. The capacity reactance, or

$$X_c = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.1416 \times 100 \times .000022} = 72.4 \text{ ohms}$$

(note that 22 microfarads are reduced to .000022 farad before substituting in the formula. Why? See page 1,042).

Substituting values as calculated in equation (3), page 1,050.

$$Z = \sqrt{4^2 + (94.2 - 72.4)^2} = \sqrt{491} = 22.2 \text{ ohms.}$$

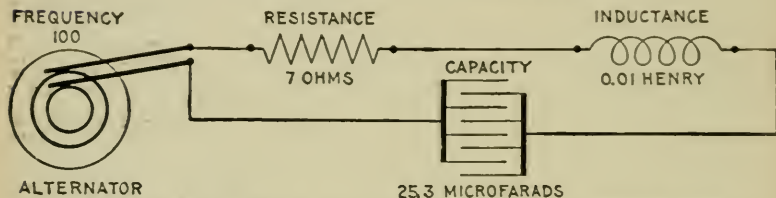


FIG. 1,303.—Diagram of a resonant circuit. A circuit is said to be resonant when the inductance and capacity are in such proportion that the one neutralizes the other, the circuit then acting as though it contained only resistance. In the above circuit  $X_L = 2\pi fL = 2 \times 3.1416 \times 100 \times .01 = 6.28$  ohms;  $X_c = 1 \div (2 \times 3.1416 \times 100 \times .000253) = 6.28$  ohms whence the resultant reactance  $= X_L - X_c = 6.28 - 6.28 = 0$  ohms.  $Z = \sqrt{R^2 + (X_L - X_c)^2} = \sqrt{7^2 + 0^2} = 7$  ohms.

**Ques.** Why is capacity reactance given a negative sign?

**Ans.** Because it reacts in opposition to inductance, that is it tends to reduce the spurious resistance due to inductance.

In circuits having both inductance and capacity, the tangent of the angle of lag or lead as the case may be is the algebraic sum of the two reactances divided by resistance. If the sign be positive, it is an angle of lag; if negative, of lead.

**Resonance.**—The effects of inductance and capacity, as already explained, oppose each other. If inductance and capacity be present in a circuit in such proportion that the effect of one neutralizes that of the other, the circuit acts as though it were purely non-inductive and is said to be in a state of *resonance*.

For instance, in a circuit containing resistance, inductance, and capacity, if the resistance be, say, 8 ohms, the inductance 30, and the capacity 30, then the impedance is

$$\sqrt{8^2 + (30^2 - 30^2)} = \sqrt{8^2} = 8 \text{ ohms.}$$

The formula for inductance reactance is  $X_L = 2 \pi f L$ , and for capacity reactance,  $X_C = 1 \div (2 \pi f C)$ ; accordingly if capacity

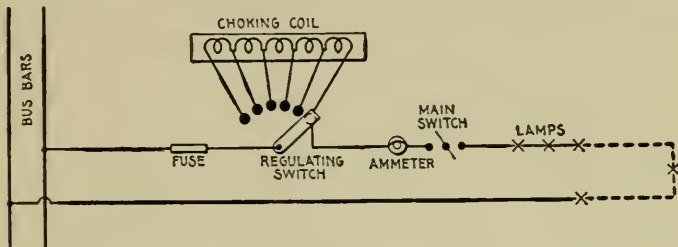


FIG. 1,304.—Application of a choking coil to a lighting circuit. The coil is divided into sections with leads running to contacts similar to a rheostat. Each lamp is provided with an automatic short-circuiting cutout, and should one, two, or more of them fail, a corresponding number of sections of the choking apparatus is put in circuit to take the place of the broken lamp or lamps, and thus keep the current constant. It must not be supposed that this arrangement of lamps, etc. is a general one; it being adopted to suit certain special conditions.

and inductance in a circuit be equal, that is, if the circuit be resonant

$$2 \pi f L = \frac{1}{2 \pi f C} \dots\dots\dots(1)$$

from which

$$f = \frac{1}{2 \pi \sqrt{C L}} \dots\dots\dots(2)$$

**Ques.** What does equation (1) show?

**Ans.** It indicates that by varying the frequency in the proper way as by increasing or decreasing the speed of the alternator, the circuit may be made resonant, this condition being obtained when the frequency has the value indicated by equation (2).



**Ques.** What is the mutual effect of inductance and capacity?

**Ans.** One tends to neutralize the other.

**Ques.** What effect has resonance on the current?

**Ans.** It brings the current in phase with the impressed pressure.

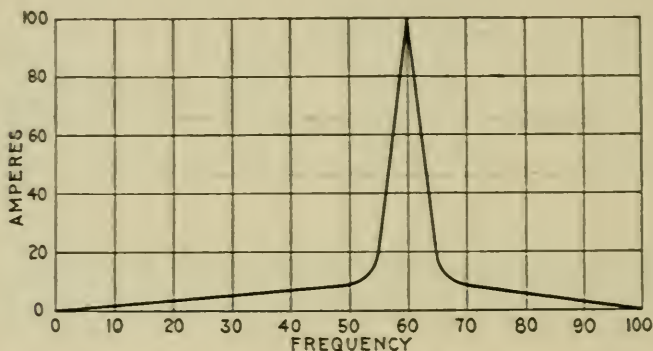


FIG. 1,305.—Curve showing variation of current by increasing the frequency in a circuit having inductance and capacity. The curve serves to illustrate the "critical frequency" or frequency producing the maximum current. The curve is obtained by plotting current values corresponding to different frequencies, the pressure being kept constant.

It is very seldom that a circuit is thus balanced unless intentionally brought about; when this condition exists, the effect is very marked, the pressure rising excessively and bringing great strain upon the insulation of the circuit.

**Ques.** Define "critical frequency."


**Ans.** In bringing a circuit to a state of resonance by increasing the frequency, the current will increase with increasing frequency until the critical frequency is reached, and then the current will decrease in value for further increase of frequency. The critical frequency occurs when the circuit reaches the condition of resonance.



**Ques.** How is the value of the current at the critical frequency determined?

**Ans.** By the resistance of the circuit.

**Skin Effect.**—This is the tendency of alternating currents to avoid the central portions of solid conductors and to flow or pass mostly through the outer portions. The so-called skin effect becomes more pronounced as the frequency is increased.

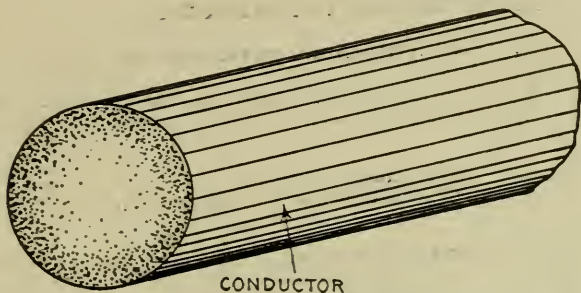

**FIG. 1,306.**—Section of conductor illustrating "skin effect" or tendency of the alternating current to distribute itself unequally through the cross section of the conductor as shown by the varied shading flowing most strongly in the outer portions of the conductor. For this reason it has been proposed to use hollow or flat conductors instead of solid round wires. However with frequency not exceeding 100 the skin effect is negligibly small in copper conductors of the sizes usually employed. Where the conductor is large or the frequency high the effect may be judged by the following examples calculated by Professor J. J. Thomson: In the case of a copper conductor exposed to an electromotive force making 100 periods per second at 1 centimetre from the surface, the maximum current would be only .208 times that at the surface; at a depth of 2 centimetres it would be only .043; and at a depth of 4 centimetres less than .002 part of the value at the surface. If the frequency be a million per second the current at a depth of 1 millimetre is less than one six-millionth part of its surface value. The case of an iron conductor is even more remarkable. Taking the permeability at 100 and the frequency at 100 per second the current at a depth of 1 millimetre is only .13 times the surface value; while at a depth of 5 millimetres it is less than one twenty-thousandth part of its surface value. The disturbance of current density may be looked upon as a self-induced eddy current in the conductor. It necessarily results in an increase of ohmic loss; as compared with a steady current: proportional to the square of the total current flowing and consequently gives rise to an apparent increase of ohmic resistance. The coefficient of increase of resistance depends upon the dimensions and the shape of the cross section, the frequency and the specific resistance. A similar but distinct effect is experienced in conductors due to the neighborhood of similar parallel currents. For example in a heavy multicore cable the non-uniformity of current density in any core may be considered as partly due to eddy currents induced by the currents in the neighboring cores and partly to the self-induced eddy current. It is only the latter effect which should rightly be considered as comprised under the term *skin effect*.

**Ques.** What is the explanation of skin effect?

**Ans.** It is due to eddy currents induced in the conductor.

Consider the wire as being composed of several small insulated wires placed closely together. Now when a current is started along these separate wires, mutual induction will take place between them, giving rise to momentary reverse pressures. Those wires which are nearer the center, since they are completely surrounded by neighboring wires, will clearly have stronger reverse pressures set up in them than those on or near the outer surface, so that the current will meet less opposition near the surface than at the center, and consequently the flow will be greater in the outer portions.

**Ques.** What is the result of skin effect?

**Ans.** It results in an apparent increase of resistance.

The coefficient of increase of resistance depends upon the dimensions and the shape of the cross section, the frequency, and the specific resistance.

Hughes, about 1883, called attention to the fact that the resistance of an iron telegraph wire was greater for rapid periodic currents than for steady currents.

In 1888 Kelvin showed that when alternating currents at moderately high frequency flow through massive conductors, the current is practically confined to the skin, the interior portions being largely useless for the purpose of conduction. The mathematical theory of the subject has been developed by Kelvin, Heaviside, Rayleigh, and others.

## CHAPTER XLVII

## ALTERNATING CURRENT DIAGRAMs

Whenever an alternating pressure is impressed on a circuit, part of it is spent in overcoming the resistance, and the rest goes to balance the reverse pressure due to self-induction.

The total pressure applied to the circuit is known as the *impressed pressure*, as distinguished from that portion of it called the *active pressure* which is used to overcome the resistance, and that portion called the *self-induction pressure* used to balance the reverse pressure of self-induction.

The intensity of the reverse pressure induced in a circuit due to self-induction is proportional to the *rate of change in the current strength*.

Thus a current, changing at the rate of one ampere per second, in flowing through a coil having a coefficient of self-induction of one henry, will induce a reverse pressure of one volt.

**Ques.** Describe how the rate of change in current strength varies, and how this affects the reverse pressure.

**Ans.** The alternating current varies from zero to maximum strength in one-quarter period, that is, in one-quarter revolution of the generating loop or  $90^\circ$  as represented by the sine curve in fig. 1,307. Now, during, say, the first 10 degrees of rotation (from 0 to A), the current jumps from zero value to A', or 4

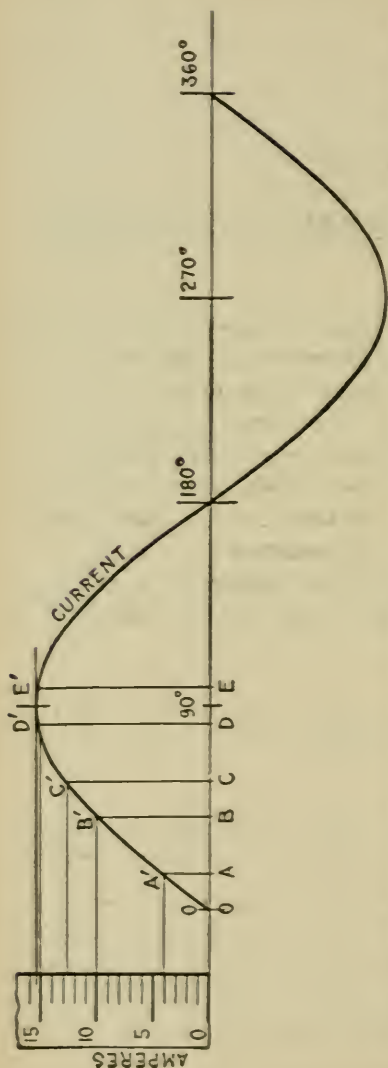


FIG. 1,307. — Sine curve showing that the rate of change in the strength of an alternating current is greatest when the current is least, and zero when the current is at a maximum. This is evident from the diagram, since during any the first 10° as OA, the current increases 4 amperes; during BC, 2½ amperes; during DE it rises and falls ½ ampere. The reverse pressure of self-induction being proportional to the rate of change of the current, is a maximum when the current is zero, and zero when the current is at its maximum, giving a phase difference of 90° between reverse pressure of self-induction and current.

amperes, according to the scale; during some intermediate 10 degrees of the quarter revolution, as from B to C, the current increases from B' to C' or 2½ amperes, and during another 10 degrees as from D to E, at the end of one-quarter revolution where the sine curve reaches its amplitude, it rises and falls ½ ampere. It is thus seen that the rate of change varies from a maximum when the current is least, to zero when the current is at its maximum. Accordingly, the reverse pressure of self-induction being proportional to the rate of change in the current strength, is greatest when the current is at zero value, and zero when the current is at its maximum.

This relation is shown by curves in fig. 1,308, and it should be noted that *the reverse pressure and current are 90° apart in phase*. For this reason many alternating current problems may be solved graphically by the use of right angle triangles, the sides, drawn to some arbitrary scale, to represent the quantities involved, such as resistance, reactance, impedance, etc.

**Properties of Right Angle Triangles.**—In order to understand the graphical method of solving alternating current problems, it is necessary to know why certain relations exist between the sides of a right angle triangle. For instance, in every right angle triangle:

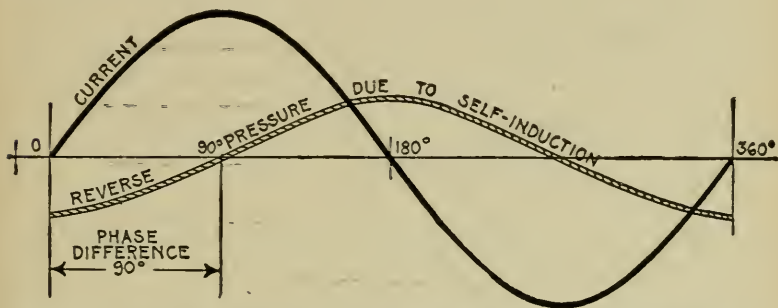


FIG. 1,308.—Sine curves showing phase relation between current and reverse pressure of self-induction. This reverse pressure, being proportional to the rate of change in the current strength, is greatest when the current is at zero value, and zero when the current is maximum, and in phase is 90° behind the current.

*The square of the hypotenuse is equal to the sum of the squares on the other two sides.*

That is, condensing this statement into the form of an equation:


$$\text{hypotenuse}^2 = \text{base}^2 + \text{altitude}^2 \dots\dots\dots (1)$$

the horizontal side being called the base and the vertical side, the altitude.

This may be called the equation of the right angle triangle.

**Ques.** Why is the square of the hypotenuse of a right angle triangle equal to the sum of the squares of the other two sides?

**Ans.** This may be explained with the aid of fig. 1,309. Draw a line AB, 4 inches in length and erect a perpendicular BC, 3

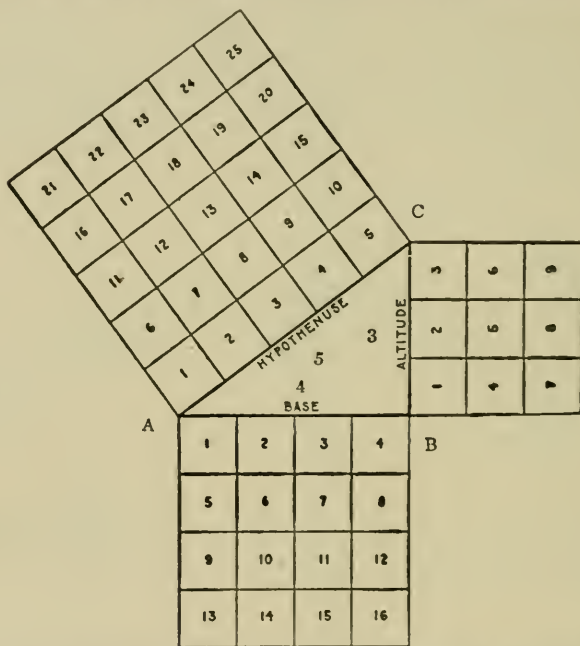

**FIG. 1,309.**—In a right angle triangle the square on the hypotenuse is equal to the sum of the squares on the other two sides. That is;  $\text{hypotenuse}^2 = \text{base}^2 + \text{altitude}^2$ . Draw AB, 4 inches long, and BC, 3 inches long and at right angles to AB. Join AC, which will be found to be 5 inches long. From the diagram, it must be clear that the square on AC = sum of squares on AB and BC; that is,  $5^2 = 4^2 + 3^2$ . Further,  $4^2 = 5^2 - 3^2$ ;  $3^2 = 5^2 - 4^2$ ;  $5 = \sqrt{4^2 + 3^2}$ ;  $4 = \sqrt{5^2 - 3^2}$ ;  $3 = \sqrt{5^2 - 4^2}$ .

inches in height; connect A and C, giving the right angle triangle ABC. It will be found that AC the hypotenuse of this triangle is 5 inches long. If squares be constructed on all



three sides of the triangle, the square on the hypotenuse will have an area of 25 sq. ins.; the square on the base, 16 sq. ins., and the square on the altitude, 9 sq. ins. Then from the figure  $5^2 = 4^2 + 3^2$ , that is  $25 = 16 + 9$ .

Repeating equation (1), it is evident from the figure that

$$\left. \begin{array}{l} \text{hypotenuse}^2 \\ 5^2 \end{array} \right\} = \left\{ \begin{array}{l} \text{base}^2 + \text{altitude}^2 \\ 4^2 + 3^2 \end{array} \right\}$$

that is,

$$25 = 16 + 9.$$

In the right angle triangle, the following relations also hold:

$$\text{base}^2 = \text{hypotenuse}^2 - \text{altitude}^2 \dots \dots \dots (2)$$

$$(4^2 = 5^2 - 3^2)$$

$$\text{altitude}^2 = \text{hypotenuse}^2 - \text{base}^2 \dots \dots \dots (3)$$

$$(3^2 = 5^2 - 4^2)$$

In working impedance problems, it is not the square of any of the quantities which the sides of the triangle are used to represent that is required, but the quantities themselves, that is, the sides. Hence extracting the square root in equations (1), (2) and (3), the following are obtained:

$$\text{hypotenuse} = \sqrt{\text{base}^2 + \text{altitude}^2} \dots \dots \dots (4)$$

$$(5 = \sqrt{4^2 + 3^2})$$

$$\text{base} = \sqrt{\text{hypotenuse}^2 - \text{altitude}^2} \dots \dots \dots (5)$$

$$(4 = \sqrt{5^2 - 3^2})$$

$$\text{altitude} = \sqrt{\text{hypotenuse}^2 - \text{base}^2} \dots \dots \dots (6)$$

$$(3 = \sqrt{5^2 - 4^2})$$



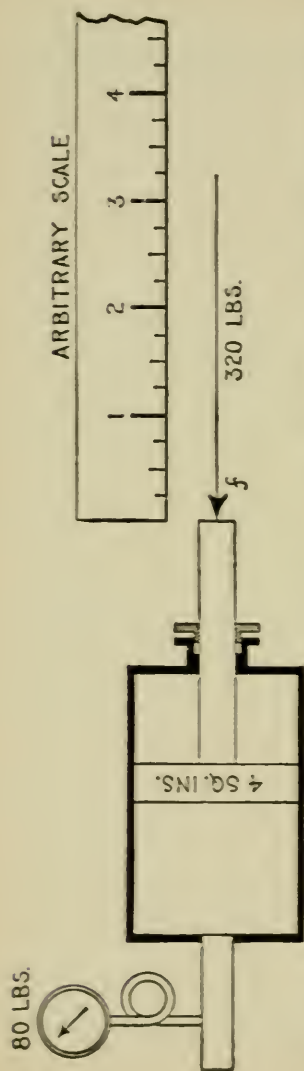


FIG. 1,310.—Diagram illustrating the representation of forces by straight lines. If 80 lbs. of steam be applied to a piston of 4 square inches area, the total pressure acting on the piston is  $4 \times 80 = 320$  lbs. This may be balanced by an equal and opposite force. To represent the latter by a line, select any convenient scale whose divisions represent any convenient number of pounds—1, 2, 3, 4, or, as here taken, 25 lbs. If the scale selected be divided into inches with  $\frac{1}{4}$ -inch divisions, then each  $\frac{1}{4}$  inch represents a force of 25 lbs.; or, as usually stated,  $1'' = 100$  lbs. Strictly speaking  $1''$  is equivalent to 100 lbs. Draw the line  $f = 3.2$  ins., then its length represents the magnitude of the force or 320 lbs., that is,  $3.2 \times 100 = 320$  lbs.

**Representation of Forces by Lines.**—A single force may be represented in a drawing by a straight line, 1, the point of application of the force being indicated by an extremity of the line, 2, the intensity of the force by the length of the line, and 3, the direction of the force by the direction of the line, an arrow head being placed at an extremity defining the direction.

Thus in fig. 1,310, the force necessary to balance the thrust on the steam piston may be represented by the straight line  $f$  whose length measured on any convenient scale represents the intensity of the force, and whose direction represents the direction of the force.

**Composition of Forces.**—This is the operation of finding a *single force whose effect is the same as the combined effect of two or more given forces*. The required force is called the *resultant* of the given forces.

The composition of forces may be illustrated by the effect of the wind and tide on a sailboat as in fig. 1,311. Supposing the boat be acted upon by the wind so that in a given time, say half an hour, it would be moved in the direction and a distance represented by the line AB, and that in the same time the tide would carry it from A to C. Now, lay down AB, to any convenient scale, representing the effect of the wind, and AC that

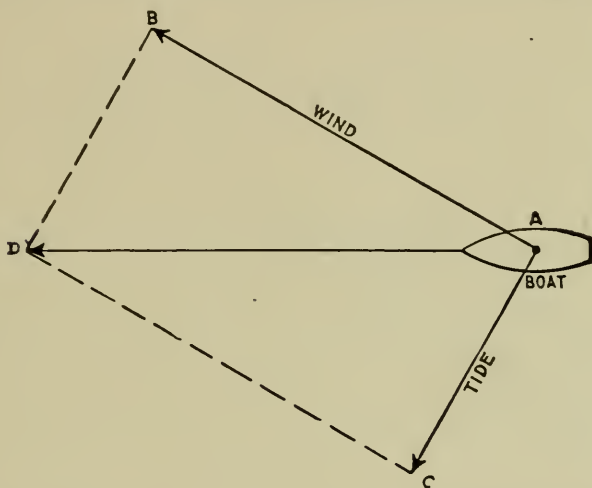


FIG. 1,311.—Parallelogram of forces for boat acted upon by both wind and tide.

of the tide, and draw BD equal and parallel to AC, and CD equal and parallel to AB, then the diagonal AD will represent the direction and distance the boat will move under the combined effect of wind and tide.

**Ques.** In fig. 1,311 what is the line AD called?

**Ans.** The *resultant*, that is, it represents the actual movement of the boat resulting from the combined forces of wind and tide.

**Ques.** What are the forces, AB and AD in fig. 1,311, represented by the sides of the parallelogram, and which act upon a body to produce the resultant, called?

**Ans.** The *components*.

**EXAMPLE.**—Two forces, one of 3 lbs. and one of 4 lbs. act at a point *a* in a body and at right angles, what is the resultant?

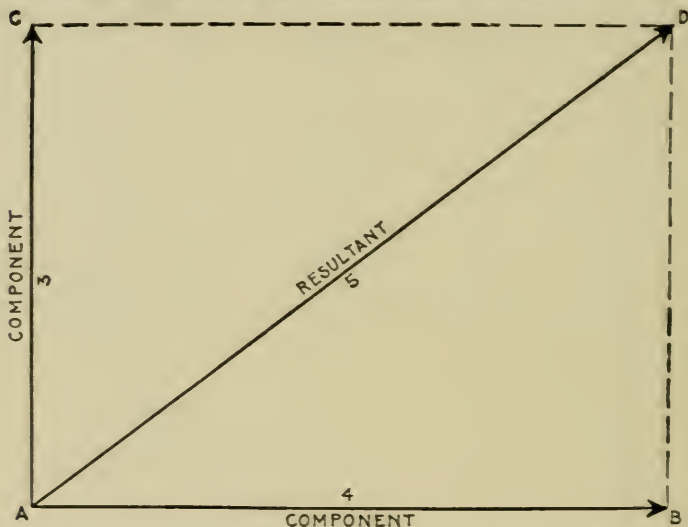


FIG. 1,312.—Parallelogram of forces; method of obtaining the resultant of two components acting at right angles.

Take any convenient scale, say 1 in. = 1 lb., and lay off (fig. 1312.)  $AB = 4$  ins. = 4 lbs.; also,  $AC$  (at right angles to  $AB$ ) = 3 ins. = 3 lbs. Draw  $CD$  and  $BD$  parallel to  $AB$  and  $AC$  respectively, and join  $AD$ . The line  $AD$  is the resultant of the components  $AB$  and  $AC$ , and when measured on the same scale from which  $AB$  and  $AC$  were drawn will be found to be 5 inches long, which represents 5 lbs. acting in the direction  $AD$ .

**Circuits containing Resistance and Inductance.**—In circuits of this kind where the impressed pressure encounters

both resistance and inductance, it may be looked upon as split up into two components, as already explained, one of which is necessary to overcome the resistance, and the other, the inductance. That is, the impressed pressure is split up into

1. *Active pressure*, to overcome resistance;
2. *Self-induction pressure* to overcome inductance.

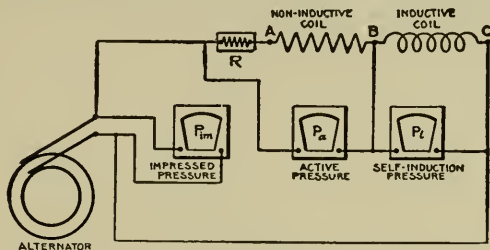


FIG. 1,313.—Diagram illustrating the *active*, and *self-induction* pressures, or the two components of the impressed pressure in circuits containing resistance and inductance. The active pressure is the volts required to overcome the resistance of the circuit. In the figure only the portion from A to C is considered as having resistance (the rest being negligibly small) except at R, a resistance equivalent to that of the inductive coil is inserted next to the non-inductive coil, so  $P_a$  will give the total "ohmic drop" or active pressure, that is, the pressure necessary to force any equivalent direct current from A to C. This active pressure  $P_a$  or component of the impressed pressure is in phase with the current. The other component or self-induction pressure  $P_l$  that is the reactance drop necessary to overcome the reverse pressure of self-induction and is at right angles to the current and  $90^\circ$  ahead of the current in phase. It is registered by a voltmeter between B and C, less the pressure due to ohmic resistance of the inductive coil. The impressed pressure  $P_{im}$  then or total pressure required to force electricity around the circuit *not including the resistance* R, (which is removed from the circuit when the reading of the impressed pressure is taken), is equal to the square root of the sum of the squares of the two components, that is,  $P_{im} = \sqrt{P_a^2 + P_l^2}$ .

The active pressure is *in phase with the current*.

The self induction pressure is *at right angles to the current and 90 degrees ahead of the current in phase*.

**Ques.** Why is the active pressure in phase with the current?

**Anſ.** The pressure used in overcoming resistance is from Ohm's law,  $E = RI$ . Hence, when the current is zero,  $E$  is zero, and when the current is a maximum  $E$  is a maximum. Hence, that component of the impressed pressure necessary to overcome the resistance must be *in phase with the current*.

### Ques. Why is this?

Ans. Since the *reverse pressure of self induction* is  $90^\circ$  behind the current, the component of the impressed pressure necessary to overcome the reverse pressure of self induction, being opposite to this, will be represented as being  $90^\circ$  ahead of the current.

The distinction between the reverse pressure of self-induction, that is, the induced pressure, and the pressure necessary to overcome self-induction should be carefully noted. They are two equal and opposite

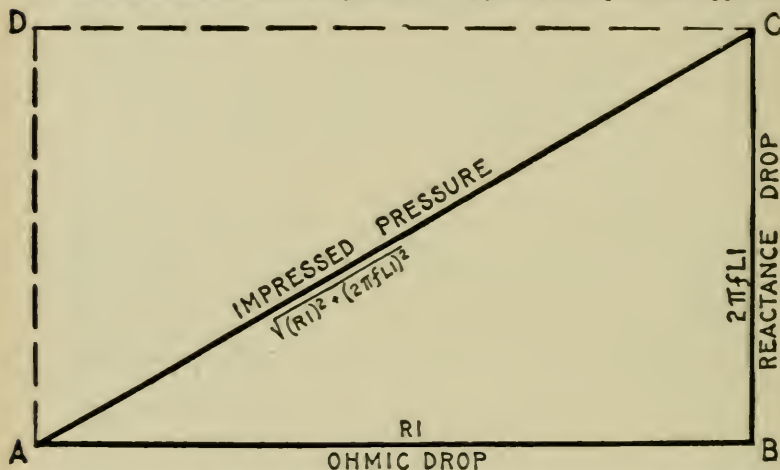


FIG. 1,314.—Graphical method of obtaining the impressed pressure in circuits containing resistance and inductance, having given the ohmic drop and reactance drop due to inductance. With any convenient scale lay off  $AB$  = ohmic drop and erect the perpendicular  $BC$  = reactance drop (using same scale). Join  $AC$ , whose length (measured with same scale) will give the impressed pressure. Constructing a parallelogram with dotted lines  $AD$  and  $CD$ , it is evident that  $AC$  is the *resultant* of the two components  $AB$  and  $BC$ , or its equal  $AD$ .

forces, that is, two balancing forces just as is shown in fig. 1,310. Here, in analogy, the thrust of the piston may represent the induced pressure and the equal and opposite force indicated by the arrow  $f$ , the component of the impressed pressure necessary to balance the induced pressure.

**The Active Pressure or "Ohmic Drop."**—The component of the impressed pressure necessary to overcome resistance, is from Ohm's law:

that is  $\text{active pressure} = \text{ohmic resistance} \times \text{virtual current}$

$$E_a = R_o I_v \dots \dots \dots (1)$$

this is the "ohmic drop" and may be represented by a line AB, fig. 1,314 drawn to any convenient scale, as for instance, 1 in. = 10 volts.

**The Self-induction Pressure or "Reactance Drop."**—The component of the impressed pressure necessary to overcome the induced pressure, is from Ohm's law:

$\text{inductance pressure} = \text{inductance reactance} \times \text{virtual current};$

that is,

$$E_i = X_i I_v \dots \dots \dots (2)$$

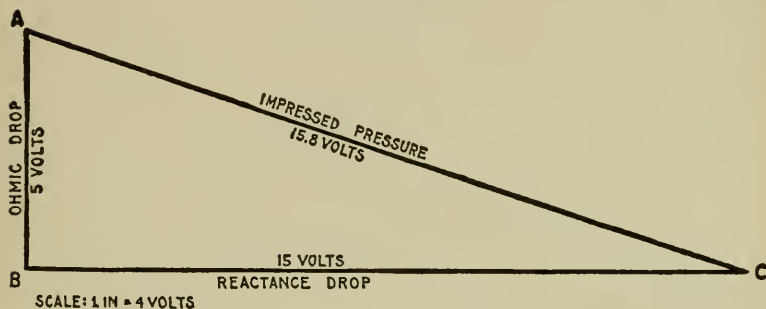


FIG. 1,315.—Diagram for impressed pressure on circuit containing 5 volts ohmic drop and 15 volts reactance drop.

Now the reactance  $X_i$ , that is the spurious resistance, is obtained from the formula

$$X_i = 2 \pi f L \dots \dots \dots (3)$$

as explained on page 1,038, and in order to obtain the volts necessary to overcome this spurious resistance, that is, the "reactance drop" as it is called, the value of  $X_i$  in equation (3) must be substituted in equation (2), giving

$$E_i = 2 \pi f L I \dots \dots \dots (4)$$

writing simply  $I$  for the virtual pressure.

Since the pressure impressed on a circuit is considered as made up of two components, one in phase with the current and one at right angles to the current, the component  $E_i$  or "reactance drop" as given in equation (4) may be represented by the line BC in fig. 1.314, at right angles to AB, and of a length BC, measured with the same scale as was measured AB, to correspond to the value indicated by equation (4).



EXAMPLE.—In an alternating circuit, having an ohmic drop of 5 volts, and a reactance drop of 15 volts, what is the impressed pressure?

With a scale of say,  $\frac{1}{4}$  inch = one volt, lay off, in fig. 1,315,  $AB = 5$  volts =  $1\frac{1}{4}$  in., and, at right angles to it,  $BC = 15$  volts =  $\frac{15}{4}$  or  $3\frac{3}{4}$  ins. Join  $AC$ ; this measures 3.95 inches, which is equivalent to  $3.95 \times 4 = 15.8$  volts, the impressed pressure. By using good paper, such as bristol board, a

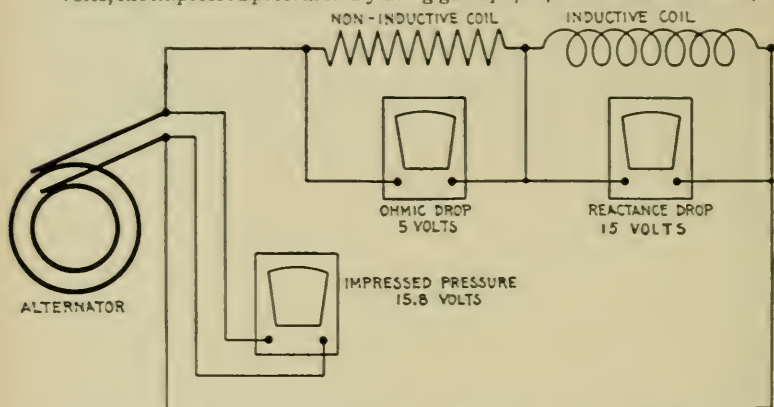


FIG. 1,316.—Diagram of circuit containing 5 volts ohmic drop, and 15 volts reactance drop.

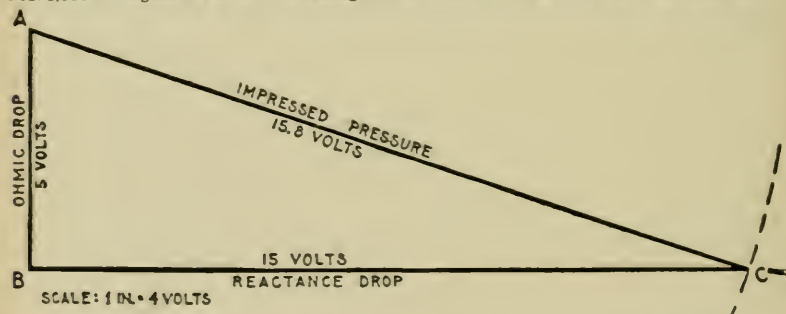


FIG. 1,317.—Diagram for obtaining reactance drop in circuit containing 5 volts ohmic drop, and 15.8 volts impressed pressure.

6H pencil, engineers' scale and triangles or square, such problems are solved with precision. By calculation impressed pressure =  $\sqrt{5^2 + 15^2} = 15.8$  volts. Note that the diagram is drawn with the side  $BC$  horizontal instead of  $AB$ —simply to save space.



EXAMPLE.—In an alternating circuit, having an ohmic drop of 5 volts and an impressed pressure of 15.8 volts, what is the reactance drop?

In fig. 1,317, draw a horizontal line of indefinite length and at any point B erect a perpendicular AB = 5 volts. With A as center and radius of length equivalent to 15.8 volts, describe an arc cutting the horizontal line at C. This gives BC, the reactance drop required, which by measurement is 15 volts.

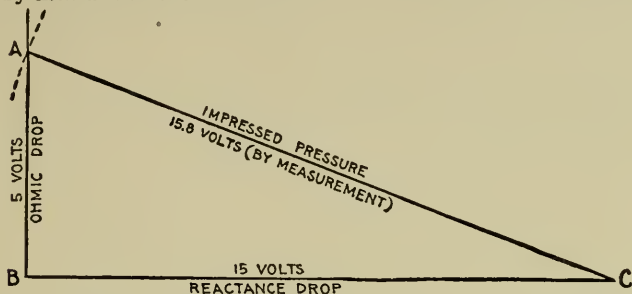


FIG. 1,318.—Diagram for obtaining ohmic drop in the circuit fig. 1,316 when impressed pressure and reactance drop are given. Lay off BC to scale = reactance drop; draw AB at right angle and of indefinite length; with C as center and radius of length = impressed pressure, describe an arc cutting ohmic drop line at A, then AB = ohmic drop = 5 volts by measurement.

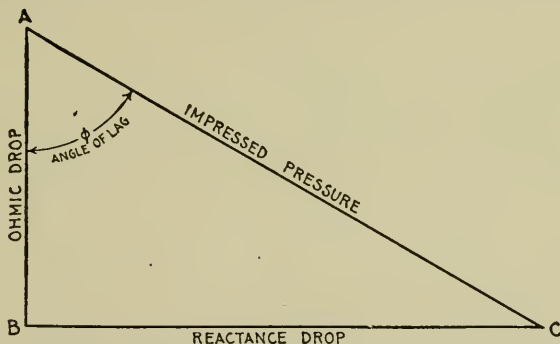


FIG. 1,319.—Graphical method of finding angle of lag when the ohmic drop and reactance drop are given. The angle of lag  $\phi$ , is that angle included between the impressed pressure and the ohmic drop lines, that is, between AC and AB.

EXAMPLE.—An alternating current of 10 amperes having a frequency of 60, is impressed on a circuit containing a resistance of 5 ohms and an inductance of 15 milli-henrys. What is the impressed pressure?

The active pressure or ohmic drop is  $5 \times 10 = 50$  volts.

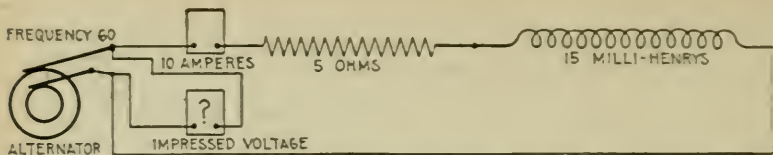


FIG. 1,320.—Diagram of circuit containing 5 ohms resistance, 15 millj-henrys inductance, with 8 ampere 60 frequency current.

The inductance reactance or  $X_L$  is  $2 \times 3.1416 \times 60 \times .015 = 5.66$  ohms  
 Substituting this and the current value 10 amperes in the formula for inductance pressure or reactance drop (equation 2 on page 1,077) gives  
 $E_L = 5.65 \times 10 = 56.5$  volts.

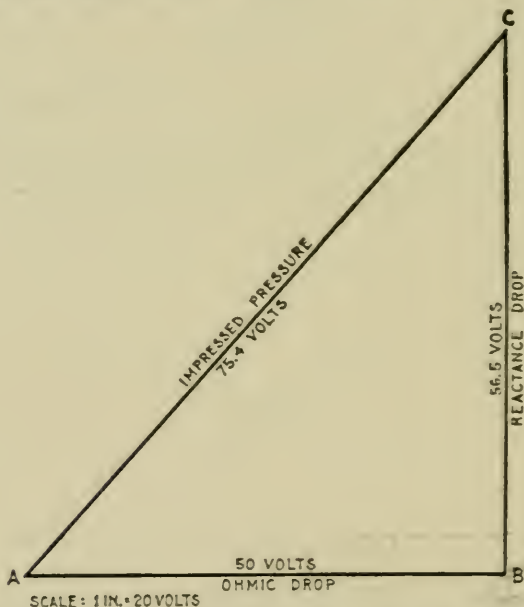


FIG. 1,321.—Diagram for impressed pressure on circuit containing 5 ohms resistance, and inductance of 15 milli-henrys, the current being 10 amperes with frequency of 60.

In fig. 1,321, lay of  $AB = 50$  volts, and  $BC = 56.6$  volts. Using a scale of 20 volts to the inch gives  $AB = 2.5$  ins., and  $BC = 2.83$  ins. Joining  $AC$  gives the impressed voltage, which by measurement is 75.4 volts.

In some problems it is required to find the impedance of a circuit in which the ohmic and spurious resistances are given. This is done in a manner similar to finding the impressed pressure.

Ohmic resistance and spurious resistance or inductance reactance both tend to reduce an alternating current. Their



FIG. 1,322.—Graphical method of obtaining the impedance in circuits containing resistance and inductance, having given the resistance and reactance, that is, the ohmic resistance and spurious resistance. With any convenient scale lay off  $AB = \text{resistance}$ , and erect the perpendicular  $BC = \text{reactance}$  (using the same scale); join  $AC$ , whose length (measured with the same scale) will give the *impedance*.

combined action or impedance is equal to the square root of the sum of their squares, that is,

$$\text{impedance} = \sqrt{\text{resistance}^2 + \text{reactance}^2}$$

This relation is represented graphically by the side of a right angle triangle as in fig. 1322, in which the hypotenuse corresponds to the impedance, and the sides to the resistance and reactance.

EXAMPLE.—In a certain circuit the resistance is 4 ohms, and the reactance 3 ohms. What is the impedance?

In fig. 1 323, lay off, on any scale  $AB = 4$  ohms and erect the perpendicular  $BC = 3$  ohms. Join  $AC$ , which gives the impedance, and which is, measured with the same scale, 5 ohms.

EXAMPLE.—A coil of wire has a resistance of 20 ohms and an inductance of 15 milli-henrys. What is its impedance for a current having a frequency of 100?

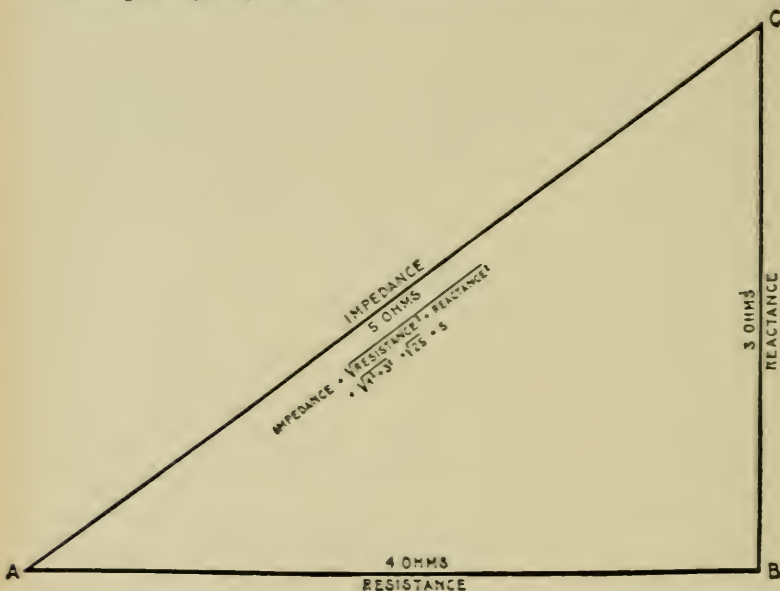


FIG. 1.323.—Diagram for obtaining the impedance of a circuit containing 4 ohms resistance and 3 ohms reactance.

The ohmic value of the inductance, that is, the reactance is

$$2 \pi f L = 2 \times 3.1416 \times 100 \times .015 = 9.42 \text{ ohms.}$$

In fig. 1,324, lay off, on any scale,  $AB = 20$  ohms, and the perpendicular  $BC$  to length  $= 9.42$  ohms. Join  $AC$ , which gives the impedance, which is, measured on the same scale, 22.1 ohms.

EXAMPLE.—What is the angle of lag in a circuit having a resistance of 4 ohms and a reactance of 3 ohms?

Construct the impedance diagram in the usual way as in fig. 1,325, then the angle included between the impedance and resistance lines

(denoted by  $\phi$ ) is the angle of lag, that is, the angle BAC. By measurement with a protractor it is 37 degrees. By calculation the tangent of the angle of lag or

$$\tan \phi = \frac{BC}{AB} = \frac{3}{4} \text{ or } .75$$

From the table on page 451, the angle is approximately 37°.

FIG. 1,324.—Diagram for impedance of circuit containing 20 ohms resistance, and inductance of 15 millihenrys, when the frequency is 100.


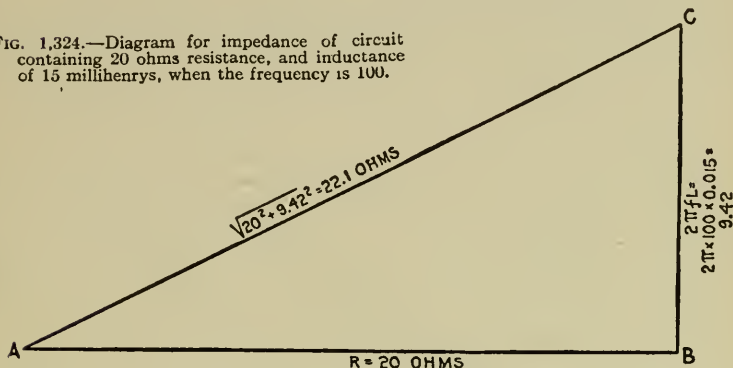


FIG. 1,325.—Diagram showing angle of lag for current containing 4 ohms resistance and 3 ohms reactance.

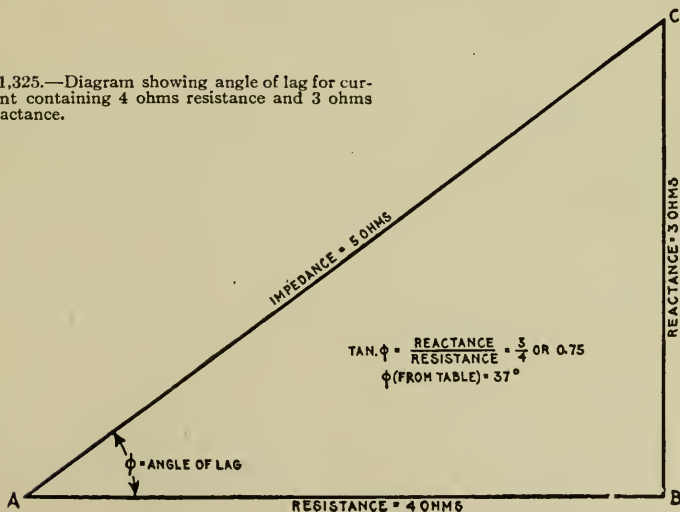

**Circuits containing Resistance and Capacity.**—The effect of capacity in an alternating current circuit is to cause the current to lead the pressure, since the reaction of a condenser, instead of tending to prolong the current, tends to drive it back.

Careful distinction should be made between capacity *in series* with a circuit and capacity *in parallel* with a branch of a circuit. The discussion here refers to capacity in series, which

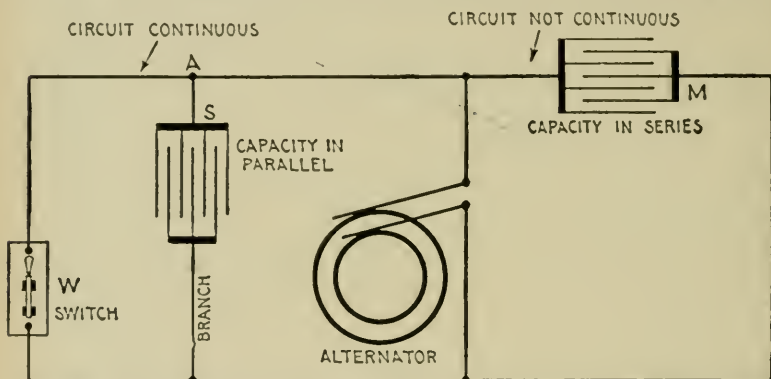


FIG. 1,326.—Circuit diagram illustrating the distinction between *capacity in series* and *capacity in parallel*. The condition for *capacity in series* is that the circuit must be discontinuous as at M; for *capacity in parallel* the main circuit must be continuous; this means that the capacity must be inserted in a branch of the main circuit as at A. In the figure the capacity S is connected *in series* with respect to the branch, that is, the branch is discontinuous, but it is *in parallel* with respect to the main circuit, when the latter is continuous, that is, when the switch W is closed. If W be opened, the main circuit becomes discontinuous and S is changed from *in parallel* to *in series* connection.

means that the circuit is not continuous but the ends are joined to a condenser, as shown at the right in fig. 1,326, so that no current can flow except into and out of the condenser.

**Ques.** In circuits containing resistance and capacity upon what does the amount of lead depend?

**Ans.** Upon the relative values of the resistance and the capacity reactance.

**Ques.** Describe the action of a condenser when current is applied.

**Ans.** When the current begins to flow into a condenser, that is, when the flow is maximum, the back pressure set up by the condenser (called the *condenser pressure*) is zero, and when the flow finally becomes zero, the condenser pressure is a maximum.

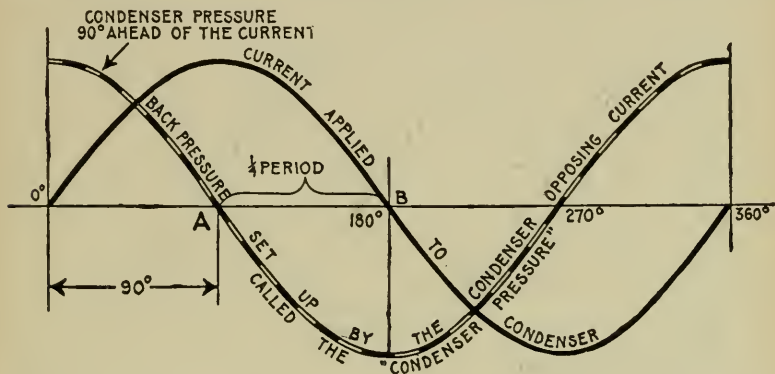


FIG. 1,327.—Current and pressure curves showing that the condenser pressure is  $90^\circ$  ahead of the current. A current flowing into a condenser encounters a gradually increasing pressure which opposes it, beginning from zero pressure when the current enters at maximum flow and increasing to the same value as the current pressure, at which time the current ceases to flow. Hence, since the current varies from zero to maximum in one quarter period, or  $90^\circ$ , the phase difference between current and condenser pressure is  $90^\circ$ . The condenser pressure reaching a positive maximum when the current starts from zero on the positive wave, is  $90^\circ$  ahead of the current.

**Ques.** What does this indicate?

**Ans.** It shows that the phase difference between the wave representing the condenser pressure and the current is  $90^\circ$ , as illustrated in fig. 1,327.

**Ques.** Is the condenser pressure ahead or behind the current and why?

**Ans.** It is ahead of the current. The condenser pressure, when the condenser is discharged being zero, the current enters



at maximum velocity as at *A* in fig. 1,327, and gradually decreases to zero as the condenser pressure rises to maximum at *B*, this change taking place in one-quarter period. Thus the condenser pressure, which opposes the current, being at a maximum when the current begins its cycle is  $90^\circ$  ahead of the current, as is more clearly seen in the last quarter of the cycle (fig. 1,327).

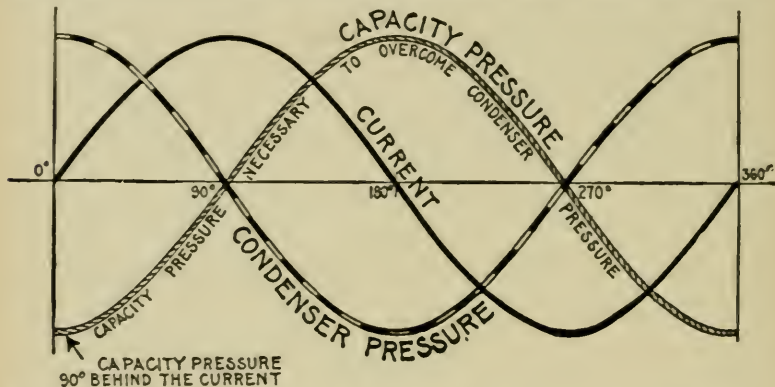


FIG. 1,328.—Current and pressure curves, showing phase relation between the current, condenser pressure, and impressed or *capacity* pressure necessary to overcome the condenser pressure. The capacity pressure, since it must overcome the condenser pressure, is equal and opposite to the condenser pressure, that is, the phase difference is  $180^\circ$ . The condenser pressure being  $90^\circ$  ahead of the current, the impressed pressure is  $90^\circ$  behind the current.

**Ques.** What is the phase relation between the condenser pressure and the pressure applied to the condenser to overcome the condenser pressure?

**Ans.** The pressure applied to the condenser to overcome the condenser pressure, or as it is called, the *capacity* pressure, must be opposite to the condenser pressure, or  $90^\circ$  behind the current.

In circuits containing resistance and capacity, the total pressure impressed on the circuit, or *impressed pressure*, as it is called, is made up of two components:

1. The *active pressure*, or pressure necessary to overcome the resistance;

The active pressure is in phase with the current.

2. The *capacity pressure*, or pressure **necessary** to overcome the condenser pressure,

The capacity pressure is 90 degrees behind the current.

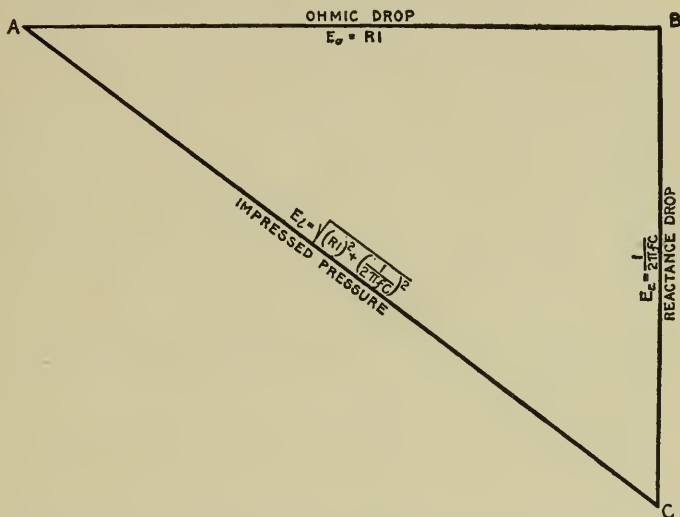


FIG. 1.329.—Graphical method of obtaining the impressed pressure in circuits containing resistance and capacity, having given the ohmic drop and reactance drop due to capacity. With any convenient scale, lay off  $AB = \text{ohmic drop}$ , and at right angles to  $AB$  draw  $BC = \text{reactance drop}$  (using the same scale). Join  $AC$ , whose length (measured with the same scale) will give the *impressed pressure*. The mathematical expressions for the three quantities are given inside the triangle, and explained in the text.

Problems involving resistance and capacity are solved similarly to those including resistance and inductance.

**The Active Pressure or "Ohmic Drop."**—This, as before explained is represented, in fig. 1.329, by a line  $AB$ , which in magnitude equals, by Ohm's law, the product of the resistance multiplied by the current, that is,

$$E_a = R_c I_g \dots \dots \dots (1)$$

**The Capacity Pressure or "Reactance Drop."**—This component of the impressed pressure, is, applying Ohm's law,

*capacity pressure = capacity reactance  $\times$  virtual current.*

$$E_c = X_c I_r \dots \dots \dots (2)$$

That is, the expression for capacity reactance  $X_c$ , that is, for the value of capacity in ohms is, as explained on page 1,048,

$$X_c = \frac{1}{2\pi f C} \dots \dots \dots (3)$$

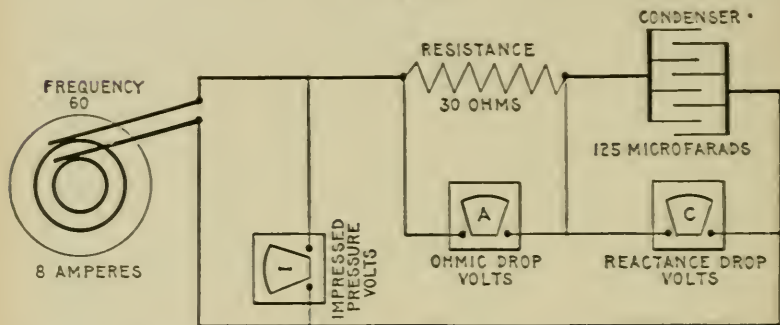


FIG. 1,330.—Diagram of circuit containing a resistance of 30 ohms and capacity of 125 microfarads. The calculation for impressed pressure, ohmic drop, and reactance drop for a current of 8 amperes at frequency 60 is given in the example on page 1,089, the diagram for impressed pressure being given in fig. 1,331.

Substituting this value of  $X_c$  in equation (2) and writing  $I$  for virtual current.

$$E_c = \frac{I}{2\pi f C} \dots \dots \dots (4)$$

**CAUTION**—The reader should distinguish between the 1 (one) in (3) and the letter  $I$  in (4); both look alike.

Since the capacity pressure is  $90^\circ$  behind the current, it is represented in fig. 1,329, by a line  $BC$ , drawn *downward*, at right angles to  $AB$ , and of a length corresponding to the capacity pressure, that is, to the reactance drop.

**The Impressed Pressure.**—Having determined the ohmic and reactance drops and represented them in the diagram, fig. 1,329, by lines  $AB$  and  $BC$  respectively, a line  $AC$  joining  $A$  and  $C$ , will then be the resultant of the two component pressures, that is, it will represent the *impressed pressure* or total pressure applied to the circuit.

In the diagram it should be noted that the active pressure is called the *ohmic drop*, and the capacity pressure, the *reactance drop*.

EXAMPLE.—A circuit as shown in fig. 1,330 contains a resistance of 30 ohms, and a capacity of 125 microfarads. If an alternating current of 8 amperes with frequency 60 be flowing in the circuit, what is the ohmic drop, the reactance drop, and the impressed pressure?

The ohmic drop or active pressure is, substituting in formula (1) on page 1,087,

$$E_a = 30 \times 8 = 240 \text{ volts}$$

which is the reading of voltmeter A in fig. 1,330.

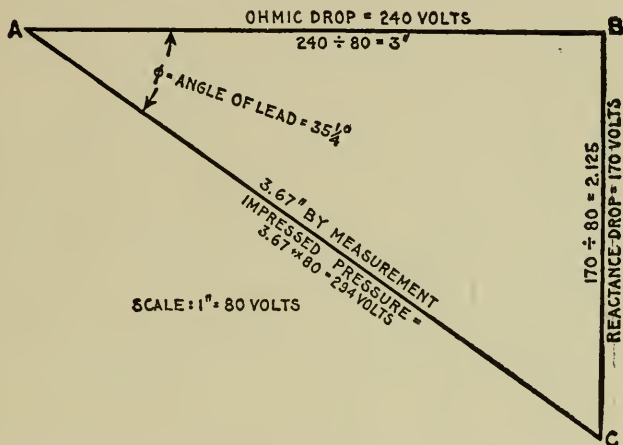


FIG. 1,331.—Diagram for obtaining the impressed pressure of the circuit shown in fig. 1,330.

The reactance drop or

$$E_c = \frac{I}{2\pi f C} = \frac{8}{2 \times 3.1416 \times 60 \times .000125} = 170 \text{ volts}$$

in substituting, note that the capacity C of 125 microfarads is reduced to .000125 farad.

Using a scale of say 1 inch = 80 volts, lay off in fig. 1,331, AB equal to the ohmic drop of 240 volts; on this scale AB = 3 inches. Lay off at right angles, BC = reactance drop = 170 volts = 2.125 inches. Join AC, which gives the impressed voltage, (that is the reading of voltmeter I in fig. 1,330,) which measures 294 volts.


By calculation, impressed pressure =  $\sqrt{240^2 + 170^2} = 294 \text{ volts}$ .

EXAMPLE.—In the circuit shown in fig. 1,330, what is the angle of lead?

The tangent of the angle of lead is given by the quotient of the reactance divided by the resistance of the circuit. That is,

$$\tan \phi = \frac{\text{reactance}}{\text{resistance}} = \frac{\text{reactance drop}}{\text{resistance drop}}$$
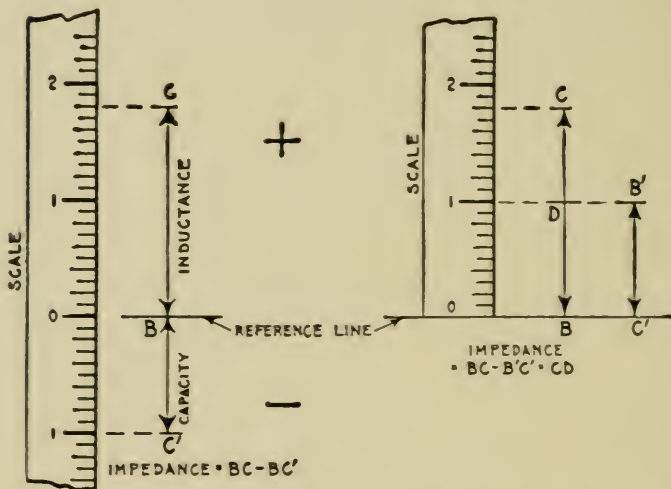
$$\tan \phi = \frac{E_c}{E_a} = \frac{I}{2\pi f C} \div E_a \dots \dots \dots (1)$$



FIGS. 1,332 and 1,333.—Diagrams for circuits containing inductance and capacity. Since inductance and capacity act  $180^\circ$  apart, their reactances, or their ohmic drops may be represented by oppositely directed lines. These may be drawn above and below a reference line, as in fig. 1,332, and their algebraic sum taken, or both may be drawn on the same side of the reference line and their difference in lengths, as CD, fig. 1,333, measured. Recourse to a diagram for obtaining the resultant reactance in circuits containing inductance and capacity is unnecessary as it is simply a matter of taking the difference of two quantities.

The tangent is given a negative sign because lead is opposed to lag and because the positive value is assigned to lag. Substituting in (1)

$$\tan \phi = \frac{170}{240} \text{ or } \frac{2.125''}{3''} = -.71$$

the angle corresponding is approximately  $35\frac{1}{4}^\circ$  (see table page 451)

**Circuits Containing Inductance and Capacity.**—The effect of capacity in a circuit is exactly the opposite of inductance, that is, one tends to neutralize the other. The method of representing each graphically has been shown in the preceding figures. Since they act oppositely, that is  $180^\circ$  apart, the reactance due to each may be calculated and the values thus found, represented by oppositely directed vertical lines: the inductance resistance upward from a reference line, and the

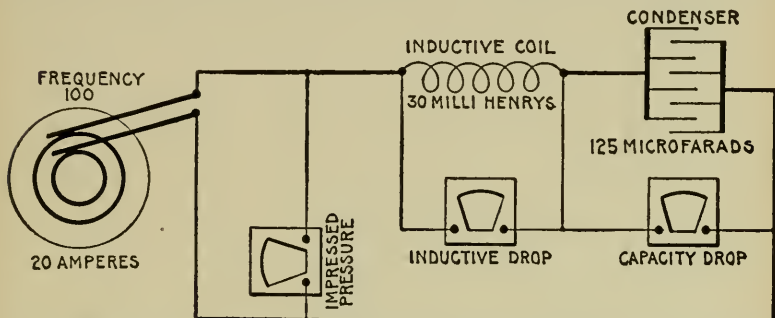


FIG. 1,334.—Diagram of circuit containing 30 millihenrys inductance and 125 microfarads capacity, with current of 20 amperes, 100 frequency.

capacity resistance downward from the same reference line. The difference then is the resultant impedance. This method is shown in fig. 1,332, but it is more conveniently done as in fig. 1,333.

**EXAMPLE.**—In a circuit, as in fig. 1,334, containing an inductance of 30 milli-henrys and a capacity of 125 microfarads, how many volts must be impressed on the circuit to produce a current of 20 amperes having a frequency of 100.

The inductance reactance is

$$X_i = 2\pi fL = 2 \times 3.1416 \times 100 \times .03 = 18.85 \text{ ohms.}$$

Substituting this and the current value of 20 amperes in the formula for inductance pressure

$$E_i = R_i I = 18.85 \times 20 = 377 \text{ volts.}$$

Reducing 125 microfarads to .000125 farad, and substituting in the formula for capacity pressure

$$E_c = \frac{I}{2\pi fC} = \frac{20}{2 \times 3.1416 \times 100 \times .000125} = 255 \text{ volts.}$$

A diagram is unnecessary in obtaining the impressed pressure since it is simply the difference between inductance pressure and capacity pressure (the circuit being assumed to have no resistance), that is

$$\text{impressed pressure} = E_l - E_c = 377 - 255 = 122 \text{ volts.}$$

**EXAMPLE.**—A circuit in which a current of 20 amperes is flowing at a frequency of 100, has an inductance reactance of 18.25 ohms, and a capacity of 125 microfarads. What is the impedance?

The reactance due to capacity is

$$X_c = \frac{1}{2\pi fC} = \frac{1}{2 \times 3.1416 \times 100 \times .000125} = 12.76 \text{ ohms.}$$

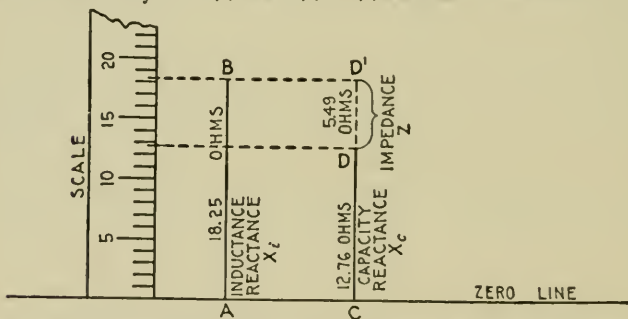


FIG. 1,335.—Impedance diagram for circuit (of above example) containing inductance and capacity. With any convenient scale, erect a perpendicular  $AB = 18.25$  ohms, and  $CD = 12.76$  ohms. Continue  $CD$  by dotted line to  $D'$  so that  $CD' = AB$ , then  $DD' = AB - CD = \text{inductance reactance} - \text{capacity reactance}$ , which is equal to the impedance. Expressed by letters  $Z = X_l - X_c = DD'$ , which by measurement = 5.49 ohms.

The impedance of the circuit then is the difference between the two reactances, that is impedance = inductance reactance - capacity reactance, or

$$Z = X_l - X_c = 18.25 - 12.76 = 5.49 \text{ ohms.}$$

**Circuits Containing Resistance, Inductance, and Capacity.**—When the three quantities resistance, inductance, and capacity, are present in a circuit, the combined effect is easily



understood by remembering that inductance and capacity always act oppositely, that is, they tend to neutralize each other. Hence, in problems involving the three quantities, the resultant of inductance and capacity is first obtained, which, together with the resistance, is used in determining the final effect.

Capacity introduced into a circuit containing inductance reduces the latter and if enough be introduced, inductance will be neutralized, giving a resonant circuit which will act as though only resistance were present.

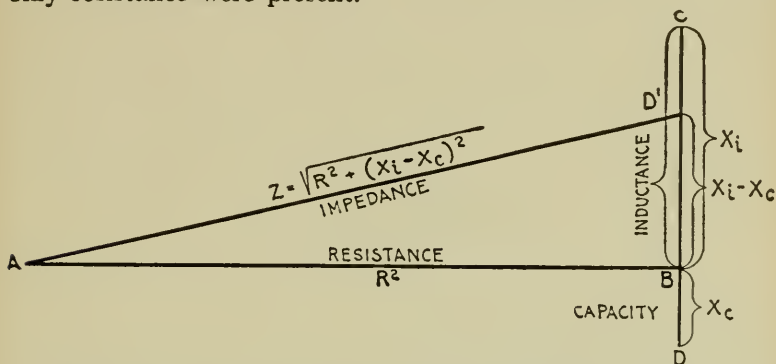


FIG. 1,336.—Impedance diagram for circuit containing resistance, inductance and capacity. The symbols correspond to those used in equation (1) below. In constructing the diagram from the given values, lay off  $AB$  = resistance; at  $B$ , draw a line at right angles, on which lay off above the resistance line,  $BC$  = inductive reactance, and below,  $BD$  = capacity reactance, then the resultant reactance =  $BC - BD = BD'$ . Join  $A$  and  $D'$ , then  $AD'$  = impedance.

**Ques.** What is the expression for impedance of a circuit containing resistance, inductance and capacity?

**Ans.** It is equal to the square root of the sum of the resistance squared plus the square of inductance reactance minus capacity reactance.

This is expressed plainer in the form of an equation as follows:

impedance =  $\sqrt{\text{resistance}^2 + (\text{inductance reactance} - \text{capacity reactance})^2}$   
or, using symbols,

$$Z = \sqrt{R^2 + (X_L - X_C)^2} \dots\dots\dots (1)$$

**Ques.** If the capacity reactance be larger than the inductance reactance, how does this affect the sign of  $(X_i - X_c)^2$ ?

**Ans.** The sign of the resultant reactance of inductance and capacity will be negative if capacity be the greater, but since in the formula the reactance is squared, the sign will be positive.

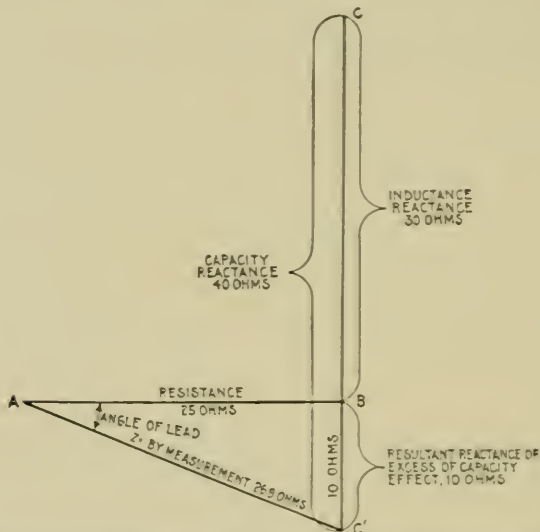


FIG. 1,337.—Impedance diagram of a circuit containing 25 ohms resistance, 30 ohms inductance, and 40 ohms capacity. The resultant reactance being due to excess of capacity, the impedance line AC' falls *below* the horizontal line AB, indicating that the current *leads* pressure.

**EXAMPLE.**—What is the impedance in a circuit having 25 ohms resistance, 30 ohms inductance reactance, and 40 ohms capacity reactance?

To solve this problem graphically, draw the line AB, in fig. 1,337, equal to 25 ohms resistance, using any convenient scale.

At B draw upward at right angles BC = 30 ohms; draw from C downward CC' = 40 ohms. This gives -BC' (= BC - CC') showing the capacity reactance to be 10 ohms in excess of the inductance reactance. Such a

circuit is equivalent to one having no inductance but the same resistance and 10 ohms capacity reactance.

The diagram is completed in the usual way by joining AC giving the required impedance, which by measurement is 26.9 ohms.

By calculation,  $Z = \sqrt{25^2 + (30 - 40)^2} = \sqrt{25^2 + (-10)^2} = 26.9$ .

### Form of Impedance Equation without Ohmic Values.—

Using the expressions  $2\pi fL$  for inductance reactance and  $\frac{1}{2\pi fC}$

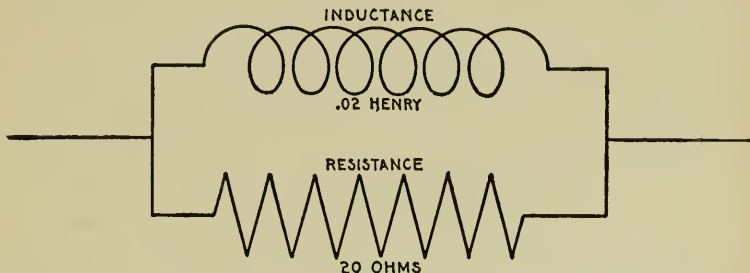


FIG. 1,338.—EXAMPLE: A resistance of 20 ohms and an inductance of .02 henry are connected in parallel as in the diagram. What is the impedance, and how many volts are required for 50 amperes, when the frequency is 78.6? SOLUTION: The time constants are not alike, hence the geometric sum of the reciprocals must be taken as the reciprocal of the required impedance. That is, the combined conductivity will be the hypotenuse of the right triangle, of which the ohmic conductivity and the reactive conductivity are the two sides, respectively. Accordingly:  $\frac{1}{R} = \frac{1}{20} = .05$ , and  $\frac{1}{2\pi fL} = \frac{1}{10} = .1$ , from which,

$$\frac{1}{R} = \sqrt{\left(\frac{1}{R_1}\right)^2 + \left(\frac{1}{2\pi fL}\right)^2} = .111. \text{ Whence } Z = \frac{1}{.111} = 9 \text{ ohms.}$$

for capacity reactance, and substituting in equation (1) on page 1,093 gives the following:

$$Z = \sqrt{R^2 + \left(2\pi fL - \frac{1}{2\pi fC}\right)^2} \dots\dots\dots (2)$$

which is the proper form of equation (1) to use in solving problems in which the ohmic values of inductance and capacity must be calculated.

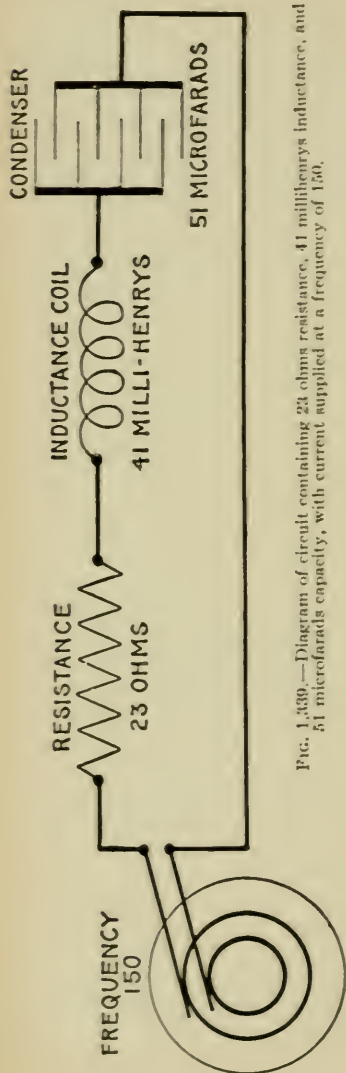


FIG. 1,339.—Diagram of circuit containing 23 ohms resistance, 41 millihenrys inductance, and 51 microfarads capacity, with current supplied at a frequency of 150.

EXAMPLE.—A current has a frequency of 150. It passes through a circuit, as in fig. 1,339, of 23 ohms resistance, of 41 millihenrys inductance, and of 51 microfarads capacity. What is the impedance?

The inductance reactance or

$$X_i = 2\pi fL = 2 \times 3.1416 \times 150 \times .041 = 38.64 \text{ ohms}$$

(note that 41 henrys are reduced to .041 henry before substituting in the above equation).

The capacity reactance, or

$$X_c = \frac{1}{2\pi fC} = \frac{1}{2 \times 3.1416 \times 150 \times .000051} = 20.8 \text{ ohms}$$

(note that 51 microfarads are reduced to .000051 farad before substituting in the above equation).

Substituting the values as calculated

for  $2\pi fL$  and  $\frac{1}{2\pi fC}$  in equation (2)

$$Z = \sqrt{23^2 + (38.64 - 20.8)^2} = 29.1 \text{ ohms.}$$

To solve the problem graphically, lay off in fig. 1,340, the line AB equal to 23 ohms resistance, using any convenient scale. Draw upward and at right angles to AB the line BC = 38.64 ohms inductance reactance, and from C lay off downward CC' = 20.8 ohms capacity reactance. The resultant reactance

is  $BC'$  and being above the horizontal line  $AB$  shows that inductance reactance is in excess of capacity reactance by the amount  $BC'$ . Join  $AC'$  which gives the impedance sought, and which by measurement is 29.1 ohms.

In order to obtain the **impressed pressure in circuits containing resistance, inductance and reactance**, an equation similar to (2) on page 1,095 is used which is made up from the following :

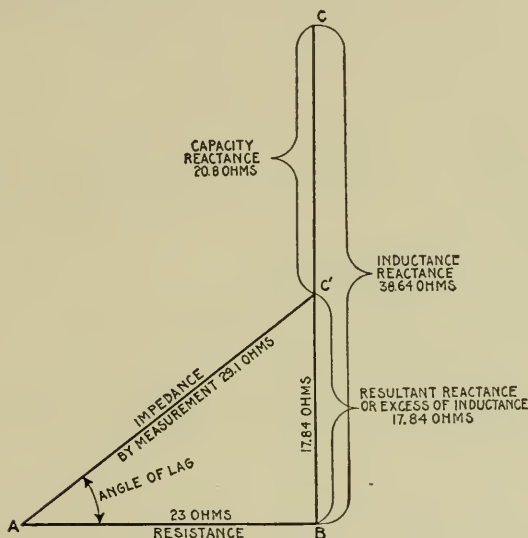


FIG. 1,340.—Impedance diagram for the circuit shown in fig. 1,339. Note that the resultant reactance being due to excess of inductance, the impedance line  $AC'$  falls *above* the horizontal line  $AB$ . This indicates that the current *lags* behind the pressure.

$$E_o = RI \dots \dots \dots (3)$$

$$E_i = 2\pi f LI \dots \dots \dots (4)$$

$$E_c = \frac{I}{2\pi f C} \dots \dots \dots (5)$$

When all three quantities, resistance, inductance, and capacity are present, the equation is as follows:

$$\text{impressed pressure} = \sqrt{\text{ohmic drop}^2 + (\text{inductive drop} - \text{capacity drop})^2}$$

$$E_{im} = \sqrt{E_o^2 + (E_i - E_c)^2} \dots \dots \dots (6)$$

Substituting in this last equation (6), the values given in (3), (4) and (5)

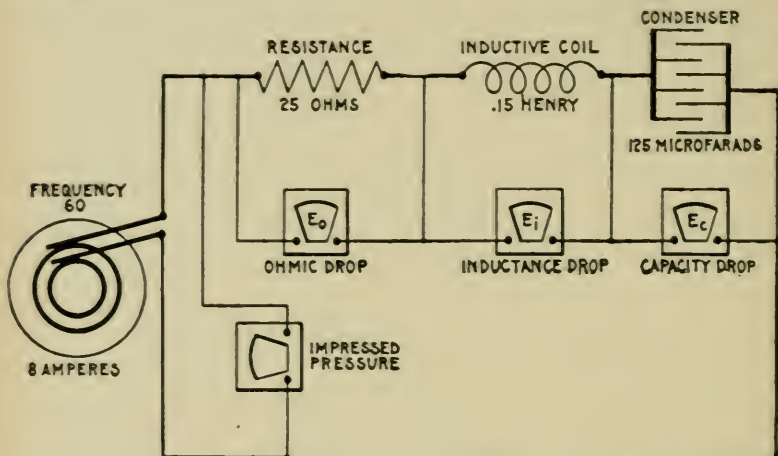


FIG. 1,341.—Diagram of circuit containing 25 ohms resistance, .15 henry inductance, and 125 microfarads capacity, with current of 8 amperes at 60 frequency.

$$E_{im} = \sqrt{R^2 I^2 + \left(2\pi f LI - \frac{I}{2\pi f C}\right)^2}$$

$$= I \sqrt{R^2 + \left(2\pi f L - \frac{1}{2\pi f C}\right)^2} \dots \dots \dots (7)$$

**Ques.** What does the quantity under the square root sign in equation (7) represent?

**Ans.** It is the impedance of a circuit possessing resistance, inductance, and capacity.

### Ques. Why?

Ans. Because it is that quantity which multiplied by the current gives the pressure, which is in accordance with Ohm's law.

EXAMPLE.—An alternator is connected to a circuit having, as in fig. 1,341, 25 ohms resistance, an inductance of .15 henry, and a capacity of 125 microfarads. What pressure must be impressed on the circuit to allow 8 amperes to flow at a frequency of 60?

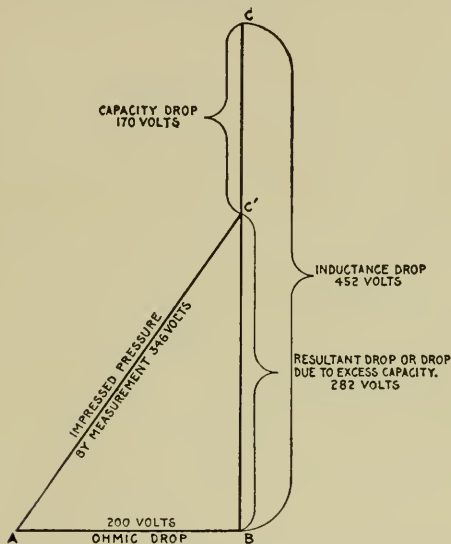


FIG. 1,342.—Diagram for finding the pressure necessary to be impressed on the circuit shown in fig. 1,341, to produce a current of 8 amperes.

The ohmic drop is

$$E_o = RI = 25 \times 8 = 200 \text{ volts.}$$

The inductance drop is

$$E_i = 2\pi f LI = 2 \times 3.1416 \times 60 \times .15 \times 8 = 452 \text{ volts}$$

The capacity drop is

$$E_c = \frac{I}{2\pi f C} = \frac{8}{2 \times 3.1416 \times 60 \times .000125} = 170 \text{ volts.}$$



Substituting the values thus found,

$$\begin{aligned}\text{impressed pressure} &= \sqrt{E_o^2 + (E_t - E_o)^2} \\ &= \sqrt{200^2 + (452 - 170)^2} \\ &= \sqrt{200^2 + 282^2} \\ &= \sqrt{119524} \\ &= 345.7 \text{ volts.}\end{aligned}$$

## CHAPTER XLVIII

# THE POWER FACTOR

The determination of the power in a direct current circuit is a simple matter since it is only necessary to multiply together the volts and amperes to obtain the output in watts. In the case of alternating current circuits, this holds true only when the current is in phase with the pressure—a condition rarely found in practice.

When the current is not in phase with the pressure, the product of volts and amperes as indicated by the voltmeter and ammeter must be multiplied by a coefficient called the *power factor* in order to obtain the *true watts*, or actual power available.

There are several ways of defining the power factor, any of which requires some explanation. The power factor may be defined as: *The number of watts indicated by a wattmeter, divided by the apparent watts*, the latter being the *watts as measured by a voltmeter and ammeter*.

The power factor may be expressed as being equal to

$$\frac{\text{true power}}{\text{apparent power}} = \frac{\text{true watts}}{\text{apparent watts}} = \frac{\text{true watts}}{\text{volts} \times \text{amperes}}$$

**Ques.** What are the true watts?


**Ans.** The watts as measured by a wattmeter.

**Ques.** What are the apparent watts?

**Ans.** The watts obtained by multiplying together the simultaneous voltmeter and ammeter readings.

**Ques.** What is usually meant by power factor?

**Ans.** The multiplier used with the apparent watts to determine how much of the power supplied is available.

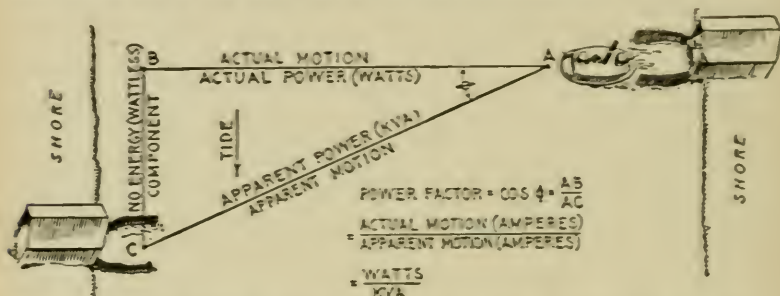

**FIG. 1.343.**—Marine analogy of power factor. A ferry boat in crossing a river to a slip C would head for some point B up stream from C to allow for the effect of the tide. Under such conditions the actual motion (referred to the water) would be from A to B, and the apparent motion, from A to C. Accordingly, the energy expended in propelling the boat from A to B in still water, will propel it from A to C when the tide is running in the direction of the arrow. The effect of the tide is the same as that of inductance or capacity in an alternating circuit, that is, it puts the applied force or thrust (impressed volts) out of phase with the motion of the boat (amperes), this phase difference being indicated by the angle BAC or φ. Now, work (watts) is the product of two factors, pressure (volts) and distance (amperes); accordingly, the apparent work done in propelling the boat from A to C is the product of the thrust of the paddle wheels multiplied by AC, which in analogy corresponds to the product of voltmeter and ammeter readings at the alternator, called "kva." Actually, however, the power is only applied from A to B, the boat being carried sidewise by the tide, as it crosses, a distance BC which represents no energy expended by the paddle wheels. In analogy, the actual power, expended in propelling boat from A to B corresponds to the wattmeter reading in an alternating current power circuit. To obtain the actual work done on the boat, the product of its apparent motion X thrust must be multiplied by a coefficient or power factor because the thrust is applied at an angle to the apparent motion, the power factor being equal to the cosine of this angle, (φ) or AB ÷ AC. Similarly, when there is phase difference between pressure and alternating current, the voltmeter and ammeter readings must be multiplied by the power factor or cos φ to give the output of an alternator available for external work, the excess power indicated by ammeter and voltmeter readings, performing no external work, but causing objectionable heating of the alternator.

**Ques.** Upon what does the power factor depend?

**Ans.** Upon the relative amounts of resistance inductance and capacity contained in the circuit.

**Ques.** How does the power factor vary in value?

**Ans.** It varies from one to zero.

The power factor, as will be shown later, is equal to the *cosine of the angle of phase difference*; its range then is from one to zero because these are the limiting values of the cosine of an angle (neglecting the + or - sign).

**Ques.** What is the effect of lag or lead of the current on the power factor?

**And.** It causes it to become less than one.

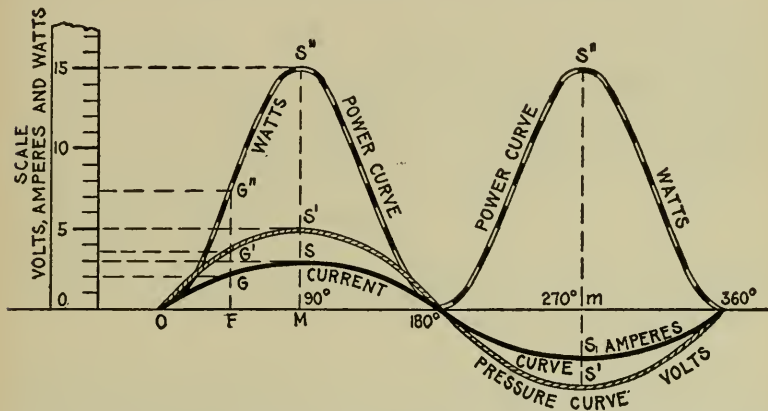


FIG. 1,344.—Method of drawing the power curve from the pressure and current curves. As shown, the same scale is used for all curves. This as a rule, makes the power curve inconveniently high, hence it is usually drawn to smaller scale as in fig. 1,345.

**How to Obtain the Power Curve.**—Since under any phase condition, the power at any instant is equal to the product of the pressure multiplied by the current at that instant, a curve may be easily plotted from the pressure and current curves, giving the instantaneous values of the power through a complete cycle.

In fig 1,344, from the zero line of the current and pressure curves, draw any ordinate as at F cutting the current curve at G and the pressure

curve at  $G'$ . The values for current and pressure at this point are from the scale, 2 amperes and 3.7 volts. Since watts = amperes  $\times$  volts, the ordinate  $FG$  is to be multiplied by ordinate  $FG'$  that is,

$$2 \times 3.7 = 7.4.$$

Project up through  $F$  the ordinate  $FG'' = 7.4$ , and this will give one point on the power curve.

Similarly at another point, say  $M$ , where the current and pressure are maximum

$$MS \times MS' = MS'', \text{ that is}$$

$$3 \times 5 = 15$$

giving  $S''$  another point on the curve. Obtaining several points in this way the power curve is then drawn through them as shown.

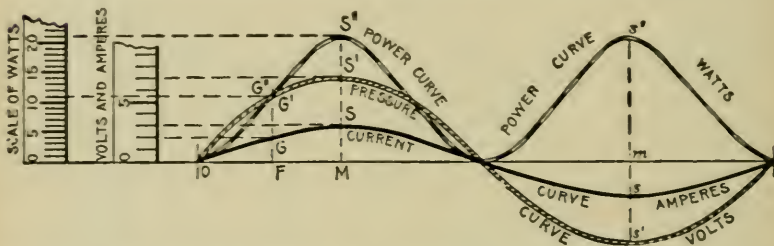


FIG. 1,345.—Usual method of drawing power curve from the pressure and current curves. A smaller scale is employed for the power curve in order to reduce its height.

**Ques.** Why is the power curve positive in the second half of the period when there are negative values of current and pressure?

**Ans.** Because the product of two negative quantities is positive.

**Ques.** Does fig. 1,344 represent the usual way of drawing a power curve?

**Ans.** Since ordinates of the power curve are products of the current and pressure ordinates, they will be of inconvenient

length if drawn to the same scale; it is therefore customary to use a different scale for the power ordinates, as in fig. 1,345.

The illustration is lettered identical with fig. 1,344, with which it should be compared.

**Synchronism of Current and Pressure; Power Factor Unity.**—The current and pressure would be in phase as represented in fig. 1,346 were it possible to have a circuit contain-

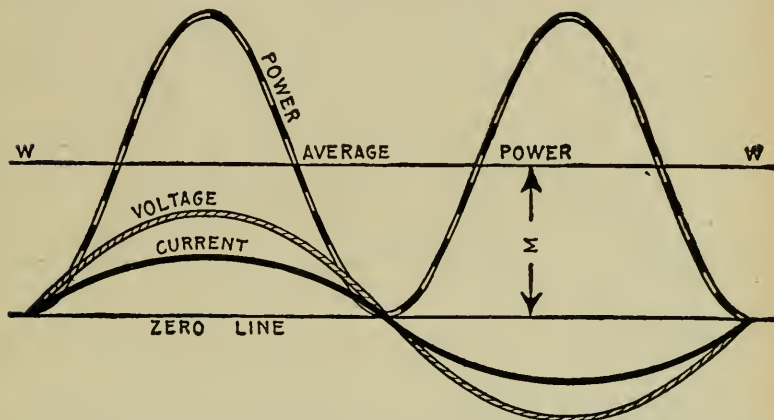


FIG. 1,346.—Synchronism of current and pressure. Power curve showing that the power factor is unity. This is indicated by the fact that the power curve does not project below the base or zero line.

ing resistance only. In actual practice all circuits contain at least a small amount of reactance.

A circuit supplying nothing but incandescent lamps comes very nearly being all resistance, and may be so considered in the discussion here. Fig. 1,347 illustrates a circuit containing only resistance. In such a circuit the pressure and current (as shown in fig. 1,346) pass through zero and through their maximum values together.

Multiplying instantaneous values of volts and amperes will give the power curve, as before explained, whose average value is half-way between the zero line and the maximum of the curve; that part of the power curve above the line of average power  $WW$ , exactly filling the open space below the line  $WW$ . That is,

$$\begin{aligned}\text{average power} &= \text{maximum power} \div \sqrt{2} \\ &= \frac{\text{maximum voltage} \times \text{maximum current}}{\sqrt{2}} \\ &= \text{virtual voltage} \times \text{virtual current}.\end{aligned}$$

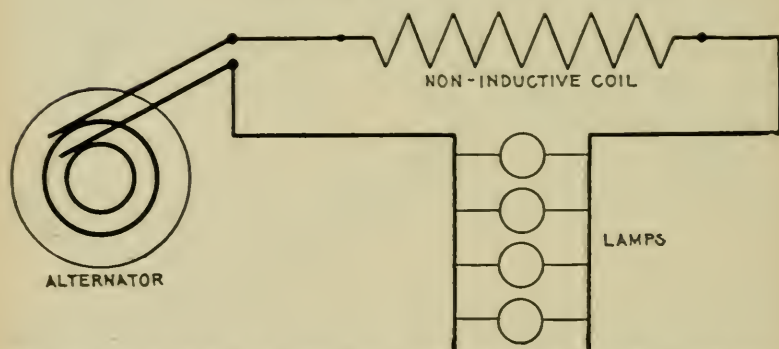


FIG. 1,347.—Diagram of circuit containing only resistance; in such a circuit the power factor is unity.

This latter is simply the product of the voltmeter and ammeter readings which gives the watts just the same as in direct current.

**Ques.** What should be noticed about the power curve?

**Ans.** Its position with respect to the zero line; it lies wholly above the zero line which denotes that all the power delivered to the circuit except that dissipated by friction is useful, that is, the



power factor is unity. Hence, to keep the power factor as near unity as possible is one of the chief problems in alternating current distribution.

**Ques.** Can the power factor be less than unity if the current and pressure be in phase?

**Ans.** Yes, if the waves of current and voltage be distorted as in fig. 1,348.

**Effect of Lag and Lead.**—In an alternating circuit the amount of power supplied depends on the phase relationship of the current and pressure. As just explained, when there is

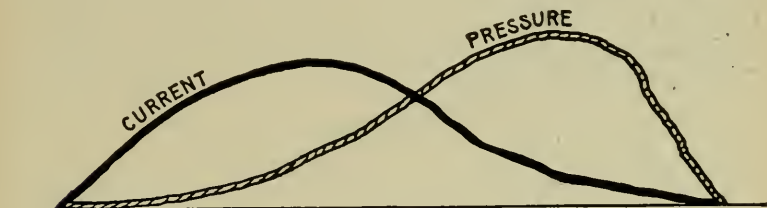


FIG. 1,348.—Case of synchronism of current and pressure with power factor less than unity. Suppose the waves of current and voltage to be in phase, but distorted in form, and not symmetrical, so that they do not run uniformly together, as shown in the figure. Then the real power factor may not be unity, although indicated as such by the power factor meter. However, the switchboard instruments are made to show the angle of lag as the power factor, because the error due to wave distortion is generally too small to be considered.

synchronism of current and pressure, that is, when they are in phase (as in fig. 1,346) the power factor is unity, assuming no distortion of current and pressure waves. In all other cases the power factor is less than unity that is, *the effect of lag or lead is to make the power factor less than unity.*

The effect of lag on the power factor may be illustrated by fig. 1,349, in which the angle between the pressure and current, or the angle of lag is taken as  $40^\circ$ , corresponding to a power factor of .766. Plotting the power curve from the products

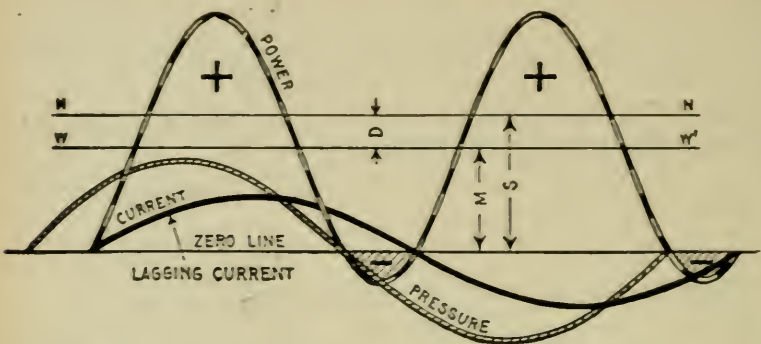


FIG. 1,349.—Effect of lag on the power factor. When the current lags behind the pressure the power factor becomes less than unity. It will be seen that the power curve projects below the zero line giving the shaded area which represents negative power which must be subtracted from the + areas above the zero line to get the net power. In the figure the line WW' is drawn at a height corresponding to the average power, and HN at a height corresponding to the average power that would be developed if the current were in phase with the pressure. The power factor then is represented by  $M \div S$ , and by inspection of the figure it is seen that this is less than unity.

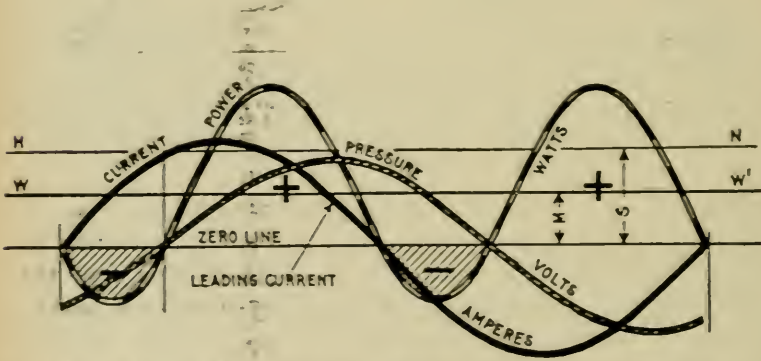


FIG. 1,351.—Effect of lead on the power factor. When the current is in advance of the pressure the power factor becomes less than unity. The curve, as shown, projects below the zero line, giving the shaded area which represents negative power which must be subtracted from the + areas above the zero line to get the net power. As in fig. 1,349, the line WW' at a height M represents the average power, and HN the average power for synchronism of current and pressure. The power factor then is  $M \div S$  which is less than unity.

of instantaneous volts and amperes taken at various points, the power curve is obtained, a portion of which lies below the horizontal line. The significance of this is that at certain times, the current is flowing in the opposite direction to that in which the impressed pressure would send it. During this part of the period

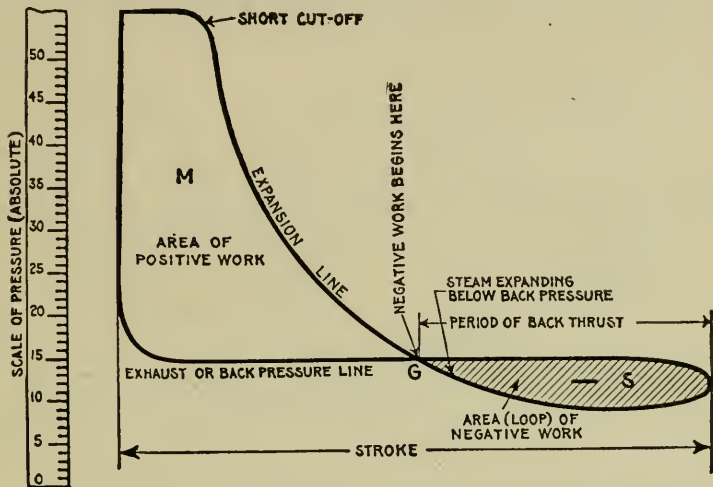


FIG. 1,351.—Steam engine analogy of power factor. The figure represents an indicator card of an engine in which the steam distribution is such that the steam is expanded below the back pressure line, that is below the pressure of the exhaust. This results in *negative work* which must be overcome by the *momentum* or *kinetic energy* previously stored in the fly wheel, and which is represented on the diagram by the shaded loop S. If the exhaust valve had opened at G, the amount of work done during the revolution would be represented by the area M, but continuing the expansion below the back pressure line, the work done is  $M - S$ . This latter case as compared with the first when expansion does not continue below the back pressure line gives an efficiency (power factor) of  $(M - S) \div M$ , the shaded area representing so much loss.

conditions are reversed, and the power (indicated by the shaded area), instead of being supplied by the source to the circuit, is being supplied by the circuit to the source.

This condition is exactly analogous to the case of a steam engine, expanding the steam below the back or exhaust pressure, a condition sometimes caused by the action of the governor in considerably reducing

the cut off for very light load. An indicator diagram of such steam distribution is shown in fig. 1,351. This gives a negative loop in the diagram indicated by the shaded section.

It must be evident that the average pressure of the shaded loop portion of the diagram must be subtracted from that of the other portion, because during the expansion below the exhaust pressure line, the back pressure is in excess of the forward pressure exerted on the piston by the expanding steam, and the engine would accordingly reverse its motion, *were it not for the energy previously stored up in the fly wheel in the form of momentum*, which keeps the engine moving during this period of back thrust. Evidently the shaded area must be subtracted from

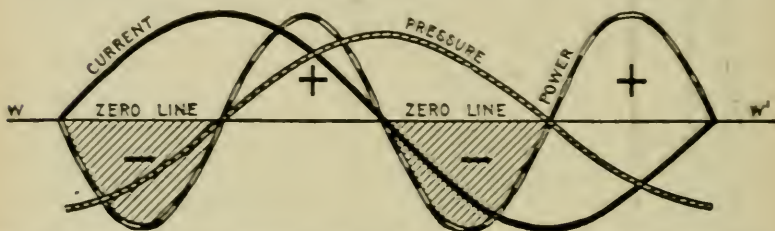


FIG. 1,352.—Power curve illustrating the so-called wattless current in which case the power factor is zero. By noting that the curve projects equally on each side of the zero line, the + power areas equal the negative power areas, hence the summation of these areas for the period is zero, that is, the two + areas minus the two shaded areas equal zero. It should be noted that the line of average power  $WW'$ , which is visible in the other figures, here coincides with the zero line, and the average power then is zero, since the positive part above the zero line is equal to and offsets the negative (shaded) part below the line. This is the case of "wattless" current and (considering a circuit with resistance so small that it may be considered as zero) shows plainly the possibility of having full load current and voltage on a circuit yet delivering no power, the current simply surging to and fro without an actual transfer of power.

the positive area to obtain the net work done during the stroke. Hence following the analogy as far as possible if  $M$  work (watts) be done during each revolution (cycle) when steam does not expand below back pressure (when current and pressure are in phase), and  $S$  negative work (negative watts) be done when steam expands below back pressure (when there is lag), the efficiency (power factor) is  $(M - S) \div M$ .

**"Wattless Current"; Power Factor Zero.**—When the power factor is zero, it means that the phase difference between the current and the pressure is  $90^\circ$ .

The term *wattless current*, as understood, does not indicate an absence of electrical energy in the circuit; its elements are there,

but not in an available form for external work. The false power due to the so called wattless current pulsates in and out of the circuit without accomplishing any useful work.

An example of wattless current, showing that the power factor is zero is illustrated in fig. 1,353. Here the angle of lag is  $90^\circ$ , that is, the current is  $90^\circ$  behind the pressure.

The power curve is constructed from the current and pressure curves, and, as shown in the diagram, it lies as much below the zero line

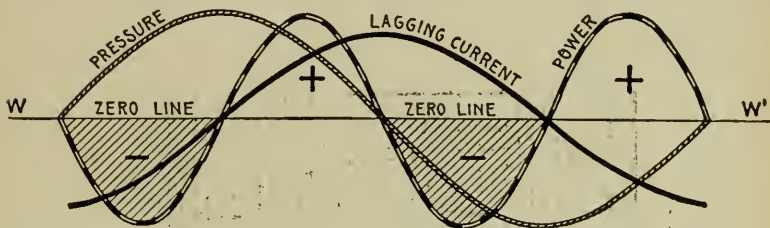


FIG. 1,353.—Example of wattless current showing that the power factor is zero when the phase difference between current and pressure is  $90^\circ$ . For zero power factor the current may lead  $90^\circ$  as in fig. 1,352, or lag  $90^\circ$  as here shown. Since the shaded or negative areas = the plus areas, the average power (indicated by  $WW'$  which coincides with the zero line) is zero, that is the circuit is carrying current under pressure yet delivering no power, hence, the power factor is zero.

as above, that is, the two plus power areas which occur during each period are equal to the two negative (shaded) power areas, showing that the circuit returns as much energy as is sent out. Hence, the total work done during each period is zero, indicating that although a current be flowing, this current is not capable of doing external work.

**Ques.** Is the condition as just described met with in practice?

**Ans.** No.

**Ques.** Why not?

**Ans.** The condition just described involves that the circuit have no resistance, all the load being reactance, but it is impossible to have a circuit without some resistance, though the



resistance may be made very small in comparison to the reactance so that a close approach to wattless current is possible.

**Ques.** Give some examples where the phase difference is very nearly  $90^\circ$ .

**Ans.** If an alternator supply current to a circuit having a very small resistance and very large inductance, the current would lag nearly  $90^\circ$  behind the pressure. The primary current of a transformer working with its secondary on open circuit is a practical example of a current which represents very little energy.

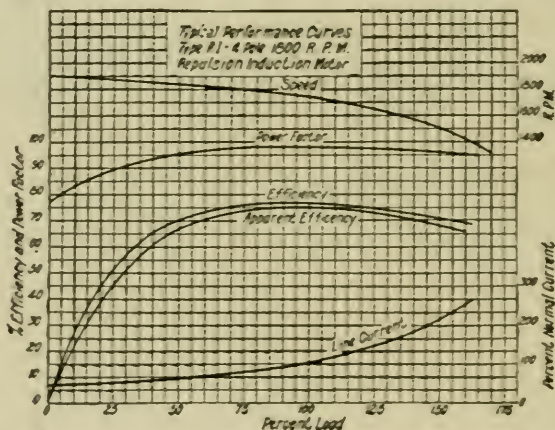


FIG. 1,354.—Performance curves of General Electric single phase repulsion induction motor.

**Ques.** When the phase difference between the current and pressure is  $90^\circ$ , why is the current called “wattless”?

**Ans.** Because the product of such a current multiplied by the pressure does not represent any watts *expended*.

A man lifting a weight, and then allowing it to descend the same distance to its initial position, as shown in figs. 1,355 to 1,357, presents a mechanical analogy of wattless current.

Let the movement of the weight represent the current and the weight the pressure. Then calling the weight 10 pounds (volts), and the distance two feet (amperes). The work done by the man (alternator) on the weight in lifting it is




$$\begin{aligned} 10 \text{ pounds} \times 2 \text{ feet} &= 20 \text{ foot pounds} \dots\dots\dots (1) \\ (10 \text{ volts} \times 2 \text{ amperes} &= 20 \text{ watts.}) \end{aligned}$$

The work done on the man by the weight in forcing his hand down as his muscles relax is

$$\begin{aligned} 10 \text{ pounds} \times 2 \text{ feet} &= 20 \text{ foot pounds} \dots\dots\dots (2) \\ (10 \text{ volts} \times 2 \text{ amperes} &= 20 \text{ watts.}) \end{aligned}$$

WORK DONE BY MAN.  
WEIGHT ACQUIRES  
POTENTIAL ENERGY

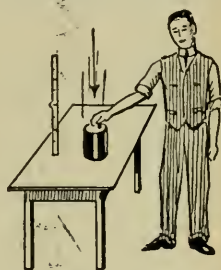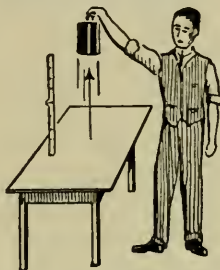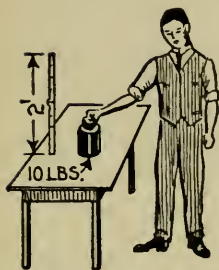WORK DONE BY WEIGHT.  
MAN ACQUIRES  
POTENTIAL ENERGY.



FIGS. 1.355 to 1.357.—Mechanical analogy of wattless current. If a man lift a weight any distance, as from the position of fig. 1.355 to position of fig. 1.356, he does a certain amount of work on the weight giving it potential energy. When he lowers it to its original position, as in fig. 1.357, the weight loses the potential energy previously acquired, that is, it is given back to the man, the "system" (man and weight) having returned to its original condition as in fig. 1.355. During such a cycle, the work done by the man on the weight is equal to the work done by the weight on the man and no useful external work has been accomplished.

From (1) and (2) it is seen that the *work done by the man on the weight is equal to the work done by the weight on the man*, hence no useful work has been accomplished; that is, the potential energy of the weight which it originally possessed has not been increased.

**Why the Power Factor is equal to  $\cos \phi$ .**—In the preceding figures showing power curves for various phase relations between current and pressure, the curves show the instantaneous values of the fluctuating power, but what is of more importance, is to determine the average power developed.



When the current is in phase with the pressure, it is a simple matter, because the power or

$$\text{watts} = \text{amperes} \times \text{volts}$$

that is, the product of the ammeter and voltmeter readings will give the power. However, the condition of synchronism of current and pressure hardly ever exists in practice, there being more or less phase difference.

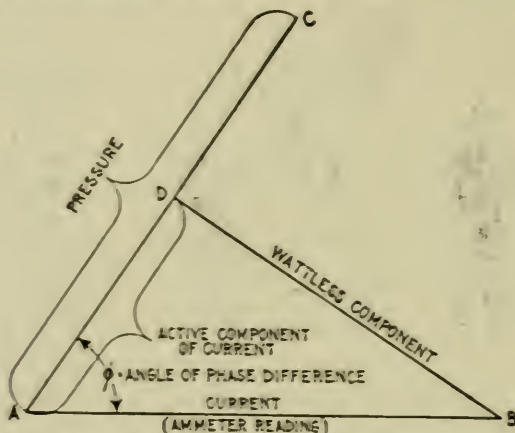


FIG. 1,258.—Method of obtaining the active component of the current; diagram illustrating why the power factor is equal to  $\cos \phi$ . If AB and AC be respectively the given current and pressure, or readings of the ammeter and voltmeter, and  $\phi$  the angle of phase difference between current and pressure, then drawing from B, BD perpendicular to AC will give AD the active component. Now, true power =  $AC \times AD$ , but  $AD = AB \cos \phi$ , hence true power =  $AC \times AB \cos \phi$ . Again, apparent power =  $AC \times AB$ , and since true power = apparent power  $\times$  power factor, the power factor =  $\cos \phi$ .

When the current is not in phase with the pressure, it is considered as made up of two components at right angles to each other.

1. The active component, in phase with the pressure;
2. The wattless component, at right angles to the pressure.

With phase difference between current and pressure the product of ammeter and voltmeter readings do not give the true

power, and in order to obtain the latter, the *active component* of the current in phase with the pressure must be considered, that is,

$$\text{true power} = \text{volts} \times \text{active amperes} \dots \dots \dots (1)$$

The active component of the current is easily obtained graphically as in fig. 1,358.

With any convenient scale draw AB equal to the current as given or read on the ammeter, and AC, equal to the pressure, making the angle  $\phi$  between AB and AC equal to the phase difference between the current and pressure.

From B, draw the line BD perpendicular to AC, then BD will be the wattless component, and AD (measured with the same scale as was used for AB) the active component of the current, or that component in phase with the pressure.

Hence from equation (1)

$$\text{true power} = \text{AC} \times \text{AD} \dots \dots \dots (2)$$

Now in the right triangle ABD

$$\frac{\text{AD}}{\text{AB}} = \cos \phi$$

from which

$$\text{AD} = \text{AB} \cos \phi \dots \dots \dots (3)$$

Substituting this value of AD in equation (2) gives

$$\text{true power} = \text{AC} \times \text{AB} \cos \phi \dots \dots \dots (4)$$

Now the power factor may be defined as: *that quantity by which the apparent watts must be multiplied in order to give the true power.* That is

$$\text{true power} = \text{apparent watts} \times \text{power factor} \dots \dots (5)$$

Comparing equations (4) and (5),  $\text{AC} \times \text{AB}$  in (4) is equal to the apparent watts, hence, the power factor in (5) is equal to  $\cos \phi$ . That is, *the power factor is numerically equal to the cosine of the angle of phase difference between current and pressure.*

**EXAMPLE I.**—An alternator supplies a current of 200 amperes at a pressure of 1,000 volts. If the phase difference between the current and pressure be  $30^\circ$ , what is the true power developed?

In fig. 1,359, draw AB to scale, equal to 200 amperes, and draw AC of indefinite length making an angle of  $30^\circ$  with AB. From B, draw BD perpendicular to AC which gives AD, the active component, and which measured with the same scale as was used in laying off AB, measures 173.2 amperes. The true power developed then is

$$\text{true watts} = 173.2 \times 1,000 = 173.2 \text{ kw.}$$

The true power may be calculated thus:

From the table  $\cos 30^\circ = .866$ , hence

$$\text{true watts} = 200 \times 1,000 \times .866 = 173.2 \text{ kw.}$$

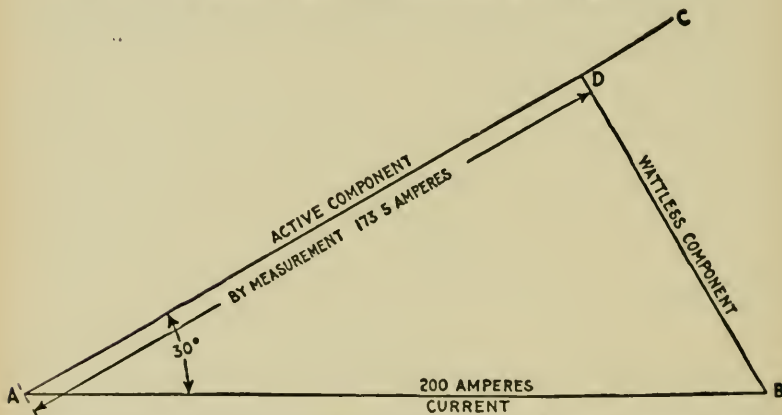


FIG. 1,359.—Diagram for obtaining the active component of the current in a circuit having a current of 200 amperes and angle of lag of  $30^\circ$ .

**EXAMPLE II.**—If in an alternating current circuit, the voltmeter and ammeter readings be 110 and 20 and the angle of lag  $45^\circ$ , what is the apparent power and true power?

The apparent power is simply the product of the current and pressure readings or

$$\text{apparent power} = 20 \times 110 = 2,200 \text{ watts}$$

The true power is the product of the apparent power multiplied by the cosine of the angle of lag.  $\cos 45^\circ = .707$ , hence

$$\text{true power} = 2,200 \times .707 = 1,555.4 \text{ watts.}$$

**Ques.** Does the power factor apply to capacity reactance in the same way as to inductance reactance?

**Ans.** Yes. The angles of lag and of lead, are from the practical standpoint, treated as if they lay in the first quadrant of the circle. Even the negative sign of the tangent  $\phi$  when it occurs is simply used to determine whether the angle be one of lag or of lead, but in finding the value of the angle from a table it is treated as a positive quantity.

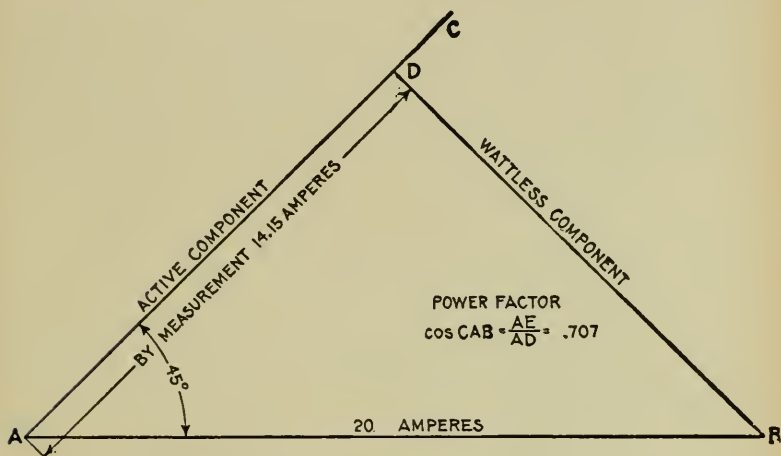


FIG. 1,360.—Diagram for obtaining the power factor for example II. With convenient scale, lay off  $AB = 20$  amperes. From  $A$  draw  $AC$  at  $45^\circ$  to  $AB$ , and from  $B$ , draw  $BD$  perpendicular to  $AC$ . Then, the power factor which is equal to cosine of angle of lag,  $= AD \div AB = (\text{by measurement}) 14.15 \div 20 = .707$ .

**Ques.** In introducing capacity into a circuit to increase the power factor what should be considered?

**Ans.** The cost and upkeep of the added apparatus as well as the power lost in same.

**Ques.** How is power lost in a condenser?

**Ans.** The loss is principally due to a phenomenon known as *dielectric hystereses*, which is somewhat analogous to magnetic hysteresis. The rapidly alternating charges in a condenser placed in an alternating circuit may be said to cause alternating polarization of the dielectric, and consequent heating and loss of energy.

**Ques.** When is inductance introduced into a circuit to increase the power factor?

**Ans.** When the phase difference is due to an excess of capacity.

**EXAMPLE.**—A circuit having a resistance of 3 ohms, and a resultant reactance of 4 ohms, is connected to a 100 volt line. What is: 1, the impedance, 2, the current, 3, the apparent power, 4, the angle of lag, 5, the power factor, and 6, the true power?

1. *The impedance of the circuit.*

$$Z = \sqrt{3^2 + 4^2} = 5 \text{ ohms.}$$

2. *The current.*

$$\text{current} = \text{volts} \div \text{impedance} = 100 \div 5 = 20 \text{ amperes.}$$

3. *The apparent power.*

$$\text{apparent power} = \text{volts} \times \text{amperes} = 100 \times 20 = 2,000 \text{ watts.}$$

4. *The tangent of the angle of lag.*

$$\tan \phi = \text{reactance} \div \text{resistance} = 4 \div 3 = 1.33. \text{ From table of natural tangents (page 451) } \phi = 53^\circ.$$

5. *The power factor.*

The power factor is equal to the cosine of the angle of lag, that is, power factor =  $\cos 53^\circ = .602$  (from table).

6. *The true power.*


The true power is equal to the apparent watts multiplied by the power factor, or

$$\begin{aligned} \text{true power} &= \text{volts} \times \text{amperes} \times \cos \phi \\ &= 100 \times 20 \times .602 = 1,204 \text{ watts.} \end{aligned}$$

**Ques.** Prove that the power factor is unity when there is no resultant reactance in a circuit.

**Ans.** When there is no reactance,  $\tan \phi$  which is equal to reactance  $\div$  resistance becomes  $0 \div R = 0$ . The angle  $\phi$

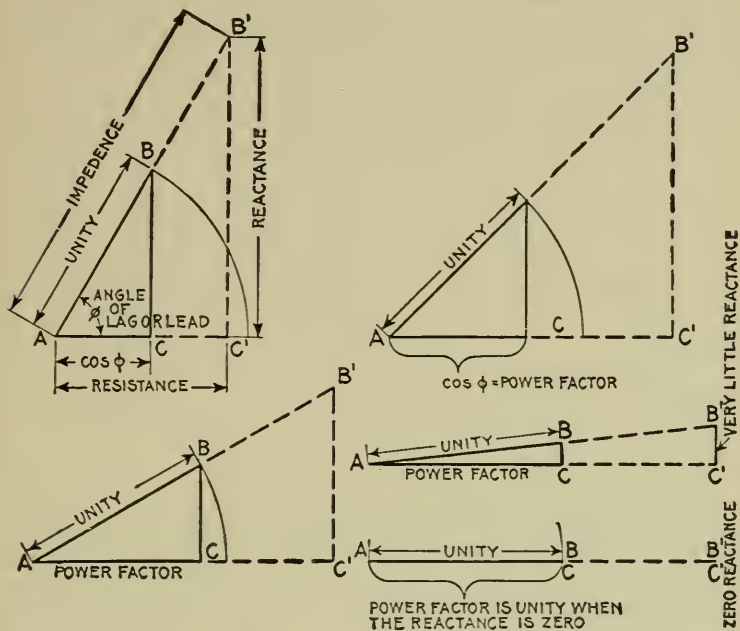(the phase difference angle) whose tangent is 0 is the angle of 0 degrees. Hence, the power factor which is equal to  $\cos \phi = \cos 0^\circ = 1$ .



FIGS. 1,361 to 1,365.—Diagrams illustrating why the power factor is unity or one when there is no resultant reactance in the circuit, that is, when the circuit is resonant, or has only resistance. The power factor is equal to the cosine of the angle of lag (or lead). In the figures this angle is BAC or  $\phi$  and the value of the *natural cosine* AC gives the power factor. By inspection of the figures, it is evident that decreasing the reactance decreases the angle  $\phi$  and increases  $\cos \phi$  or the power factor. The circular arc in each figure being at unity distance from the center A, the power factor with decreasing reactance evidently approaches unity as its limit, this limit being shown in fig. 1,365 where the reactance  $B'C' = 0$ .

**Ques.** What is the usual value of the power factor in practice?

**Ans.** Slightly less than one.



**Ques.** Why is it desirable to keep the power factor near unity?

**Ans.** Because with a low power factor, while the alternator may be carrying its full load and operating at a moderate temperature, the consumer is paying only for the actual watts which are sent over the line to him.

For instance, if a large alternator supplying 1,000 kilowatts at 6,600 volts in a town where a number of induction motors are used on the

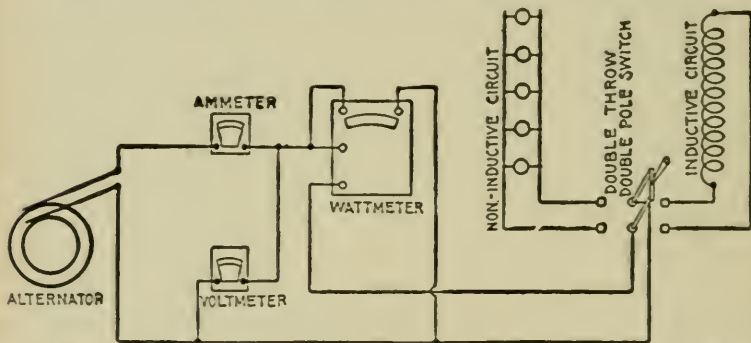


FIG. 1,366.—Diagram illustrating power factor test, when on non-inductive and inductive circuits. The instruments are connected as shown and by means of the double throw switch can be put on either the non-inductive or inductive circuit. First turn switch to left so that current passes through the lamps: for illustration, the following readings are assumed: ammeter 10, voltmeter 110, and wattmeter 1,100. The power factor then is wattmeter reading  $\div$  volts  $\times$  amperes =  $1,100 \text{ actual watts} \div 1,100 \text{ apparent watts} = 1$ , that is, on non-inductive circuit the power factor is unity. Now throwing the switch to the right connecting instruments with the inductive circuits, then for illustration the following readings may be assumed: ammeter 8, voltmeter 110, and wattmeter 684. Now, as before, power factor = wattmeter reading  $\div$  volts  $\times$  amperes =  $684 \div (8 \times 110) = 684 \div 880 = .78$ .

line be operating with a power factor of say .625 during a great portion of the time, the switchboard instruments connected to the alternator will give the following readings:

Voltmeter 6,600 volts; ammeter 242.4 amperes; power factor meter .625.

The apparent watts would equal 1,600,000 watts or 1,600 kilowatts, which, if multiplied by the power factor .625 would give 100,000,000 watts or 1,000 kilowatts which is the actual watts supplied. The alternator and line must carry 242.4 amperes instead of 151 amperes and the difference  $242.4 - 151 = 91.4$  amperes represents a *wattless current* flowing in the circuit which causes useless heating of the alternator.



The mechanical power which is required to drive the alternator is equivalent to the actual watts produced, since that portion of the current which lags, is out of phase with the pressure and therefore requires no energy.

**Ques.** How are alternators rated by manufacturers in order to avoid disputes?

**Ans.** They usually rate their alternators as producing so many kilovolt amperes instead of kilowatts.

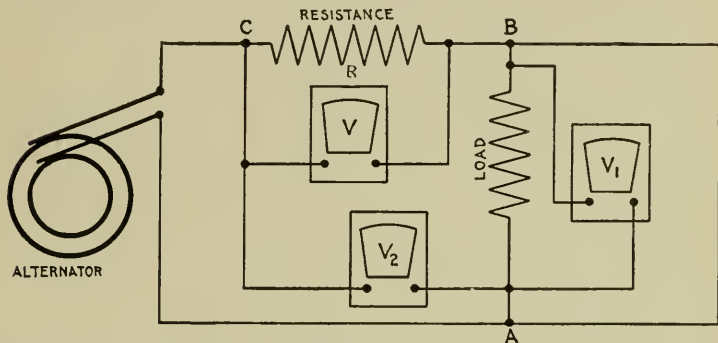


FIG. 1,367.—Ayrton and Sumpner method of alternating current power measurement. Three voltmeters are required, and accordingly the method is sometimes called the three voltmeter method. It is a good method where the voltage can be regulated to suit the load. In the figure, let the non-inductive resistance  $R$  be placed in series with the load  $AB$ . Measure the following voltages:  $V$  across the terminals of  $R$ ,  $V_1$  across the load  $AB$ , and  $V_2$  across both, that is from  $A$  to  $C$ . Then, true watts =  $(V_2^2 - V_1^2 - V^2) \div 2R$ . The best conditions are when  $V = V_1$ , and, if  $R = \frac{1}{2}$  ohm, then  $W = V_2^2 - V_1^2 - V^2$ .

**Ques.** What is a kilovolt ampere (kva)?

**Ans.** A unit of apparent power in an alternating current circuit which is equal to one kilowatt when the power factor is equal to one.

The machine mentioned on page 1,120 would be designed to carry 151 amperes without overheating and also carry slight overloads for short periods. It would be rated as 6.6 kilovolts and 151 amperes which would equal approximately 1,000 kilowatts when the power factor is 1 or unity, and it should operate without undue heating. Now the lower the power factor becomes, the greater the heating trouble will be in trying to produce the 1,000 actual kilowatts.

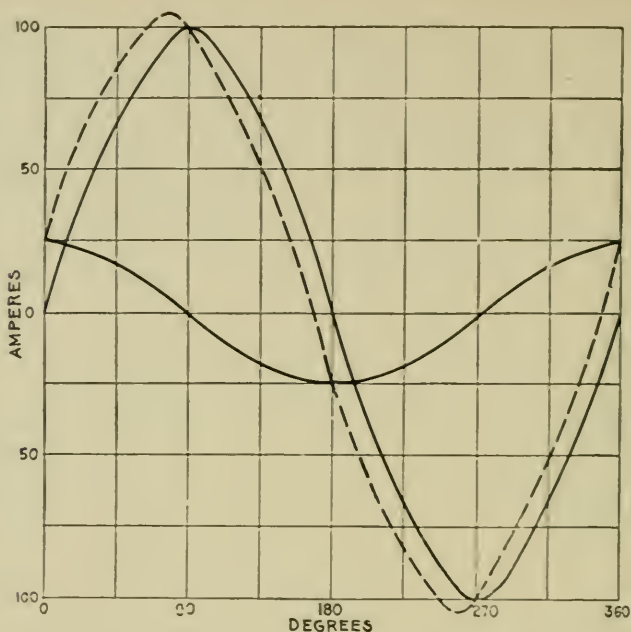


FIG. 1,365—Curves illustrating *power factor*. In a circuit having no capacity or inductance, the power is given by the product of the respective readings of the voltmeter and ammeter, as in the case of a direct current. In the case of a circuit having capacity or inductance, this product is higher than the true value as found by a wattmeter, and is known as the *apparent watts*. The ratio *true watts* ÷ *apparent watts* is known as the *power factor*. The current flowing in an inductive circuit, such as the primary of a transformer, is really made up of two components, as already explained, one of which (the load or active component), is in phase with the pressure, while the other the magnetizing component, is at right angles to it, that is, it attains its crest value when the other is at zero, and vice versa. To illustrate, take a complete cycle divided into 360 degrees and lay out on it the current required to correspond to a given load on the secondary of a transformer, say a crest value of 100 amperes, and at right angles to this lay out the current required for exciting the magnetic circuit of the transformer, giving A, merely for purposes of illustration, a crest value of 25 amperes. Combining these curves, the dotted curve in the figure is obtained and which represents the resultant current that would be indicated by an ammeter placed in the primary circuit of the transformer. It will be noted that this current attains its maximum at a point  $14^{\circ} 2'$  later than the load current, giving the angle of lag. Multiplying the apparent watts by the cosine of the angle of lag gives the true watts. Now assuming the diagram to show the full load condition of the transformer, the angle of lag being  $14^{\circ} 2'$ , the power factor at full load is .97 (.97 being the value of the natural cosine of  $14^{\circ} 2'$  as obtained from table, such as on page 451). With no external load on the transformer, the load component of the current is that necessary to make up the core losses. For instance, at 5 amperes, while the magnetizing current remains as before at 25 amperes, the angle of lag becomes  $78^{\circ} 41'$  and the power factor .196. It is thus seen that in transformers, induction motors, etc., the power factor is a function of the load.

**Ques.** How can the power factor be kept high?

**Ans.** By carefully designing the motors and other apparatus and even making changes in the field current of motors which are already installed.

**Ques.** How is the power factor determined in station operation?

**Ans.** Not by calculation, but by reading a meter which forms one of the switchboard instruments.

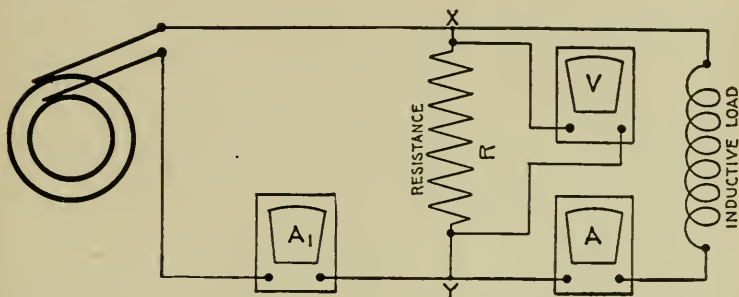


FIG. 1,368.—Fleming's combined voltmeter and ammeter method of measuring power in alternating current circuits. It is quite accurate and enables instruments in use to be checked. In the figure,  $R$  is a non-inductive resistance connected in shunt to the inductive load. The voltmeter  $V$  measures the pressure across the resistance  $XY$ .  $A$  and  $A_1$  are ammeters connected as shown. Then, true watts =  $\left( A_1^2 - A^2 - \left( \frac{V}{R} \right)^2 \right) \times \frac{R}{2}$ . If the voltmeter  $V$  take an appreciable amount of current, it may be tested as follows: disconnect  $R$  and  $V$  at  $Y$ , and see that  $A$  and  $A_1$  are alike; then connect  $R$  and  $V$  at  $Y$  again, and disconnect the load.  $A_1$  will equal current taken by  $R$  and  $V$  in parallel.

**Ques.** When is the power factor meter of importance in station operation, and why?

**Ans.** When rotary converters are used on alternating current lines for supplying direct currents and the sub-station operators are kept busy adjusting the field rheostat of the rotary to maintain a high power factor and prevent overheating of the alternators during the time of day when there is the maximum demand for current or the peak of the load.

EXAMPLE.—An alternator delivers current at 800 volts pressure at a frequency of 60, to a circuit of which the resistance is 75 ohms and .25 henry.

Determine: *a*, the value of the current, *b*, angle of lag, *c*, apparent watts, *d*, power factor, *e*, true power.

*a. Value of current*

$$\begin{aligned}\text{current} &= \frac{\text{pressure}}{\text{impedance}} = \frac{E}{\sqrt{R^2 + (2\pi fL)^2}} \\ &= \frac{800}{\sqrt{75^2 + (2 \times 3.1416 \times 60 \times .25)^2}} = 6.7 \text{ amperes}\end{aligned}$$

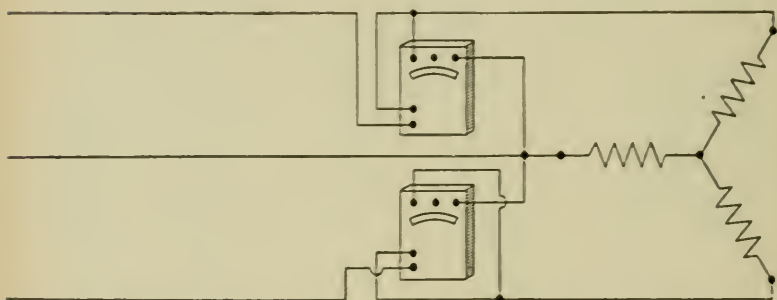


FIG. 1.369.—Wattmeter method of three phase power measurement. Two wattmeters are required in unbalanced systems as shown in the illustration. The total power transmitted is then the algebraic sum of the readings of the two wattmeters. If the power factor be greater than .5, the power is the arithmetical sum, and if it be less than .5, the power is the arithmetical difference of the readings.

*b. The angle of lag*

$$\begin{aligned}\tan \phi &= \frac{\text{reactance}}{\text{resistance}} = \frac{2\pi fL}{R} = \frac{2 \times 3.1416 \times 60 \times .25}{75} = 1.25 \\ \phi &= \text{angle of lag} = 51^\circ 15' \text{ (from table, page 451).}\end{aligned}$$

*c. The apparent power*

$$\begin{aligned}\text{apparent power} &= \text{volts} \times \text{amperes} = 800 \times 6.7 = 5,360 \text{ watts} \\ &= 5.36 \text{ kva.}\end{aligned}$$

*d. The power factor*

$$\begin{aligned}\text{power factor} &= \text{cosine of the angle of lag} \\ &= \cos 51^\circ 15' = .626.\end{aligned}$$

*e. The true power*

$$\begin{aligned}\text{true power} &= \text{apparent power} \times \text{power factor} \\ &= 5,360 \times .626 = 3,355 \text{ watts.}\end{aligned}$$

## CHAPTER XLIX

# ALTERNATORS

**Use of Alternators.**—The great increase in the application of electricity for supplying power and for lighting purposes in industry, commerce, and in the home, is due chiefly to the economy of distribution of alternating current.

Direct current may be used to advantage in densely populated districts, but where the load is scattered, it requires, on account of its low voltage, too great an investment in distributing lines. In such cases the alternator is used to advantage, for while commutators can be built for collecting direct current up to 1,000 volts, alternators can be built up to 12,000 volts or more, and this voltage increased, by step up transformers of high economy, up to 75,000 or 100,000 volts. Since the copper cost is inversely as the square of the voltage, the great advantage of alternating current systems is clearly apparent.

The use of alternating current thus permits a large amount of energy to be economically distributed over a wide area from a single station, not only reducing the cost of the wiring, but securing greater economy by the use of one large station, instead of several small stations.

The higher voltages generated by alternators enables the transmission of electrical energy to vastly greater distances than possible by a direct current system, so that the energy from many waterfalls that otherwise would go to waste may be utilized.

**Classes of Alternator.**—There are various ways of classifying alternators. They may be divided into groups, according to: 1, the nature of the current produced; 2, type of drive; 3, method of construction; 4, field excitation; 5, service requirements, etc.

From these several points of view, alternators then may be classified:

1. With respect to the current, as:

- a.* Single phase;
- b.* Poly phase.

2. With respect to the type of drive, as:

- a.* Belt or chain driven;
- b.* Direct connected.

3. With respect to construction, as:

- a.* Revolving armature;
- b.* Revolving field;
- c.* Inductor.

Homopolar and heteropolar.

4. With respect to mode of field excitation, as:

- a.* Self-exciting;
- b.* Separately excited:  
Exciter direct connected, or gear driven.
- c.* Compositely excited.

5. With respect to service requirements, as:

- a.* Slow speed;
- b.* Fly wheel;
- c.* High speed;
- d.* Water wheel type;
- e.* Turbine driven.



**Single Phase Alternators.**—As a general rule, when alternators are employed for lighting circuits, the single phase machines are preferable, as they are simpler in construction and do not generate the unbalancing voltages often occurring in polyphase work.

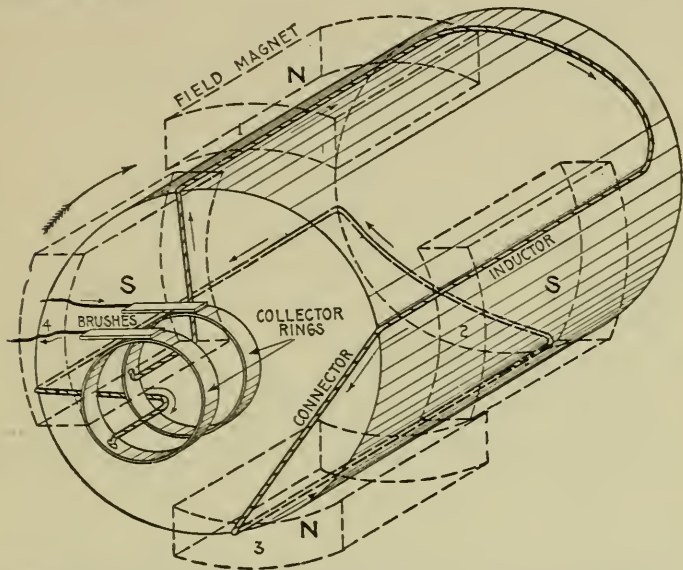


FIG. 1,370.—Elementary four-pole single phase alternator. It has four "inductors" whose pitch is the same as the pole pitch. They are connected in series and terminate at the two collector rings as shown. The poles being alternate N and S, it is evident that there will be two cycles of the current per revolution of the armature. For any number of poles then the number of cycles equals the number of poles divided by two. Applying Fleming's rule for induced currents, the direction of the current induced in the inductors is easily found as indicated by the arrows. The field magnets are excited by coils supplied with direct current, usually furnished from an external source; for simplicity this is not shown. The magnets may be considered as of the permanent type.

**Ques.** What are the essential features of a single phase alternator?

**Ans.** Fig. 1,370 shows an elementary single phase alternator. It consists of an armature, with single phase winding, field



magnets, and two collector rings and brushes through which the current generated in the armature passes to the external circuit.

**Ques.** In what respect do commercial machines differ mostly from the elementary alternator shown in fig. 1,370, and why?

**Ans.** They have a large number of poles and inductors in order to obtain the desired frequency, without excessive speed, and electro-magnets instead of permanent magnets.

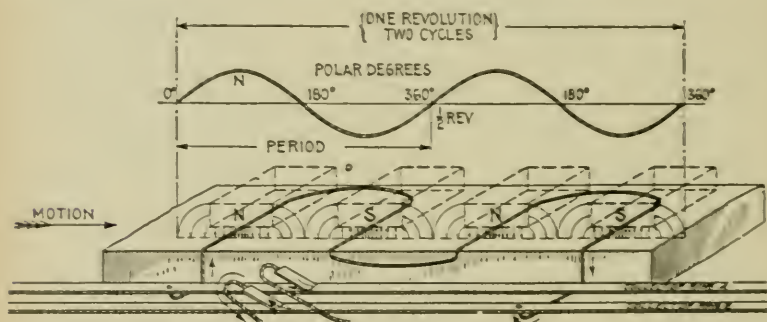



FIG. 1,371.—Developed view of elementary single phase four pole alternator and sine curve showing the alternating current or pressure generated during one revolution. The armature is here shown as a flat surface upon which a complete view of the winding is seen. If  $M$  be any position of an inductor, by projecting up to the curve gives  $N$ , the corresponding value of the current or pressure. Magnetic lines are shown at the poles representing a field decreasing in intensity from a maximum at the center to zero at points half way between the poles, this being the field condition corresponding to the sine form of wave. In actual machines the variation from the sine curve is considerable in some alternators. See figs. 1,247 and 1,248.

**Ques.** In actual machines, why must the magnet cores be spaced out around the armature with considerable distance between them?

**Ans.** In order to get the necessary field winding on the cores, and also to prevent undue magnetic leakage taking place, laterally from one limb to the next of opposite sign.

**Ques.** Is there any gain in making the width of the armature coils any greater than the pole pitch, and why?

**Ans.** No, because any additional width will not produce more voltage, but on the contrary will increase the resistance and inductance of the armature.

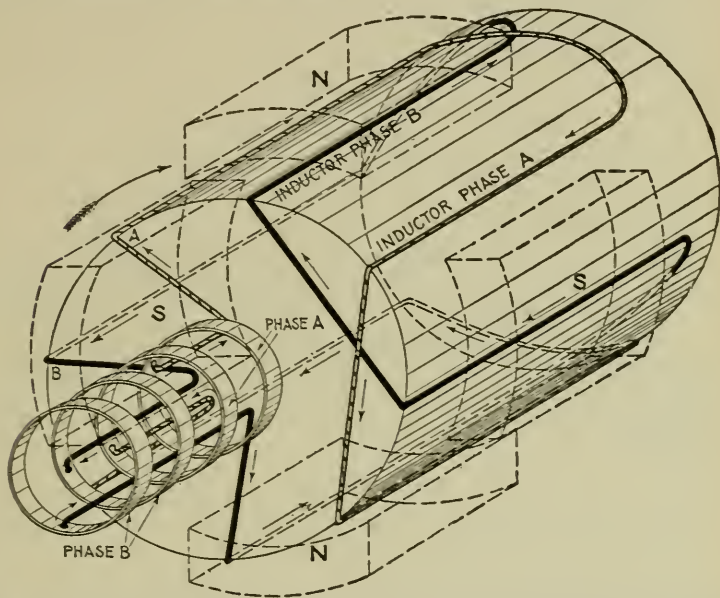

**FIG. 1,372.**—Elementary four pole two phase alternator. The winding consists of one inductor per phase per pole, that is, four inductors per phase, the inductors of each phase being connected in series by the "connectors" and terminating at the collector rings. This arrangement requires four collector rings, giving two independent circuits. The pitch of the inductors of each phase is equal to the pole pitch, and the phase difference is equal to one-half the pole pitch, that is, phase B winding begins at B, a point half-way between inductors A and A' of phase A winding. Hence when the current or pressure in phase A is at a maximum, in the ideal case, when inductor A for instance is under the center of a pole, the current or pressure in B is zero, because B is then half-way between the poles.

**Polyphase Alternators.**—A multiphase or polyphase alternator is one which delivers two or more alternating currents differing in phase by a definite amount.

For example, if two armatures of the same number of turns each be connected to a shaft at 90 degrees from each other and revolved in a bipolar field, and each terminal be connected to a collector ring, two separate alternating currents, differing in phase by 90 degrees, will be delivered to the external circuit. Thus a two phase alternator will deliver two currents differing in phase by one-quarter of a cycle, and similarly a three phase alternator (the three armatures of which are set 120 degrees from each other) will deliver three currents differing in phase by one-third of a cycle.

In practice, instead of separate armatures for each phase, the several windings are all placed on one armature and in such sequence that the

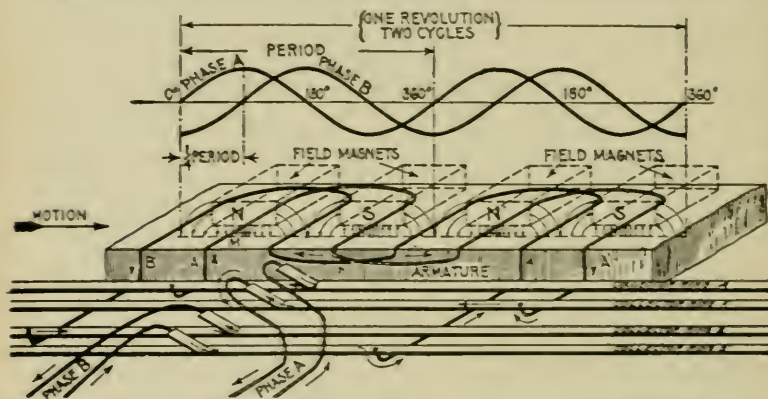


FIG. 1,373—Developed view of elementary two phase four pole alternator and sine curves, showing the alternating current or pressure generated during one revolution of the armature. The complete winding for the three phases are here visible, the field magnets being represented as transparent so that all of the inductors may be seen. By applying Fleming's rule, as the inductors progress under the poles, the directions and reversals of current are easily determined, as indicated by the sine curves. It will be seen from the curves that four poles give two cycles per revolution. Inductors A, and B are lettered to correspond with fig. 1,372, with which they should be compared.

currents are generated with the desired phase difference between them as shown in the elementary diagrams 1,372 and 1,373 for two phase current, and figs. 1,374 and 1,375 for three phase current.

**Ques.** What use is made of two and three phase current?

**Ans.** They are employed rather for power purposes than for lighting, but such systems are often installed for both services.

**Ques.** How are they employed in each case?

**Ans.** For lighting purposes the phases are isolated in separate circuits, that is, each is used as a single phase current. For driving motors the circuits are combined.

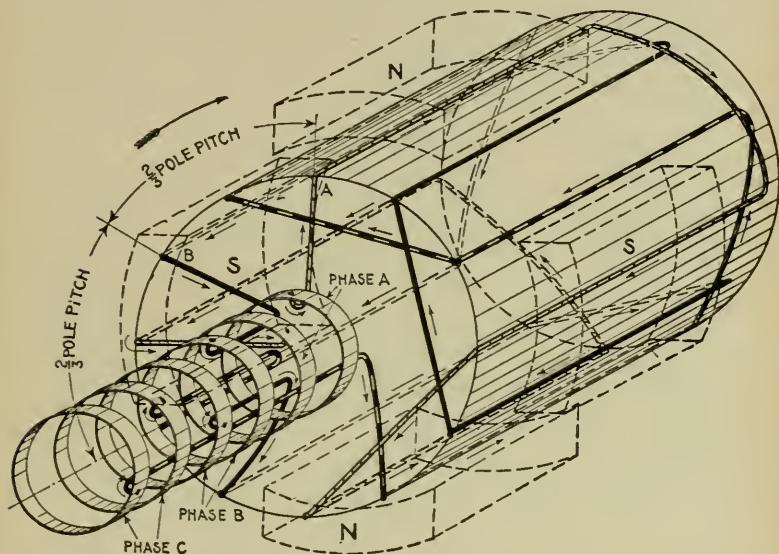


FIG. 1,374.—Elementary four pole three phase alternator. There are three sets of inductors, each set connected in series and spaced on the drum with respect to each other two-thirds pole pitch apart. As shown, six collector rings are used, but on actual three phase machines only three rings are employed, as previously explained. The inductors have distinctive coverings for the different phases. The arrows indicate the direction in which the induced pressures tend to cause currents.

**Ques.** Why are they combined for power purposes?

**Ans.** On account of the difficulty encountered in starting a motor with single phase current.

Ferarris, of Italy, in 1888 discovered the important principle of the production of a rotating magnetic field by means of two or more

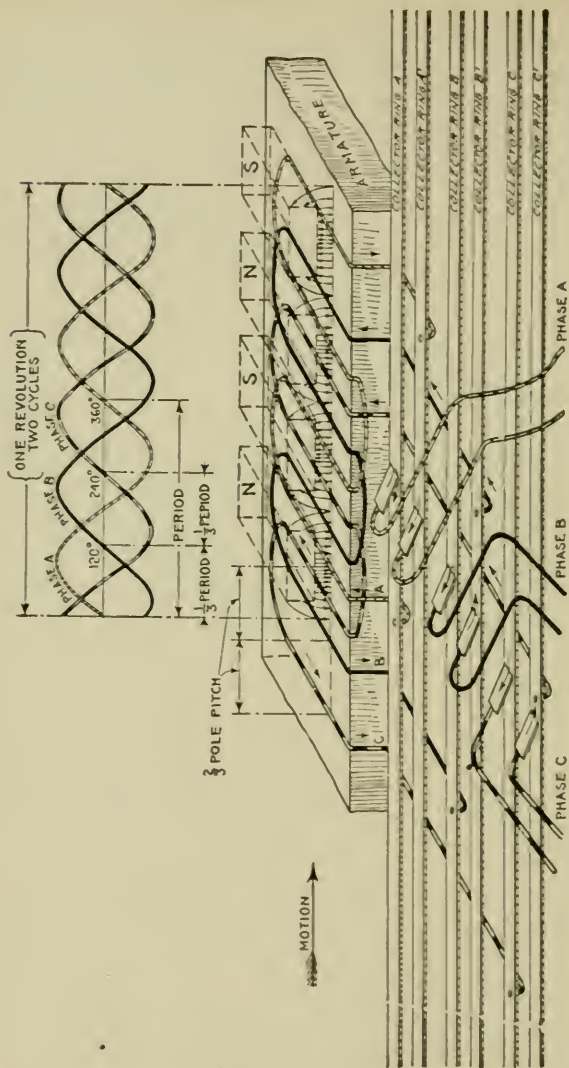


FIG. 1.375.—Elementary four-pole three-phase alternator and sine curves showing current or pressure conditions for one revolution. Six collector rings are shown giving three independent circuits. The pitch of the inductors for each phase is the same as the pole pitch, and the phase difference is equal to two-thirds of the pole pitch, giving the sequence of current or pressure waves as indicated by the sine curves. The waves follow each other at  $\frac{1}{3}$  period, that is, the phase difference is 120 degrees. Inductors A, B, and C, the beginning of each phase winding, are lettered to correspond with fig. 1.374, with which they should be compared.



alternating currents displaced in phase from one another, and he thus made possible by means of the induction motor, the use of polyphase currents for power purposes.

**Ques.** What is the difficulty encountered in starting a motor with single phase current?

**Ans.** A single phase current requires either a synchronous motor to develop mechanical power from it, or a specially constructed motor of dual type, the idea of which is to provide a

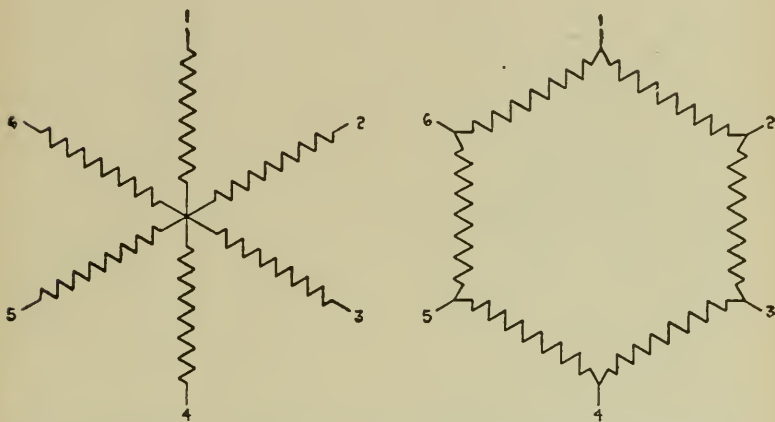


FIG. 1,376.—Diagram of six phase winding with star grouping, being equivalent to a three phase winding in which the three phases are disconnected from each other and their middle points united at a common junction.

FIG. 1,377.—Diagram of six phase winding with mesh grouping.

method of getting rotation by foreign means and then to throw in the single phase current for power.

**Six Phase and Twelve Phase Windings.**—These are required for the operation of rotary converters. The phase difference in a six phase winding is 60 degrees and in a twelve

phase winding 30 degrees. A six phase winding can be made out of a three phase winding by disconnecting the three phases from each other, uniting their middle points at a common junction, as shown by diagram fig. 1,376. This will give a star grouping with six terminals.

In the case of a mesh grouping, each of the three phases must be cut into two parts and then reconnected as shown in fig. 1,377.

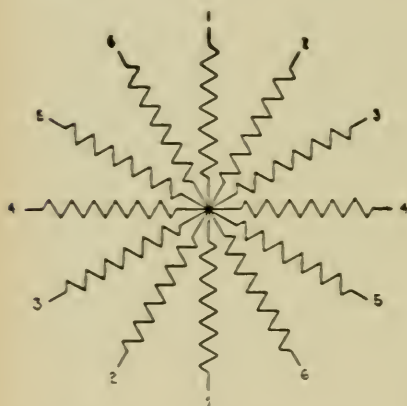


FIG. 1,378.—Diagram of twelve phase winding star grouping.

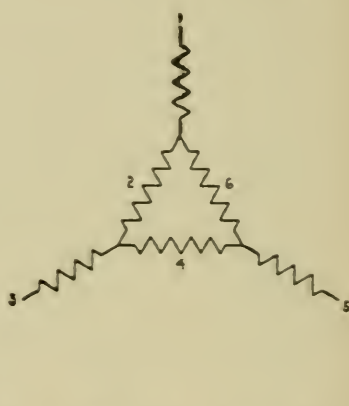


FIG. 1,379.—Diagram of six phase winding consisting of combination of mesh and star grouping.

As the phase difference of a twelve phase winding is one-half that of a six phase winding, the twelve phases may be regarded as a star grouping of six pairs crossed at the middle point of each pair as shown in fig. 1,378, or in mesh grouping for converters they may be arranged as a twelve pointed polygon. They may also be grouped as a combination of mesh and star as shown in fig. 1,379, which, however, is not of general interest.



**Belt or Chain Driven Alternators.**—The mode in which power is transmitted to an alternator for the generation of current is governed chiefly by conditions met with where the machine is to be installed.

In many small power stations and isolated plants the use of a belt drive is unavoidable. In some cases the prime mover is already installed and cannot be conveniently arranged for

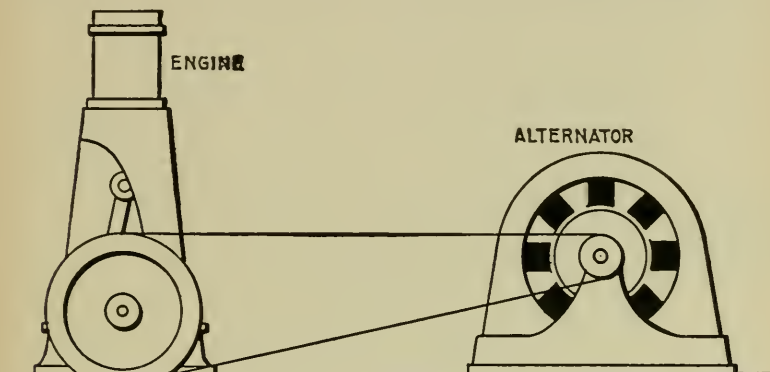


FIG. 1,380.—Belt-driven alternator. By use of a belt, any desired speed ratio is obtained, enabling the use of a high speed alternator which, being smaller than one of slow speed, is cheaper. It affords means of drive for line shaft and has other advantages, but requires considerable space and is not a "positive" drive. Belting exerts a side pull which results in friction and wear of bearings. Means for tightening the belt as shown in fig. 1,381, or equivalent, must be provided.

direct connection, in others the advantage to be gained by an increase in speed more than compensates for the loss involved in belt transmission.

There are many places where belted machines may be used advantageously and economically. They are easily connected to an existing source of power, as, for instance, a line shaft used for driving other machinery, and for comparatively small installations they are lower in first cost than direct connected

machines. Moreover, when connected to line shaft they are run by the main engine which as a rule is more efficient than a small engine direct connected.

Where there is sufficient room between pulley centers, a belt is a satisfactory medium for power transmission, and one that is largely used. It is important that there be liberal distance between centers, especially in the case of generators or motors belted to a medium or slow speed engine, because, owing to the high speed of rotation of the electric machines, there is

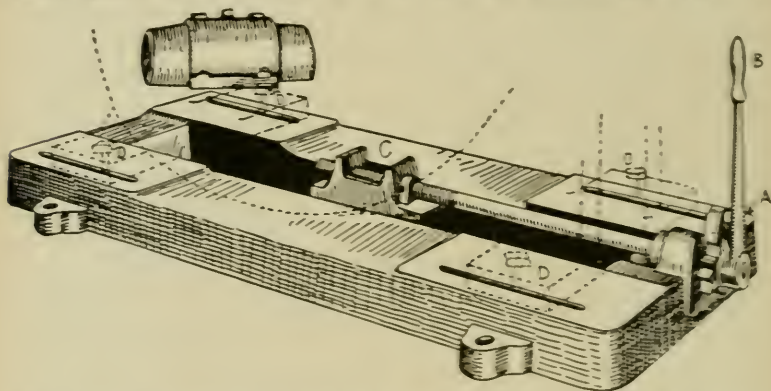


FIG. 1,381.—Sub-base and ratchet device for moving alternator to tighten belt. A ratchet A, operated by lever B, works the block C by screw connection, causing it to move the pulley. The latter, engaging with the frame, causes it to move, thus providing adjustment for belt. After tightening belt, the bolts D, which pass through the slots in the sub-base, are tightened, thus securing the machine firmly in position.

considerable difference in their pulley diameters and the drive pulley diameter; hence, if they were close together, the arc of contact of the belt with the smaller pulley would be appreciably reduced, thus diminishing the tractive power of the belt.

**Ques.** What provision should be made in the design of an alternator to adapt it to belt drive?

**Ans.** Provision should be made for tightening the belt.

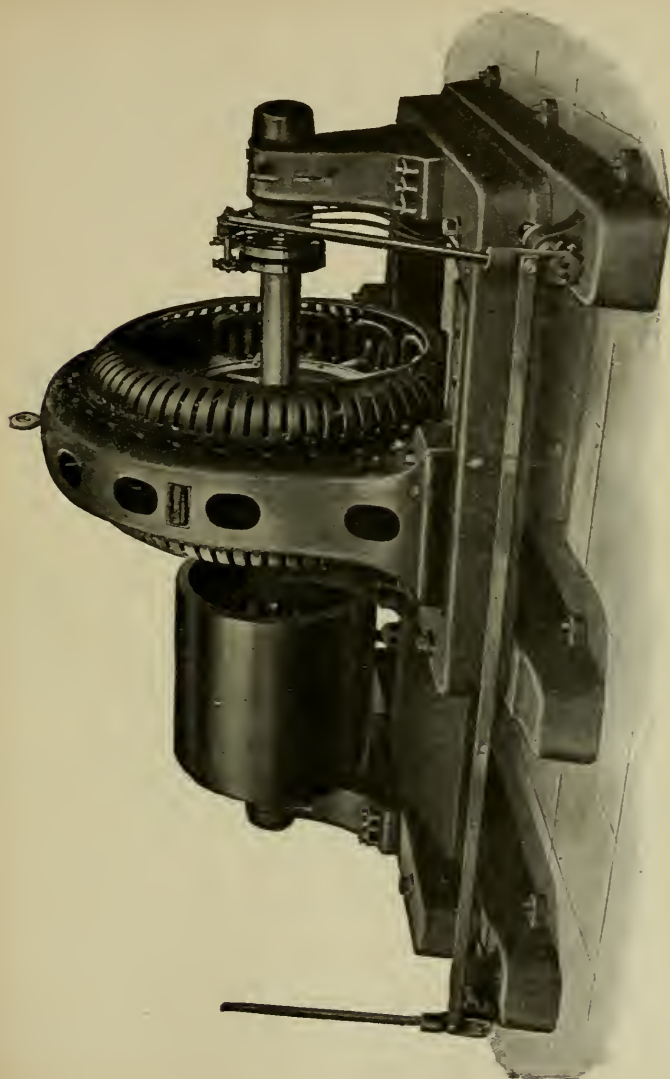


FIG. 1,382.—Allis-Chalmers pedestal type, belted alternator. The bearings have spherical seats and are self aligning.

The bearings are of the ring oiling form with large oil reservoirs.

**Ques.** How is this done?

**Ans.** Sometimes by an idler pulley, but usually by mounting the machine on a sub-base provided with slide rails, as in fig. 1,381, the belt being tightened by use of a ratchet screw which moves the machine along the base.

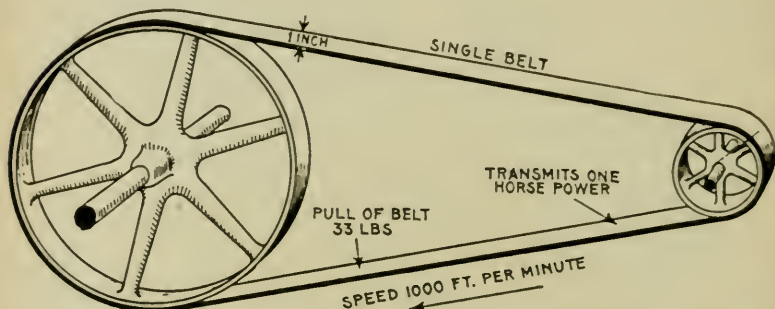


FIG. 1,383.—Diagram illustrating rule for horse power transmitted by belts. *A single belt travelling at a speed of 1,000 feet per minute will transmit one horse power; a double belt will transmit twice that amount, assuming that the thickness of a double belt is twice that of a single belt. This is conservative practice, and a belt so proportioned will do the work in practically all cases. The above rule corresponds to a pull of 33 lbs. per inch of width. Many designers proportion single belts for a pull of 45 lbs. For double belts of average thickness, some writers say that the transmitting efficiency is to that of single belts as 10 is to 7. This should not be applied to the above rule for single belts, as it will give an unnecessarily large belt.*

**Ques.** Give a rule for obtaining the proper size of belt to deliver a given horse power.

**Ans.** *A single belt travelling at a speed of one thousand feet per minute will transmit one horse power; a double belt will transmit twice that amount.*

This corresponds to a working strain of 33 lbs. per inch of width for single belt, or 66 lbs. for double belt.

Many writers give as safe practice for single belts in good condition a working tension of 45 lbs. per inch of width.


**Ques.** What is the best speed for maximum belt economy?

**Ans.** From 4,000 to 4,500 feet per minute.

**EXAMPLE.**—What is the proper size of double belt for an alternator having a 16 inch pulley, and which requires 50 horse power to drive it at 1,000 revolutions per minute full load?

The velocity of the belt is

$$\begin{array}{rcll} \text{circumference in feet} \times \text{revolutions} & = & \text{feet per minute} \\ \frac{16}{12} \times 3.1416 & \times & 1,000 & = & 4,188. \end{array}$$

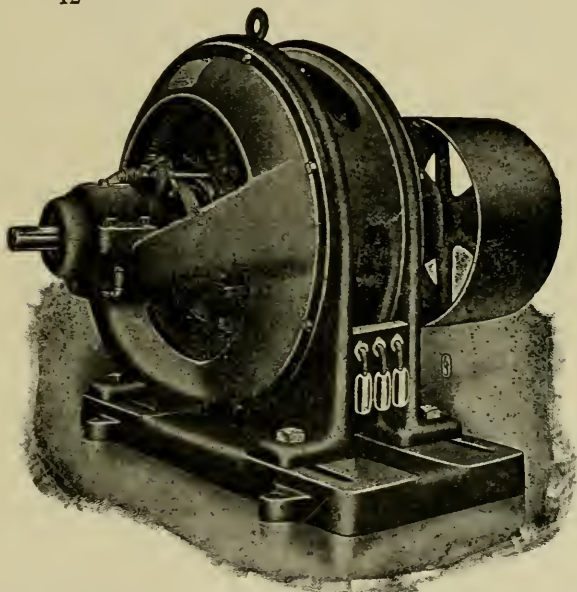

**FIG. 1,384.**—Fort Wayne revolving field belt driven alternator. It is designed for belted exciter, having a shaft extension at the collector ring end for exciter driving pulley.

Horse power transmitted per inch width of double belt at 4,188 feet speed


$$2 \times \frac{4,188}{1,000} = 8.38.$$

Width of double belt for 50 horse power

$$50 \div 8.33 = 5.97, \text{ say } 6 \text{ inch.}$$

**Ques.** What are the advantages of chain drive?

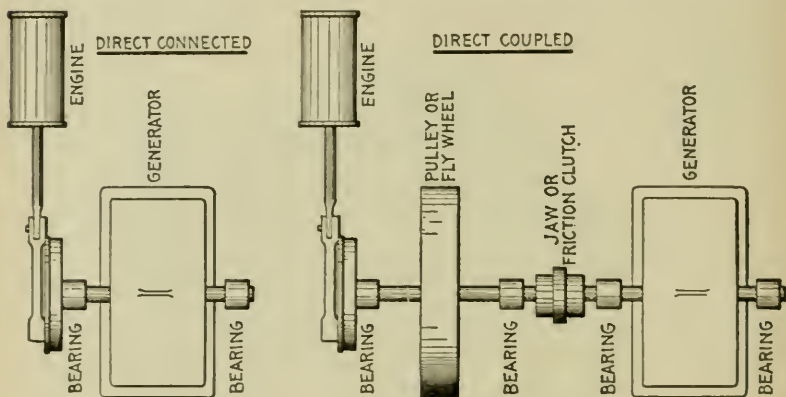**Ans.** The space required is much less than with belt drive, as the distance between centers may be reduced to a minimum. It is a positive drive, that is, there can be no slip. Less liability of becoming detached, and, because it is not dependent on



FIGS. 1,385 and 1,386.—Diagram showing the distinction between *direct connected* and *direct coupled* units. In a direct connected unit, fig. 1,385, the engine and generator are permanently connected on one shaft, there being one bed plate upon which both are mounted. An engine and generator are said to be direct coupled when each is independent, as in fig. 1,386, being connected solely by a jaw or friction clutch or equivalent at times when it is desired to run the generator. At other times the generator may be disconnected and the engine run to supply power for other purposes.

frictional contact, the diameters of the sprockets may be much less than pulley diameter for belt drive.

**Ques.** What are some objections?

**Ans.** A lubricant is required for satisfactory operation, which causes more or less dirt to collect on the chain, requiring



frequent cleaning; climbing of teeth when links and teeth become worn; noise and friction.

**Direct Connected Alternators.**—There are a large number of cases where economy of space is of prime importance, and to meet this condition the alternator and engine are direct con-

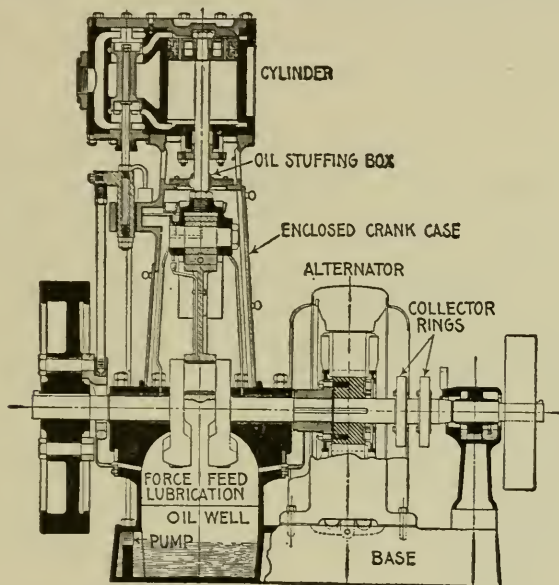


FIG. 1.387 —Endberg direct connected, or "engine type" alternator. In many places direct connected units are used, owing to the great saving in floor space, convenience of operation, and absence of belts.

nected, meaning, that there is no intermediate gearing such as belt, chain, etc., between engine and alternator.

One difficulty encountered in the direct connection of engine and alternator is the fact that the most desirable rotative speed of the engine is less than that of the alternator. Accordingly a compromise is made by raising the engine speed and lowering the alternator speed.



The insistent demand for direct connected units in the small and medium sizes, especially for direct current units, was the chief cause resulting in the rapid and high development of what is known as the "high speed automatic engine."

Increasing the engine speed means that more horse power is developed for any given cylinder dimensions, while reducing the speed of the generator involves that the machine must be larger for a given output, and in the case of an alternator more poles are required to obtain a given frequency, resulting in increased cost.

The compactness of the unit as a whole, simplicity, and general advantages are usually so great as to more than offset any additional cost of the generator.

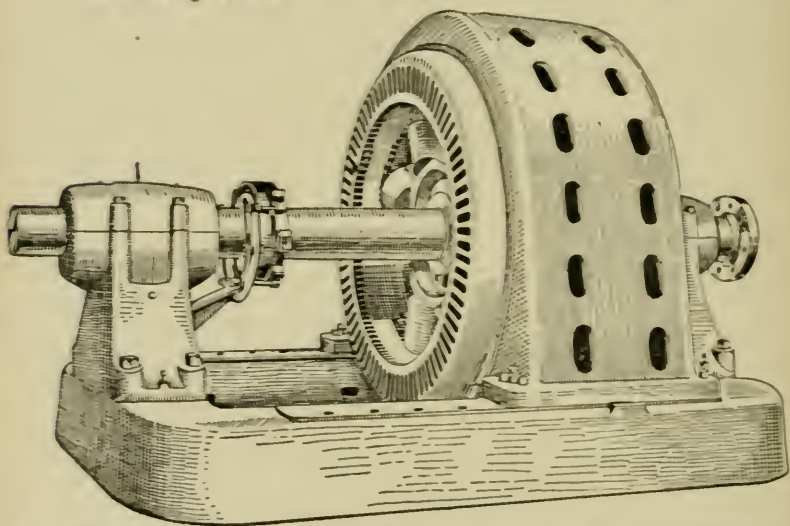


FIG. 1,388.—Crocker-Wheeler 2,000 kva. 2,400 volt coupled type alternator. The coupled type of alternator is desirable for use with steam, gas, and oil engines, and water wheels where it is inconvenient to mount the alternator on the engine shaft or to extend the engine base to accommodate a bearing. This type consists of alternator complete with shaft and bearings similar to belt type machines, but with bearings not necessary designed for the side pull of belts.

**Ques.** What is the difference between a direct connected and a direct coupled unit?

**Ans.** A direct connected unit comprises an engine and generator permanently connected; direct coupling signifies that

engine and generator are each complete in itself, that is, having two bearings, and are connected by some device such as friction clutch, jaw clutch, or shaft coupling.

**Revolving Armature Alternators.**—This type of alternator is one which has its parts arranged in a manner similar to a dynamo, that is, the armature is mounted on a shaft so it can

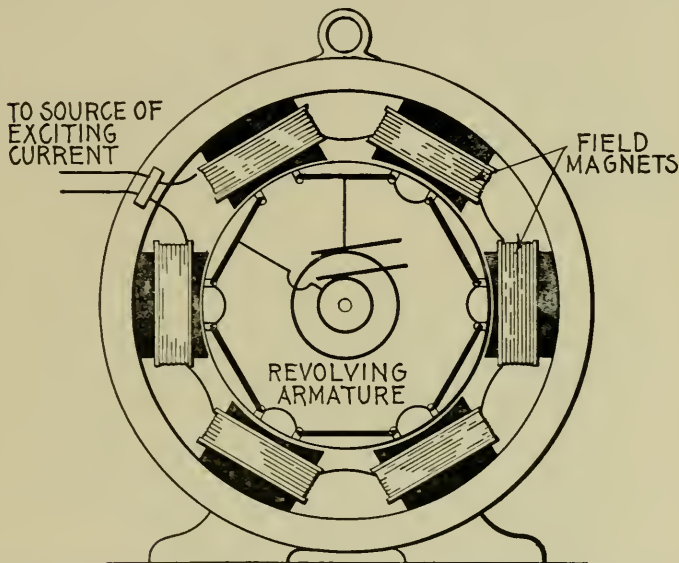


FIG. 1,389.—Revolving armature alternator. Revolving armatures are suitable for machines generating current at comparatively low pressure, as no difficulty is experienced in collecting such current. Revolving armature alternators are also suitable for small power plants, isolated lighting plants, where medium or small size machines are required.

revolve while the field magnets are attached to a circular frame and arranged radially around the armature, as shown in fig. 1,389. It may be single or polyphase, belt driven, or direct connected.

**Ques.** When is the revolving type of armature used and why?

**Ans.** It is used on machines of small size because the pressure generated is comparatively low and the current transmitted by the brushes small, no difficulty being experienced in collecting such a current.

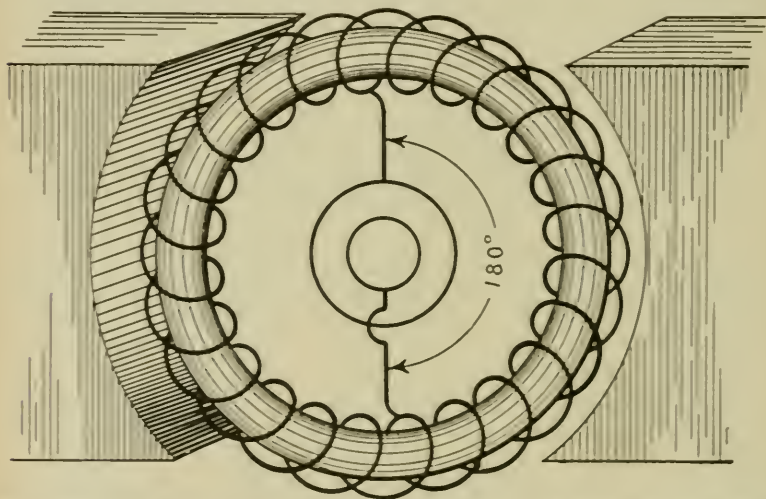


FIG. 1,390.—Ring wound dynamo arranged as alternator by replacing commutator with collector rings connected to the winding at points 180° apart.

**Ques.** Could a dynamo be converted into an alternator?

**Ans.** Yes.

**Ques.** How can this be done?

**Ans.** By placing two collector rings on one end of the armature and connecting these two rings to points in the armature winding 180° apart, as shown in fig. 1,390.


**Ques.** Would such arrangement as shown in fig. 1,390 make a desirable alternator?

**Ans.** No.

Alternating current windings are usually different from those used for direct currents. One distinction is the fact that a simple open coil winding may be, and often is, employed, but the chief difference is the intermittent action of the inductors.

In a direct current Gramme ring winding a certain number of coils are always active, while those in the space between the pole pieces are not generating. In this way a practically steady pressure is produced by a large fraction of the coils.

In the case of an alternator all of the coils are either active or inactive at one time. Hence, the winding need cover only as much of the armature as is covered by the pole pieces.

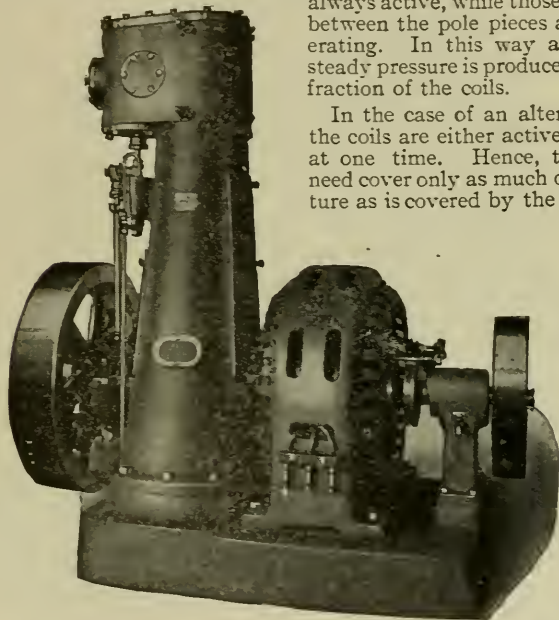

**FIG. 1,391.**—Engberg alternating current generating set; shown also in cross section in fig. 1,387. The set comprises a vertical engine and alternator, direct connected and placed on one base. The lubrication system comprises an oil pump situated in the base of the engine, pumping the oil from an oil reservoir up into a sight feed oil cup which leads to a distributing oil trough on the inside of the engine frame, from here oil pipes lead to all movable bearings, which are grooved to insure proper distribution of oil. The oil is drained from bearings into the base, filtered and repumped. A water shed partition is provided in the engine frame, preventing any water passing from the cylinder down into the engine base and mixing with the oil, consequently leaving good, clean oil in the oil reservoir at all times. The details of the lubrication system are shown in fig. 1,387.

**Revolving Field Alternators.**—In generating an electric current by causing an inductor to cut magnetic lines, it makes no difference whether the cutting of the magnetic lines is effected by moving an inductor across a magnetic field or moving the magnetic field across the inductor.

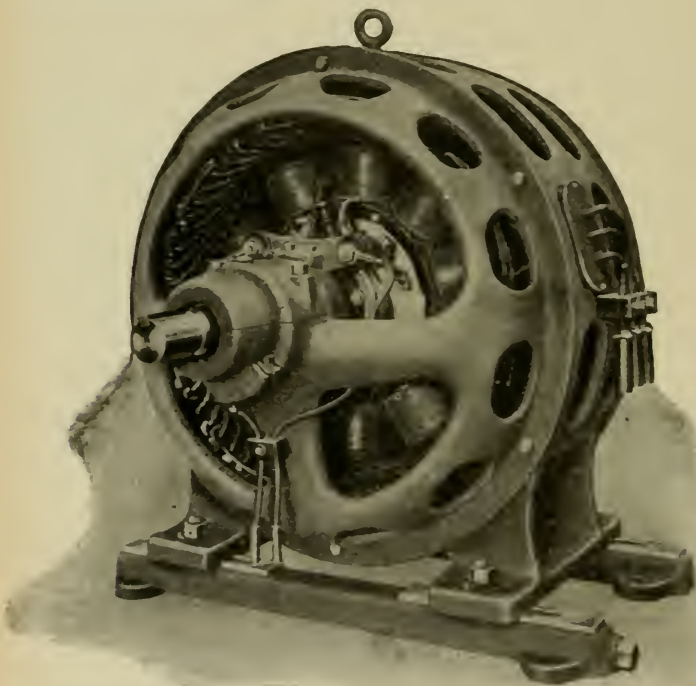


FIG. 1.332.—Allis-Chalmers revolving field self-contained belted type alternator.

*Motion is purely a relative matter*, that is, an object is said to move when it changes its position with some other object regarded as stationary; it may be moving with respect to a



second object, and at the same time be at rest with respect to a third object. Thus, a dory has a speed of four miles per hour in still water; if it be run up stream against a current flowing four miles per hour it would move at that speed with respect to the water, yet remain at rest with respect to the earth.

It must be evident then that motion, as stated, being a purely relative matter, it makes no difference whether the armature

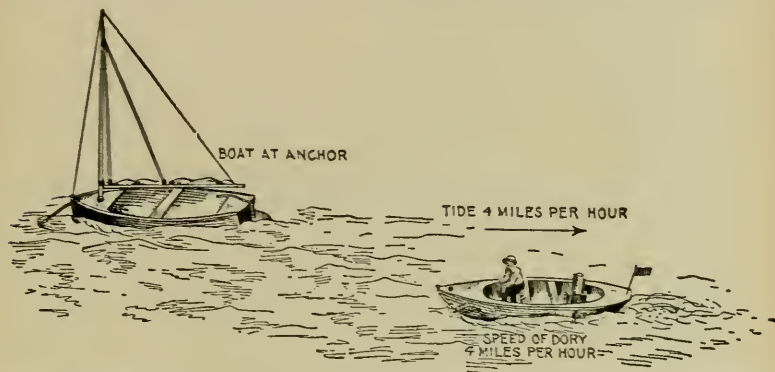


FIG. 1.333.—Marine view, showing that motion is purely a relative matter. In order that there may be motion something must be regarded as being stationary. In the above illustration a catboat is shown at anchor in a stream which is flowing at a rate of four miles per hour in the direction of the arrow. The small dory running at a speed of four miles per hour against the current is *moving* at that velocity *relative* to the current, yet is at a standstill relative to the catboat. In this instance both catboat and dory are moving with respect to the water if the latter be regarded as stationary. Again if the earth be regarded as being stationary, the two boats are at rest and the water is moving relative to the earth.

of a generator move with respect to the field magnets, or the field magnets move with respect to the armature, so far as inducing an electric current is concerned.

For alternators of medium and large size there are several reasons why the armature should be stationary and the field magnets revolve, as follows:

1. By making the armature stationary, superior insulation methods may be employed, enabling the generation of current at very much higher voltage than in the revolving armature type.
2. Because the difficulty of taking current at very high pressures from collector rings is avoided.

The field current only passes through the collector rings. Since the field current is of low voltage and small in comparison with the main current, small brushes are sufficient and sparking troubles are avoided.

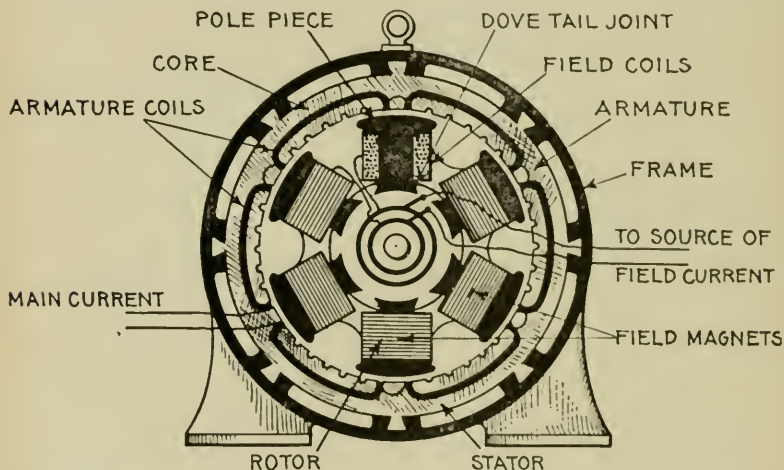


FIG. 1,394.—Diagram showing essential parts of a revolving field alternator and method of joining the parts in assembling.

3. Only two collector rings are required.
4. The armature terminals being stationary, may be enclosed permanently so that no one can come in contact with them.

**Ques.** What names are usually applied to the armature and field magnets with respect to which moves?

**Ans.** The "stator" and the "rotor."



The terms armature and field magnets are to be preferred to such expressions. An armature is an armature, no matter whether it move or be fixed, and the same applies to the field magnets. There is no good reason to apply other terms which do not define the parts.

**Ques.** Explain the essential features of a revolving field alternator.

**Ans.** The construction of such alternators is indicated in the diagram, fig. 1,394. Attached to the shaft is a field core, which carries the latter, consisting of field coils fitted on pole pieces which are dovetailed to the field core. The armature is built into the frame and surrounds the magnets as shown. The field current, which is transmitted to the magnets by slip rings and brushes, consists of direct current of comparatively low pressure, obtained from some external source.

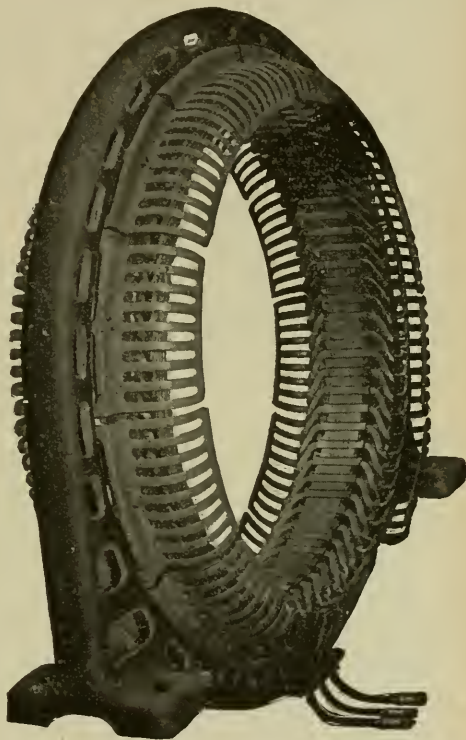


FIG. 1,395.—Western Electric stationary armature and frame of engine driven alternator. It is of cast iron and surrounds the laminated iron core in which the armature windings are embedded. Heavy steel clamping fingers hold the core punchings in place and numerous ventilating ducts are provided in the core at frequent intervals to allow free circulation of cool air. The armature coils are form wound, insulated, and retained in the core slots by means of wedges.

**Inductor Alternators.**—In this class of alternator both armature and field magnets are stationary, a current being induced in the armature winding by the action of a so called inductor in moving through the magnetic field so as to periodically vary its intensity.

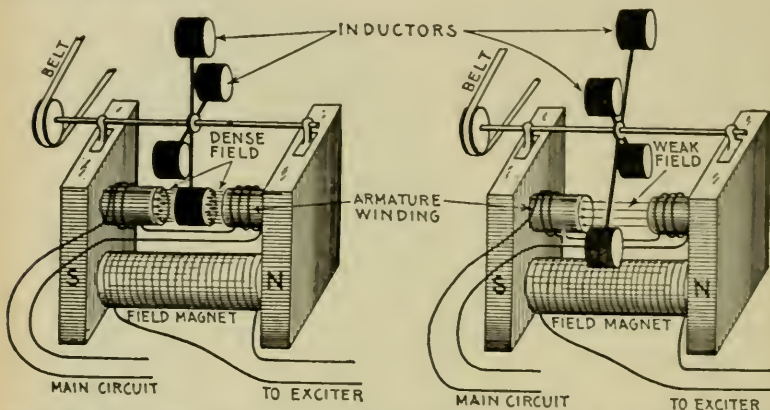



FIG. 1.396 and 1.397.—Elementary inductor alternator; diagram showing principle of operation. It consists of a field magnet, at the polar extremities of which is an armature winding both being stationary as shown. Inductors consisting of iron discs are arranged on a shaft to rotate through the air gap of the magnet poles. Now in the rotation of the inductors, when any one of them passes through the air gap as in fig. 1.396, the reluctance or magnetic resistance of the air gap is greatly reduced, which causes a corresponding increase in the number of magnetic lines passing through the armature winding. Again as an inductor passes out of the air gap as in fig. 1.397, the number of magnetic lines is greatly reduced; that is, when an inductor is in the air gap, the magnetic field is dense, and when no inductor is in the gap, the field is weak; a variable flux is thus made to pass through the armature winding, inducing current therein. The essential feature of the inductor alternator is that iron only is revolving, and as the design is usually homopolar, the magnetic flux in its field coils is not alternating but undulating in character. Thus, with a given maximum flux through each polar mass, the total number of armature turns required to produce a given voltage is just twice that which is required in an alternator having an alternating instead of an undulating flux through its field windings. The above and the one shown in figs. 1.398 and 1.399 are examples of real inductor alternators, those shown in the other cuts are simply so called inductor alternators, the distinction being that, as above, the *inductor* constitutes no part of the field magnet.

**Ques.** What influence have the inductors on the field flux?

**Ans.** They cause it to undulate; that is, the flux rises to a maximum and falls to a minimum value, but does not reverse.

**Ques.** How does this affect the design of the machine as compared with other types of alternator?

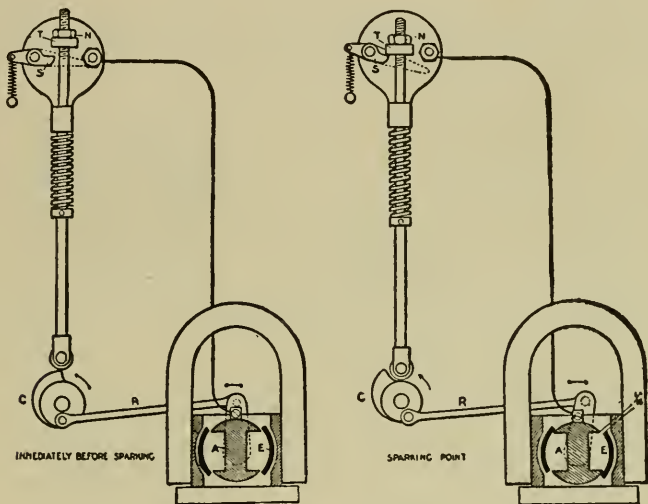**Ans.** With a given maximum magnetic flux through each polar mass, the total number of armature turns necessary to produce a given pressure is twice that which is required in an alternator having an alternating flux through its armature windings.



FIGS. 1,398 and 1,399.—A low tension ignition system with an inductor magneto of the oscillating type. The inductor E is rotated to and fro by means of a link R, one end of which is attached to the inductor crank, and the other to the igniter cam C. Two views are shown: immediately before and after sparking. S is the grounded electrode of the igniter; T an adjustable hammer which is secured in position by a lock nut N.

**Ques.** Is the disadvantage due to the necessity of doubling the number of armature turns compensated in any way?


**Ans.** Yes, the magnetic flux is not reversed or entirely changed in each cycle through the whole mass of iron in the

armature, the abrupt changes being largely confined to the projections on the armature surface between the coils.

**Ques.** What benefit results from this peculiarity?

**Ans.** It enables the use of a very high magnetic flux density in the armature without excessive core loss, and also the use of a large flux without an excessive increase in the amount of magnetic iron.

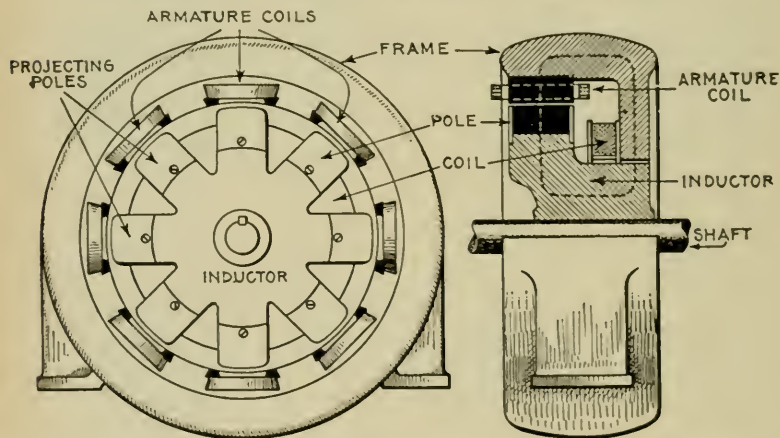The use of a large flux permits a reduction in the number of armature turns, thus compensating, more or less, for the disadvantage due to the operation of only one-half of the armature coils at a time.




**Figs. 1,400 and 1,401.**—One form of inductor alternator. As shown, the frame carries the stationary armature, which is of the slotted type. Inside of the armature is the revolving inductor, provided with the projections built up of wrought iron or steel laminations. The circular exciting coil is also stationary and encircles the inductor, thus setting up a magnetic flux around the path indicated by the dotted line, fig. 1,401. The projecting poles are all, therefore, of the same polarity, and as they revolve, the magnetic flux sweeps over the coils. Although this arrangement does away with collector rings, the machines are not so easily constructed as other types, especially in the large sizes. The magnetizing coil becomes large and difficult to support in place, and would be hard to repair in case of breakdown. Inductor alternators have become practically obsolete, except in special cases, as inductor magnetos used for ignition and other purposes requiring a very small size machine. The reasons for the type being displaced by other forms of alternator are chiefly because only half as great a pressure is obtained by a flux of given amount, as would be obtained in the ordinary type of machine. It is also more expensive to build two armatures, to give the same power, than to build one armature. This type has still other grave defects, among which may be mentioned enormous magnetic leakage, heavy eddy current losses, inferior heat emissivity, and bad regulation.

**Classes of Inductor Alternator.**—There are two classes into which inductor alternators may be divided, based on the mode of setting of their polar projections:

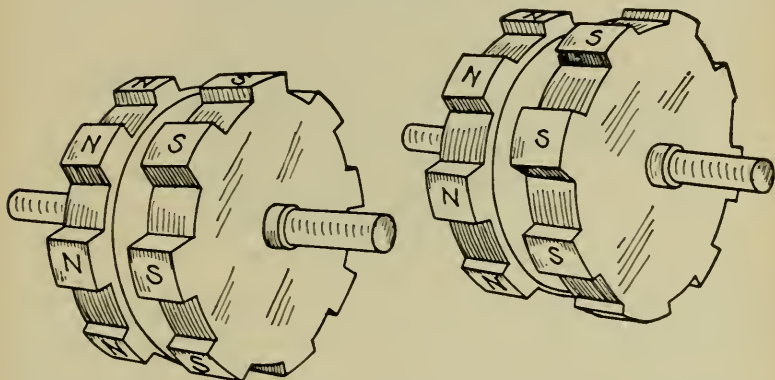1. Homopolar machines;
2. Heteropolar machines.

**Homopolar Inductor Alternators.**—In this type the positive polar projections of the inductors are set opposite the negative polar projections as shown in fig. 1,402. When the polar projections are set in this manner, the armature coils must be “staggered” or set displaced along the circumference with respect to one another at a distance equal to half the distance from the positive pole to the next positive pole.



FIGS. 1,402 and 1,403.—Homopolar and heteropolar “inductors”. Homopolar inductors have their N and S poles opposite each other, while in the heteropolar type, they are “staggered” as shown.

**Heteropolar Inductor Alternators.**—Machines of this class are those in which the polar projections are themselves staggered, as shown in fig. 1,403, and therefore, do not require the staggering of the armature coils. In this case, a single armature of double width may be used, and the rotating inductor then acts as a *heteropolar magnet*, or a magnet which presents alternatively positive and negative poles to the armature, instead of presenting a series of poles of the same polarity as in the case of a *homopolar magnet*.

**Use of Inductor Alternators.**—Morday originally designed and introduced inductor alternators in 1866. They are not the prevailing type, as their field of application is comparatively narrow. They have to be very carefully designed with regard to magnetic leakage in order



to prevent them being relatively too heavy and costly for their output, and too defective with respect to their pressure regulation, other defects being heavy eddy current losses and inferior heat conductance.

**Hunting or Singing in Alternators.**—Hunting is a term applied to the state of two parallel connected alternators running out of step, or not synchronously, that is, “see sawing.” When

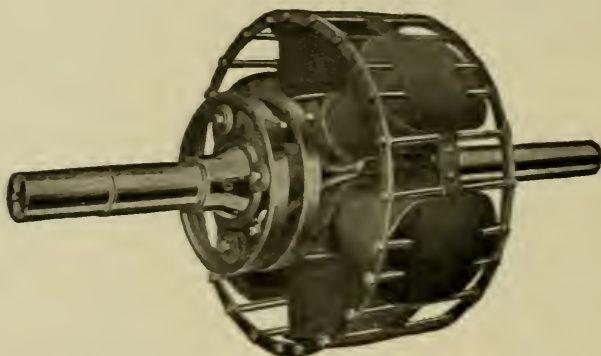


FIG. 1,404.—Revolving field of Port Wayne alternator equipped with *amortisseur* winding. The object of this winding is to check any tendency toward *hunting* when the alternator is to be run as a synchronous motor, either for rotary condenser or power service. The *amortisseur* winding consists of heavy copper bars, placed around and through the pole faces and short circuited at the ends by heavy copper rings; it serves as a starting winding to bring the rotor up to speed as an induction motor, and also serves as a damping device to neutralize any tendency toward “hunting” caused by variation in speed of the generator supplying the current.

the current wave of an alternator is peaked and two machines are operated in parallel it is very difficult to keep them in step, that is in synchronism. Any difference in the phase relation which is set up by the alternation will cause a local or synchronizing current to flow between the two machines and at times it becomes so great that they must be disconnected.

Alternators which produce a smooth current wave and are maintained at uniform speed by properly designed governors,

operate fairly well in parallel, but are not entirely free from hunting, and other means are provided to overcome the difficulty.

When heavy copper flanges, called dampers, are put over the polar projections or copper bars laid in grooves on the pole face and short circuited by connecting rings (called amortisseur

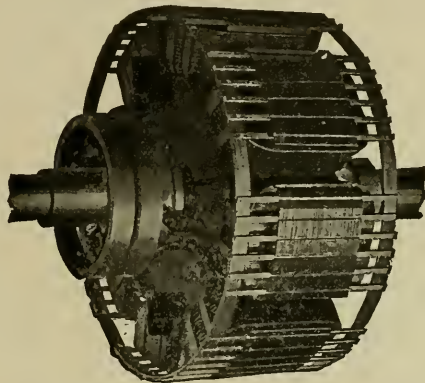


FIG. 1,405.—Westinghouse field with amortisseur or "damper" winding for 75 kva. and larger belted alternators, which prevents hunting and reduces eddy currents in the pole pieces. The copper bars of the amortisseur cage winding are arranged in partially closed slots in the pole pieces.

winding), the powerful induced currents which are produced when the alternators get out of step tend to quickly re-establish the phase relation.

Two examples of a field provided with amortisseur winding is shown in figs. 1,404 and 1,405.

---

NOTE.—Amortisseur windings are often erroneously called "squirrel cage" windings on account of similarity of construction. The latter term should be reserved for its proper significance as being the name of the type of armature winding generally used for induction motors, the name being suggested by the resemblance of the finished armature to the wheel of a squirrel cage. A comparison of figs. 1,405 and 1,746 will show the distinction. In a squirrel cage winding there is a large number of bars uniformly spaced; an amortisseur winding consists of a comparatively small number of bars, usually unevenly spaced, that is they are divided into groups with considerable space between the groups, as in fig. 1,405, and less pronounced in fig. 1,404. The bars are short circuited by rings the same as in squirrel cage winding.



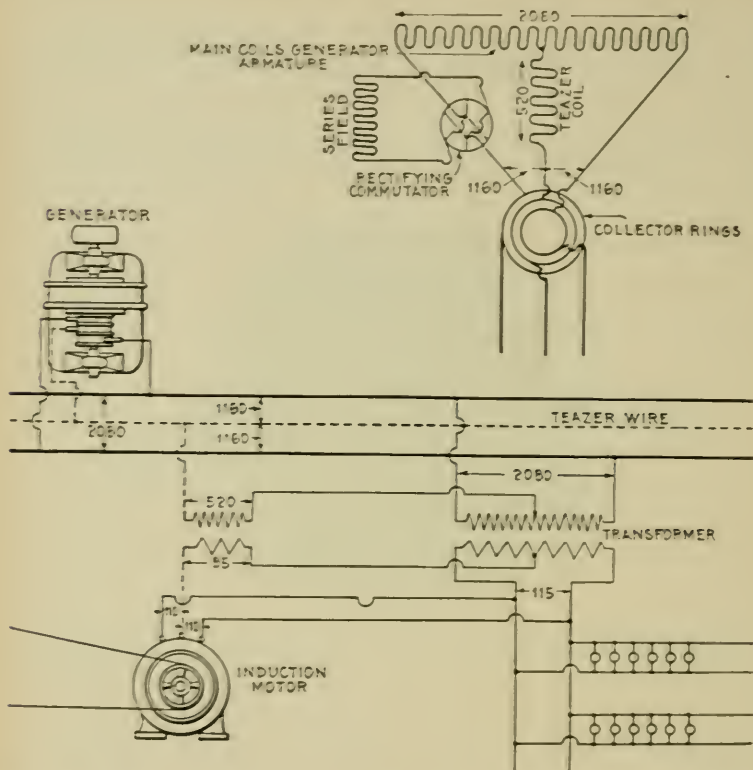


FIG. 1,496.—Diagram of monocyclic system, showing monocyclic armature and transformer connections. The monocyclic system is a single phase system primarily intended for the distribution of lights with an incidental load of motors. The lighting load is entirely connected to one single phase circuit, and the motors are started and operated from this circuit with the assistance of the teaser wire. The long coil indicates the main winding of the armature, which is similar in its arrangement and size to the ordinary armature winding of a single phase alternator. The short coil which connects at one end to the middle point of the coil above mentioned, and at the other to a third collector ring is called the "teaser" coil. Its use is to generate a pressure in quadrature with that of the main coil. This pressure is combined with the main pressure of the alternator by transformers, so as to give suitable phase relations for operating induction motors. In the diagram the voltage has been assumed to be 2,080 volts, and the voltages marked to correspond with the generated pressure. The coils of the alternator armature are connected, as shown, to two main leads and to a teaser wire. Between each end of the main coil and the end of the teaser coils, a resultant pressure is generated. These resultants are about 12 per cent. larger than half the main pressure. They also have a phase difference.

**Monocyclic Alternators.**—This type of alternator was designed prior to the introduction of the polyphase systems, to overcome the difficulties encountered in the operation of single phase alternators as motors. A single phase alternator will not start from rest as a motor, but must first be started and brought

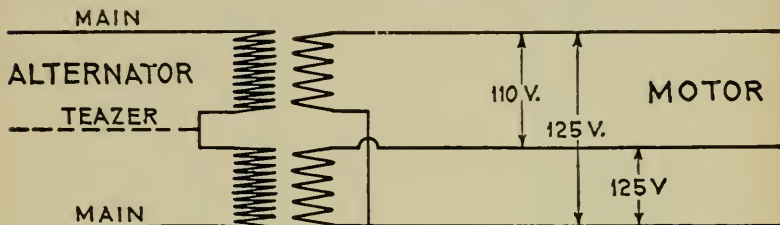


FIG. 1,407.—Monocyclic system diagram showing transformer connections.

up to the proper speed before being connected with single phase mains. This condition constituted a serious difficulty in all cases where the motor had to be stopped and started at comparatively frequent intervals.


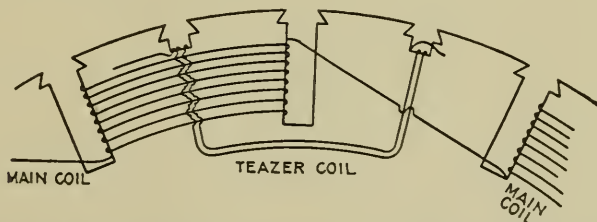


FIG. 1,408.—Diagram showing section of monocyclic alternator armature illustrating the armature winding. The main coils are wound on every other tooth, and the teaser coils are placed in quadrature with them, as shown.

The monocyclic alternator is a single phase machine provided with an additional coil, called a *teaser coil*, wound in two phase relationship with, and connected to the center of the main single

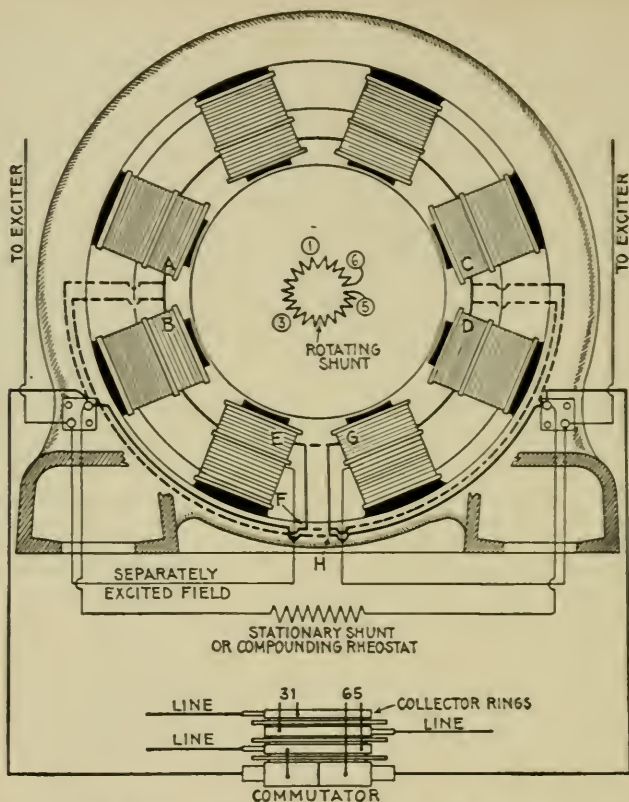

**FIG. 1,409.**—Diagram showing connections of General Electric Monocyclic alternator. For 2,300 volt machine, connect as shown by solid lines. For 1,150 volt machine, omit connections A to B, C to D, E to F, and G to H, and connect as shown by dotted lines. The armature of a standard monocyclic alternator rotates in a counter clockwise direction facing the commutator. When the alternator is loaded, the voltage between the teaser coil and the two terminals of the main coil may be different; therefore, it is necessary to have the commutator connected in corresponding ends of the main coil. If the machine has not been arranged for clockwise rotation, the following change in the connections on the commutator-collector must be made if the machine is to be run in parallel with another. Fig. 1,410 shows the connections of monocyclic alternators. In fig. 1,409, the studs on the commutator-collector marked 1 and 6 are the terminals of the main coil. These should be reversed. The numbers are stamped on the ends of the stud and may be seen with the assistance of a mirror. By reference to this diagram it is a simple matter to trace out the connections with a magneto, after the armature leads are disconnected and the brushes raised.

phase coil. It is provided with three collector rings; two for the single phase coil, and one for the free end of the *teaser coil*.

By this arrangement ordinary single phase incandescent lighting can be accomplished by means of a single pair of wires taken from the single phase coil. Where three phase motors have to be operated, however, a third wire, called the *power wire*, which is usually smaller than the main single phase wires is carried


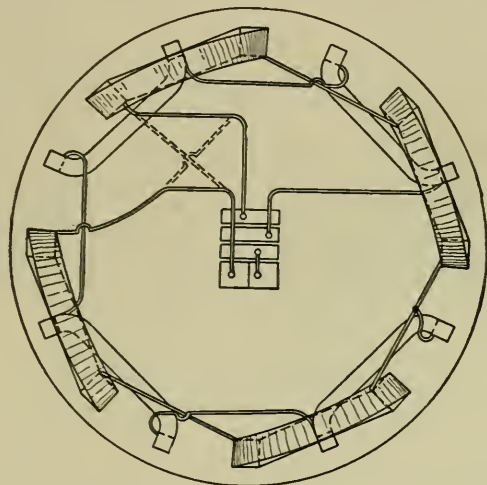


FIG. 1,410.—Diagram showing connections of General Electric monocyclic alternator. The solid lines show standard connections for counter-clockwise rotation; the broken lines show connection changed for clockwise rotation.

to the point at which the motor is located, and by the use of two suitably connected transformers three phase currents are obtained from the combined single phase and power wires for operating the motors.

Fig. 1,406 shows the connections of the monocyclic system and it is only necessary to carry the teaser wire into buildings where motors are to be used.

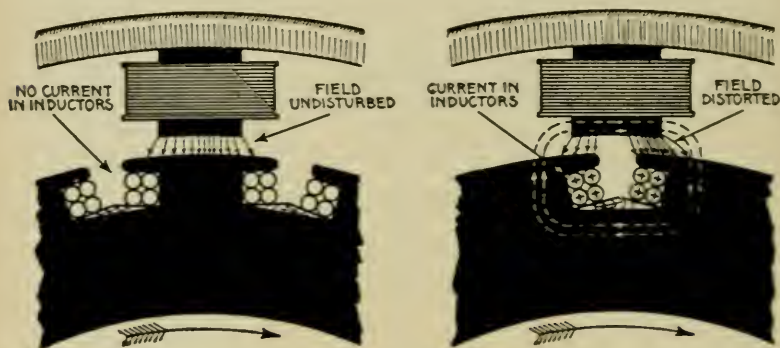**Armature Reaction.**—Every conductor carrying a current creates a magnetic field around itself, whether it be embedded in iron or lie in air. Armature inductors, therefore, create magnetic fluxes around themselves, and these fluxes will, in part, interfere with the main flux from the poles of the field magnet. The effect of these fluxes is:



FIGS. 1,411 and 1,412.—Section of armature and field showing *distorting effect* of armature reaction on the field. When a coil is opposite a pole as in fig. 1,411, no current is flowing (assuming no self induction) and the field is undisturbed, but, as the inductors pass under a pole face as in fig. 1,412, current is induced in them, and lines of force are set up as indicated by the dotted lines. This distorts the main field so that the lines of force are crowded toward the forward part of the pole face as shown.

1. To distort the field, or
2. To weaken the field.

These disturbing fluxes form, in part, stray fluxes linked around the armature inductors tending to choke the armature current.

**Ques.** Explain how the field becomes distorted by armature reaction.

**Ans.** Considering a slotted armature and analyzing the electrical conditions as the inductors move past a pole piece, it will be observed: 1, when the coil is in the position shown in

fig. 1,411, the current will be zero, assuming no armature self-induction, consequently for this position the armature coil has no disturbing effect upon the field set up by the field magnet; 2, when the inductors have moved under the pole face, as in fig. 1,412, currents will be induced in them, and they will tend to set up a magnetic field as indicated by the dotted lines, and in direction, by the arrow heads. The effect of this field will be to distort the main field, strengthening one side of the pole and weakening the other side.

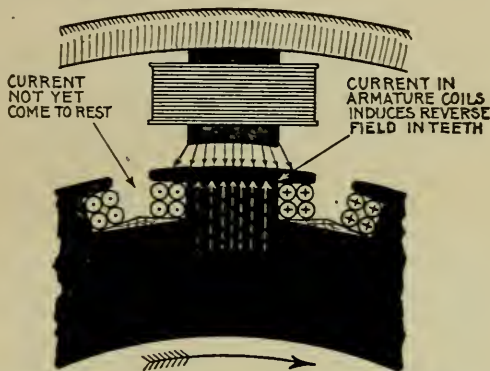


FIG. 1,413.—Section of armature and field showing *weakening effect* of armature reaction in the field. Self-induction being present (as it almost always is), the current lags more or less behind the pressure, so that when the coil is in the position of zero induction, as shown, the current has not yet come to rest. Accordingly, lines of force (indicated by the dotted lines) are set up by the current flowing through the coils which are in opposition to the field, thus weakening the latter. The dots and crosses in inductor sections, have their usual significance in defining the direction of current, representing respectively the heads and tails of arrows.

**Ques.** Explain how the field becomes weakened by armature reaction.

**Ans.** In all armatures there is more or less inductance which causes the current to lag behind the pressure a corresponding amount. Accordingly, the current does not stop flowing at the same instant that the pressure becomes zero, therefore, when the coil is in the position of zero pressure, as in fig. 1,413,



the current is still flowing and sets up a magnetic field which opposes the main field as indicated by the dotted arrows, thus weakening the main field.

**Ques.** In what kind of armature is this effect especially pronounced?

**Ans.** In slotted armatures provided with coils of a large number of turns.

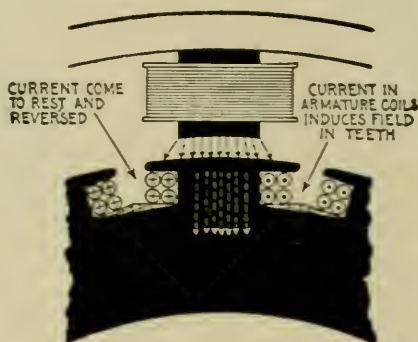


FIG. 1,414.—Section of armature and field showing *strengthening effect* of armature reaction when the current leads the pressure. If the circuit contain an excess of capacity the current will lead the pressure, so that when the coil is in the position of zero induction, as shown, the current will have come to rest and reversed. Accordingly, lines of force (indicated by the dotted lines) are set up by the current flowing through the coil and which are in the same direction as the lines of force of the field, thus strengthening the latter.

**Ques.** What would be the effect if the current lead the pressure?

**Ans.** It would tend to strengthen the field as shown in fig. 1,414.

The value of the armature ampere turns which tend to distort and to diminish or augment the effect of the ampere turns on the field magnet is sometimes calculated as follows:

$$A = \frac{.707 \times I \times T \times P}{s}$$

in which

A = armature ampere turns;

I = current per phase;

T = turns per pole per phase;

P = number of phases;

s = product of the distribution and pitch factors of the winding.

This value of ampere turns, combined at the proper phase angle with the field ampere turns gives the value of the ampere turns available for producing useful flux.


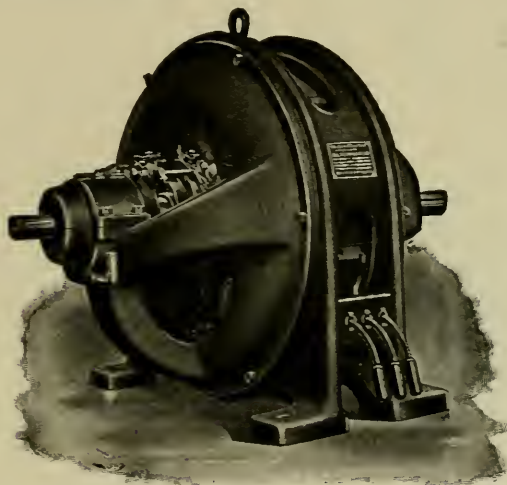
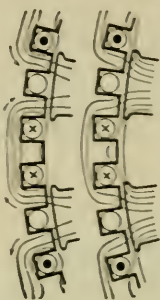
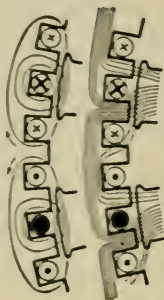



FIG. 1.415.—Fort Wayne separately excited belt driven alternator, a form adapted for installation in small plants where low power factor is to be encountered. This condition exists in a line where power is supplied to induction motors, transformers or other inductive apparatus. The type here shown is built in sizes from 37½ kw. to 200 kw., 60 cycles, two or three phases and voltages of 240, 450, 600, 1,150 or 2,300 volts. They may be operated as single phase alternators by using two of the phases and may then be rated at 70 per cent. of the polyphase rating. The field is excited by direct current at a pressure of 125 volts. These alternators may be used as synchronous motors and for this duty are fitted with amortisseur winding in the pole faces which does not interfere with their use as alternators.

**Single Phase Reactions.**—Unlike three phase currents, a single phase current in an alternator armature produces a periodic disturbance of the flux through the machine. In the magnet system this disturbance is of twice the normal frequency, while in the armature core it is the

POSITION 2

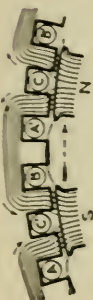

POSITION 1

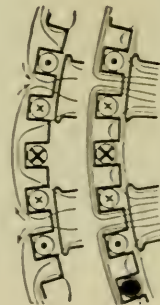

MAGNETOMOTIVE FORCE IN  
FIELD DUE TO FIELD MAGNETS  
ALONE.

FIELD DUE TO ARMATURE  
CURRENTS ALONE WHEN  
 $\cos \phi = 1$ .

RESULTANT FIELD SHOW-  
ING DISTORTION

FIELD DUE TO ARMATURE  
CURRENTS ALONE WHEN  
 $\cos \phi = 0$

RESULTANT FIELD SHOW-  
ING DEMAGNETIZATION

FIGS. 1,410 TO 1,425.—Diagrams illustrating superposition of fields. In the figures magnetic curves representing the effect of the armature currents in several different cases are superposed upon the magnetic curves assumed to be due to the field magnet. The uppermost line shows the primary field due to the exciting coils on the magnet poles. They are shown passing into the armature teeth in two principal positions, where the middle of a pole is: 1, opposite a tooth, and the magnets are not excited. If there be no lag, the places of strongest current will be opposite the poles. As shown in the right hand figure when the current in one phase B, is at its maximum, those in the other phases A and C will be of half strength. In the left hand figure when the current in one phase B, is at its zero value, those in the other phases will be of equal value, or 87 per cent. of the maximum. In the third line is shown the effect of superposing these fields due to the current upon those due to the magnets as depicted in the first line. Inspection of this resultant field shows how the armature current distorts the field without altering the total number of lines per pole. In the fourth and fifth lines are shown the effects of a lagging current. A lag of  $90^\circ$  is assumed; and in that case the maximum current occurs in any inductor one quarter period after the pole has passed, or at a distance of half a pole pitch behind the middle point of the pole, as in the fourth line. When these armature fields are superposed on those of the magnets in the first line the resultant fields are those depicted in the fifth line. On inspection it will be seen that in this case there is no distortion, but a diminution of the flux from each pole, as the lines due to the armature currents, tending to pass through the pole cores in the sense opposite to those of the primary magnetism, must be deducted from the total. The twelve lines per pole are correspondingly reduced to eight; and, of these eight, four go astray constituting a leakage field. This illustrates the effect of a lagging current in demagnetizing the field magnets and in increasing the dispersion.

same as the normal frequency. In both cases the eddy currents which are set up, produce a marked increase in the load losses, and thus tend to give the machine a higher temperature rise on single phase loading.

Designers continue to be singularly heedless of these single phase reactions, resulting in many cases of unsatisfactory single phase alternators. Single phase reactions distort the wave form of the machine.

**Three Phase Reactions.**—The action of the three phase currents in an alternator is to produce a resultant field which is practically uniform, and which revolves in synchronism with the field system. The resultant three phase reaction, because of its uniformity, produces no

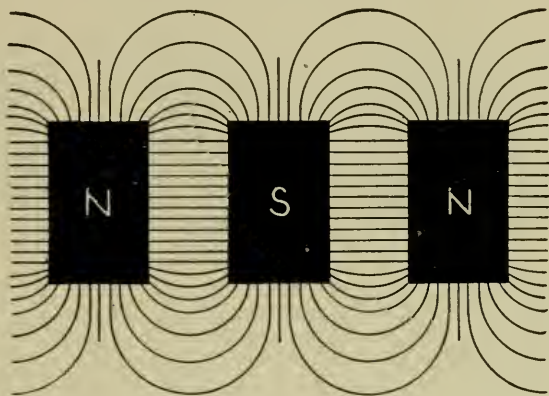


FIG. 1,426.—Diagram showing lateral field between adjacent poles.

great increase in the load losses of the machine, the small additional losses which are present being due to windings not being placed actually in space at  $120^\circ$ , and to the local leakage in the teeth.

**Magnetic Leakage.**—In the design of alternators the drop of voltage on an inductive load is mainly dependent upon the magnetic leakages, primary and secondary. They increase with the load, and, what is of more importance, they increase with the fall of the power factor of the circuit on which they may be working. This is one reason why certain types of alternator,

though satisfactory on a lighting circuit, have proved themselves unsatisfactory when applied to a load consisting chiefly of motors.

The designer must know the various causes which contribute to leakage and make proper allowance.

In general, to keep the leakage small, the pole cores should be short, and of minimum surface, the pole shoes should not have too wide a span nor be too thick, nor present needless



FIGS. 1,427 and 1,428.—Diagram showing respectively the character of stray field between adjacent straight poles, and between adjacent poles with shoes. Across the slightly V-shaped spaces the stray field passes in lines that, save near the outer part, are nearly straight. Quite straight they would not be, even were the sides parallel, because the difference of magnetic pressure increases from the roots towards the pole ends. At the roots, where the cores are attached to the yoke, the magnetic pressure difference is almost zero. It would be exactly zero if there were not a perceptible reluctance offered by the joints and by the metal of the yoke. The reluctance of the joint causes a few of the lines to take paths through the air by a leakage which adds to the useful flux. At the tops of the cores there is a difference of magnetic pressure equal to the sum of the ampere-turns on the two cores, tending to drive magnetic lines across. This difference of magnetic pressure increases regularly all the way up the cores from root to top; hence, the average value may be taken as equal to the ampere turns on one core. The stray field, therefore, will steadily increase in density from the bottom upwards. In addition to this stray field between the pole cores there is also a stray field between the projecting tips or edges of the pole shoes, as shown in fig. 1,428. In some machines the dispersion due to the pole shoes is greater than that between the flanks of the cores.

corners, and the axial length of the pole face and of the armature core should not be too great in proportion to the diameter of the working face.

To keep the increase of leakage between no load and full load from undue magnitude, it is required that armature reactions



shall be relatively small, that the peripheral density of the armature current (ampere-conductors per inch) be not too great, and that the pole cores be not too highly saturated when excited for no load.

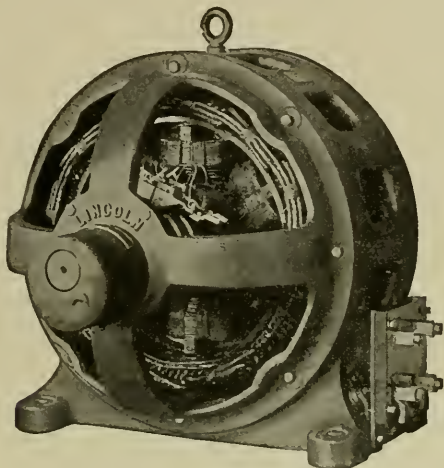


FIG. 1,429.—Lincoln revolving field alternator. The frame has openings for ventilation, the fanning action of the pole pieces causing a current of air to pass not only over the end of the windings, as is usual with other designs, but also through ventilating slots in the windings themselves. The armature core laminations are annealed after punching and before assembling to guard against the crystalizing effect of the punching. The armature coils are form wound and insulated before being placed in the slot. There is also slot insulation which is put in the slot previous to inserting the coil. When the winding is completed, it is tested with a pressure of 4 to 10 times the normal voltage of the machine. The bearings are self-aligning. The machine is normally designed to operate at a power factor of approximately 70 per cent., which means that at that power factor, the armature and fields at full load will heat equally. If it have a higher power factor than 70 per cent. it means that the field windings will run considerably cooler than the armature windings with full load. If the power factor be lower than this, it will mean that the field windings will run hotter than the armature on full load; however, the machine is designed so that harmful heating does not occur on full load with greater power factor than 40 per cent.

The general character of the stray field between adjacent poles is shown in figs. 1,427 and 1,428 for straight poles and those having shoes



**Field Excitation of Alternators.**—The fields of alternators require a separate source of direct current for their excitation, and this current should be preferably automatically controlled. In the case of alternators that are not self exciting, the dynamo which generates the field current is called the *exciter*.

The excitation of an alternator at its rated overload and .8 power factor would not, in some cases, if controlled by hand, exceed 125 volts, although, in order to make its armature voltage respond quickly to changes in the load and speed, the excitation of its fields may at times be momentarily varied by an automatic regulator between the limits of 70 and 140 volts.



FIG. 1,430.—Western Electric armature for self-excited alternator. The main winding is placed at the bottom of the slots, each coil being surrounded by an armour of horn fibre. The exciter winding occupies a very small portion of the slot, being placed on top of the main winding, and connected to the commutator immediately in front of the core and between core and collector rings as shown.

The exciter should, in turn, respond at once to this demand upon its armature, and experience has shown that to do this its shunt fields must have sufficient margin at full load to deliver momentarily a range from 25 to 160 volts at its armature terminals.

It is obvious from the above that an exciter suitable for use with an automatic regulator must commutate successfully over a wide range in voltage, and, if properly designed, have liberal margins in its shunt fields and magnetic circuits.

Alternator fields designed for and operated at unity power factor have often proved unsatisfactory when the machines were called upon to deliver their rated kva. at .8 power factor or lower. This is due to the increased field current required at the latter condition and results, first, in the overheating of the fields and, second, in the necessity of raising the direct current exciting voltage above 125 volts, which often requires the purchase of new exciters.

**Ques.** What is a self-excited alternator?

**Ans.** One whose armature has, in addition to the main winding, another winding connected to a commutator for furnishing direct field exciting current, as shown in fig. 1,480.

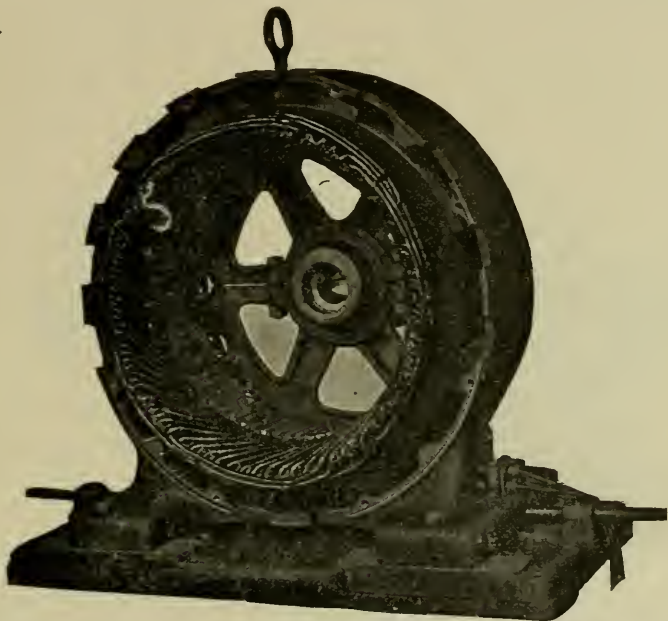


FIG. 1,431.—Frame, bed plate and armature winding for Westinghouse bracket bearing poly-phase alternator.

**Ques.** How is a direct connected exciter arranged?

**Ans.** The exciter armature is mounted on the shaft of the alternator close to the spider hub, or in some cases at a distance sufficient to permit a pedestal and bearing to be mounted between the exciter and hub. In other designs the exciter is placed between the bearing and hub.

Figs. 1,432 and 1,433 are examples of direct connected exciter alternators, in fig. 1,432 the exciter being placed between the field hub and bearing, and in fig. 1,433, beyond the bearing.

**Ques.** What is the advantage of a direct connected exciter?

**Ans.** Economy of space.

This is apparent by comparing figs. 1,432 and 1,433 with fig. 1,434 which shows a belted exciter.

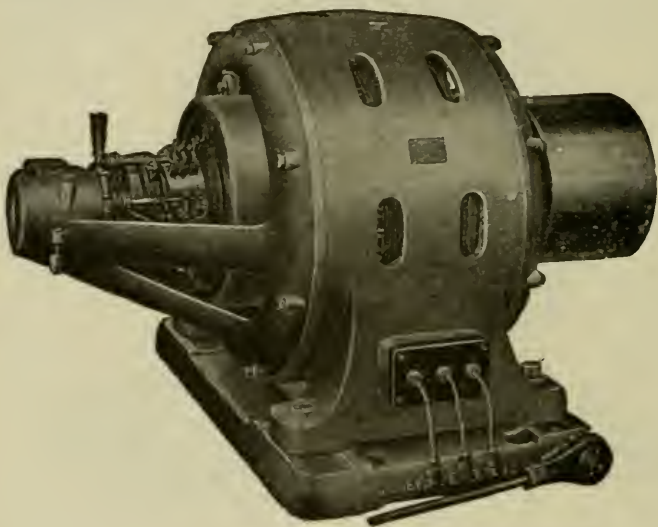


FIG. 1,432.—General Electric alternator with direct connected exciter mounted on shaft between field hub and bearing. In the smaller sizes, the magnet frame is bolted to the bearing bracket, but in the larger sizes special construction is used depending upon the conditions to be met. The exciters are capable of furnishing the desired excitation for low power factors.

**Ques.** What is the disadvantage of a direct connected exciter?

**Ans.** It must run at the same speed as the alternator, which is slower than desirable, hence the exciter must be larger for a

given output than the gear driven type, because the latter can be run at high speed and accordingly be made proportionally smaller.

**Ques.** What form of gear is generally used on gear driven exciters?

**Ans.** Belt gear.

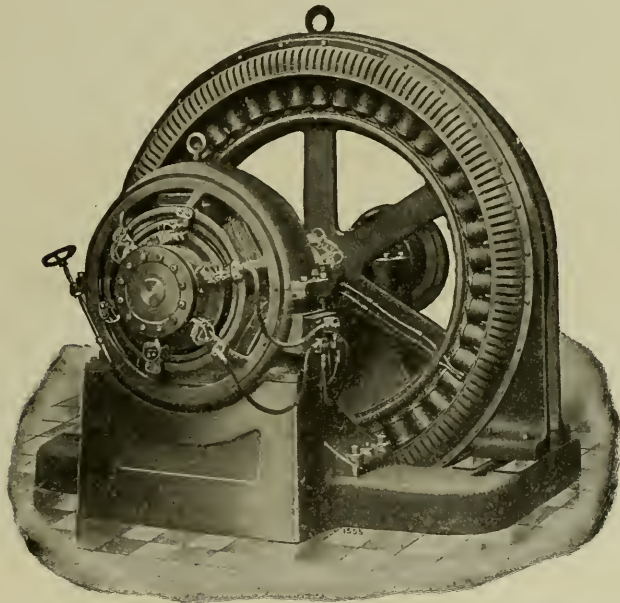


FIG. 1433.—Fort Wayne alternator with direct connected exciter mounted on the field shaft at such distance as to permit a pedestal and bearing to be mounted between the exciter and revolving field. In the view, the bearing is hidden by the exciter, only the foot of the pedestal being visible.

**Ques.** What are the advantages of gear driven exciters?

**Ans.** Being geared to run at high speed, they are smaller and therefore less costly than direct connected exciters. In large

plants containing a number of alternators one exciter may be used having sufficient capacity to excite all the alternators, and which can be located at any convenient place.

**Ques.** What is the disadvantage of gear driven exciters?

**Ans.** The space occupied by the gear.



FIG. 1434.—Diagram showing a Westinghouse 50 kva., 2,400 volt, three phase, 60 cycle revolving field separately excited alternator direct connected to a steam engine. The exciter is belted to the alternator shaft, the driving pulley being located outside the main bearing. The small pulley on the exciter gives an indication of its high speed as compared with that of the alternator.

In the case of a chain drive very little space is required, but for belts, the drive generally used, there must be considerable distance between centers for satisfactory transmission.

**Slow Speed Alternators.**—By slow speed is here understood relatively slow speed, such as the usual speeds of reciprocating engines. A slow speed alternator is one designed to run at a speed slow enough that it may be direct connected to an engine.



Such alternators are of the revolving field type and a little consideration will show that they must have a multiplicity of field magnets to attain the required frequency.

In order that there be room for the magnets, the machine evidently must be of large size, especially for high frequency.



FIG. 1,435.—Crocker-Wheeler 350 kva., slow speed alternator direct connected to a Corliss engine. In front is seen a belted exciter driven from a pulley on the main shaft between the alternator and the large band wheel. The latter serves to give the additional fly wheel effect needed for close speed regulation.

EXAMPLE.—How many field magnets are required on a two phase alternator direct connected to an engine running 240 revolutions per minute, for a frequency of 60?

An engine running 240 revolutions *per minute* will turn  
 $240 \div 60 = 4$  revolutions *per second*.

A frequency of 60 requires

$60 \div 4 = 15$  cycles per phase per revolution, or  
 $15 \times 2 = 30$  poles per phase.



Hence for a two phase alternator the total number of poles required is  
 $30 \times 2 = 60$ .

It is thus seen that a considerable length of spider rim is required to attach the numerous poles, the exact size depending upon their dimensions and clearance.



FIG. 1.436.—Three Crocker-Wheeler 75 kva., slow speed alternators direct connected to high speed engines. The alternator is styled slow speed although connected to a high speed engine, because what is considered high engine speed is slow speed for alternator operation. The alternators have direct connected exciters which are plainly seen in the illustration placed on an extension of bearing pedestal. Direct connected exciters on units of this kind do not, as a rule, assume too bulky proportions, because of the high engine speed.

**Fly Wheel Alternators.**—The diameter of the revolving fields on direct connected alternators of very large sizes becomes so great that considerable fly wheel effect is obtained, although the revolutions be low. By giving liberal thickness to the rim

of the spider, the rotor then answers the purpose of a fly wheel, hence no separate fly wheel is required. In fact, the revolving element resembles very closely an ordinary fly wheel with magnets mounted on its rim, as illustrated in fig. 1,437.

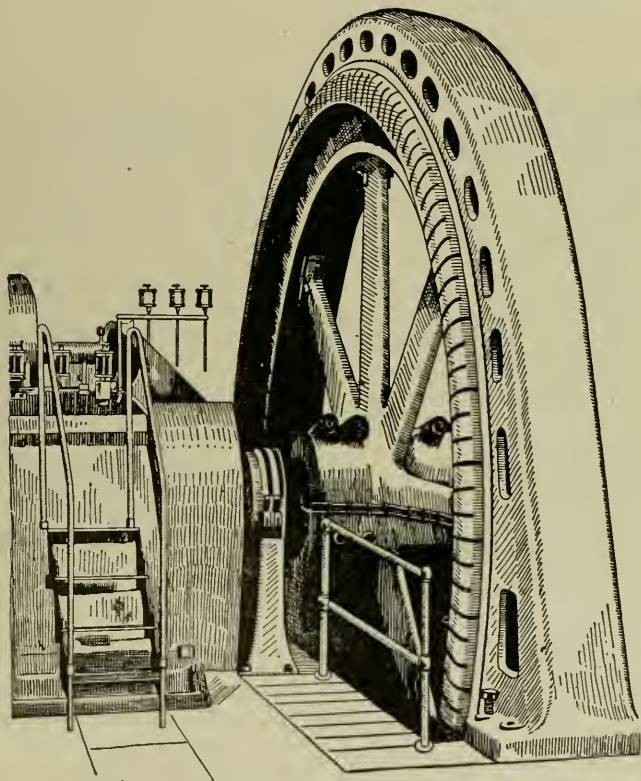


FIG. 1,437.—General Electric 48 pole 750 kw., three phase fly wheel type alternator. It runs at a speed of 150 revolutions per minute, giving a frequency of 60 cycles per second and a full load pressure of 2,300 volts. The slip rings and leads to the field winding are clearly shown in the figure. The field magnets are mounted directly on the rim of the spider, which resembles very closely a fly wheel, and which in fact it is—hence the name “fly wheel alternator.”

**High Speed Alternators.**—Since alternators may be run at speeds far in excess of desirable engine speeds, it must be evident that both size and cost may be reduced by designing them for high speed operation.

Since the desired velocity ratio or multiplication of speed is so easily obtained by belt drive, that form of transmission is generally used for high speed alternators, the chief objection

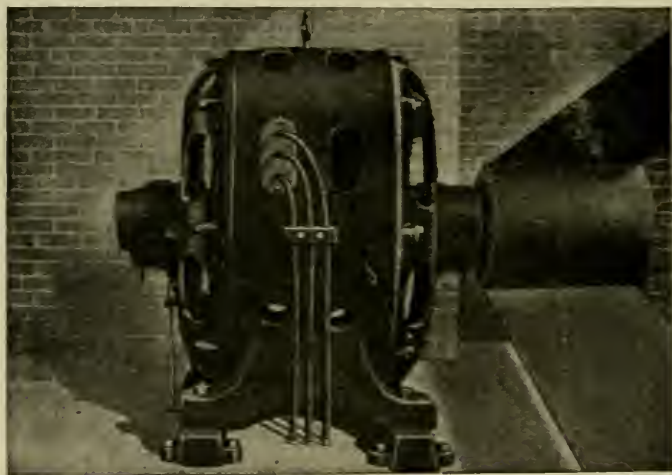


FIG. 1,438.—Allis-Chalmers high speed belted type alternator. The small pulley at the right and the angle of the belt suggest the high speed at which such alternators are run, a 50 kva. machine turning 1,200 revolutions per minute.

being the space required. Accordingly where economy of space is not of prime importance, a high speed alternator is usually installed, except in the large sizes where the conditions naturally suggest a direct connected unit.

An example of high speed alternator is shown in fig. 1,438. Machines of this class run at speeds of 1,200 to 1,800 or more, according to size.

No one would think of connecting an alternator running at any such speed direct to an engine, the necessary speed reduction proper for engine operation being easily obtained by means of a belt drive.

No one would think of connecting an alternator running at such speeds direct to an engine, the necessary speed reduction proper for engine operation being easily obtained by means of a belt drive.

**Water Wheel Alternators.**—In order to meet most successfully the requirements of the modern hydro-electric plant, the alternators must combine those characteristics which result in high electrical efficiency with a mechanical strength of the moving elements which will insure uninterrupted service, and

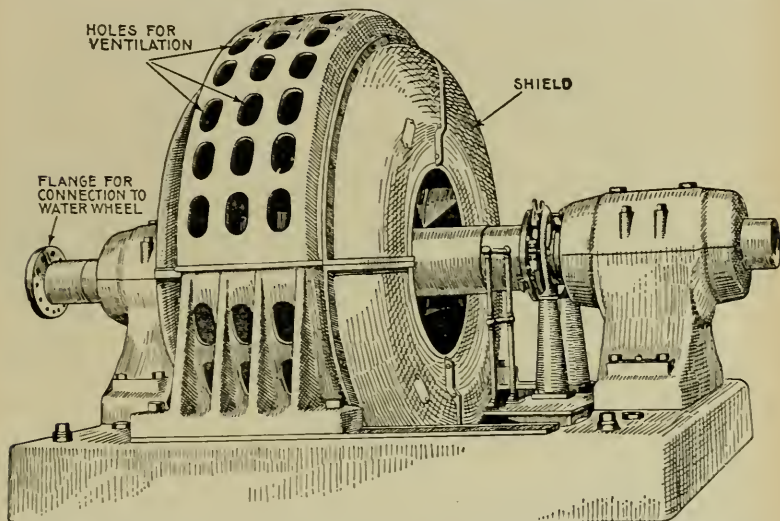


FIG. 1,439.—Allis-Chalmers 5,000 kva., 450 R. P. M., 6,600 volt, 60 cycle, 3 phase, horizontal water wheel alternator. The shaft is extended for the reception of a flange coupling for direct connection to water wheel. Owing to the wide range in output of the generating units and also in the speed at which they must operate to suit varying conditions of head, types of wheels used, and other features pertaining to water power developments, it has been necessary to design a very complete line of machines for this work. The bearings are of the ring oiling type with large oil reservoirs.

an ample factor of safety when operating at the relatively high speeds often used with this class of machine.

When selecting an alternator for water wheel operation a careful analysis of the details of construction should be made in



order to determine the relative values which have been assigned by the designers to the properties of the various materials used. Such analysis will permit the selection of a type of machine best adapted to the intended service and which possesses the required characteristics of safety, durability and efficiency.

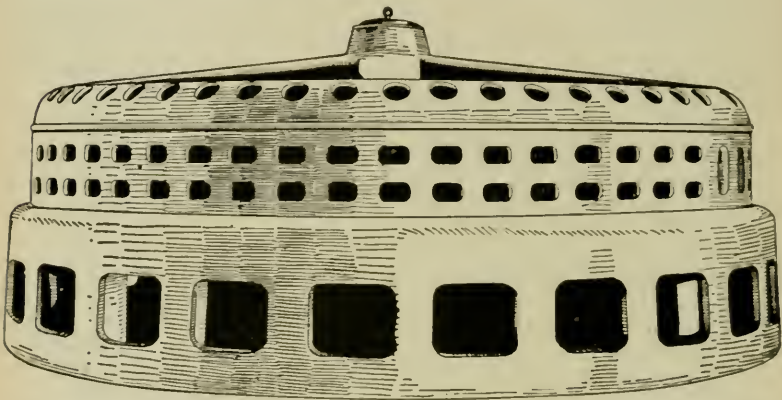


FIG. 1,440.—Stator of 500 k.w. Allis-Chalmers alternator for direct connection to vertical shaft hydraulic turbine.

The large use of electric power transmitted by means of high pressure alternating current has led to the development of a large number of water powers and created a corresponding demand for alternators suitable for direct connection to water wheels.

**Ques.** Name two forms of water wheel alternator.

**Ans.** Horizontal and vertical.


Examples of horizontal and vertical forms of water wheel alternator are shown in figs. 1,439 and 1,440.

**Ques.** How should the rotor be designed?

**Ans.** It should be of very substantial construction.


**Ques. Why?**

**Ans.** Because water wheel alternators are frequently required to operate safely at speeds considerably in excess of normal.

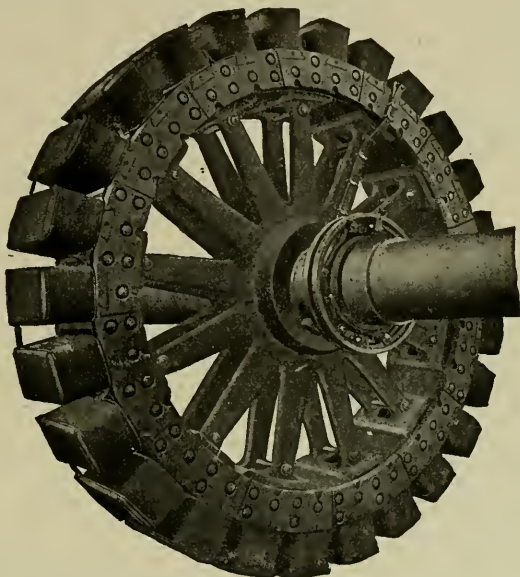

**FIG. 1,441.**—Allis-Chalmers revolving field for water wheel alternator. In this type of alternator it is essential that the rotating part be designed to have a liberal factor of safety not only at the ordinary operating speed, but also at speeds much in excess of normal. Frequently machines are required to operate safely at a speed 50 to 75 per cent. in excess of normal, so that there may be no danger in case the water wheel races. In most machines the field spider is of steel cast in a single piece for the smaller alternators and in two or more parts for the larger sizes. For alternators running at high peripheral speed, the rim is built up of steel laminations supported by a cast steel spider; the latter serves merely to rotate the rim, which is in itself able to withstand all stresses due to the high speed. The field poles are laminated, being built up of steel punchings held between malleable iron or bronze end plates, the latter being used on high speed machines. With but very few exceptions the poles are attached by dovetail projections that fit into corresponding slots. Steel tapered keys are driven in alongside the dovetails, and the pole pieces cannot become loose. All field coils, except on a few of the smallest machines, are of edgewise wound copper strip. This style of coil is essential for revolving field alternators where the pressure on the insulation, due to centrifugal force, is so great that cotton insulation on round wire will not stand. Current is led into the rings by means of carbon brushes, the number of brushes being such that the current density at the rubbing contact is kept within conservative limits. At least two brushes per ring are always provided so that one can be removed for inspection without interrupting the exciting current. In large machines the brush holder studs are mounted on a stand supported from the base; in small alternators they are usually fastened to the cap of one of the bearing pedestals.



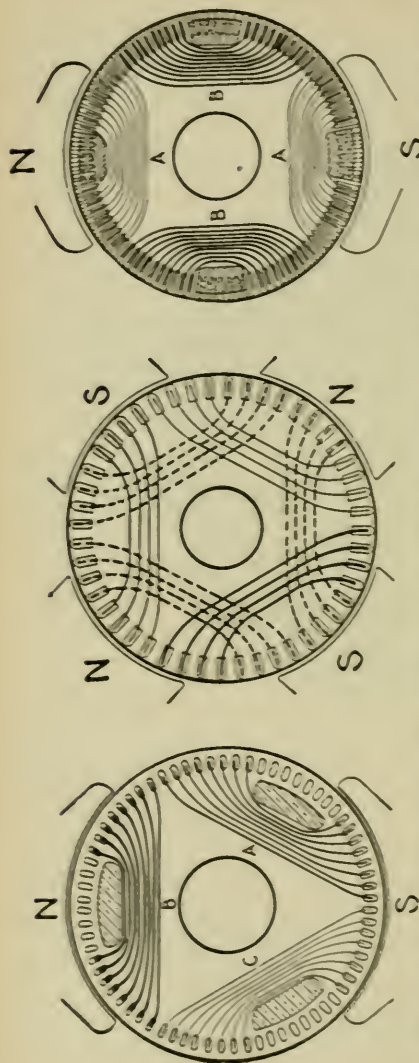

**FIGS. 1,442 to 1,444.**—Diagram of turbine alternator windings for revolving armature. Fig. 1,442 illustrates a two pole design in which all overlapping is avoided. It has 72 slots of which only 48 are filled, giving 8 slots per phase. The projecting claws from the brass end shield which hold the coils in position are shown in section. Fig. 1,443 shows a four pole design having 48 slots or 4 slots per phase per pole, the coils being made up of 8 inductors per slot taped together, the end bends forming two ranges. Fig. 1,444 shows a two pole design for a two phase armature with 18 slots per pole per phase. The even slots are spaced out as for 108 slots, but of these, 4 lots of 7 each are not stamped out, and 8 of those stamped are left empty, so that there are 72 slots filled.

**Ques.** What special provision is made for cooling the bearings?

**Ans.** They are in some cases water cooled.

**Turbine Driven Alternators.**—Although the principle of operation of the steam turbine and that of the reciprocating engine are decidedly unlike, the principle of operation of the high speed turbine driven alternator does not differ from that of generators designed for being driven by other types of engine or by water wheels. There are, therefore, with the turbine driven alternator no new ideas for

the operator who is familiar with the older forms to acquire.

It must be obvious that the proportions of such extra high speed machines must be very different from those permissible in generators of much slower speeds.

**Ques. How does a turbine rotor differ from the ordinary construction ?**

Ans. It is made very small in diameter and unusually long.

**Ques. Why?**

Ans. To reduce vibration and centrifugal stresses.

**Ques. What are the two classes of turbine driven alternators?**

Ans. They are classed as vertical or horizontal.

**Ques. How do they compare?**

Ans. The vertical type requires less floor space than the horizontal design, and while a step bearing is necessary to carry the weight of the moving element, there is very little friction in the main bearings.

The horizontal machine, while it occupies more space, does not require a step bearing.

**Ques. Describe a step bearing.**

Ans. It consists of two cylindrical cast iron plates bearing upon each other and having a central recess between them into which lubricating oil is forced under considerable pressure by a steam or electrically driven pump, the oil passing up from beneath.

**Ques. What auxiliary is generally used in connection with a step bearing?**

Ans. A weighted accumulator is sometimes installed in

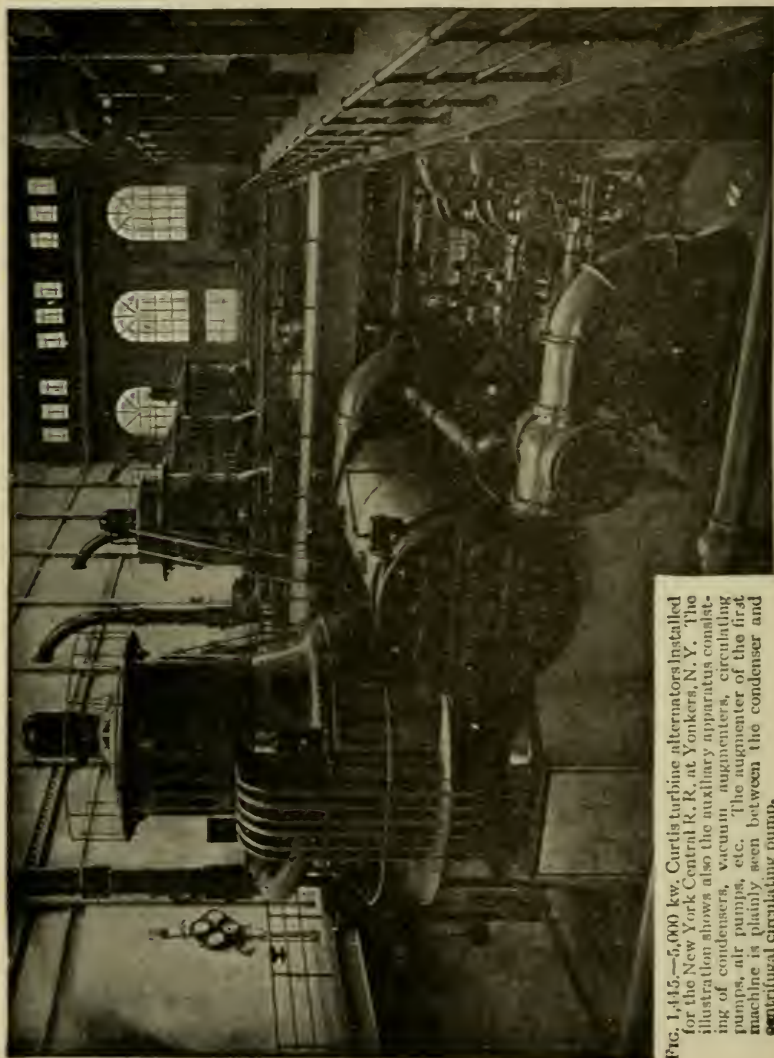


FIG. 1,445.—5,000 kw. Curtis turbine alternators installed for the New York Central R. R. at Yonkers, N. Y. The illustration shows also the auxiliary apparatus consisting of condensers, vacuum augmenters, circulating pumps, air pumps, etc. The augmentser of the first machine is plainly seen between the condenser and centrifugal circulating pump.

connection with the oil pipe as a convenient device for governing the step bearing pumps, and also as a safety device in case the pumps fail.

**Alternators of Exceptional Character.**—There are a few types of alternator less frequently encountered than those already described. The essentials of such machines are here briefly given.

**Asynchronous Alternators.**—In these machines, the rotating magnet, which, with definite poles, is replaced by a rotor having closed circuits. In general construction, they are similar to asynchronous induction motors having short circuited rotors; for these alternators, when operating as motors, run at a speed slightly below synchronism and act as generators when the speed is increased above that of synchronism. Machines of this class are not self-exciting, but require an alternating or polyphase current previously supplied to the mains to which the stationary armature is connected.

Asynchronous alternators may be advantageously used in central stations that may be required to sustain a very sudden increase of load. In such cases, one or more asynchronous machines might be kept in operation as a non-loaded motor at a speed just below synchronism until its output as a generator is required; when by merely increasing the speed of the engine it will be made to act as a generator, thus avoiding the delays usually occurring before switching in a new alternator.

**Image Current Alternators.**—When the generated frequency of alternators excited by low frequency currents is either the sum or the difference of the excitation and rotation frequencies, any load current flowing through the armature of the machine is exactly reproduced in its field circuit. These reproduced currents are characteristic of all types of asynchronous machines, and are called "image currents," as they are actually the reflection from the load currents delivered by the armature circuit.

As the exciter of a machine of this type carries "image currents" proportional to the generated currents, its size must be proportional to the capacity of the machine multiplied by the ratio of the excitation and generated frequencies; therefore, in the commercial machines, the excitation frequency is reduced to the minimum value possible; from two to five cycles per second being suitable for convenient employment.

These machines as heretofore constructed are not self-exciting, but as the principle of image current enables the construction of self-exciting alternators, it will be of advantage to have a general understanding of the separately excited machine under different conditions of excitation.

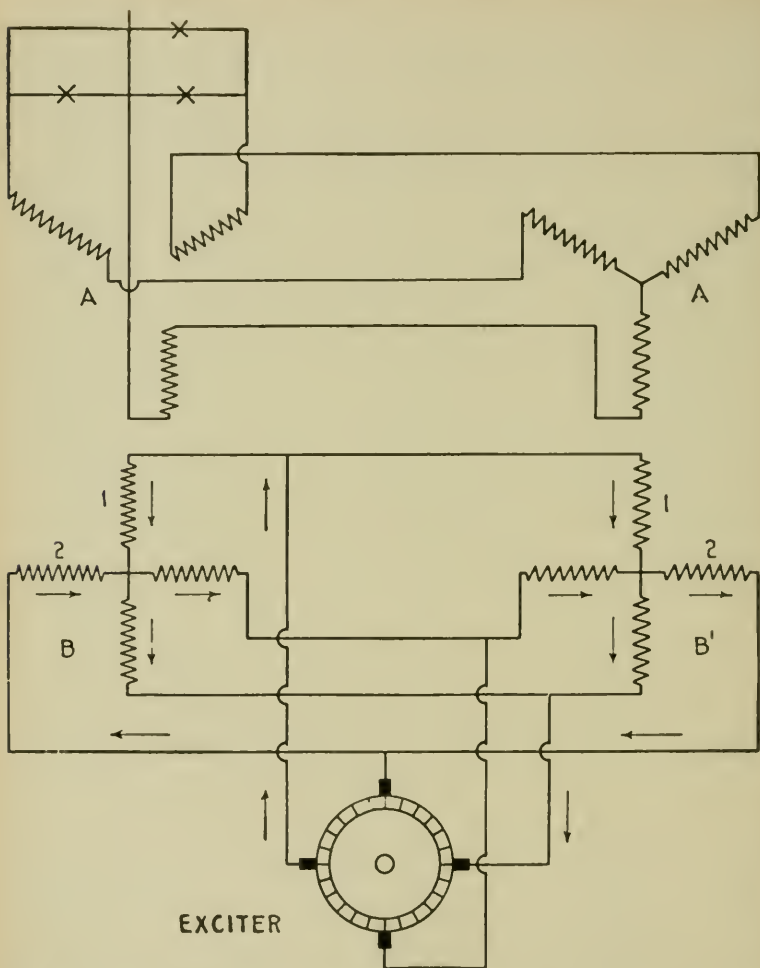


FIG. 1446.—Diagram of constant pressure image current alternator connections. The image or reproduced currents are characteristic of all types of asynchronous machines, and are called image currents because they are actually the reflection from the load currents delivered by the armature circuit. The principle of operation is explained in the accompanying text.



When the generated frequency of the machine is equal to the difference of the excitation and rotation frequencies, the magnetization of the machine is higher under a non-inductive load than under no load. This is principally due to the ohmic resistance of the field circuit, which prevents the image current from entirely neutralizing the magnetomotive force of the armature current. In other words, the result of the magnetomotive force of the armature and image currents not only tends to increase the no load magnetization of the machine at non-inductive load, but depresses the original magnetization at inductive load, so that the terminal voltage of the machine increases with non-inductive load, and decreases with inductive load.

Again, the generated frequency is equal to the sum of the excitation and rotation frequencies, the resistance of the field circuit reacts positively; that is, it tends to decrease the magnetization, and consequently the terminal voltage of the machine at both inductive and non-inductive loads.

In the constant pressure machine, the two effects are combined and opposed to one another.

The connections of two alternators with diphas excitation are shown by fig. 1,446.

**Extra High Frequency Alternators.**—Alternators generating currents having a frequency up to 10,000 or 15,000 cycles per second have been proposed several times for special purposes, such as high frequency experiments, etc. In 1902 Nikola Tesla proposed some forms of alternators having a large number of small poles, which would generate currents up to a frequency of 15,000 cycles per second.

Later, the Westinghouse Company constructed an experimental machine of the inductor alternator type for generating currents having a frequency of 10,000 cycles per second. This machine was designed by Samms. It had 200 polar projections with a pole pitch of only 0.25 inch, and a peripheral speed of 25,000 feet per minute. The armature core was built up of steel ribbon 2 inches wide and 3 mils thick. The armature had 400 slots with one wire per slot, and a bore of about 25 inches. The air gap was only 0.03125 inch. On constant excitation the voltage dropped from 150 volts at no-load to 123 volts with an output of 8 amperes.

**Self-Exciting Image Current Alternators.**—The type of machine described in the preceding paragraph can be made self-exciting by connecting each pair of brushes, which collect the current from the armature, with a field coil so located that the flux it produces will be displaced by a pre-determined angle depending on the number of phases required, as shown by fig. 1,447. The direction of the residual magnetism of the machine is shown by the arrows A, A.



When the armature is rotated, a pressure will be generated between the brushes 2 and 4, and a current will flow from C through the coils XX to B, producing a flux through the armature at right angles to the residual magnetism and establishing a resultant magnetic field between D, B, and D, C. This field will generate a pressure between the brushes 1 and 3, and a current will flow D through XX to E in such a direction that it will at first be opposed to the residual magnetism, and afterward

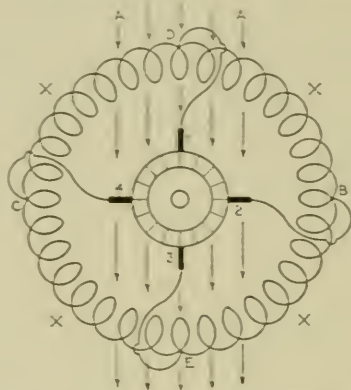


FIG. 1,447.—Diagram of connections of self-exciting image current alternator.

reverse the direction of the latter. At the moment the residual magnetism becomes zero, the only magnetism left in the machine will be due to the currents from the brushes 2 and 4, and their field combining with the vertical reversed field will produce a resultant polar line between B and E. As these operations are cyclic, they will recur at periodic intervals, and the phenomena will become continuous. The negative field thus set up in the air gap of the machine will cut the conductors of the stator and will be cut by the conductors of the rotor in such a manner that the electromotive forces generated between the brushes of the armature will be equal and opposite to those between the terminals of the stator.

## CHAPTER L

## CONSTRUCTION OF ALTERNATORS

The construction of alternators follows much the same lines as dynamos, especially in the case of machines of the revolving armature type. Usually, however, more poles are provided than on direct current machines, in order to obtain the required frequency without being driven at excessive speed.

The essential parts of an alternator are:


1. Field magnets;
2. Armature;
3. Collector rings;

and in actual construction, in order that these necessary parts may be retained in proper co-relation, and the machine operate properly there must also be included:

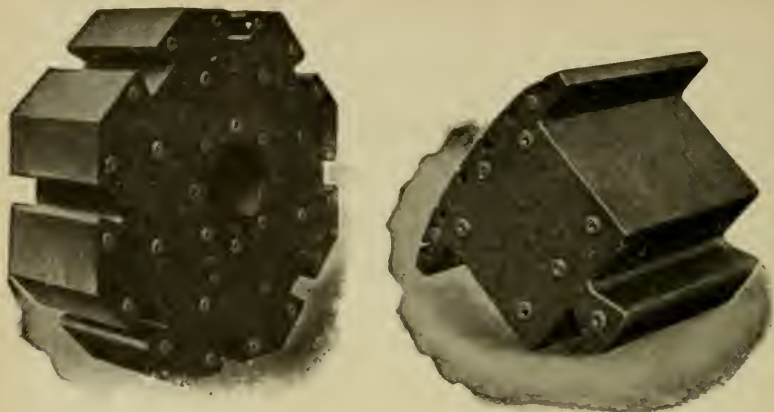4. Frame;
5. Bed plate;
6. Pulley.

**Field Magnets.**—The early forms of alternator were built with permanently magnetized steel magnets, but these were later discarded for electro-magnets.

Alternators are built with three kinds of electro-magnets, classed according to the manner in which they are excited, the machines being known as,



FIGS. 1,448 and 1,449.—Westinghouse laminated hub and laminated pole piece for revolving field having squirrel cage winding. Thin steel is used for the laminations of both hub and pole piece; these are assembled and firmly riveted together under hydraulic pressure. The laminations are of the same thickness in both hub and spider.




FIGS. 1,450 to 1,452.—Views of Triumph pole pieces. These consist of laminated punchings securely clamped between two cast steel end plates. The laminations are shaped with polar horns or shoes as shown, and which serve to keep the field coils securely wedged in position. In some designs the horns are separate. The two holes in each pole piece are for through bolts which secure the pole piece and coil to the spider run. Dovetail joints are sometimes used instead of through bolts, as in figs. 1,448 and 1,449.

1. Self-excited;
2. Separately excited;
3. Compositely excited.

**Ques.** What is a self-excited alternator?


**Ans.** One in which the field magnets are excited by current from one or more of the armature coils, or from a separate winding (small in comparison with the main winding), the current being transformed into direct current by passing it through a commutator.

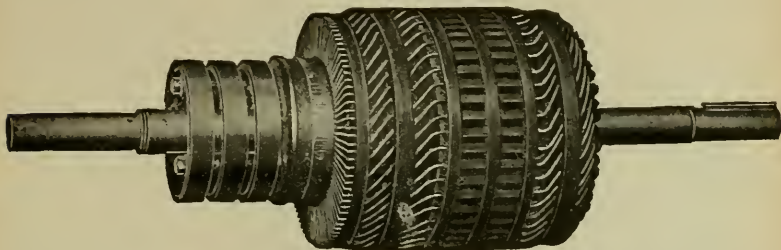

**FIG. 1,453.**—Fort Wayne armature for self-excited alternator. There are two independent windings, one for the main current, and one for the exciting current. The winding for the latter current occupies a very small amount of space, and is placed in the slots on top of the main winding. The commutator to which the exciter winding is connected, is located between the collector rings and the core. It is of standard construction with end clamps holding the bars in place on the insulated commutator drum. The armature coils are form wound and the core is built of sheet steel laminations, annealed and japanned to prevent hysteresis and eddy current losses. Ventilated openings are provided to allow a free circulation of air both around the ends of the windings and through ducts in the laminated core. The core is clamped by bolts between the flanges of the armature spider which is keyed to the shaft. These flanges have cylindrical extensions with ribbed surfaces, which form a support for the ends of the armature coils. The ribbed surfaces form air passages from the core outward around the ends of the coils, thus ventilating both core and coils.

Fig. 1,453 shows an armature of a self-excited machine, the exciting current being generated in a separate winding and passed through a commutator.

**Ques.** For what class of service are self-exciting alternators used?

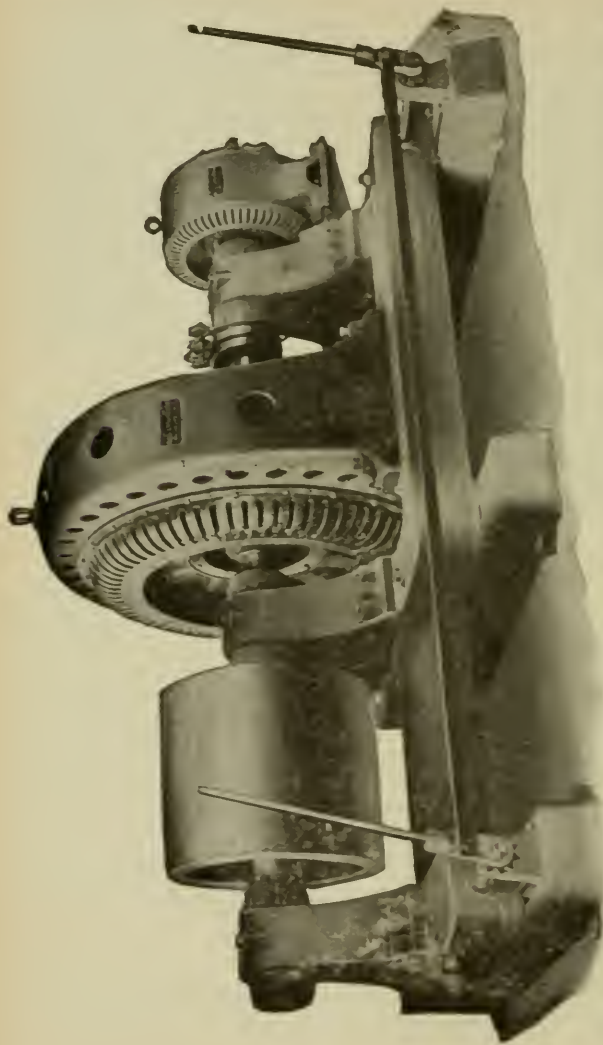

**FIG. 1,454.**—Allis-Chalmers three bearing type alternator with exciter direct connected. The bearing pedestals are bolted to a substantial cast-iron base having, in the large sizes, sufficient length to permit shifting frame sideways along the base to give access to the field and armature coils. The field coils are designed for 120 volt excitation, and are wound edgewise with copper strip. There is a liberal margin of field excitation to take care of overloads or for operation on loads of low power factor. The regulating qualities are as good as can be obtained without making the machine unnecessarily large and expensive. By regulation is meant the percentage rise in voltage when full load is thrown off, field excitation and speed being held constant; the percentage is referred to normal full load voltage. An alternator with poor regulation will show large variations in voltage with changes in load, the pressure falling whenever a load is thrown on and rising when it is thrown off. These changes will be especially pronounced if the load is inductive. A badly designed alternator might show very fair regulation on non-inductive load and yet be unable to give full voltage on inductive load.

Ans. They are employed in small power plants and isolated lighting plants where inductive loads are encountered.

**Ques.** What is a separately excited alternator?

Ans. One in which the field magnets are excited from a small dynamo independently driven or driven by the alternator shaft, either direct connected or by belt as shown in fig. 1,455.

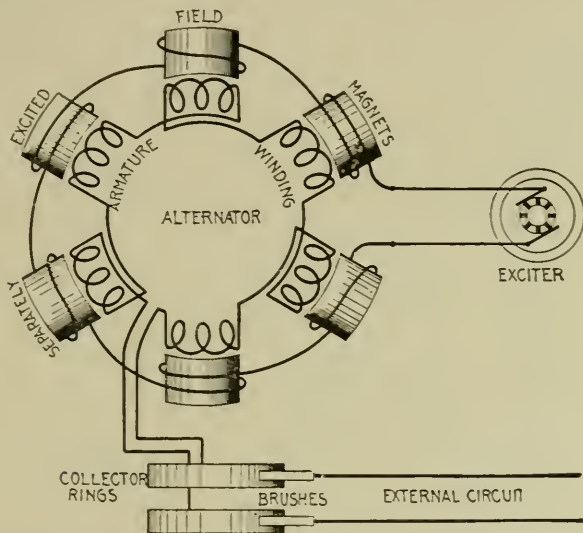


FIG. 1,455.—Diagram of separately excited alternator. The field winding is supplied with direct current, usually at 125 volts pressure by a small dynamo called the "exciter." The latter may be driven by independent power, or by belt connection with the main shaft, and in some cases the exciter is directly connected to the alternator shaft.

**Ques.** What is a compositely excited alternator?

Ans. A composite alternator is similar to a compound wound dynamo in that it has two field windings. In addition to the regular field coils which carry the main magnetizing current from the exciter, there is a second winding upon two or upon all of the



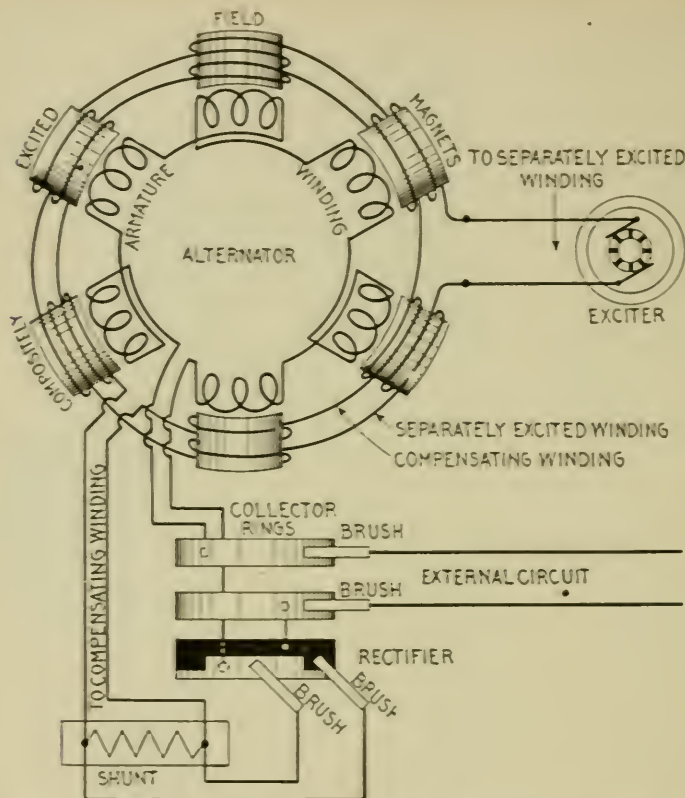


FIG. 1,456.—Diagram of compositely excited alternator. The current for exciting the field magnets is obtained, partly from an exciter and partly from the windings of the alternator, being transformed into direct current by the rectifier. The connections are as shown. One end of the armature winding is connected to one of the collector rings; the other end, to the light part of the rectifier, as shown, the solid black part of the rectifier being connected to the other collector ring. Two brushes bear on adjacent teeth of the rectifier and are connected to the compensating winding circuit across which is a shunt. These connections are shown more clearly in fig. 1,457. In operation the separately excited coils set up the magnetism necessary for the generation of the voltage at no load. The main current coming from the armature is shunted, part going through the shunt and the remainder around the compensating winding, forming the additional magnetism necessary to supply the voltage to overcome the armature impedance. This composite method of field excitation is very similar to that used on a compound wound dynamo. As shown, both field windings encircle every pole, but in some machines the rectified current will traverse a few poles only, the current from the exciter traversing the remainder.

pole pieces, carrying a rectified current from the alternator which strengthens the field to balance the losses in the machine, and also if so desired, the losses on the line as shown in fig. 1,456.

**Ques.** What is a magneto?

**Ans.** A special form of alternator having permanent magnets for its field, and used chiefly to furnish current for gas engine ignition and for telephone call bells.

Details of construction and operation are shown in figs. 1,458 to 1,461

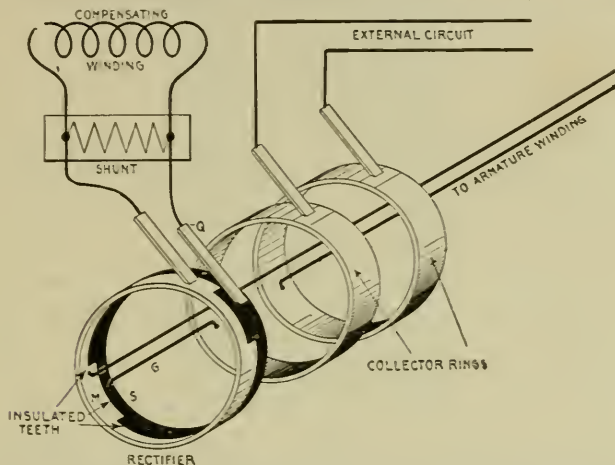


FIG. 1,457.—Diagram showing construction of rectifier and connections of compositely excited alternator. The rectifier consists of two castings M and S with teeth which fit together as shown, being insulated so they do not come in contact with each other. Every alternate tooth being of the same casting is connected together, the same as though joined by a conducting wire. There are as many teeth as there are poles. One end of the armature winding is connected direct to one of the collector rings, while the other is connected to M of the rectifier, the circuit being through brushes P and Q, the shunt, and compensating winding to the other collector ring. The brushes P and Q contact with adjacent teeth, when one is in contact with the solid black casting the other touches the light casting. The principle of action is the same as a commutator, briefly: to reverse the connections terminating at the brushes P and Q in synchronism with the reversals of the alternating current induced in the armature winding, thus obtaining direct current for the compensating field winding. The shunt resistance placed across the compensating winding circuit permits adjusting the compounding of the machine to the circuit on which it is to work, since by varying the resistance the percentage of the total current passing through the compensating winding can be changed. It will be seen by tracing the path of the current for each direction in the armature winding that while the rectifier causes the current to flow in the same direction in the compensating field winding, it still remains alternating in the external circuit.


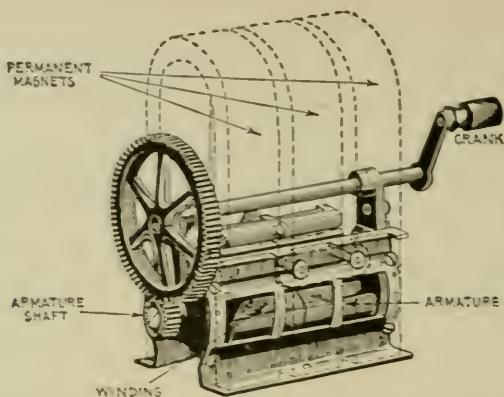


FIG. 1,458.—Connecticut magneto; view showing permanent magnets in dotted lines. It consists of three permanent U shape magnets, between the poles of which is a shuttle type armature. The latter is geared to a hand crank in sufficient velocity ratio to give the desired speed without too rapid turning of the crank. This type of magneto is used to generate current for operation of telephone call bells.

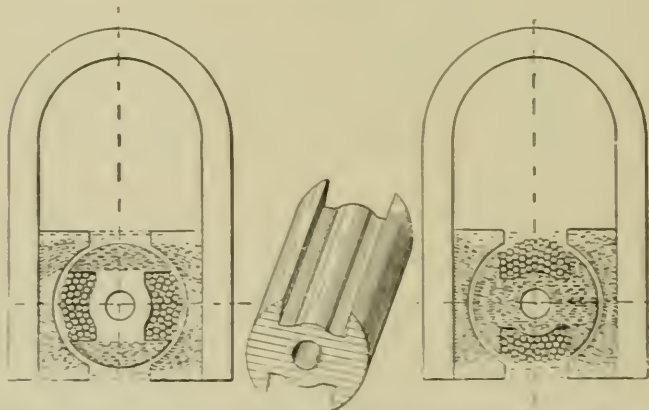

FIGS. 1,459 to 1,461.—Diagram illustrating the operation of a magneto. The shuttle shaped armature is wound from end to end with insulated wire, so that when rotated, a powerful alternating current is produced in the windings by cutting the magnetic lines, whose varying strength is shown by the shaded portions in the two views. When in the position shown in the first diagram, the lines of force mostly converge at the top and bottom, finding a direct path through the metal end flanges of the shuttle. When in the position shown in the second diagram, the lines are converged so as to pass through the armature core. Fig. 1,460 shows detail of the armature core.

**Ques.** What are the two principal types of field magnet?

**Ans.** Stationary and revolving.

**Ques.** What is the usual construction of stationary field magnets?

**Ans.** Laminated pole pieces are used, each pole being made up of a number of steel stampings riveted together and bolted or



**FIG. 1.462.**—Stationary field of Fort Wayne multiphase revolving armature alternator; view showing brass girds on pole pieces for synchronous motor operation. When designed for this use the machine is provided with amortisseur winding on the poles. As shown in the illustration this winding consists of a brass collar around the pole tip with a cross rib integral with the collar, fitting in a slot in the pole face parallel to the shaft. This construction assists in bringing the machine up to synchronous speed as an induction motor, ordinarily checks any tendency toward hunting and does not in any way affect the operation of the machine as an alternator. The main field winding should be connected through switches on the field frame in order that the field circuit may be broken up to eliminate any danger that might arise from induced voltage. It is not advisable to throw on a full rated voltage and a compensator should, therefore, be provided to reduce the pressure.

preferably cast into the frame of the machine. The field coils are machine wound and carefully insulated. After winding they are taped to protect them from mechanical injury. Each coil is then dipped in an insulating compound and afterwards baked to render it impervious to moisture.

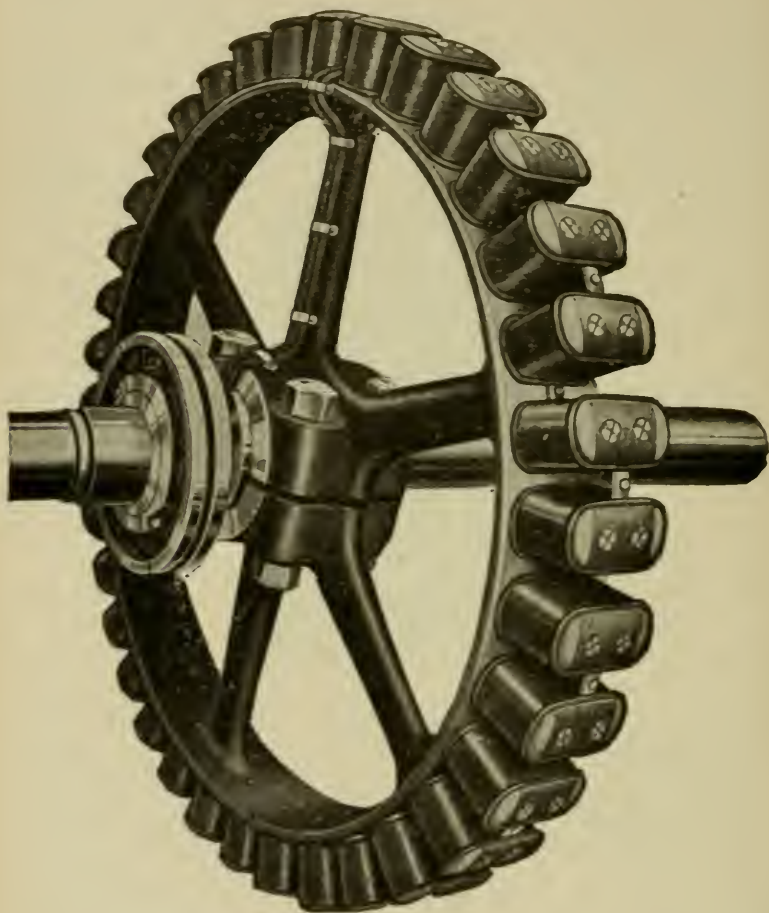


FIG. 1.463.—Triumph 36 pole fly wheel type revolving field. The spider has the form of a fly wheel having spokes and rim to which the field magnets are attached by through bolts. The field coils are of copper strap bent on end, the kind generally used on large machines. The series connection of the coils is plainly shown, also the two cables leading via one of the spokes to the slip rings.



**Ques.** Describe the construction of a revolving field.

**Ans.** The entire structure or rotor consists of a shaft, hub or spider, field magnets and slip rings. The magnet poles consist of laminated iron stampings clamped in place by means of through bolts which, acting through the agency of steel end plates, force the laminated stampings into a uniform, rigid mass. This mass is magnetically sub-divided into so many small parts that the heating effect of eddy currents is reduced to a minimum. The cores are mounted upon a hub or spider either by dovetail construction or by means of through bolts, according to the centrifugal force which they must withstand in operation, either method permitting the easy removal of any particular



FIG. 1.464.—Wagner cast steel hub with dovetail grooves for attaching the revolving field magnets. Such construction is generally used on machines of small and medium size.



FIG. 1.465.—Wagner laminated pole piece with horns stamped in one piece. The laminations are held together between two end pieces by through rivets, as shown.



field pole if necessary. The field coils are secured upon the pole pieces either by horns in one piece with the laminations, or separate and bolted. All the coils are connected in series, cable leads connecting them to slip rings placed on the shaft.

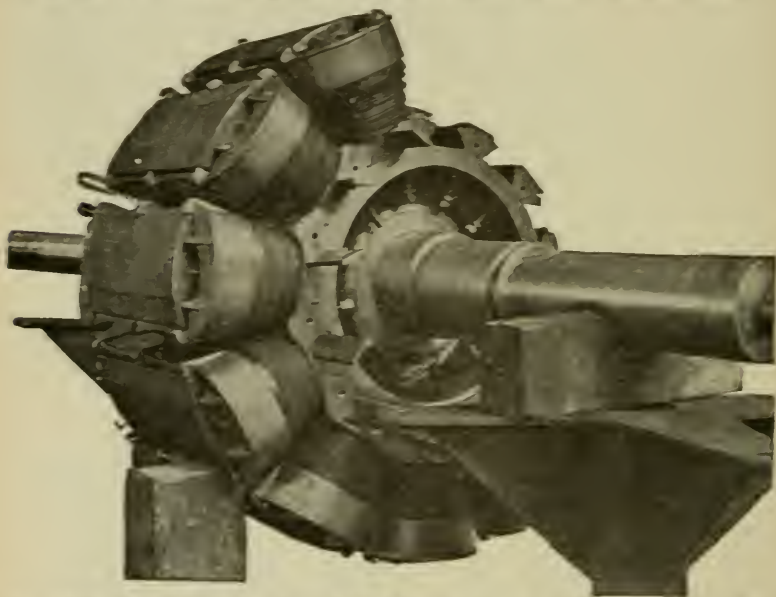


FIG. 1466.—Wagner revolving field of 500 kilowatt alternator during construction. Illustrating the method of attaching the field magnets to the pole by tapered horns. After the notched ends of the pole pieces are added, and the grooves in the iron tapered horns, which are plainly seen, are driven in, this making a tight joint which will not shake loose.

**Ques.** What are slip rings?

**Ans.** Insulated rings mounted upon the alternator shaft to receive direct current for the revolving field, as distinguished from collector rings which collect the alternating currents generated in an alternator of the revolving armature type.

In construction provision is made for attaching the field winding leads. The rings are usually made of cast iron and are supported

mechanically upon the shaft, but are insulated from it and from one another.

The current is introduced by means of brushes as with a commutator. Carbon brushes are generally used.

A good design of slip ring should provide for air circulation underneath and between the rings.

**Ques.** What form of spider is used on large alternators?

**Ans.** It is practically the same form



FIG. 1,467.—General Electric field coil, showing one method of winding. In the smaller machines the wire is wound on spools which are slipped over the pole pieces, which are built of sheet iron, spreading at the pole face so as to secure not only a wide polar arc for the proper distribution of the magnetic flux, but also to hold the field windings in place.



as a fly wheel, consisting of hub, spokes, and rim to which the magnets are bolted.

FIG. 1,468.—General Electric field coil showing another method of winding. The field coils on the larger machines consist of a single strip of flat copper, wound on edge as shown, so that the surface of every turn is exposed to the air for cooling. The flat sides of the copper strip rest against each other and the entire coil forms a structure of great solidity which can be easily removed for inspection and repair.

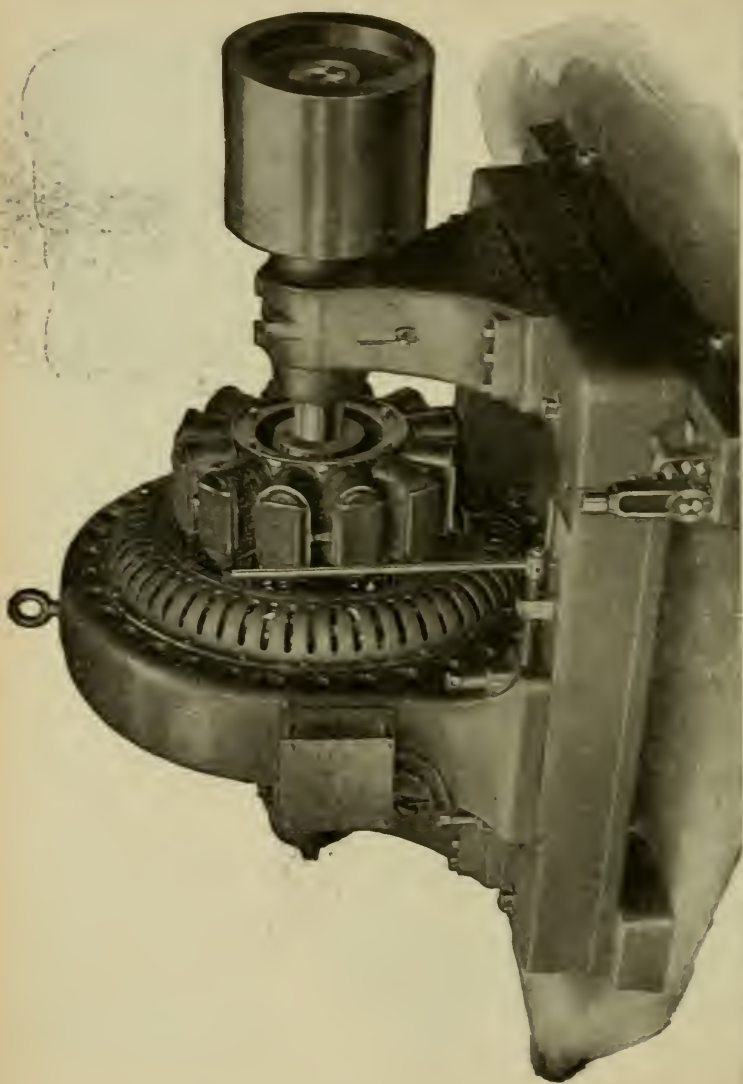


FIG. 1,410.—Allis-Chalmers 60 kva, belted two bearing alternator on base arranged so the armature can be shifted sideways as shown, to give access to the field and armature coils.

On alternators of the fly wheel type the spider rim is made of sufficient weight to obtain full fly wheel effect, thus making a separate fly wheel unnecessary.


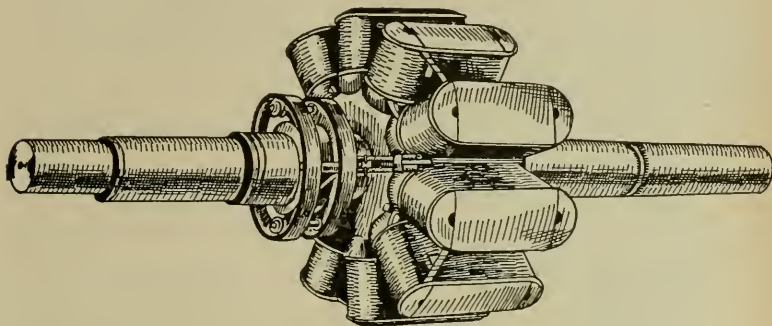


FIG. 1,470.—Revolving field of Fort Wayne 10 pole alternator. In construction, the cores of the field poles are built up from punchings of laminated steel, and assembled under considerable pressure between malleable iron or steel end plates and riveted together. Substantial insulation is placed on the pole cores and over this is wound the field coils of cotton covered wire. After the wire is in place, the completed poles are baked to expel any moisture and are then treated with insulating varnish. They are then assembled on a laminated spider, being held in place by dovetail joints made tight by the use of taper keys. Special casting plates are finally fastened in place over the dove tails effectually closing them. The assembly of the field is completed by the insertion of the shaft into the field spider under heavy hydraulic pressure. All the coils are connected in series, cable leads connecting them to slip rings placed on the shaft. Each slip ring is provided, with a double type brush holder, making it possible to clean brushes while the alternator is in service, by simply removing one brush at a time.

FIG. 1,471.—General Electric slip rings; view showing construction and attachment of cable leads to field winding. They are so designed that all surfaces of the rings have easy access to the air, in order to obtain good ventilation. *Slip rings*, through which current is transmitted to a revolving field, are to be distinguished from *collector rings* whose function it is to "collect" or transmit the alternating currents induced in the armature to the brushes.

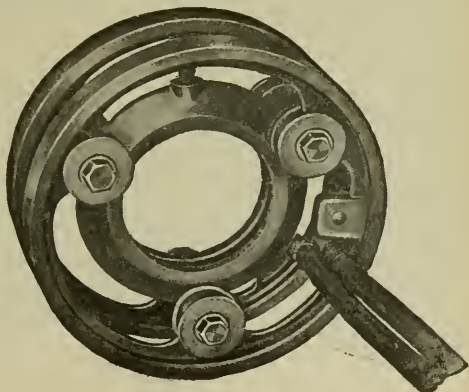

**Armatures.**—In construction, armatures for alternators are similar to those employed on dynamos; they are in most cases simpler than direct current armatures due to the smaller number of coils, absence of commutator with its multi-connections, etc. Alternator armatures may be classified in several ways:

1. With respect to operation, as

- a.* Revolving;
- b.* Stationary.

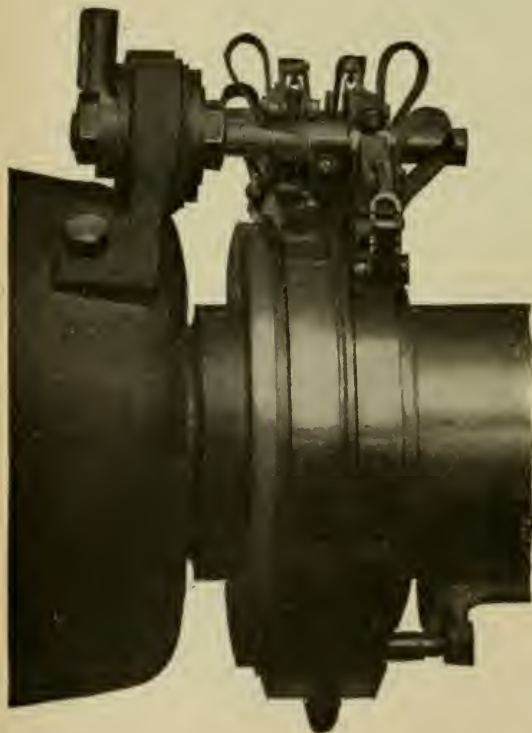


FIG. 1,472.—Allis-Chalmers brush holder and slip rings. The latter are made of cast copper, which the builders claim to be more satisfactory than cast iron. On some of the large low speed machines the collector rings are split, but on the majority of alternators they are in one piece. Current is led into the rings by means of carbon brushes, the number of brushes being such that the current density at the rubbing contact is kept within conservative limits. At least two brushes per ring are provided, so that one can be removed for inspection without interrupting the exciting current. In large machines the brush holder studs are mounted on a stand supported from the base; on small alternators they are usually fastened to the cap of one of the bearing pedestals.



FIG. 1,473.—Fort Wayne multi-phase revolving armature alternator, designed for use in small power plants and isolated lighting plants where inductive loads are encountered. Built for pressures of 120, 240, 480, and 600 volts. These voltages have been recommended by the American Institute of Electrical Engineers, and will cover the needs of any set of conditions ordinarily met with. These standard voltages not only permit economical distribution, but they are such that no transformers are necessary to reduce the line pressure for ordinary cases. For transmitting power relatively long distances, 600 volts is usually employed. Where there is a demand for 480 volt service, a 480 volt alternator should be selected and if lower voltages are also desired an auto-transformer may be furnished by means of which 240 volts can be obtained. When 120 volt circuits are necessary for lighting, etc., the 240 volt pressure can be still further reduced to 120 volts by means of another auto-transformer. However, this double reduction will rarely be found necessary.


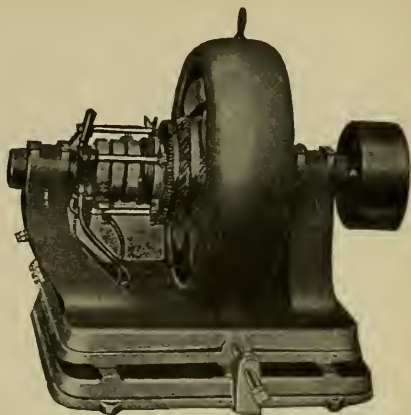


FIG. 1,474.—Western Electric stationary armature. In this type of armature, the core upon which the winding is placed, is built into the frame as shown, the core teeth projecting inwardly like internal gear teeth, forming a cylindrical chamber for the revolving field. The core is built up of iron, laminated and japanned to prevent eddy currents and hysteresis losses. The laminations are rigidly bolted between two heavy end plates. The armature coils are of copper bar impregnated with insulating compound. They are held in the slots by wedges which allow their ready removal for inspection or repairs.

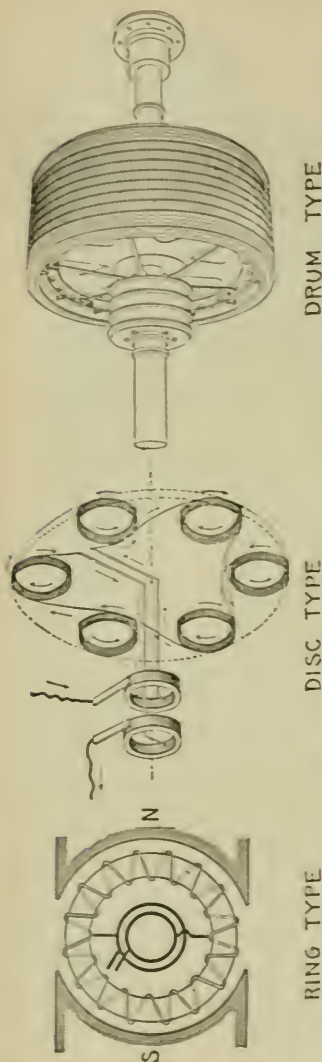



FIGS. 1,471 to 1,477.—Various types of armature; fig. 1,474 ring armature; fig. 1,475 disc armature; fig. 1,476 drum armature. The latter type is now almost universally used, the others being practically obsolete. A Gramme ring wound and connected to collector rings as in fig. 1,474, will yield an alternating current. In a multipolar field, the ring will need multipolar connections alternated at points corresponding to the pitch of the poles. Fig. 1,475 illustrates the so-called "Siemens" disc armature. The armature coils are arranged around the periphery of a thin disc. The field magnets consist of two crowns of fixed coils, with iron cores arranged so that their free poles are opposite one another. This type was created in 1878 by Herr von Hefner, engineer to Messrs. Siemens and Halske. Fig. 1,476 shows a modern drum armature of a three-phase machine. It is similar in appearance to a direct current armature except for the absence of the commutator and its connections. The drum armature is the prevailing type.

2. With respect to the core, as

- a. Ring;
- b. Disc;
- c. Drum.

Ring and disc armatures are practically obsolete and need not be further considered. A ring armature has the inherent defect that the copper inside the ring is inactive.

Disc armatures were employed by Pacinotti in 1878, and afterwards adopted by Brush in his arc lighting dynamos.

The design failed for mechanical reasons, but electrically it is, in a sense, an improvement upon the Gramme ring, in that inductors on both sides of the ring are active, these being connected together by circumferential connectors from pole to pole, thus, corresponding to the end connections on modern drum armatures.

3. With respect to the core surface, as

- a. Smooth core;
- b. Slotted core.

In early dynamos the armature windings were placed upon an iron core with a smooth surface. A chief disadvantage of this arrangement is that the magnetic drag comes upon the inductors and tends to displace them around the armature. To prevent

## DOVETAIL GROOVES



FIG. 1,478.—A style of disc largely used for armature cores. The teeth are provided with dovetail grooves near the circumference. After the coil is inserted in a groove, a wooden wedge is driven in the groove which encloses the coil and secures it firmly in position. This obviates the necessity of bands to resist the centrifugal force acting on the inductors.

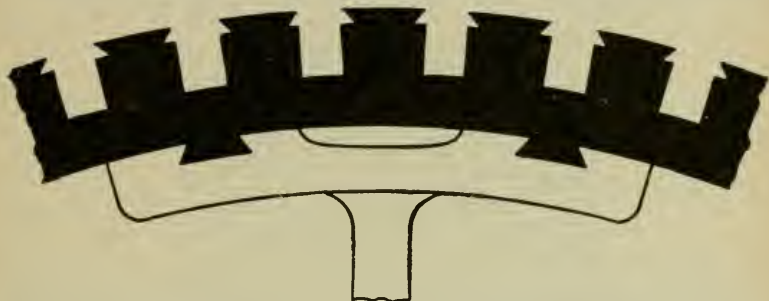


FIG. 1,479.—Large revolving armature construction with segmental discs dovetailed to spider spokes.

## FRAME

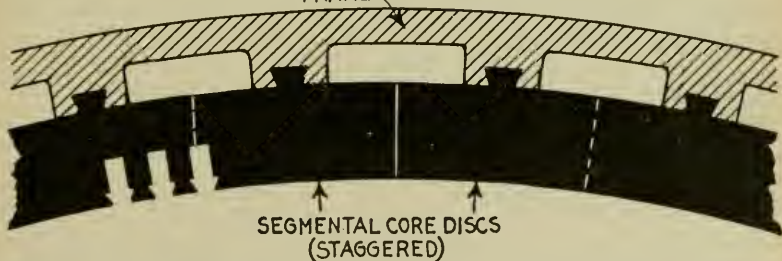
SEGMENTAL CORE DISCS  
(STAGGERED)

FIG. 1,480.—Construction of large stationary armature; view showing section of core and frame. The core discs are in segments and are attached to the frame by dovetail joints as shown. The joints are staggered in building up the core, that is, they are overlapped so as not to unduly increase the reluctance of the magnetic circuit. Dovetail joints obviate the use of through bolts which, if not insulated, are liable to give rise to eddy currents by short circuiting the discs.

this, projecting metal pieces called *driving horns* were fixed into the core so as to take the pressure, but they proved unsatisfactory. This defect together with the long air gap necessary in smooth core construction resulted in the type being displaced by slotted core armatures.

A slotted core is one whose surface is provided with slots or teeth which carry the inductors, as shown in the accompanying illustrations, and is the type almost universally used. The inductors are laid in the slots, the sides and bottoms of which are first carefully insulated by troughs of mica-canvas, micanite or other suitable insulating material.

**Ques.** What are the advantages of slotted core armatures?

**Ans.** The teeth protect the inductors, retain them in place against the electrical drag and centrifugal force, and the con-

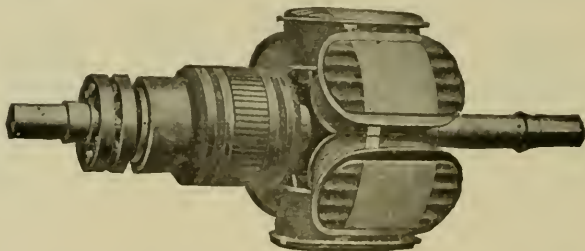


FIG. 1,481.—General Electric revolving field and exciter armature. This is an example of direct connected exciter construction. In this arrangement the armature of the exciter is carried on the alternator shaft at the end farthest from the pulley. In the smaller sizes the magnet frame is bolted to the bearing bracket, but in the larger sizes special construction is used depending upon the conditions to be met. On all alternators of standard design, the field is built for 125 volts excitation and on account of the increased danger from induced voltage, in case the machine is used as a synchronous motor, the builders consider any higher voltage undesirable.

struction permits a reduction of air gap to a minimum, thus reducing the amount of copper required for the field.

**Armature Windings.**—In general, the schemes for armature windings for alternators are simpler than those for direct current machines, as in the majority of cases the inductors are an even multiple of the number of poles, and the groupings are usually symmetrical with respect to each pole or each pair of poles. Furthermore, as a general rule, all the inductors of any one phase are in series with one another; therefore, there is only one circuit per

phase, and this is as it should be, since alternators are usually required to generate high voltages. These general principles establish the rule, that in the circuit in a single phase armature, and in the individual circuits in a polyphase armature, the

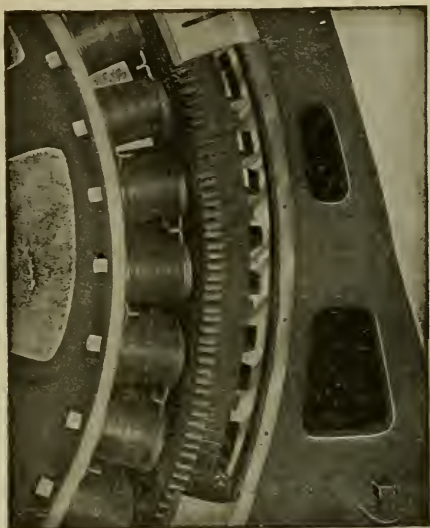


FIG. 1,482.—Section of General Electric Alternator showing method of dovetailing core laminations to frame. The latter is made in two general styles, known as the *box type* and *skeleton type*. The **box type** consists of a single casting for the smaller sizes, but for large capacity alternators the frame castings are usually divided into upper and lower sections. The **skeleton type** consists of two side castings between which substantial spacing rods are set at regular intervals. The core consists of the usual sheet iron lamination slotted and assembled; they are mounted on the inner periphery of the frame, making lap joints (that is "staggered" as in fig. 1,480), each section being dovetailed to the frame. Heavy clamping rings or end plates are mounted on both sides of the core by means of bolts, and supporting fingers extend along the slot projections. The design is such as to provide for air circulation as shown in figs. 1,483 and 1,484.

winding is never re-entrant, but the circuits have definite endings and beginnings. In exceptional cases, as those of polyphase converters, re-entrant circuits are employed, and the armature windings are so constructed that a commutator can be

connected to them exactly as in direct current machines. These armatures are usually of the lap wound drum type.

Alternator windings are usually described in terms of the number of slots per phase per pole. For instance, if the armature of a 20 pole three phase machine have 300 slots it has 15 slots

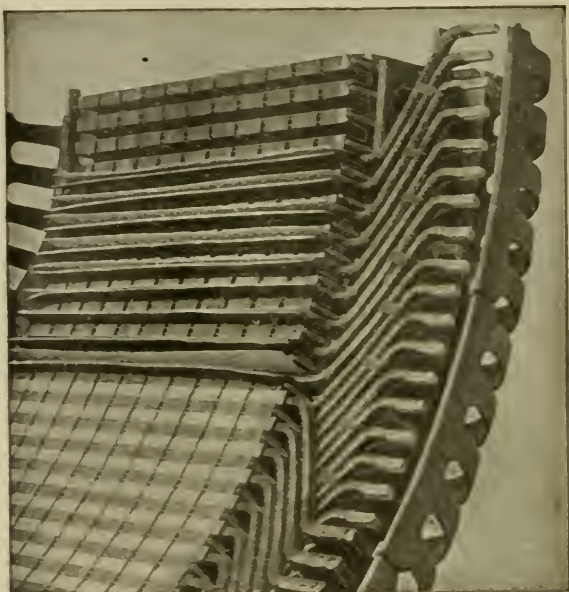


FIG. 1,483.—Section of General Electric alternator frame showing air ducts and supporting fingers extending along the slot projections. The air circulation is provided for by means of ducts formed by suitable spacing blocks inserted at intervals between the laminations, as shown here and in fig. 1,484. The armature coils are form wound and designed so they can be readily replaced in case of injury. They are taped and treated with an impregnating compound, in the usual way, then inserted in the armature slots in an armour of horn fibre and retaining wedges of wood are dovetailed into the slot walls.

per pole or 5 slots per each phase per pole, and will be described as a five slot winding. Therefore, in order to trace the connections of a winding, it is necessary to consider the number of slots per pole for any one phase, on one of the following assumptions:



1, that each slot holds one inductor; 2, that there is one side of a coil in each slot; and 3, that one side of a coil is subdivided so as to permit of its distribution in two or more adjacent slots.

The voltage depends upon the number of inductors in a slot, but the breadth coefficient and wave form are influenced by the number of slots per pole, and not by the number of inductors within the slots.



FIG. 1,484.—Section of General Electric stationary armature showing method of assembling the coils. These are form wound and are held in the slots by suitable wedges, the open slot construction permitting the use of form wound coils that can be easily removed and replaced in case of damage. Where heavy windings project beyond the laminations, an additional support is provided by means of an insulated metal ring, to which the outer ends of the coils are fastened; the coils are thereby protected from mechanical displacement, or distortion due to the magnetic disturbances caused by violent fluctuations of the load or short circuits. The figure shows a section of a supporting ring of this type and indicates the method of connecting the coils to it. In order to admit of the prompt replacement of damaged coils, sufficient space is usually provided between the alternator bearings to allow ample movement of the armature to permit of ready access to both armature and field coils. Where space necessitates the use of a short shaft, access to the windings may be had by disconnecting some of the coils and lifting the upper half of the armature.



**Classification of Windings.**—The fact that alternators are built in so many different types, gives rise to numerous kinds of armature winding to meet the varied conditions of operation. In dividing these forms of winding into distinctive groups, they may be classified, according to several points of view, as follows.

1. With respect to the form of the armature, as:
  - a. Revolving;
  - b. Stationary.
2. With respect to the mode of progression, as:
  - a. Lap winding;
  - b. Wave winding.
3. With respect to the relation between number of poles and number of coils, as:
  - a. Half coil winding;
  - b. Whole coil winding.
4. With respect to the number of slots, as:
  - a. Concentrated or uni-coil winding;
  - b. Distributed or multi-coil winding.
    - Partially distributed;
    - Fully distributed.
5. With respect to the form of the inductors, as:
  - a. Wire winding;
  - b. Strap winding;
  - c. Bar winding.
6. With respect to the number of coils per phase per pole, as:
  - a. One slot winding;
  - b. Two slot winding;  
etc.

7. With respect to the kind of current delivered, as:

- a. Single phase winding;
- b. Two phase winding;
- c. Three phase winding.



FIG. 1,485.—Section of Western Electric stationary armature core showing laminations clamped in place, and ventilating ducts. The stator or stationary armature consists of soft iron laminations assembled in the magnet frame with stator coils embedded in the core slots. The laminations are punched separately and then carefully annealed to reduce hysteresis losses. After annealing, a coat of japan is applied, effectively preventing the flow of eddy currents in the assembled core. The frame is cast iron and of the box type construction. The frames of the smaller sizes are cast in one piece, while frames of the larger sizes are split to facilitate installation. Large openings are provided in the box type frame, in order to improve the ventilation. The laminations are securely held in place in the frame by heavy end rings and by steel clamping fingers which are firmly bolted to the frame. The outer circumference of the core is dovetailed to the frame, and the inner circumference is slotted to receive the windings. The alignment of the slots is insured by means of metal wedges, and no filing is done on the slots, so that each lamination is always insulated from the next one. Numerous ventilating ducts allow the free circulation of cool air through and around the coils. The open slot construction is employed and the coils are fitted into insulating troughs which offer excellent mechanical and electric protection. The coils are held in place by suitable wedges.

8. With respect to the shape of the coil ends, as:

- a. Single range;
- b. Two range;
- etc.

In addition to these several classes of winding, there are a number of miscellaneous windings of which the following might be mentioned:

- a. Chain or basket winding;
- b. Skew coil winding;
- c. Fed-in winding;



FIG. 1486.—Method of assembling form wound coils. The picture shows a section of a General Electric armature with part of the coils in place. A layer of insulating material is first placed in the slots, before inserting the coils as seen at the left. When the coils are in place and surrounded by this layer of insulating material the retaining wedges are inserted in the notches, thus closing the slots and protecting the coils from mechanical injury. A few wedges are seen in position at the right.

- d. Imbricated winding;
- e. Mummified winding;
- f. Spiral winding;
- g. Shuttle winding;
- h. Creeping winding;
- i. Turbine alternator winding.

**Ques.** Define a revolving and a stationary winding.

**Ans.** The words are self-defining; a winding is said to be revolving or stationary according as the armature forms the rotor or stator of the machine.

**Ques.** What is the significance of the terms lap and wave as applied to alternator windings?

**Ans.** They have the same meaning as they do when applied to dynamo windings.

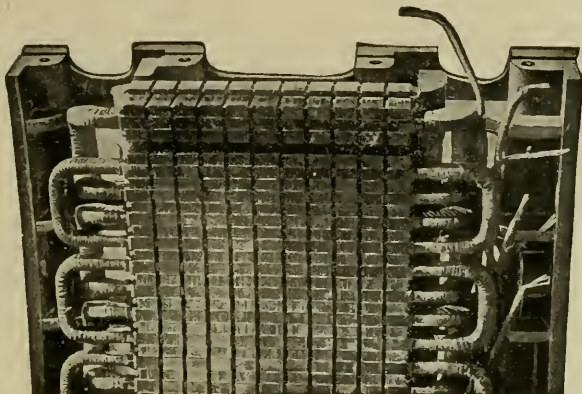



FIG. 1,487.—Section of General Electric stationary armature ventilating ducts and winding in position.

These are described in detail in Chapter XVIII. Briefly a lap winding is one composed of lap coils; a wave winding is one which roughly resembles in its diagram, a section of waves.

**Half Coil and Whole Coil Windings.**—The distinction as to whether the adjacent sides of consecutive coils are placed together under one pole or whether they are separated a distance equal to the pole pitch, gives rise to what is known as half coil and whole coil windings.


A half coil or hemitropic winding is one in which the coils in any phase are situated opposite every other pole, that is, a winding in which there is only one coil per phase per pair of poles, as in fig. 1,488.

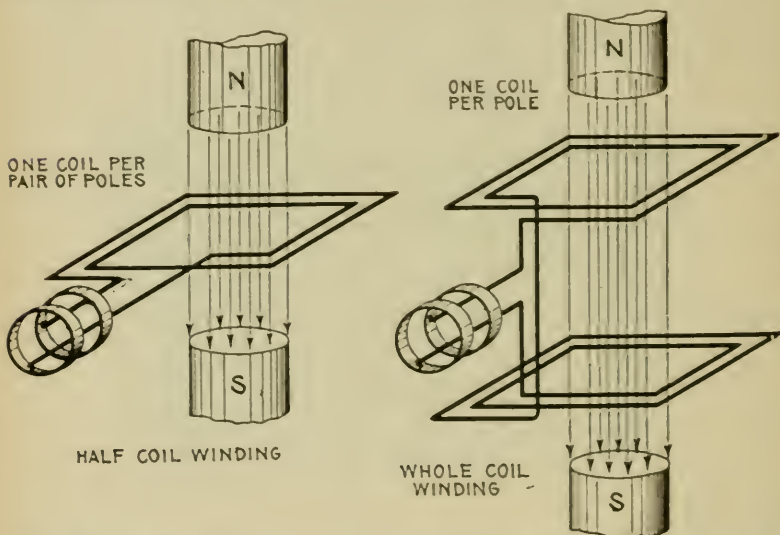A whole coil winding is one in which there is one coil per phase per pole, as in fig. 1,489, the whole (every one) of the poles being subtended by coils.




FIGS. 1,488 and 1,489.—Elementary bipolar alternators with half coil and whole coil windings. In a half coil winding there is one coil per phase per pair of poles; in a whole coil winding there is one coil per phase per pole.

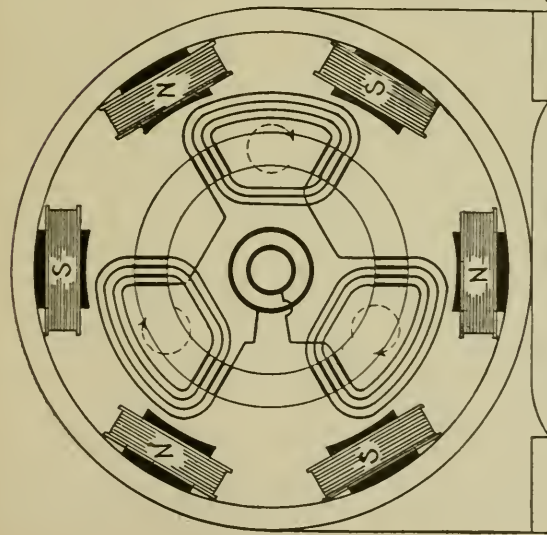**Concentrated or Uni-Coil Winding.**—Fig. 1,492 shows the simplest type of single phase winding. It is a one slot winding and is sometimes called “monotooth” or “uni-coil” winding. The surface of the armature is considered as divided into a series of large teeth, one tooth to each pole, and each tooth is wound with one coil, of one or more turns per pole. Since



HALF COIL WINDING

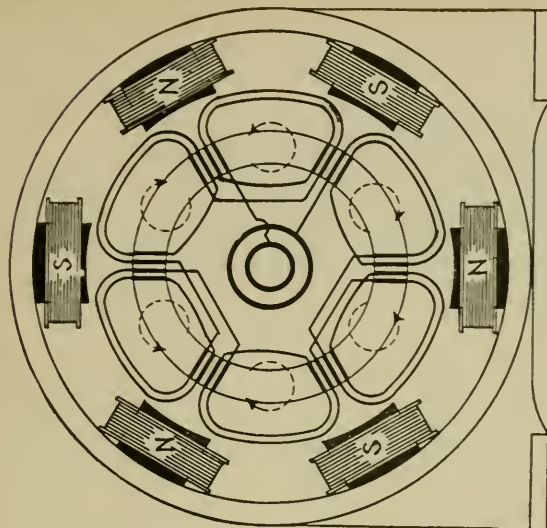

WHOLE COIL WINDING

FIG. 1,490.—Multi-polar revolving armature alternator with half coil winding, shown in radially developed diagram to clearly indicate the path of the winding. A half coil or hemitropic winding has a slightly higher reactance than a winding in which two distinct coils are used in the same slot, one going forward and the other backward. The most usual three phase windings are of the half coil type as the three sets of coils are equispaced over a pair of poles.


FIG. 1,491.—Multi-polar revolving armature alternator with whole coil winding shown in radially developed diagram to clearly indicate the path of the winding.




all the turns of the coil are placed in single slots, the winding is called "concentrated."

**Ques.** What are the features of concentrated windings?

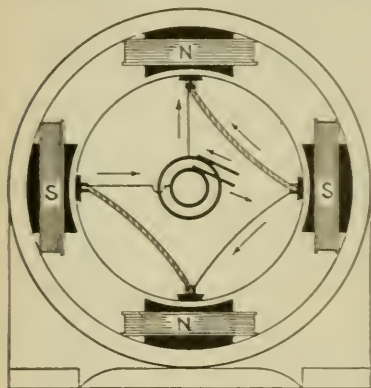**Ans.** Cheap construction, maximum voltage for a given number of inductors. Concentrated windings have greater armature reaction and inductance than other types hence the terminal voltage of an alternator with concentrated winding



CONCENTRATED HALF  
COIL WINDING

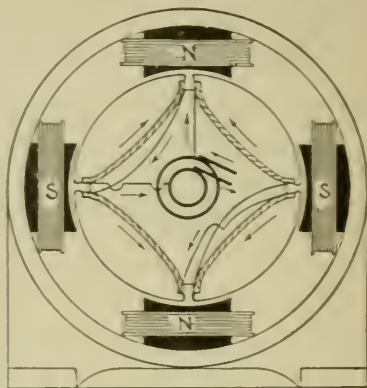

CONCENTRATED WHOLE  
COIL WINDING

**FIGS. 1,492 and 1,493.**—Concentrated windings. A concentrated winding is one in which the armature has only one tooth per phase per pole, that is, the number of teeth equals the number of poles. A concentrated winding of the half coil type has only one side of a coil in each slot as in fig. 1,492. In the whole coil variety, each slot contains neighboring sides of adjacent coils, as in fig. 1,493. In construction, wedges are generally used for retaining the half coils, and with whole coils the teeth have projecting horns for this purpose.

falls off more than with distributed winding when the current output is increased. An alternator, therefore, does not have as good regulation with concentrated winding as with distributed winding.

**Ques.** What should be noted with respect to concentrated windings?

**Ans.** A concentrated winding, though giving higher voltage

than the distributed type with no load, may give a lower voltage than the latter at full load.

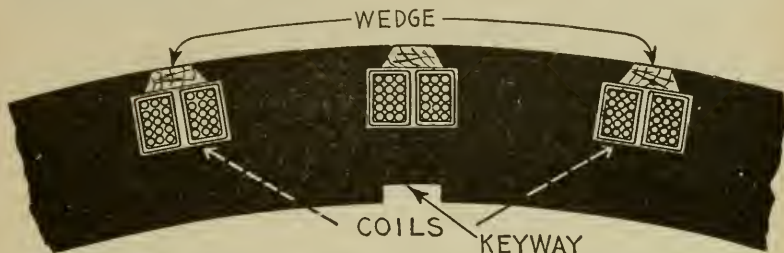


FIG. 1,494.—Laminated core with two coils in position; type of punchings used on some machines having concentrated whole coil windings. The manner of assembling the coils is shown in fig. 1,495.

**Ques.** What is the wave form with a concentrated winding?

**Ans.** The pressure curve rises suddenly in value as the armature slots pass under the pole pieces, and falls suddenly as the armature slots recede from under the pole pieces.


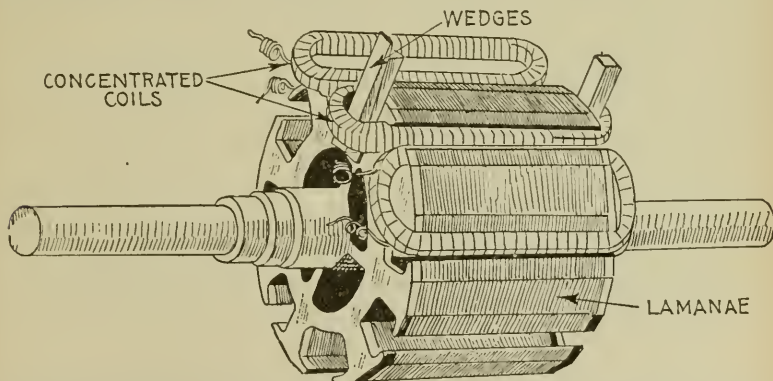


FIG. 1,495.—Westinghouse single phase concentrated coil armature; view showing method of placing coils. The coils are machine wound on formers and after being taped, varnished and baked, are spread out slightly so as to pass over the teeth and are then forced into place in the deep slots by means of wooden wedges, being securely held in place by retaining wedges, as shown in fig. 1,494.

**Distributed or Multi-Coil Windings.**—Instead of winding an armature so it will occupy only one slot per phase per pole, it may be spread out so as to fill *several slots per phase per pole*. This arrangement is called a distributed winding.

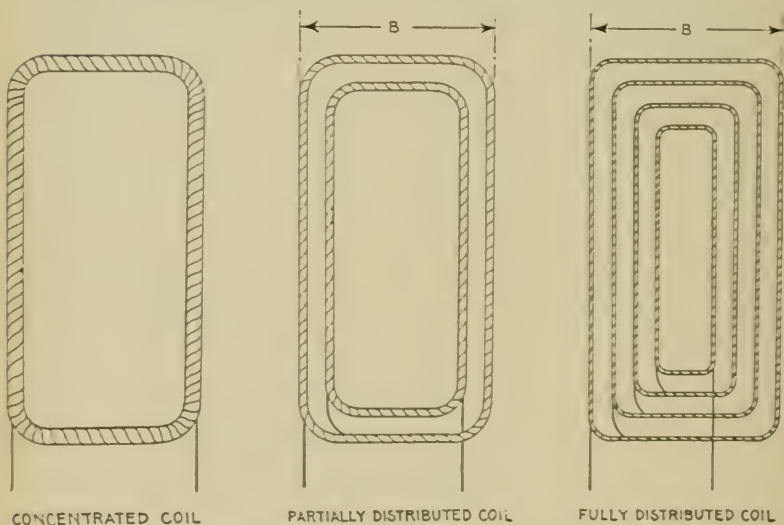To illustrate, fig. 1,496 represents a coil of say fifteen turns. This could be placed on an armature just as it is, in which case only one slot would be required for each side, that is, two in all. In place of



FIGS. 1,496 TO 1,498. — Alternator coils, showing difference between the concentrated, partially distributed, and fully distributed forms. Fig. 1,496 shows a concentrated coil in which all the wire is wound in one large coil; in the partially distributed type fig. 1,497, the wire of fig. 1,496, is wound in two or more coils or "sections" connected as shown, leaving some space inside not taken up by the subdivisions. In fig. 1,498 the wire of fig. 1,496 is *fully distributed*, being wound in a series of coils, so that all the interior space is taken up by the wire, that is to say, the spaces not occupied by the wire (the teeth when placed on the armature) are of equal size.


this thick coil, the wire could be divided into several coils of a lesser number of turns each, arranged as in fig. 1,497; it is then said to be *partially distributed*, or it could be arranged as in fig. 1,498, when it is said to be *fully distributed*.

A partially distributed winding, then, is one, as in fig. 1,499, in which the coil slots do not occupy all the circumference of the armature; that is, the core teeth are not continuous.


A fully distributed winding is one in which the entire surface of the core is taken up with slots, as in fig. 1,500.

**Ques.** In a distributed coil what is understood by the breadth of the coil?

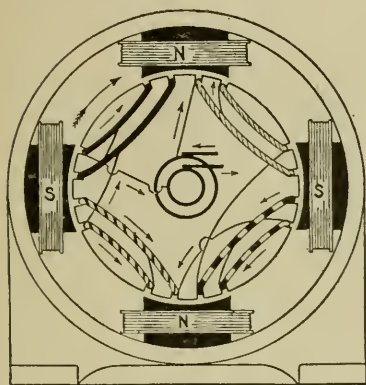**Ans.** The distance between the two outer sides, as B in figs. 1,497 and 1,498.



PARTIALLY DISTRIBUTED WINDING

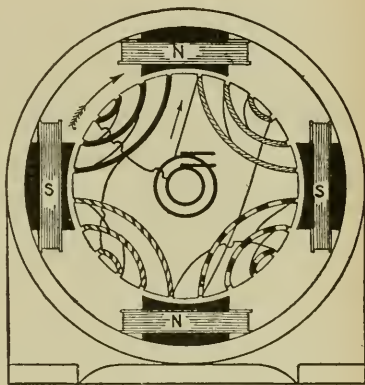

FULLY DISTRIBUTED WINDING

**FIG. 1,499.**—Partially distributed winding. Each coil unit is here divided into two concentric coils of different dimensions and connected in series, as shown in detail in fig. 1,497. This being a "whole coil" winding the several units are so connected that the winding of adjacent units proceeds in opposite directions, that is, one coil is wound clockwise, and the next counter clockwise, etc., so that the induced currents flow in a common direction as indicated by the arrows for the position shown.

**FIG. 1,500.**—Fully distributed winding. In this type of winding each coil consists of so many sub-coils that the winding occupies the entire surface of the armature core; that is, there are no extensive spaces unoccupied, the spacing being uniform as shown.

**Ques.** How far is it advisable to spread distributed coils of a single phase alternator?

**Ans.** There is not much advantage in reducing the interior

breadth much below that of the breadth of the pole faces, nor is there much advantage in making the exterior breadth greater than the pole pitch.

Undue spreading of distributed coils lowers the value of the Kapp coefficient (later explained) by reducing the breadth coefficient and makes necessary a larger number of inductors to obtain the same voltage.

The increase in the number of inductors causes more armature self-induction. From this point of view, it would be preferable to concentrate the winding in fewer slots that were closer together. This, however, would accentuate the distorting and demagnetizing reactions of the

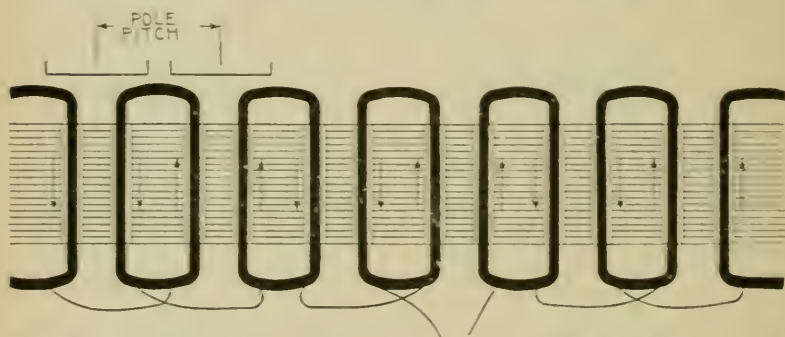


FIG. 1501.—Developed diagram of single phase concentrated whole coil winding in two slot stamping for a pole alternator. If the slots of adjacent whole coils be suitably separated by placing the winding in a slot stamping the electrical result will not differ materially from the many slot whole coil winding. But if the winding be fan-shaped, as in fig. 1502 and has coils of two poles only, it will be suitable for high voltages.

armature. Accordingly, between these two disadvantages a compromise is made, as to the extent of distributing the coils and spacing of the teeth, the proportions assigned being those which experience shows best suited to the conditions of operation for which the machine is designed.

**The Kapp Coefficient.**—A volt or unit of electric pressure is defined as the pressure induced by the cutting of 100,000,000 or  $10^8$  lines of force per second. In the operation of an alternator the maximum pressure generated may be expressed by the following equation:

$$E_{\max} = \frac{\pi f Z N}{10^8} \dots \dots \dots (1)$$

in which

$f$  = frequency;

$Z$  = number of inductors in series in any one magnetic circuit;

$N$  = magnetic flux, or total number of magnetic lines in one pole or in one magnetic circuit.

The maximum value of the pressure, as expressed in equation (1), occurs when  $\theta = 90^\circ$ .

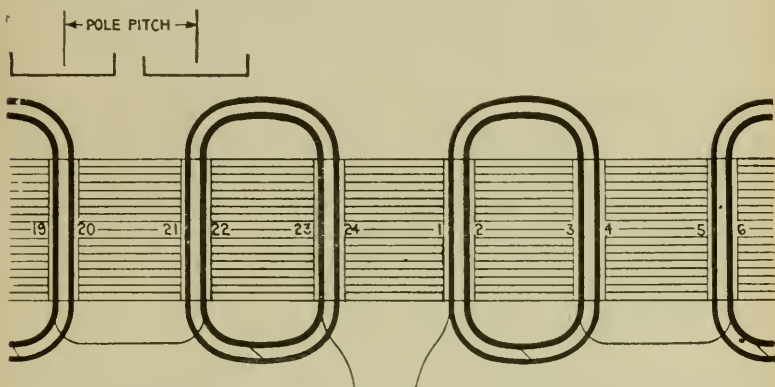


FIG. 1,502.—Developed diagram of single phase partially distributed half coil winding for six pole alternator in two slot stamping, same as in fig. 1,501. In this arrangement the direction of rotation is not reversed. It is a question as to how far the coils of a single-phase armature may be spread with advantage. There is not much advantage in reducing the interior breadth of the coils below that of the pole face, nor in widening the exterior breadth beyond that of the pole pitch.

The virtual value of the volts is equal to the maximum value divided by  $\sqrt{2}$ , or multiplied by  $\frac{1}{2} \sqrt{2}$ , hence,

$$E_{\text{virt}} = \frac{\frac{1}{2} \sqrt{2} \times \pi f Z N}{10^8} = \frac{2.22 f Z N}{10^8} \dots \dots \dots (2)$$

This is usually taken as the fundamental equation in designing alternators. It is, however, deduced on the assumptions that



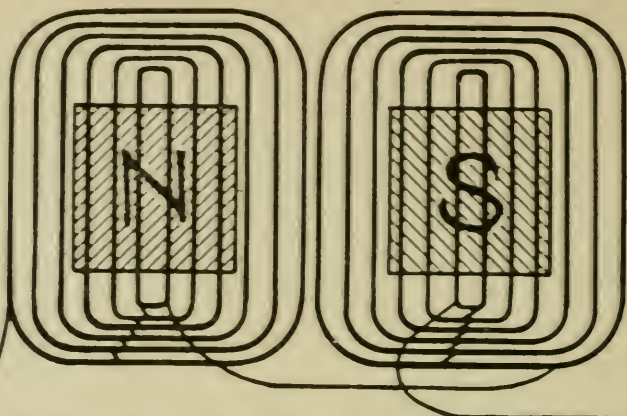


FIG. 1,503.—Developed diagram of single phase winding with fully distributed coils. As explained, excessive spreading lowers the value of the "Kapp" coefficient, and consequently the voltage; also the use of a larger number of inductors to obtain the same voltage results in an increase of armature self-induction. On the other hand, if the winding were concentrated in fewer slots and these slots were closer together, the result will be an increase in distorting and demagnetizing reactions of the armature. Therefore, a compromise between these two disadvantages must be made. The common practice is to wind in two or three slots per pole per phase.

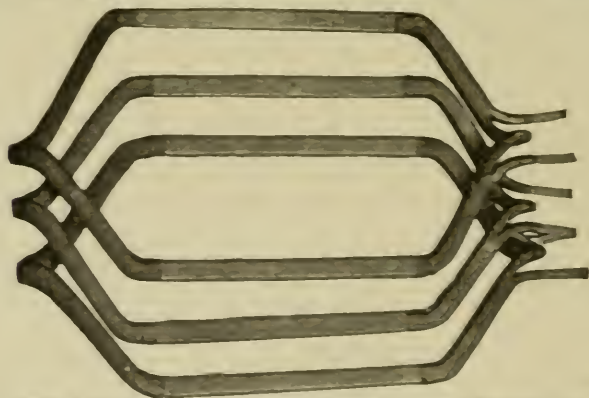


FIG. 1,504.—Allis-Chalmers lap wound coils forming a three slot distributed coil unit. In construction, after the coils have been covered with insulating materials and treated with insulating compound, the parts that lie in the slots are pressed to exact size in steam-heated moulds. This runs the insulating material into all the small spaces in the coil, excluding moisture and rendering the insulation firm and solid. The ends of the coils, where they project beyond the slots, are heavily taped.

the distribution of the magnetic flux follows a sine law, and that the whole of the loops of active inductors in the armature circuit acts simultaneously, that is to say, the winding is concentrated.

In practice, the coils are often more or less distributed, that is, they do not always subtend an exact pole pitch; moreover, the flux distribution, which depends on the shaping and breadth


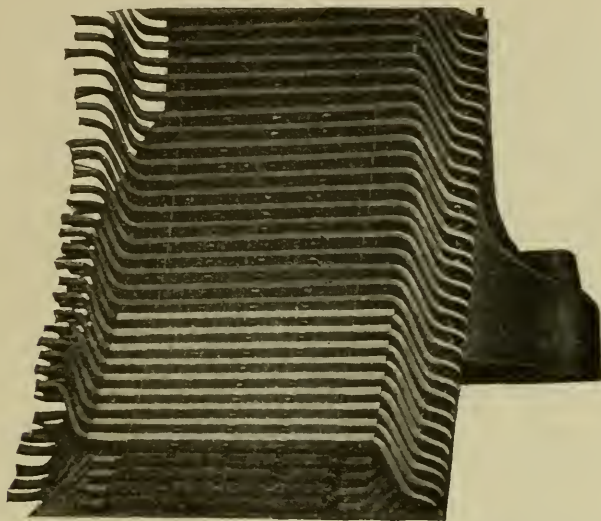


FIG. 1505.—Allis-Chalmers armature construction; view showing section of frame and two layer winding.

of the poles, is often quite different from a sine distribution. Hence, the coefficient 2.22 in equation (2) is often departed from, and in the general case equation (2) may be written
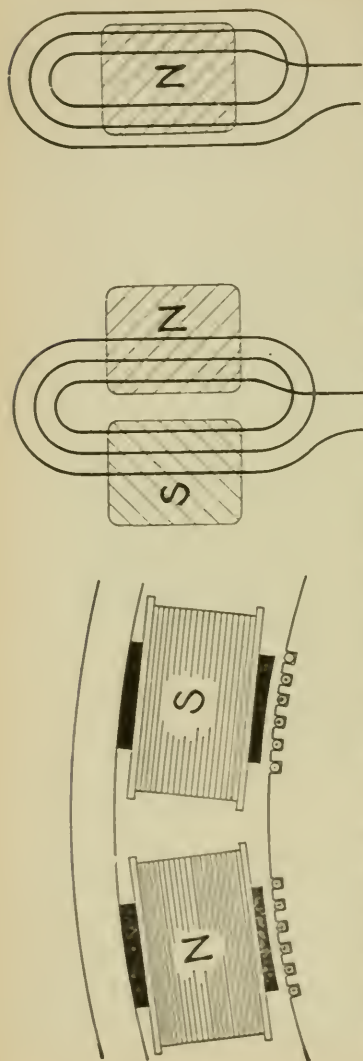
$$E_{\text{virt}} = \frac{k f Z N}{10^8} \dots \dots \dots (3)$$



FIGS. 1,506 and 1,507.—Effect of breadth of coils in distributed windings. In the section of the alternator shown in fig. 1,506 the directions of the pressures induced as the armature rotates clockwise are represented by dots for those which act towards the reader, and by crosses for those which act from the reader (the dots and crosses representing respectively the heads and tails of arrows). Since the field is not uniform but maximum at the center and gradually weakening towards the extremities, it is obvious that the maximum pressure is induced in any inductor as it passes the center of the pole, this variation being indicated by the heavier dots and crosses toward the center. Now if a number of these inductors be connected up to form a distributed coil as in fig. 1,507, the pressures induced in each will be added, but all the maximum pressure will not be induced in all at the same time, hence the total pressure induced in the distributed coil is less than it would be if the coil were concentrated as in fig. 1,506.

FIG. 1,508.—Diagram of distributed coil whose inner breadth is less than the breadth of the pole face, showing the disadvantage of such arrangement. The pressures induced in the inner windings of such a coil are opposing each other at the instant depicted, that is, while the inductors are under the pole face, such action of course being objectionable.

where  $k$  is a number which may have different values, according to the construction of the alternator. This number  $k$  is called the *Kapp coefficient* because its significance was first pointed out by Prof. Gisbert Kapp.

The value of  $k$  is further influenced by a "breadth coefficient" or "winding factor."

The effect of breadth in distributed windings is illustrated in figs. 1,506 to 1,508.

**Wire, Strap, and Bar Windings.**—In the construction of alternators, the windings may be of either wire, strap, or bar, according to which is best suited for the conditions to be met.

**Ques.** What conditions principally govern the type of inductor?

**Ans.** It depends chiefly upon the current to be carried and the space in which the inductor is to be placed.

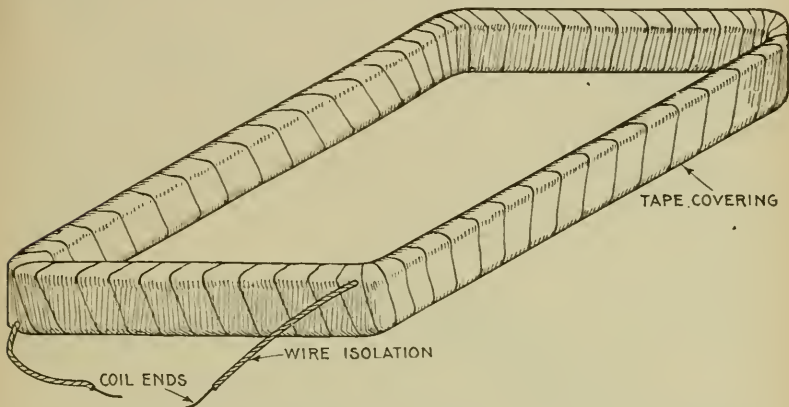


FIG. 1,509.—Simple form of alternator coil, consisting of numerous turns of insulated wire wound around a form, then covered with a tape winding, varnished and baked.

**Ques.** What kind of inductors are used on machines intended for high voltage and moderate current?

**Ans.** The winding is composed of what is called *magnet wire*, with double or triple cotton insulation.

**Ques.** Where considerable cross section is required how is a wire inductor arranged?

**Ans.** In order that the coil may be flexible several small wires in multiple are used instead of a single large wire.

**Ques.** How is the insulation arranged on inductors of this kind?

**Ans.** Bare wire is used for the wires in parallel, insulation being wrapped around them as in fig. 1,510.

This construction reduces the space occupied by the wires, and the insulation serves to hold them in place.

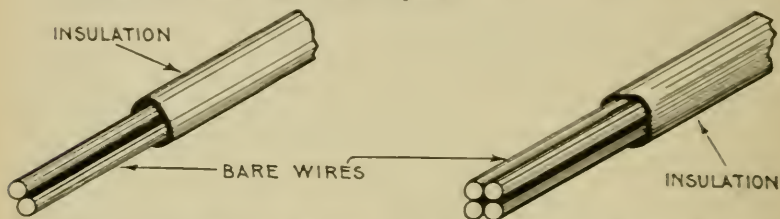


FIG. 1,510 and 1,511.—Multi-wire inductors. When the cross section of inductor necessary to carry the current is large, the use of a single wire would present difficulties in winding on account of its stiffness. Accordingly two or more smaller wires are used in parallel to secure the required cross section. Bare wire is used and the several sections encased in insulation as shown, the combination being more flexible than an equivalent single wire.


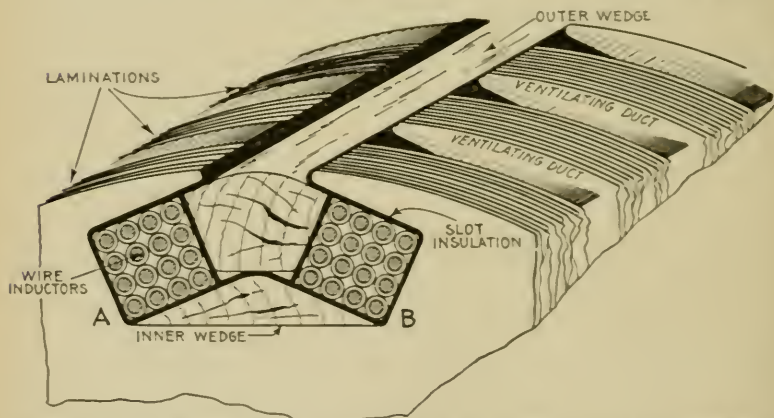


FIG. 1,512.—Two coil slot for whole coil winding. The slot has two recesses A and B for the reception of separate coils. In assembling the winding, the inner wedge is first placed in position and then the slot lined with the insulating material. This usually consists of alternate layers of mica and pressboard. The coils composed of several turns of wire or copper strip are wound in place, and after covering with a layer of insulation, the outer wedge is pushed in place to retain the inductors in position.

**Ques.** What precaution is taken in insulating a wire wound coil containing a large number of turns?

**Ans.** On account of the considerable difference of pressure between layers, it is necessary to insulate each layer of turns as well as the outside of the coil, as shown in fig. 1,513.

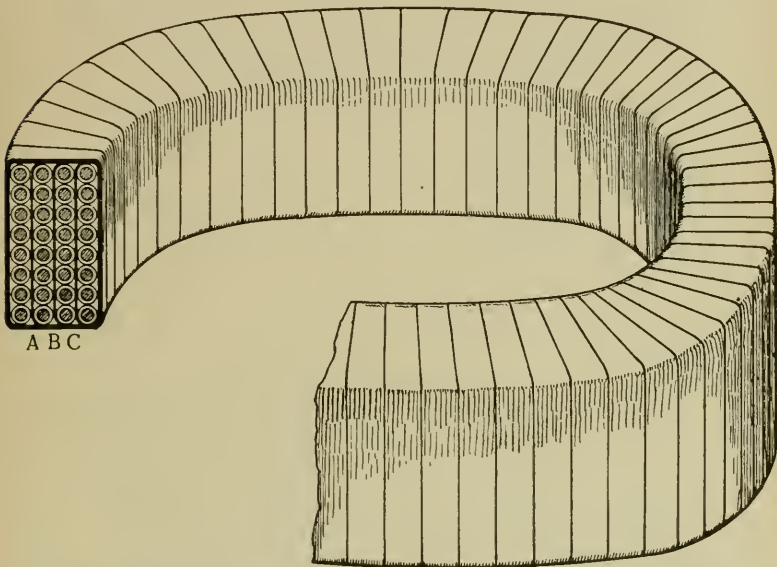

**FIG. 1,513.**—Method of winding a coil containing a large number of turns, when there is considerable difference of pressure between the layers. In such cases to guard against short circuits or breakdown of the insulation, each layer of turns is insulated from the next layer by the insulating strips A, B, C, in addition to the regular insulation around each wire. After the coil is made up it is wound with insulating tape, varnished and baked.



**Ques.** Do distributed coils require insulation between the separate layers?

**Ans.** Since they are sub-divided into several coils insulation between layers is usually not necessary.



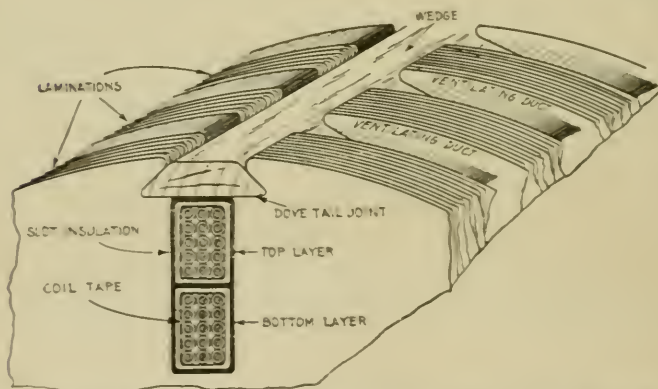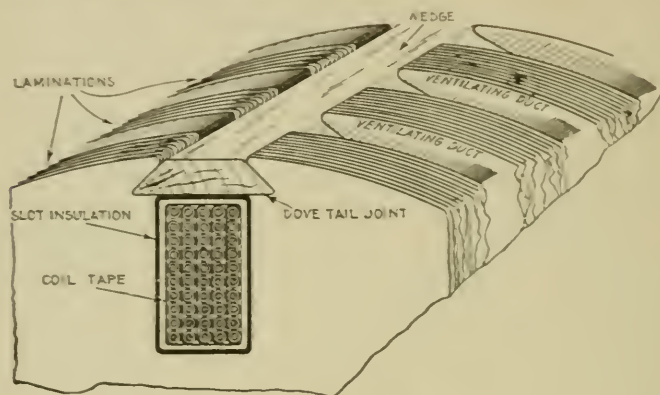**Ques. How is a coil covered?**

**Ans.** It is wound with a more or less heavy wrapping of tape depending upon the voltage.



FIGS. 1514 and 1515.—Single and double layer multi-wire inductors and methods of placing them on the core. Here the term layer means unit, in fact each unit is made up of several "layers" of wires. In fig. 1514, where so many wires are bunched together in one unit, each layer of turns is separated from those adjacent by insulating strips on account of the considerable difference of pressure between layers. This insulation is not necessary in fig. 1515 where there are two units or so called layers. In both cases the inductors are held in place by wedges driven into dovetail grooves.

Linen tape of good quality, treated with linseed oil, forms a desirable covering. Where extra high insulation is required the tape may be interleaved with sheet mica.

**Ques.** Is the insulation placed around the coils all that is necessary?

**Ans.** The slots into which the coils are placed, are also insulated.

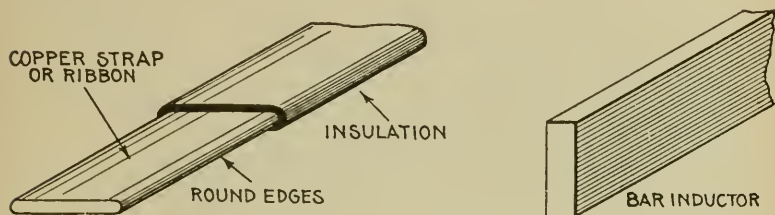


FIG. 1,516.—Copper strap or ribbon with insulation. These are generally from  $\frac{1}{4}$  to  $\frac{1}{8}$  inch thick with rounded edges as shown to avoid cutting the insulation.

FIG. 1,517.—Bar inductor. Its shape enables putting the maximum cross section of copper into the slot and is used to advantage on machines which generate large currents.

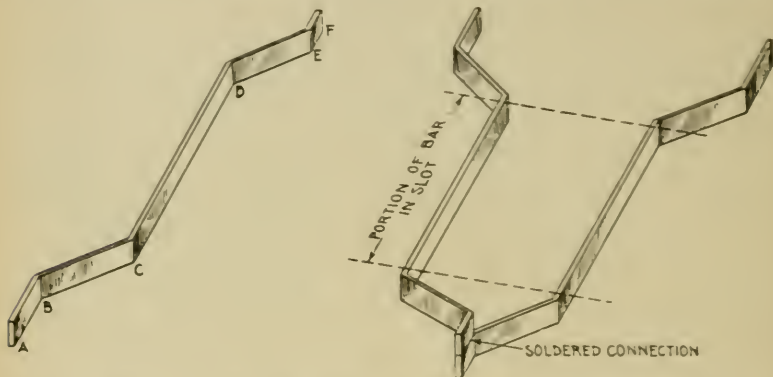


FIG. 1,518.—Style of armature core stamping used with bar wound machines. This construction, since there are no indentations in the teeth for wedges, makes it necessary to provide bands to hold the bars in place.


**Ques.** How are bar windings sometimes arranged?

**Ans.** In two layers, as in fig. 1,523.

**Single and Multi-Slot Windings.**—These classifications correspond to *concentrated* and *distributed* windings, previously described. In usual modern practice, only two-thirds of the total number of slots (assuming the spacing to be uniform)



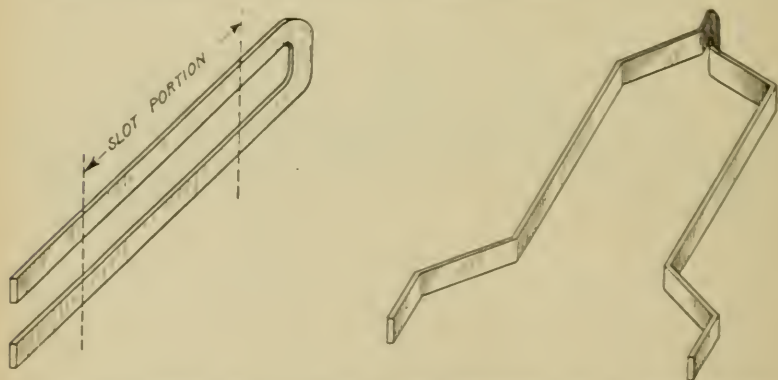FIGS. 1,519 and 1,520.—Bent bar inductor and method of connection with soldered joint. Fig. 1,519 shows one bar and shape of bent ends. The portion from C to D is placed in the slot; B to C and D to E, bent or connector sections; A to B and E to F, ends bent parallel to slot for soldering. Fig. 1,520 shows two bar inductors connected.



FIGS. 1,521 and 1,522.—Method of avoiding a soldered joint at one end of a bar inductor by using a bar of twice the length shown in fig. 1,519, and bending it into a long U form, as in fig. 1,521, after which it is spread out forming two inductors, as in fig. 1,522.

of a single phase armature are wound with coils. The reason for this may be explained by aid of fig. 1,524, which shows an armature with six slots per pole, four of which are wound. Owing to the different positions of, say, coils A and B, there will be a difference in phase between the pressure generated in them and consequently the resultant pressure of the two coils joined in series will be less than the sum of the pressure in each coil.

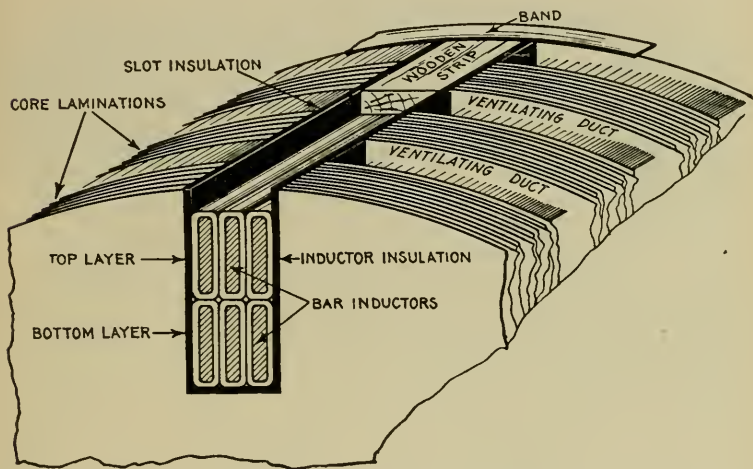


Fig. 1,523.—Arrangement in slot of two layer bar winding. With bar inductors, as must be evident from the illustration, the maximum cross section of copper can be placed in a slot of given dimension, hence a bar winding is used to advantage for alternators designed to carry a large current. Bar inductors, on account of the shape of their ends, must be placed in the slots from the top, because the bent ends do not admit of pushing them in. Straight slots are therefore necessary, the inductors being held in place by wooden strips and tie bands as shown.

Fig. 1,525 shows the pressure plotted out as vector quantities, and the table which follows gives the relative effectiveness of windings with various numbers of slot wound in series.

The figures in the last column of the table show that a large increase in the weight of active material is required if the

inductors in a single phase machine are to be distributed over more than two-thirds the pole pitch. Again, if much less than two-thirds of the surface be wound, it is more difficult to provide a sine wave of pressure.

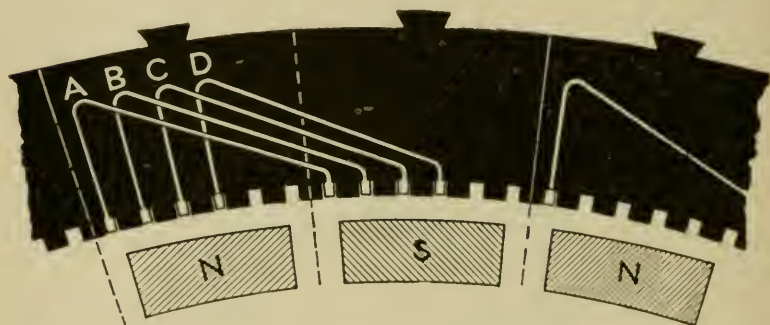


FIG. 1,524.—Diagram of single phase multi-coil or distributed winding to show characteristic differences in action and construction from single coil or concentrated winding.

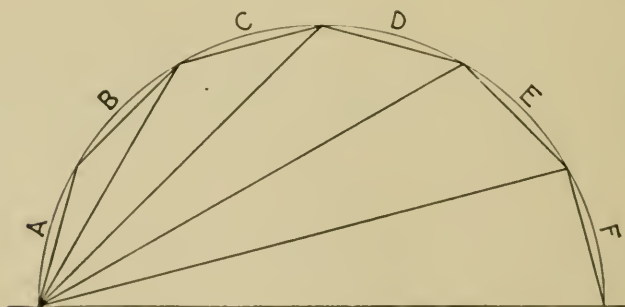


FIG. 1,525.—Vector diagram of pressures induced in the single phase multi-coil or distributed winding shown in diagram in fig. 1,524.

TABLE OF RELATIVE EFFECTIVENESS OF WINDINGS

Slots wound in series	Pressure across coils	Winding coefficient	Quantity of copper to produce same pressure
1	1	1	1
2	1.93	.97	1.03
3	2.73	.91	1.10
4	3.34	.84	1.19
5	3.72	.74	1.35
6	3.86	.64	1.56

**Ques.** What other advantage besides obtaining a sine wave is secured by distributing a coil?

**Ans.** There is less heating because of the better ventilation.

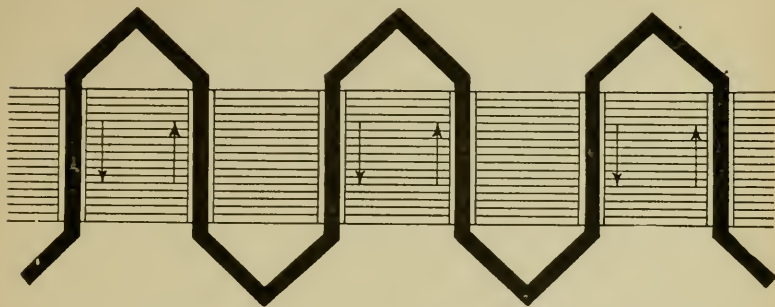


FIG. 1,526.—Developed diagram of a single phase monotooth or one slot bar winding; it is suitable only for operation at low voltage.

**Single Phase Windings.**—There are various kinds of single phase winding, such as, concentrated, distributed, hemitropic, etc. Fig. 1,527 shows the simple type of single phase winding. It is a “one slot” winding, that is, concentrated coils are used.

The armature has the same number of teeth as there are poles, the concentrated coils being arranged as shown. In designing



such a winding, the machine, for example, may be required to generate, say, 3,000 volts, frequency 45, revolutions 900 per minute.

These conditions require 720 inductors in series in the armature circuit, and as the armature is divided into six slots corresponding to the six poles, there will be 120 inductors per slot, and the coil surrounding

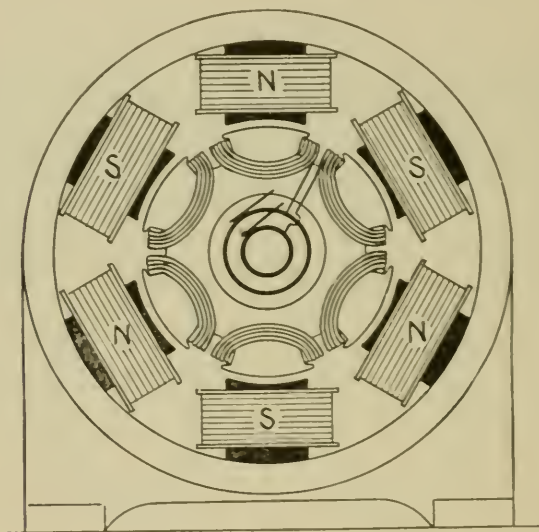


FIG. 1,527.—Diagram of six pole single phase revolving armature alternator, with monotooth or concentrated whole coil winding. For 3,000 volts at 900 revolutions per minute, 120 inductors are required. And in the case of a concentrated or monotooth winding they may be arranged in "whole coils" as above or in "half coils" (hemitropic as in fig. 1,528).

each of the six teeth on the surface of the armature will consist of 60 turns. The connections must be such as to give alternate clockwise and counter-clockwise winding proceeding around the armature.

**Ques.** In what other way could the inductors be arranged in concentrated coils?

Ans. They could be grouped in three coils of 120 turns each, as shown in fig. 1.528.

When thus grouped the arrangement is called a hemitropic winding, as previously explained.

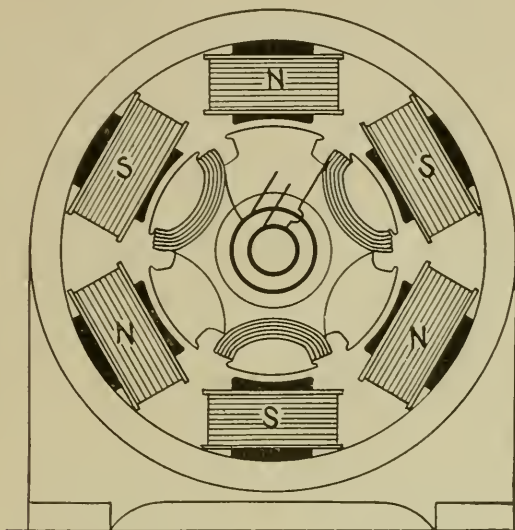


FIG. 1.528.—Diagram of six pole single phase alternator with concentrated half coil or hemitropic winding of same capacity as in fig. 1.527. There are an equal number of inductors, but in this case arranged in three instead of six coils. In this winding the direction of winding is alternately reversed so that the induced pressures do not oppose one another.

**Ques.** What is the advantage, if any, of a half coil winding?

Ans. In single phase machines a half coil winding is equivalent, electrically, to a monotooth winding, and, therefore, is not of any particular advantage; but in three phase machines, it has a decided advantage, as in such, a concentrated winding yields a higher pressure than a distributed winding.

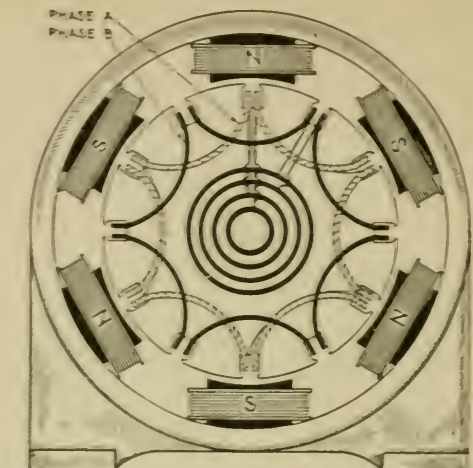


FIG. 1.529 — Two phase commutator whole coil winding. In this style winding the total number of slots is twice the number of poles, or two slot per pole per phase. It comprises two windings identical with fig. 1.527, being spaced 90 polar degrees as shown. The two circuits are independent, the windings terminating at the four collector rings.


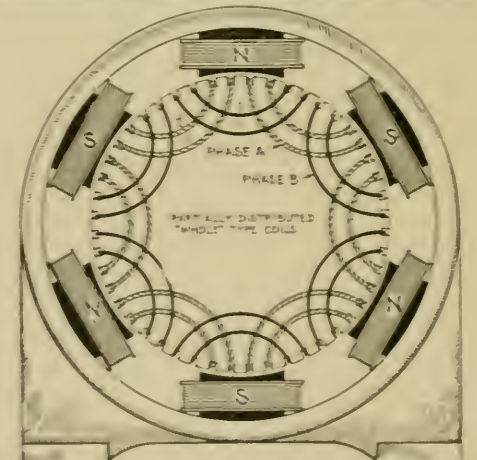


FIG. 1.530 — Two phase winding in two slots per pole per phase. The winding distributes the coils of each phase into two sections, as A and B. The coils are of the "whole" type and with six poles the total number of slots is  $4 \times 6 = 24$ , uniformly spaced as shown.

**Two Phase Armature Windings.**—This type of winding can be made from any single phase winding by providing another set of slots displaced along the surface of the armature to the extent of one-half the pole pitch, placing therein a duplicate winding.

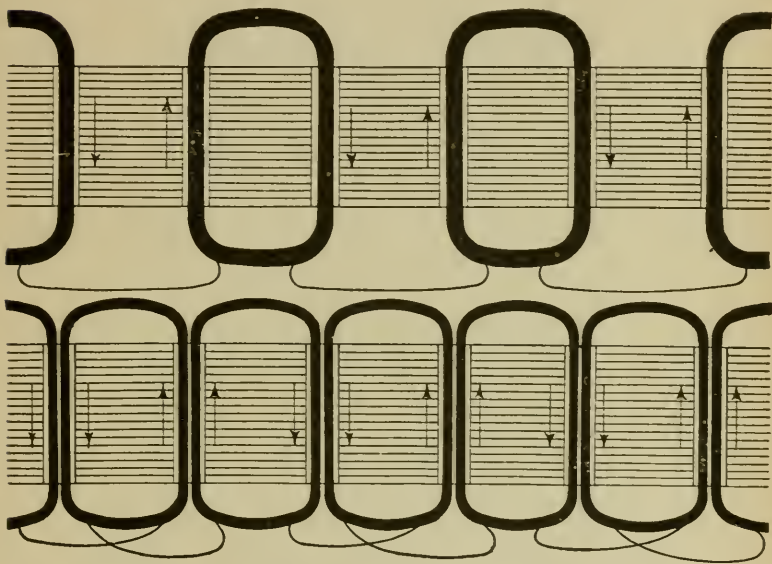For instance: If the six pole monotooth, single phase winding, shown in fig. 1,527, be thus duplicated, the result will be the one slot two-phase



FIGS. 1,531 and 1,532.—Developed diagram of the single phase monotooth windings shown in figs. 1,527 and 1,528.

winding shown in fig. 1,529, which will have twelve slots, and will require four slip rings, or two rings for each phase.

By connecting up the two windings in series, the machines could be used as a single phase, with an increase of voltage in the ratio of 1.41 to 1.

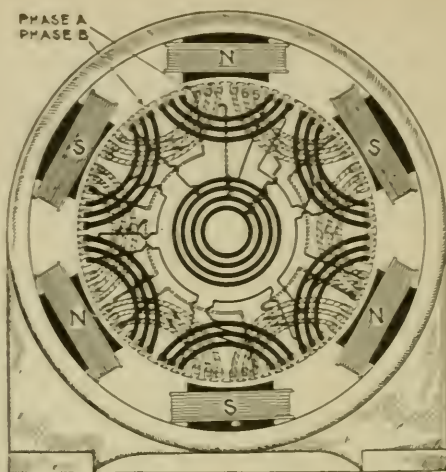


FIG. 1.533.—Two phase winding in three slots per pole per phase. The coils of each phase are of the partially distributed type, each coil being made up of three sections as shown. The direction of winding is alternately reversed.

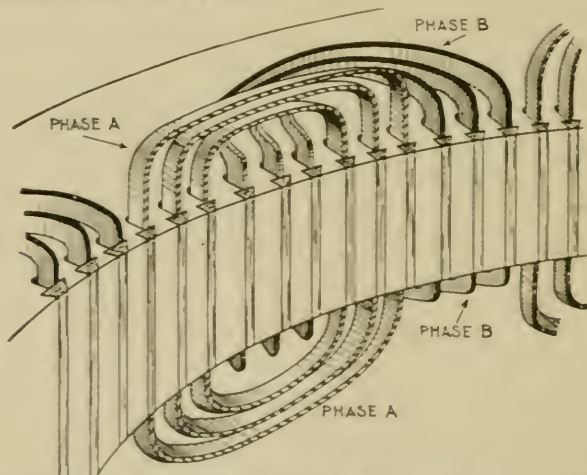


FIG. 1.534.—Section of two phase winding showing shaping of the coil ends. Every other coil is flat, while the alternates have their ends bent down as shown. With respect to the shaping of the coil ends, it is called a *two range winding*.

**Ques.** How must the coils be constructed for two phase windings?

**Ans.** They must be made of two different shapes, one bent up out of the way of the other, as in fig. 1,534.

There are numerous kinds of two phase windings; the coils may be concentrated or distributed, half coil or whole coil, etc. Fig. 1,530 shows a two phase winding with four slots per pole, and fig. 1,533 one with six slots per pole.

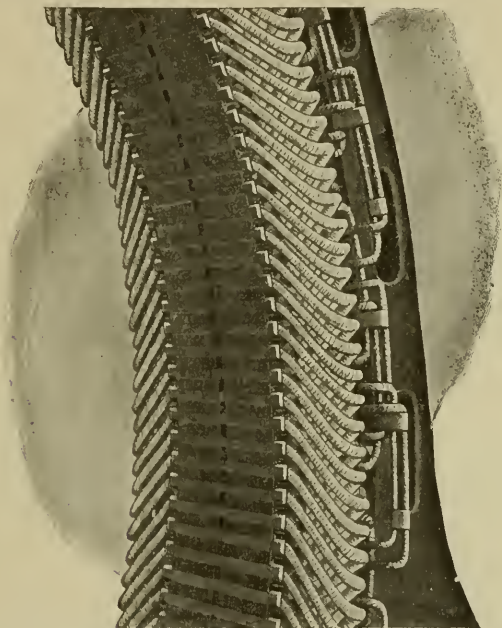


FIG. 1,535.—Section of Triumph armature showing method of arranging the three phase winding.

**Three Phase Armature Windings.**—On the same general principle applicable to two phase windings, a three phase winding can be made from any single phase winding, by placing three identical single phase windings spaced out successively along the



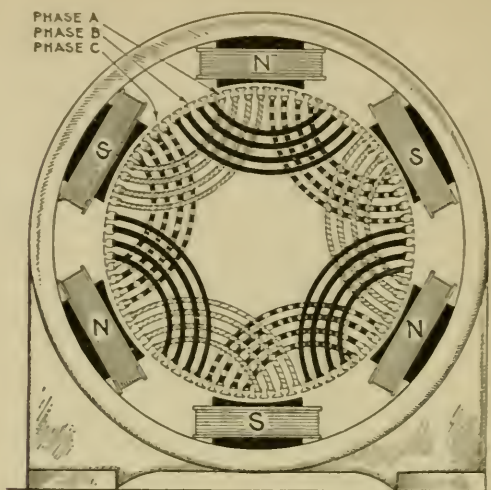


FIG. 1.536.—Three phase winding with distributed coils—wound in four slots per pole per phase; diagram showing placement of the coils.

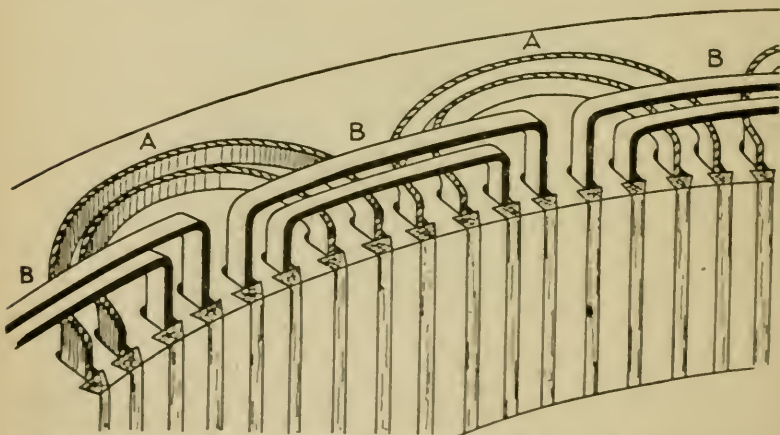


FIG. 1.537.—Treatment of coil ends in two phase, two range windings. In this arrangement *straight out* (B) and *bent up* (A) coils are used which are placed on the armature as is clearly shown in the illustration.

surface of the armature at intervals *equal to one-third and two-thirds, respectively, of the double pole pitch*, the unit in terms of which the spacing is expressed, being that pitch, which corresponds to one whole period.

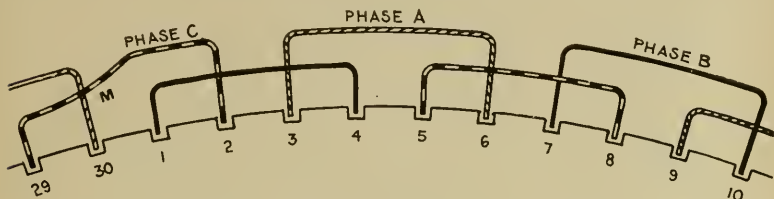


FIG. 1,538.—Three phase, 10 pole, 30 slot winding in two ranges. In this winding perfect symmetry occurs after every four poles. Accordingly in the case of an odd number of pairs of pole, one of the coils must necessarily be askew going from the inner to the outer range as at M.

Each of the three individual windings must be concentrated into narrow belts so as to leave sufficient space for the other windings between them. This limits the breadth or space occupied by the winding of any one phase to one-third of the pole pitch.

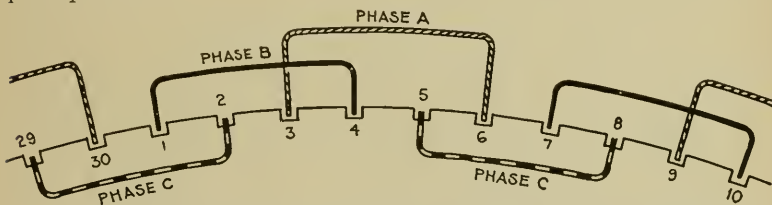



FIG. 1,539.—Three phase 10 pole 30 slot winding in three ranges. The coils of each phase are alike, those of the A phase being all in the straight out range, those in the B phase, in a bent up range, and those in the C phase in a bent down range. This arrangement has the disadvantage, that by reason of the third range, the field magnet cannot be withdrawn. This treatment of the coil ends is more clearly shown in fig. 1,540.

**Ques.** How are three phase coil ends treated?

**Ans.** They may be arranged in two ranges, as in fig. 1,538, or in three ranges, as in fig. 1,539.

**Ques.** What kind of coil must be used for three phase windings in order that the ends may be arranged in only two ranges?

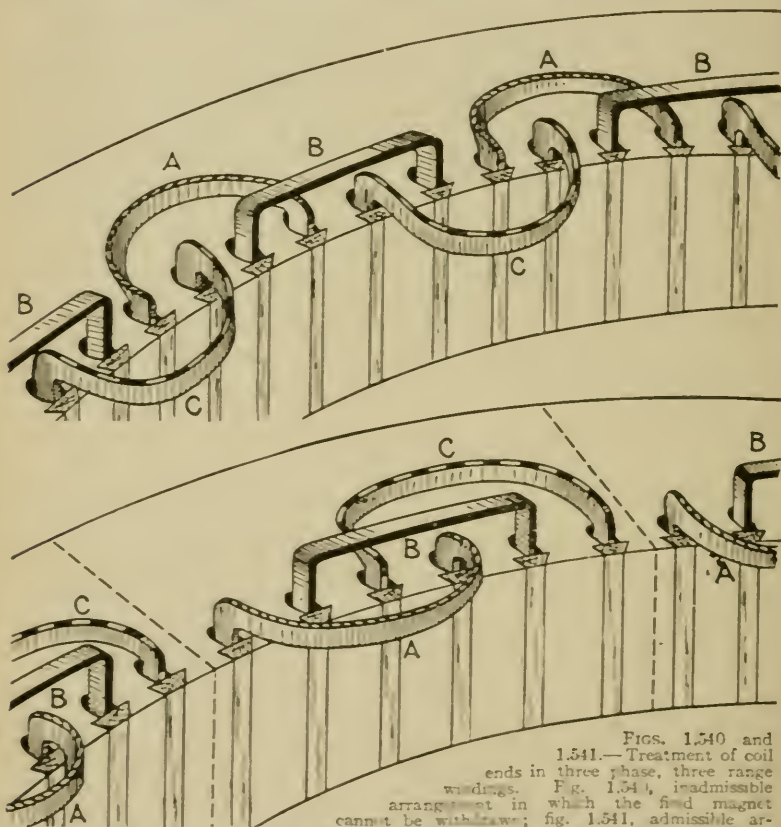**Ans.** Hemitropic or half coils; that is, the number of coil per phase must be equal to one-half the number of pole.



FIGS. 1540 and 1541.—Treatment of coil ends in three phase, three range windings. Fig. 1540, inadmissible arrangement in which the field magnet cannot be withdrawn; fig. 1541, admissible arrangement in which the armature segments can be divided. This enables the top half of armature to be removed by disconnection without unwinding any coil.

**Grouping of Phases.**—In the preceding diagrams, the general arrangement of the coils on the armature surface are shown for the numerous classes of winding. In polyphase alternators the separate windings of the various phases may be grouped in two ways:

1. Star connection;
2. Mesh connection.

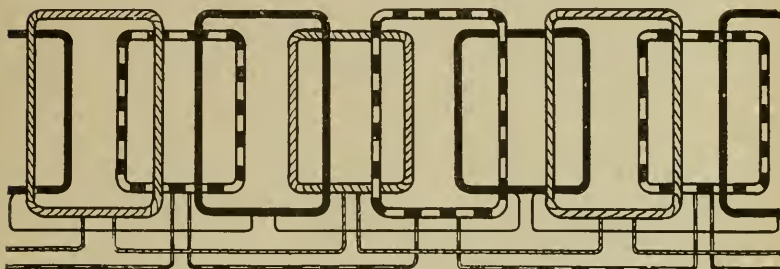


FIG. 1,542.—Three phase winding with half coils. The advantage of employing half coils is that the ends may be arranged in two ranges as shown. There is one slot per phase per pole, that is, total number of slots =  $3 \times$  number of poles.

**Ques.** Describe the two phase star connection.

**Ans.** In this method of grouping, the middle points of each of the two phases are united to a common junction M, and the

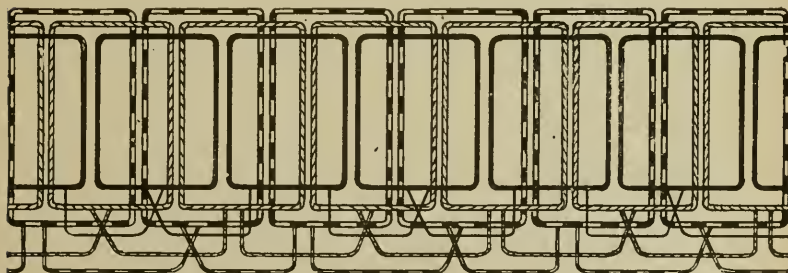


FIG. 1,543.—Three phase winding with whole coils. Two sides of adjacent coils come in one slot. Number of coils per phase = number of poles per phase. Total number of slots = 3 multiplied by number of poles per phase. Whole coils require the ends arranged in three ranges as indicated. The coils are concentrated.

four ends are brought out to four terminals  $a, a', b, b'$ , as shown in fig. 1,544, or in the case of revolving armatures, to four slip rings.

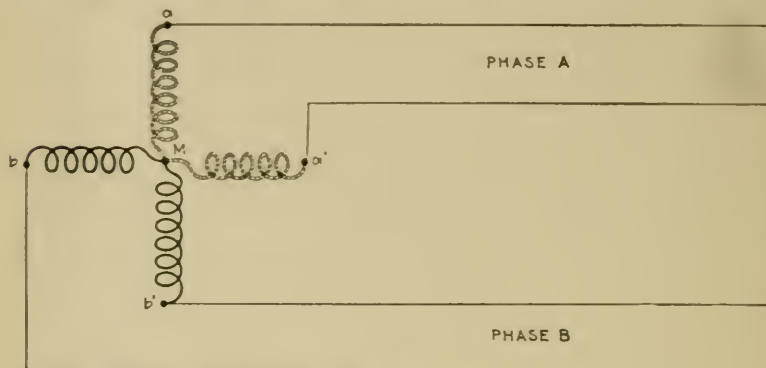


FIG. 1,544.—Diagram of two phase star grouping.

**Ques.** What does this arrangement give?

**Ans.** It is practically equivalent to a four phase system.

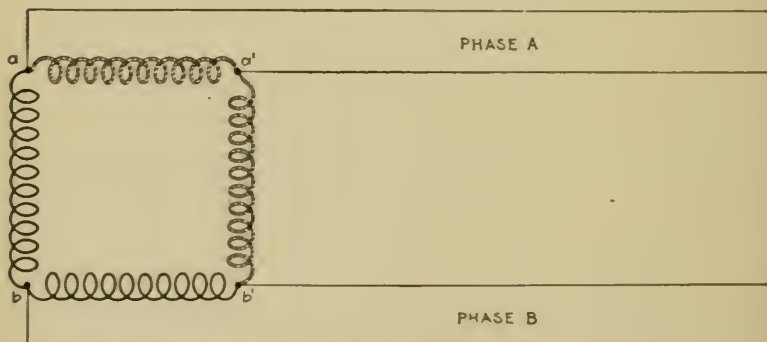


FIG. 1,545.—Diagram of two phase mesh grouping.

**Ques.** How is the two phase mesh connection arranged?

**Ans.** In this style of grouping, the two phases are divided

into two parts, and the four parts are connected up in cyclic order, the end of one to the beginning of the next, so as to form a square, the four corners of which are connected to the four terminals  $a, b, a', b'$ , as shown in fig. 1,545, or in the case of revolving armatures, to four slip rings.

**Ques. Describe a three phase star connection?**

**Ans.** In three phase star grouping, one end of each of the three circuits is brought to a common junction M, usually

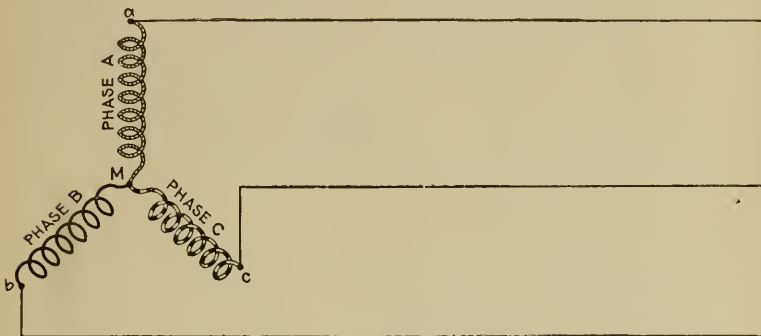


FIG. 1,546.—Diagram of three phase star grouping, commonly called Y grouping owing to its resemblance of the letter Y. The current in each main is obviously equal to the current in each phase winding, but the terminal pressure is the vector sum of the pressures in the component phase windings, that is,  $\sqrt{3}$  multiplied by the pressure in one phase.

insulated, and the three other ends are connected to three terminals  $a, b, c$ , as shown in fig. 1,546, or in the case of revolving armatures to three slip rings.

**Ques. What other name is given to this connection, and why?**

**Ans.** It is commonly called a **Y** connection or grouping owing to the resemblance of its diagrammatic representation to the letter Y.



FIG. 1547.—Radial diagram of three phase, one slot winding with Y connection.

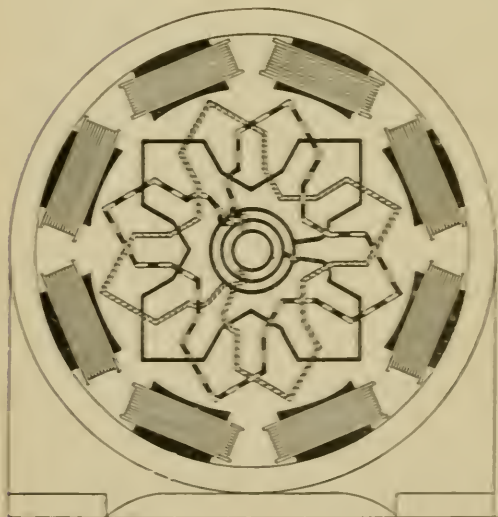
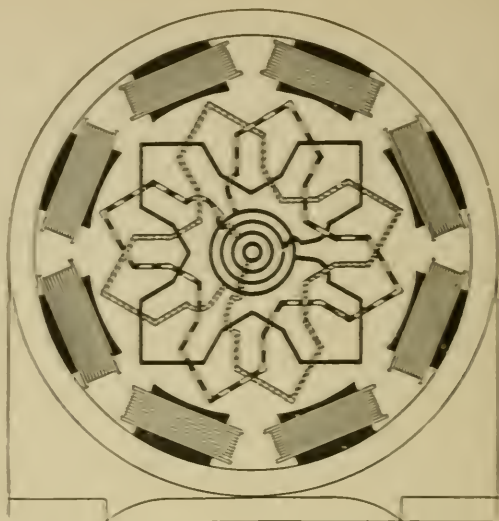


FIG. 1548.—Radial diagram of three phase one slot winding with delta connection.

**Ques.** How is a three phase mesh connection arranged?

**Ans.** The three circuits are connected up together in the form of a triangle, the three corners are connected to the three terminals, *a*, *b*, *c*, as shown in fig. 1,549, or in the case of revolving armatures to three slip rings.

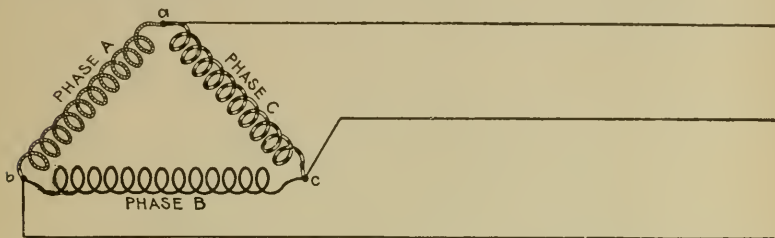


FIG. 1,549.—Diagram of three phase mesh grouping, commonly called delta grouping owing to its resemblance to the Greek letter  $\Delta$ . The voltage at the terminals is equal to the voltage in one phase, and the current in each line is equal to the vector sum of the currents in two phases, that is, it is equal to  $\sqrt{3}$  multiplied by the current in one phase.

**Ques.** What other name is given to this style of connection, and why?

**Ans.** It is commonly called a *delta* grouping on account of the resemblance of its diagrammatic representation to the Greek letter  $\Delta$ .

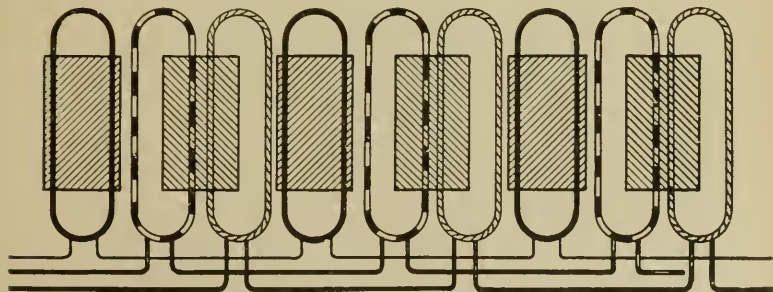


FIG. 1,550.—Three phase winding with short coils. The use of short coils as here shown, in which the coil breadth =  $\frac{2}{3}$  pole pitch, avoids the necessity of overlapping.

In polyphase working, it is evident that by the use of four equal independent windings on the armature, connected to eight terminals or slip rings, a two phase alternator can be built to supply currents of equal voltage to four independent circuits. Likewise, by the use of three equal independent windings, connected to six terminals or slip rings, a three phase alternator can be made to supply three independent circuits.

This is not the usual method employed in either case, however, as the star grouping or mesh grouping methods of connection not only

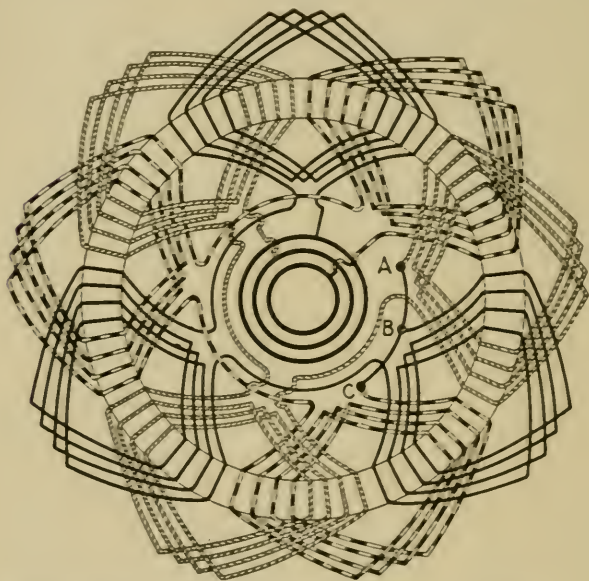


FIG. 1,551.—Radial diagram of three phase *lap* winding with star connection.

gives the same results, but also, in star grouping, a greater plurality of voltages for the same machine, and a higher voltage between its main terminals.

Radial diagrams of the arrangement and connections of Y grouping of lap windings and wave windings for three phase alternators are shown by figs. 1,551 and 1,552.

**Ques.** In three phase star grouping, what is the point where the phases join, called?

**Ans.** The star point.

**Ques.** In a three phase star connected alternator what is the voltage between any two collector rings?

**Ans.** *It is equal to the voltage generated per phase multiplied by  $\sqrt{3}$  or 1.732.*


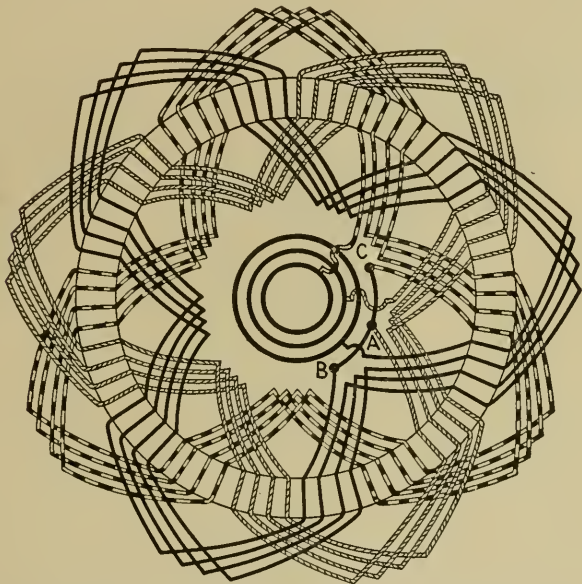


FIG. 1,552.—Radial diagram of three phase wave winding with star connection.

**Ques.** In a three phase star connected alternator what is the value of the current in each line?

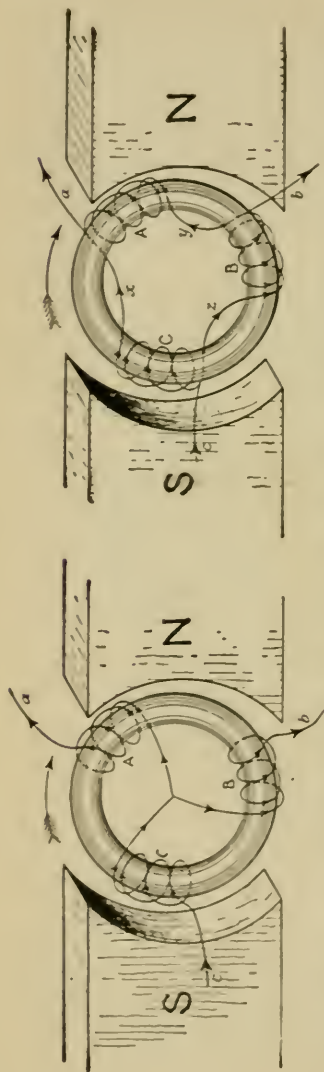**Ans.** The same as the current in each phase winding.



FIGS. 1,553 and 1,554.—Gramme ring armatures showing three phase star and mesh connections, respectively, with direction of currents in the coils. In the figures, the coils A, B, C, are spaced at equidistant positions on the ring core. The arrow heads represent the directions of the induced pressures or currents for the position shown, the rotation being clockwise. In coil A the pressure is increasing, but is in the same direction as in A, whereas in coil C it is also diminishing, but is in the opposite direction to what it is in coils A and B. As the rings rotate the three coils have similar alternations of pressure induced in them, but differ in phase. If *a*, *b* and *c* be joined to collector rings three phase currents can be supplied to the outer circuits. In fig. 1,553 at the instant represented *a* and *b* are giving their current to their lines, while *c* is receiving from its line a current equal to the sum of *a* and *b*. In fig. 1,554, at the instant represented, the currents sent out from *a* will be equal to the sum of the currents in *x* and *y*, and intermediate between them in phase. The current from *b* will be equal to the difference of the currents in *x* and *y*, and of intermediate phase, while similarly the current received by *c* will be equal to the sum of the currents in *x* and *y*.

**Ques.** What is the value of the total output in watts of a star connected alternator?

**Ans.** It is equal to the sum of the outputs of each of the three phases. When working on a non-inductive load, the total output of a star connected alternator is equal to  $\sqrt{3}$  multiplied by the product of the line current and line voltage.

**Ques.** What is the value of the line voltage in a three phase delta connected alternator?

**Ans.** It is equal to the voltage generated in each phase.




**Ques.** What is the value of the line current in a three phase delta connected alternator?

**Ans.** It is equal to the current in each phase multiplied by  $\sqrt{3}$ .

**Ques.** What is the total output of a three phase delta connected alternator working on a non-inductive load?

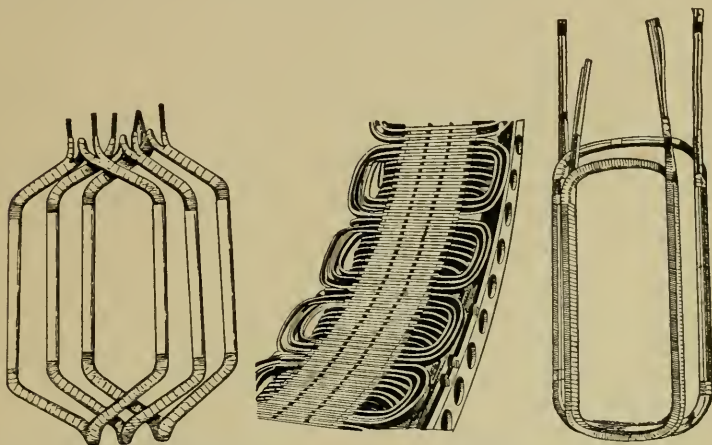**Ans.** The total watts is equal to  $\sqrt{3}$  multiplied by the product of the line current and the line voltage.



**FIGS. 1,555 to 1,557.**—Separate coils, and section of Allis-Chalmers alternator with coils in place. Numerous openings are provided in the frame through which air currents, set up by the revolving field, can pass freely and carry off heat. Shields are provided to protect the armature coils where they project beyond the core. In assembling the core spacing segments are placed at intervals to form ventilating ducts. After the coils have been covered with insulating materials and treated with insulating compound, the parts that are to lie in the slots are pressed to exact size in steam heated moulds. This runs the insulating material into all the small spaces in the coil so as to exclude moisture, it also makes the coil structure firm and solid. The projecting ends of the coils are heavily taped, suitable supports being provided for the coil connections so that they cannot become displaced on account of stresses due to short circuits or other causes. On high pressure machines the armature terminals are arranged so that it is impossible for an attendant to make accidental contact with them.

**Ques.** What are the features of the star connection?

**Ans.** It gives a higher line voltage than the delta connection for the same pressure generated per phase, hence it is suited for machines of high voltage and moderate current.



The delta connection gives a lower line voltage than the star connection for the pressure generated per phase, and cuts down the current in the inductors; since the inductors, on this account, may be reduced in size, the delta connection is adapted to machines of large current output.


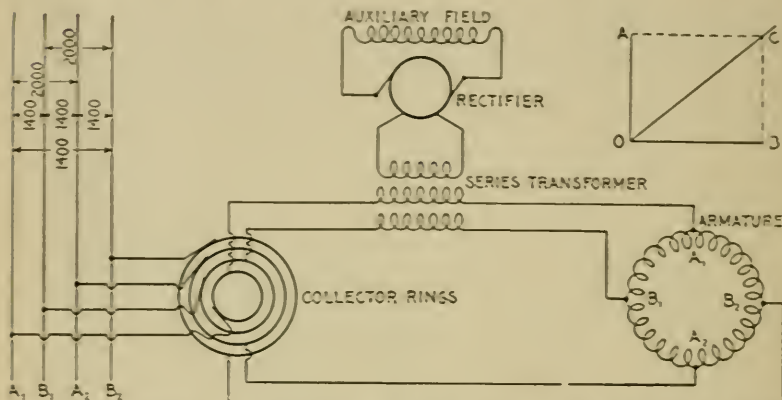


FIG. 1.558.—Diagram of Westinghouse two phase composite wound alternator, showing connections between two phase armature and a single phase rectified and composite field winding. The arrangement makes use of a series transformer, mounted on the spokes of the armature. By means of this series transformer the voltage delivered to the rectifying commutator and the fields is much less than that generated by the machine. The armature of this machine is of the closed coil single winding type, all the armature inductors being connected with each other to form a closed circuit which resembles to a certain extent the ordinary drum winding of a multi-polar direct current machine. This winding is tapped out at two points per pole just as is the continuous winding of a two phase rotary converter, these taps running to collector rings through which the currents are delivered to the outside circuits. On account of this connection of both phases to one winding, there is a definite voltage set up between the inductors of phase A, and of phase B, this voltage being shown by the figures given in the diagram. The arrangement is adapted for two phase work by fitting the series transformer for the auxiliary field excitation with two primaries connected respectively in one leg of each of the two phases; thus the transformer is excited by two currents normally  $\frac{1}{2}$  period out of phase with each other. The result upon the secondary is a combination of the effects of the two primary currents, the voltage delivered by the secondary being intermediate in phase between those pressures which would be separately set up by the two primaries. This combination effect is shown in the small diagram in the upper right hand corner of the illustration. If OA be the effect set up in the secondary of the series transformer by the primary current of phase A, and OB be the effect set up by the primary current of phase B, OC represents in magnitude and phase relation the resultant effect upon the secondary. It is readily seen that this resultant is not equal to the arithmetical sum of the two components since, to a certain extent, they work at cross purposes. However, if either one of them increase the resultant effect increases, although not in exact proportion. If the load remain balanced, the two components remaining equal to each other, the resultant OC varies in exact proportion to any changes in the components. If the load become unbalanced, the resultant swings around more nearly into phase with the larger load; thus if OB become greater, OA remaining the same, OC swings around, becoming more nearly horizontal. This requires a readjustment of the position of the brushes on the commutator to set them properly for minimum sparking, an adjustment exactly similar to that required when the power factor of the load changes.

**Ques.** How is the path and value of currents in a delta connected armature determined?

**Ans.** Starting with the inductors of one phase opposite the middle of the poles, assume the maximum current to be induced

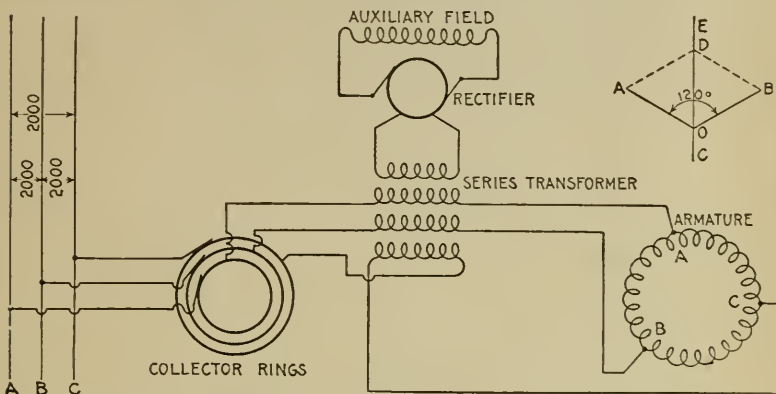

**FIG. 1,559.**—Diagram of Westinghouse three phase composite wound alternator. The armature inductors are of the closed coil or delta connected type, but are tapped at three points per pair or poles to the three collector rings. All three connections between the armature coils and the collector rings run through primary circuits of the series transformer within the armature, these three primaries each giving their own effect upon the secondary. Since the resultant of three equal alternating electromotive forces  $120^\circ$  apart is zero, so that some special arrangement must be adopted to make these electromotive forces act with instead of against each other. The arrangement is a reversal of the connections of one of the primaries of the series transformer. This is shown in the case of the lowest primary indicated in the diagram. The combination of the effects of the three primaries is again indicated in the small vector diagram in the upper right hand corner. Here OA is the effect of one primary, OB that of another  $\frac{1}{2}$  of a period displaced from the former in phase, and OC that which the third would exert were it not reversed, but the reversal brings the effect of this third coil into the phase relation OD, so that the three are only  $60^\circ$  apart. The combination of OA and OB is equal to OC, which combined again with OD gives a resultant effect, OE. In this case, as in the other, the effect upon the series field does not remain exactly proportional to the load unless the latter is balanced; in fact, an increased current through the one leg represented by OD, affects the series field as much as an equal increase in each of the other legs put together. Practically, however, any increase of the load—distributed as it must be in two legs at least—increases the field excitation so that proper regulation is secured.

**NOTE.**—In the star connected armature the proper ends to connect to the common terminal or star point are determined as follows: Assume that the inductor opposite the middle of a pole is carrying the maximum current, and mark its direction by an arrow. Then the current in the inductors on either side of and adjacent to it will be in the same direction. As the maximum current must be coming from the common terminal, the end toward which the arrow points must be connected to one of the rings, while the other end is connected to the common terminal. The current in the two adjacent inductors evidently must be flowing into the common terminal, hence the ends toward which the arrows point must be connected to the common terminal, while their other ends are connected to the remaining two rings.

at this moment; then but one-half of the same value of current will be induced at the same moment in the other two phases, and its path and value will best be shown by aid of fig. 1,560, in which X may be taken as the middle collector ring, and the maximum current to be flowing from X toward Z. It will be seen that no current is coming in through the line Y, but part of the current at Z will have been induced in the branches *b* and *c*.

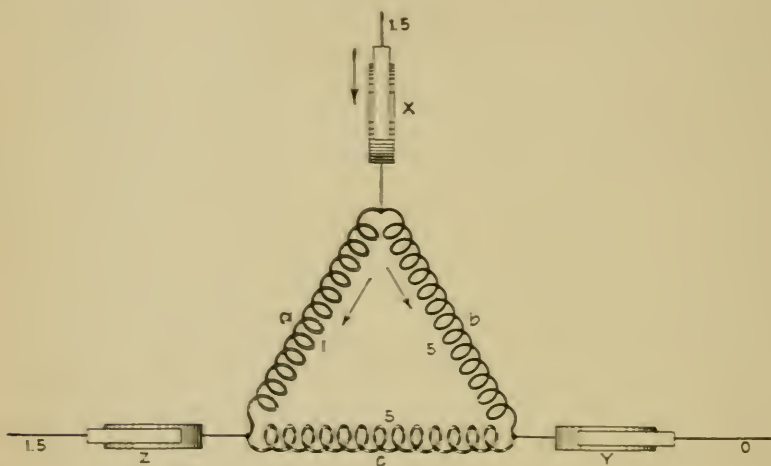


FIG. 1,560.—Diagram showing determination of path and value of current flowing in delta connected armature.

**Ques.** Since most three phase windings can be connected either Y or delta, what should be noted as to the effects produced?

**Ans.** With the same winding, the delta connection will stand 1.732 as much current as the Y connection, but will give only  $1 \div 1.732$  or .577 as much voltage.

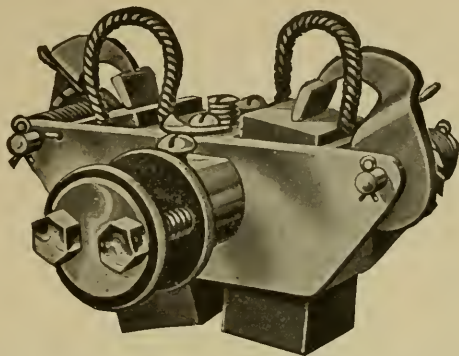


FIG. 1,561.—Triumph brushes and brush holder. The holder is of the box type provided with an adjustable tension spring, making the brushes self-feeding. Each holder is carried on insulated studs attached to a cast iron yoke which is mounted on the bearing.

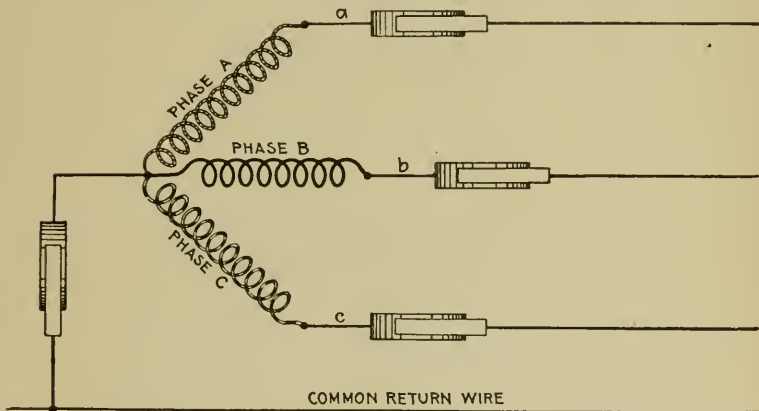


FIG. 1,562.—Diagram of Y connection with a common return wire. When the three lines leading from *a*, *b* and *c* are equal in resistance and reactance, or in other words when the system is *balanced*, the currents of the three phases are equal and are  $120^\circ$  apart in phase (each current lagging behind its pressure by the same amount as the others) and their sum is at each instant equal to zero. In this case the resultant current being equal to zero there is no need of a common return wire. However, in some cases, where power is distributed from transformers or three wire systems, the different branches are liable to become unbalanced. Under such circumstances the common return wire is sometimes used, being made large enough to take care of the maximum unbalancing that may occur in operation. The return wire is used sometimes on alternators that furnish current mostly for lighting work.

**Chain or Basket Winding.**—One disadvantage in ordinary two-range windings is that two or three separate shapes of coil are required. The cost of making, winding, and supplying spares would be less if one shape of coil could be made to do for

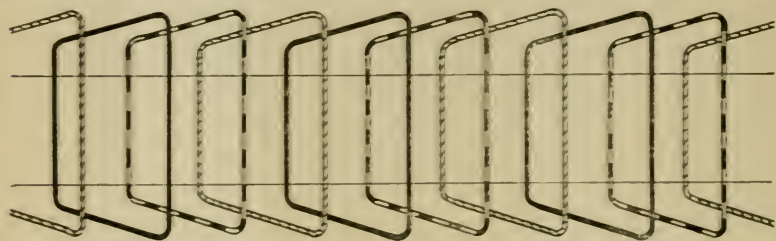


FIG. 1563.—Diagram showing chain winding. In this method of winding the coils are all similar with long and short sides. It obviates the extra cost of making coils of several different shapes. The diagram represents a winding for one slot per pole per phase.

all phases. One way of accomplishing this is by the method of chain winding, in which the two sides of each coil are made of different lengths, as shown in fig. 1563, and bent so that they can lie behind one another.

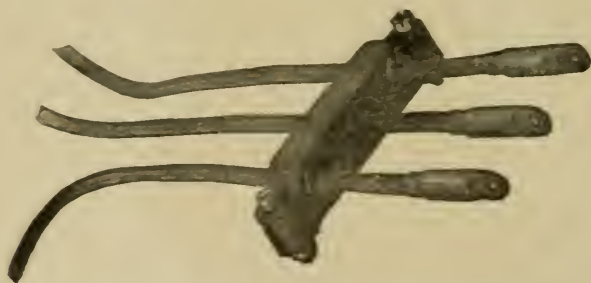


FIG. 1564.—Electric terminal block showing cables leading to three phase winding.

In the case of open slots the coils may be former wound and afterwards wedged into their places.

In chain winding the adjacent coils link one another as in a chain (hence, the name); the winding is similar to a skew coil



winding. This plan of winding is supposed to have some advantage in keeping coils of different phases further separated than the two range plan.


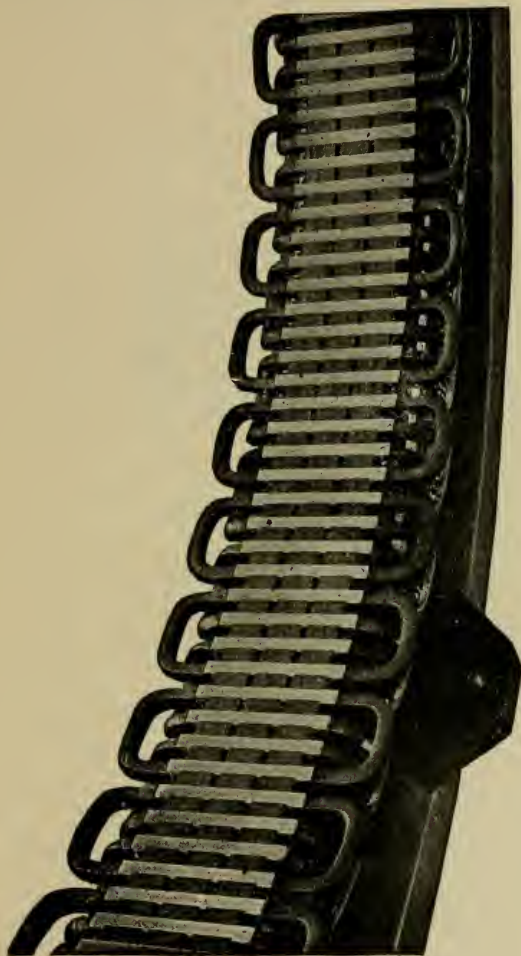


FIG. 1.565.—Section of armature winding of Allis-Chalmers 500 kw. three phase water wheel alternator. The coils are of the concentrated "half" type. Each coil is completely insulated before being placed on the core and no insulation is placed in the slot itself. The ends of the coils where they project beyond the slots are heavily taped. Where necessary suitable supports are provided for the coil connections so that they cannot become displaced on account of stresses due to short circuits or other causes. The winding is of the "chain" type. This is shown by the way the coils are connected together at the right. The armature terminals are either provided with insulated connectors or are led to a marble terminal board on which the terminals are so mounted and protected that it is impossible for an attendant to make accidental contact with them. The position of the illustration would indicate a horizontal alternator but the machine is of the vertical type; the lug on the right shows this, being used for adjusting the alternator on the foundation.

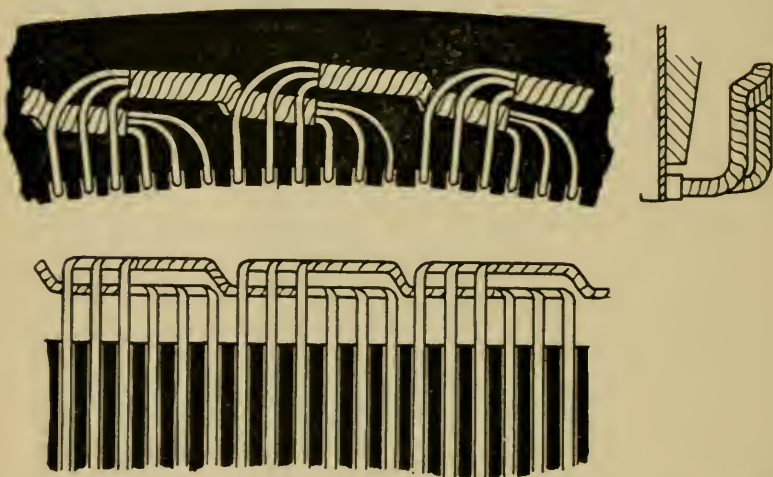

**Skew Coil Winding.**—In this type of winding the object is to shape the coils so that all may be of one pattern. This is accomplished by making the ends skew shape as shown in figs. 1,566 to 1,568.

**Fed-in Winding.**—This name is given to a type of winding possible with open or only partially closed slots, in which coils previously formed are introduced, only a few inductors at a time



FIGS. 1,566 TO 1,568.—Views of a section of skew coil winding; so called on account of the skew shape given to the coil ends in order that all the coils may be of one shape.

if necessary. They are inserted into the slots from the top, the slot being provided with a lining of horn fibre or other suitable material, which is finally closed over and secured in place by means of a wedge, or by some other suitable means. An example of a fed-in winding is shown in figs. 1,566 and 1,568.

**Imbricated Winding.**—This is a species of spiral coil winding in which the end connections are built up one above the other, either in a radial, or in a horizontal direction.

The winding is used especially on the armatures of turbine alternators and dynamos.

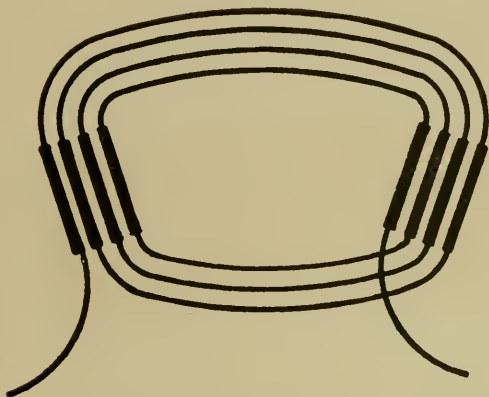


FIG. 1,569.—Diagram showing a spiral coil. This type of coil is one in which each successive turn lies entirely within the previous turn, starting with the outermost turn of the coil. The successive turns of a spiral coil are thus not of the same size, and are not over-lapping as in a "lap" coil.

**Spiral Winding.**—This is a winding in which "spiral" coils, as shown in fig. 1,560, are used. The spiral form of coil is very extensively used for armature windings of alternators.

**Mummified Winding.**—The word *mummified* as applied to a winding is used to express the treatment the coils of the winding receive in the making; that is, when a winding, after being covered with tape or other absorbent material, is saturated in an insulating compound and baked until the whole is solidified, it is said to be mummified.

**Shuttle Winding.**—This type of winding consists of a single coil having a large number of turns, wound in two slots spaced  $180^\circ$  apart. It was originally used on Siemens' armature and is now used on magnetos, as shown in figs. 1,459 to 1,461.


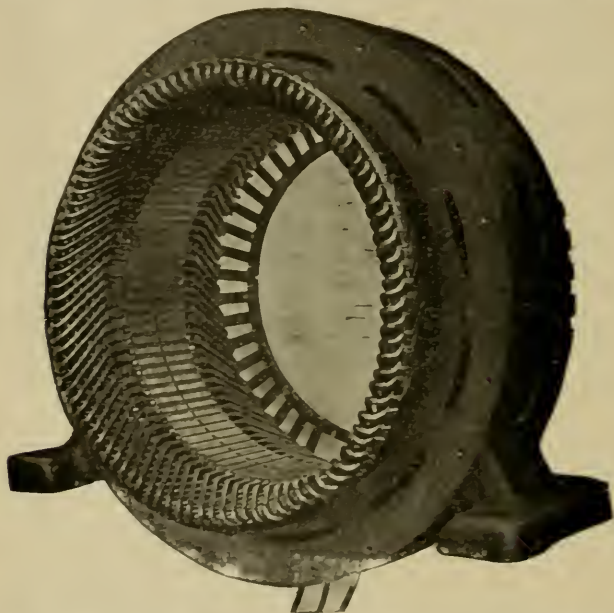


FIG. 1,570.—Frame and armature winding of Westinghouse pedestal bearing alternator. Armature frames are of cast iron and ventilated. Interior transverse ribs strengthen the frame and support the core laminations. The armature core is built up of annealed and japanned punched laminations. Armature slots are open. Armature coils are form wound, impregnated, and interchangeable; they are held in place with fiber wedges. Ventilating spaces are provided at intervals in the armature core and also between all coil ends.

**Creeping Winding.**—Another species of winding, known as a creeping winding is applicable to particular cases.

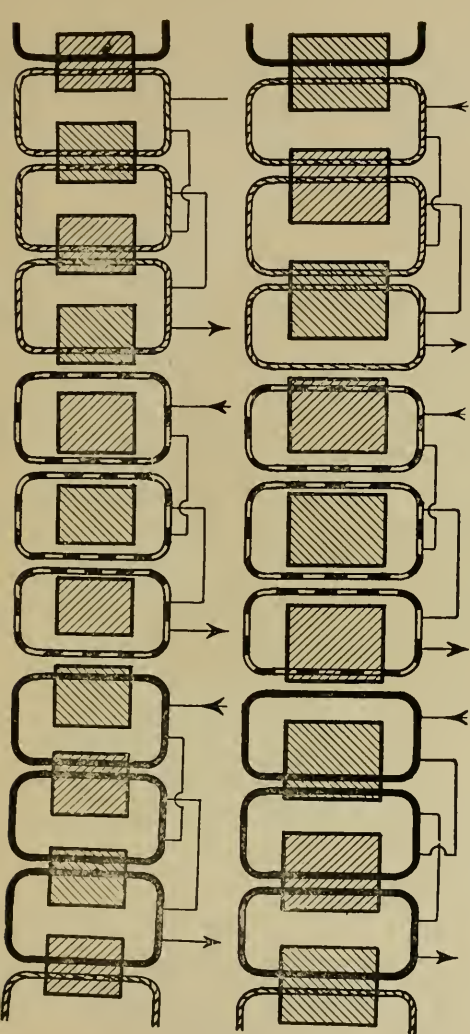If three adjacent coils, each having a pitch of 120 electrical degrees, be set side by side, they will occupy the same breadth as 4 poles, and, by repetition, will serve for any machine having a multiple of 4 poles, but cannot be used for machines with 6, 10 or 14 poles. Fig. 1,571 shows this example.



FIGS. 1,571 and 1,572.—Diagram of creeping windings. Fig. 1,571, three coils subtending four poles; fig. 1,572, nine coils subtending eight poles.

In the same way 9 coils, each of 160 electrical degrees, will occupy the same angular breadth as 8 poles.

Further, 9 coils of 200 electrical degrees will occupy the same angular breadth as 10 poles.

Now of these 9 coils, any three contiguous ones are nearly in phase, if wound alternately clockwise and counterclockwise.

For the 8 pole machine, the phase difference between adjacent coils is 20 degrees.

For the 10 pole machine, the phase difference is also 20 degrees.

The cosine of 20 degrees is .9397, consequently, if 3 adjacent coils be united in series, their joint pressure will be 2.897 multiplied by that of the middle one of the three.

The 9 coils may therefore be joined up in three groups of 3 adjacent coils, for the three phases.

By repetition, the same grouping will suit for any machine having

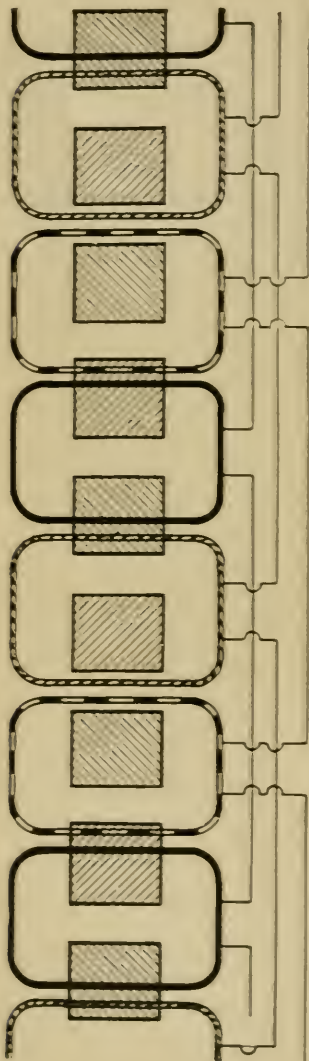


FIG. 1,573.—Developed diagram of creeping winding; nine coils subtending ten poles.


a multiple of 8 or of 10 poles. These two cases are illustrated in figs. 1,572 and 1,573. In the figures, the coils are represented as occupying two slots each, but they might be further distributed.



FIG. 1,574.—Triumph pedestal and brush rigging for large revolving field alternators. Carbon brushes are used, carried in box type brush holders. The stand or pedestal here shown is the kind used with the engine and flywheel types of alternator. The brush studs are mounted on the stand in such a manner that the brushes are easily accessible. The latter carry only the low voltage direct current necessary for exciting the field.



**Turbine Alternator Winding.**—For the reason that steam turbines run at so much higher speed than steam engines, the construction of armatures and windings for alternators intended to be direct connected to turbines must be quite different from those driven by steam engines. Accordingly, in order that the frequency be not too high, turbine driven alternators must have very few poles—usually two or four, but rarely six.

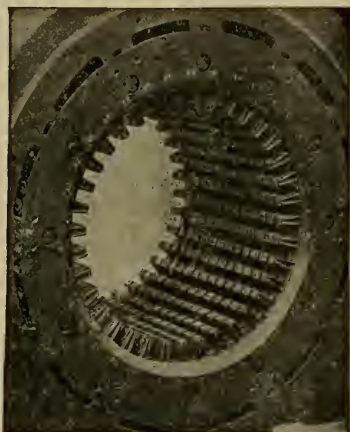

FIGS. 1,575 and 1,576.—Westinghouse turbine alternator armature construction. Fig. 1,575, View showing dovetail grooves in armature casting; fig. 1,576, laminæ assembled in dovetail grooves of armature casting.

The following table will show the relation between the revolutions and frequencies for the numbers of poles just designated.

**TABLE OF FREQUENCY AND REVOLUTIONS**

Frequency	REVOLUTIONS		
	2 pole	4 pole	6 pole
25	1,500	750	500
60	3,600	1,800	1,200
100	6,000	3,000	2,000





FIG. 1,577.—Armature of Westinghouse turbine alternator with end bells removed showing method of bracing the coil ends.

FIG. 1,578.—Stationary armature of

Westinghouse turbine alternator with part of the winding in place. Because of the small number of coils in a turbine alternator as compared with a slow speed machine of the same kva. rating, each coil carries a great amount of power on large load, particularly at times of short circuits or grounds on the external circuit.

The "throw" of the coils is large, leaving a considerable part of the winding in the end turns unsupported by the armature core. For these reasons great stresses, which are dangerous, if effective means be not adopted to withstand them, may exist between the coils. The inductors are of such cross section that they can be made rigid and insulated satisfactorily. The end turns are given a fan like form as shown, affording ventilation and effective bracing as shown in fig. 1,577. Cord lashings are, except in the smallest frames, used only for holding in the small spacing blocks between the coils.

They are not depended on to support the coils. Malleable iron braces, hard maple blocks, and brass or steel bolts with brass washers are used to withstand the mechanical stresses imposed on the armature coils by external short circuits.



From the table, it is evident that a large number of poles is not permissible, considering the high speed at which the turbine must be run.

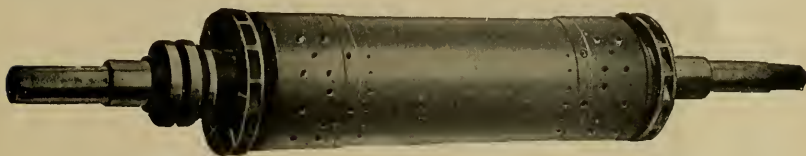


FIG. 1,579.—Two pole radial slot field. Radial slot fields are used on very small and very large alternators. The field diameters are so small that the end turns of the winding can be effectively bound into place, such binding being necessary with a radial slot machine. The shaft and disc are a one piece forging of steel.

**Ques.** How is the high voltage obtained with so few poles?

**Ans.** There must be either numerous inductors per slot or numerous slots per pole.



FIGS. 1,580 to 1,582.—Westinghouse two pole parallel slot field with ends removed showing construction. The parallel slot design of field construction is used in Westinghouse machines up to 10,000 kva. capacity. In fig. 1,581, the large holes at the end near the circumference of the cylinder are for the accommodation of the bolts that hold the bronze end discs and stub shafts. In winding, the cylinder is mounted on a horizontal turntable that rotates in a horizontal plane. The copper strap field coil winding is wound turn by turn under pressure and strip insulation is wound in between. When completed the turns are held rigidly in position with heavy brass wedges. An end disc made of bronze holds the stub shaft and is bolted to each end of the steel center. When the leads are attached to the collector rings the field is complete.

**Ques.** What form of armature is generally used?

**Ans.** A stationary armature.

**Ques.** What difficulty is experienced with revolving armatures?

**Ans.** The centrifugal force being considerable on account

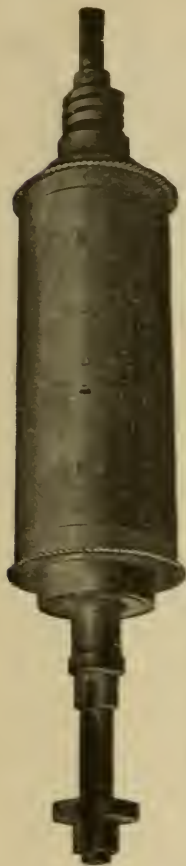


FIG. 1,583. — Westinghouse two pole parallel slot turbine alternator field.



FIG. 1,584. — Westinghouse four pole parallel slot turbine alternator field.

of the high speed, requires specially strong construction to resist it, consequently closed or nearly closed slots must be used.

**Ques.** How is the design of the rotor modified so as to reduce the centrifugal force?

**Ans.** It is made long and of small diameter.

Some examples of revolving fields are shown in figs. 1,579 to 1,584. Figs. 1,577 and 1,578 show some construction details of a stationary armature of turbine alternator.

PROPERTY OF  
A. & M. COLLEGE LIBRARY.

# **HAWKINS PRACTICAL LIBRARY OF ELECTRICITY**

**IN HANDY POCKET FORM**      **PRICE \$1 EACH**

---

*They are not only the best, but the cheapest work published on Electricity. Each number being complete in itself. Separate numbers sent postpaid to any address on receipt of price. They are guaranteed in every way or your money will be returned. Complete catalog of series will be mailed free on request.*

## **ELECTRICAL GUIDE, NO. 1**

Containing the principles of Elementary Electricity, Magnetism, Induction, Experiments, Dynamos, Electric Machinery.

## **ELECTRICAL GUIDE, NO. 2**

The construction of Dynamos, Motors, Armatures, Armature Windings, Installing of Dynamos.

## **ELECTRICAL GUIDE, NO. 3**

Electrical Instruments, Testing, Practical Management of Dynamos and Motors.

## **ELECTRICAL GUIDE, NO. 4**

Distribution Systems, Wiring, Wiring Diagrams, Sign Flashers, Storage Batteries.

## **ELECTRICAL GUIDE, NO. 5**

Principles of Alternating Currents and Alternators.

## **ELECTRICAL GUIDE, NO. 6**

Alternating Current Motors, Transformers, Converters, Rectifiers.

## **ELECTRICAL GUIDE, NO. 7**

Alternating Current Systems, Circuit Breakers, Measuring Instruments.

## **ELECTRICAL GUIDE, NO. 8**

Alternating Current Switch Boards, Wiring, Power Stations, Installation and Operation.

## **ELECTRICAL GUIDE, NO. 9**

Telephone, Telegraph, Wireless, Bells, Lighting, Railways.

## **ELECTRICAL GUIDE, NO. 10**

Modern Practical Applications of Electricity and Ready Reference Index of the 10 Numbers.

**Theo. Audel & Co., Publishers.**

**72 FIFTH AVENUE,  
NEW YORK**



THIS BOOK MAY BE KEPT OUT

**TWO WEEKS**

And is subject to a fine of Five Cents a day  
thereafter. It was taken out on  
the day indicated below :



NORTH CAROLINA STATE UNIVERSITY

S02959390

